 



Shannon decomposition



Claude Shannon
mathematician / electrical engineer
(1916 –2001)


(Ex 8.6)

Show how a 4-to-1 multiplexer can be used as a "function generator" for example to generate the OR function.

 


(Ex 8.6)

 Show how a 4-to-1 multiplexer can be used as a "function generator" for example to generate the OR function.




Multiplexer as function generator


 


(Ex 8.6)

 Show how a 4-to-1 multiplexer can be used as a "function generator" for example to generate the OR function.



Multiplexer as function generator

  


BV 6.1

Show how the function

$$f(w_1, w_2, w_3) = \sum m(0, 2, 3, 4, 5, 7)$$

can be implemented using a 3-to-8 **decoder** and an OR gate.

 


BV 6.1


Show how the function

$$f(w_1, w_2, w_3) = \sum m(0, 2, 3, 4, 5, 7)$$

can be implemented using a 3-to-8 **decoder** and an OR gate.

 

Ex 8.7

 

A majority gate outputs the same value as the majority of the inputs. The gate can for example be used in fault-tolerant logic, or in image processing circuits.

- a) (Set up the gate's truth table and minimize the function with Karnaugh map. Realize the function with AND-OR gates.)
- b) Realize the majority gate with an 8: 1 MUX.
- c) Use Shannon decomposition and realize the majority gate with a 2: 1 MUX and gates.
- d) Realize the majority gate with only 2:1 MUXes.

(8.7a)

	a	b	c	M
0	0	0	0	0
1	0	0	1	0
2	0	1	0	0
3	0	1	1	1
4	1	0	0	0
5	1	0	1	1
6	1	1	0	1
7	1	1	1	1

With AND OR gates

$$\bar{a}bc$$

$$a\bar{b}c$$

$$ab\bar{c}$$

$$abc$$

(8.7a)

	a	b	c	M
0	0	0	0	0
1	0	0	1	0
2	0	1	0	0
3	0	1	1	1
4	1	0	0	0
5	1	0	1	1
6	1	1	0	1
7	1	1	1	1

With AND OR gates

$\bar{a}bc$

$a\bar{b}c$

$ab\bar{c}$

abc

		M			
		bc			
a		00	01	11	10
		0	1	3	2
0		0	0	1	0
1		4	5	7	6
		0	1	1	1

(8.7a)

	a	b	c	M
0	0	0	0	0
1	0	0	1	0
2	0	1	0	0
3	0	1	1	1
4	1	0	0	0
5	1	0	1	1
6	1	1	0	1
7	1	1	1	1

With AND OR gates

$$\bar{a}bc$$

$$a\bar{b}c$$

$$ab\bar{c}$$

$$abc$$

		M			
a	bc	00	01	11	10
	0	0 ⁰	0 ¹	1 ³	0 ²
1	0	0 ⁴	1 ⁵	1 ⁷	1 ⁶

$$M = ac + ab + bc$$

(8.7a)

	a	b	c	M
0	0	0	0	0
1	0	0	1	0
2	0	1	0	0
3	0	1	1	1
4	1	0	0	0
5	1	0	1	1
6	1	1	0	1
7	1	1	1	1

With AND OR gates


$\bar{a}bc$

$a\bar{b}c$

$ab\bar{c}$

abc

		M			
		bc			
a		00	01	11	10
	0	0 ⁰	0 ¹	1 ³	0 ²
	1	0 ⁴	1 ⁵	1 ⁷	1 ⁶

 

$$M = ac + ab + bc$$

8.7b


	a	b	c	M
0	0	0	0	0
1	0	0	1	0
2	0	1	0	0
3	0	1	1	1
4	1	0	0	0
5	1	0	1	1
6	1	1	0	1
7	1	1	1	1

With 8-to-1 mux ...

8.7b

	a	b	c	M
0	0	0	0	0
1	0	0	1	0
2	0	1	0	0
3	0	1	1	1
4	1	0	0	0
5	1	0	1	1
6	1	1	0	1
7	1	1	1	1

With 8-to-1 mux ...

 

8.7c

	a	b	c	M
0	0	0	0	0
1	0	0	1	0
2	0	1	0	0
3	0	1	1	1
4	1	0	0	0
5	1	0	1	1
6	1	1	0	1
7	1	1	1	1

*Shannon decomposition. 2-to-1 mux
and gates.*

$$\bar{a}bc$$

$$a\bar{b}c$$

$$ab\bar{c}$$

$$abc$$

8.7c

	a	b	c	M
0	0	0	0	0
1	0	0	1	0
2	0	1	0	0
3	0	1	1	1
4	1	0	0	0
5	1	0	1	1
6	1	1	0	1
7	1	1	1	1

Shannon decomposition. 2-to-1 mux and gates.

$$\bar{a}bc$$

$$a\bar{b}c$$

$$ab\bar{c}$$

$$abc$$

$$\begin{aligned} M &= \bar{a}bc + a\bar{b}c + ab\bar{c} + abc = \\ &= \bar{a}(bc) + a(\bar{b}c + b\bar{c} + bc) = \end{aligned}$$

8.7c

	a	b	c	M
0	0	0	0	0
1	0	0	1	0
2	0	1	0	0
3	0	1	1	1
4	1	0	0	0
5	1	0	1	1
6	1	1	0	1
7	1	1	1	1

Shannon decomposition. 2-to-1 mux and gates.

$$\bar{a}bc$$

$$a\bar{b}c$$

$$ab\bar{c}$$

$$abc$$

$$\begin{aligned} M &= \bar{a}bc + a\bar{b}c + ab\bar{c} + abc = \\ &= \bar{a}(bc) + a(\bar{b}c + b\bar{c} + bc) = \end{aligned}$$

b	c	
0	0	0
0	1	1 $\bar{b}c$
1	0	1 $b\bar{c}$
1	1	1 bc

8.7c

	a	b	c	M
0	0	0	0	0
1	0	0	1	0
2	0	1	0	0
3	0	1	1	1
4	1	0	0	0
5	1	0	1	1
6	1	1	0	1
7	1	1	1	1

Shannon decomposition. 2-to-1 mux and gates.

$$\bar{a}bc$$

$$a\bar{b}c$$

$$ab\bar{c}$$

$$abc$$

$$\begin{aligned} M &= \bar{a}bc + a\bar{b}c + ab\bar{c} + abc = \\ &= \bar{a}(bc) + a(\bar{b}c + b\bar{c} + bc) = \end{aligned}$$

b	c	
0	0	0
0	1	1 $\bar{b}c$
1	0	1 $b\bar{c}$
1	1	1 bc

OR

8.7c

	a	b	c	M
0	0	0	0	0
1	0	0	1	0
2	0	1	0	0
3	0	1	1	1
4	1	0	0	0
5	1	0	1	1
6	1	1	0	1
7	1	1	1	1

Shannon decomposition. 2-to-1 mux and gates.

$$\bar{a}bc$$

$$a\bar{b}c$$

$$ab\bar{c}$$

$$abc$$

$$\begin{aligned}
 M &= \bar{a}bc + a\bar{b}c + ab\bar{c} + abc = \\
 &= \bar{a}(bc) + a(\bar{b}c + b\bar{c} + bc) = \\
 &= \bar{a}(bc) + a(b + c)
 \end{aligned}$$

b	c	
0	0	0
0	1	1 $\bar{b}c$
1	0	1 $b\bar{c}$
1	1	1 bc

OR

8.7c

	a	b	c	M
0	0	0	0	0
1	0	0	1	0
2	0	1	0	0
3	0	1	1	1
4	1	0	0	0
5	1	0	1	1
6	1	1	0	1
7	1	1	1	1


Shannon decomposition. 2-to-1 mux and gates.

$\bar{a}bc$

$a\bar{b}c$

$ab\bar{c}$

abc

 

$$\begin{aligned}
 M &= \bar{a}bc + a\bar{b}c + ab\bar{c} + abc = \\
 &= \bar{a}(bc) + a(\bar{b}c + b\bar{c} + bc) = \\
 &= \bar{a}(bc) + a(b + c)
 \end{aligned}$$

b	c	
0	0	0
0	1	1 $\bar{b}c$
1	0	1 $b\bar{c}$
1	1	1 bc

OR

8.7d

	a	b	c	M
0	0	0	0	0
1	0	0	1	0
2	0	1	0	0
3	0	1	1	1
4	1	0	0	0
5	1	0	1	1
6	1	1	0	1
7	1	1	1	1

Shannon decomposition. Only 2-to-1 muxes.

$$\bar{a}bc$$

$$a\bar{b}c$$

$$ab\bar{c}$$

$$abc$$

8.7d

	a	b	c	M
0	0	0	0	0
1	0	0	1	0
2	0	1	0	0
3	0	1	1	1
4	1	0	0	0
5	1	0	1	1
6	1	1	0	1
7	1	1	1	1

Shannon decomposition. Only 2-to-1 muxes.

$$\bar{a}bc$$

$$a\bar{b}c$$

$$ab\bar{c}$$

$$abc$$

$$M = \bar{a}(bc) + a(b+c) \quad g = bc \quad h = b+c$$

$$g = \bar{b}(0) + b(c) = \bar{b} \cdot 0 + b \cdot c$$

$$h = b+c = b + (b+\bar{b})c = \bar{b}c + b + bc = \bar{b}c + b(1+c) = \bar{b} \cdot c + b \cdot 1$$

8.7d

	a	b	c	M
0	0	0	0	0
1	0	0	1	0
2	0	1	0	0
3	0	1	1	1
4	1	0	0	0
5	1	0	1	1
6	1	1	0	1
7	1	1	1	1


Shannon decomposition. Only 2-to-1 muxes.

$$\bar{a}bc$$

$$a\bar{b}c$$

$$ab\bar{c}$$

$$abc$$

 

$$M = \bar{a}(bc) + a(b+c) \quad g = bc \quad h = b+c$$

$$g = \bar{b}(0) + b(c) = \bar{b} \cdot 0 + b \cdot c$$

$$h = b+c = b + (b+\bar{b})c = \bar{b}c + b + bc = \bar{b}c + b(1+c) = \bar{b} \cdot c + b \cdot 1$$

8.7d

	a	b	c	M
0	0	0	0	0
1	0	0	1	0
2	0	1	0	0
3	0	1	1	1
4	1	0	0	0
5	1	0	1	1
6	1	1	0	1
7	1	1	1	1


Shannon decomposition. Only 2-to-1 muxes.

$$\bar{a}bc$$

$$a\bar{b}c$$

$$ab\bar{c}$$

$$abc$$

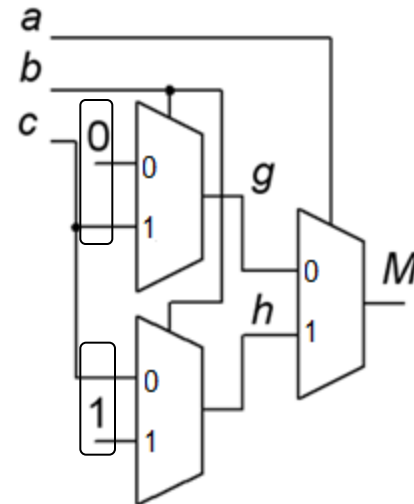

$$M = \bar{a}(bc) + a(b+c) \quad g = bc \quad h = b+c$$

$$g = \bar{b}(0) + b(c) = \bar{b} \cdot 0 + b \cdot c$$

$$h = b+c = b + (b+\bar{b})c = \bar{b}c + b + bc = \bar{b}c + b(1+c) = \bar{b} \cdot c + b \cdot 1$$

BV 6.5

For the function

$$f(w_1, w_2, w_3) = \sum m(0, 2, 3, 6)$$

use Shannon's expansion to derive an implementation using a 2-to-1 multiplexer and any necessary gates.

BV 6.5

For the function

$$f(w_1, w_2, w_3) = \sum m(0, 2, 3, 6)$$

use Shannon's expansion to derive an implementation using a 2-to-1 multiplexer and any necessary gates.

$$\begin{aligned} f(w_1, w_2, w_3) &= \sum m(000, 010, 011, 110) = \\ &= \overline{w_1} \overline{w_2} \overline{w_3} + \overline{w_1} \overline{w_2} \overline{w_3} + \overline{w_1} \overline{w_2} w_3 + \overline{w_1} w_2 \overline{w_3} = \\ &= \overline{w_1} (\overline{w_2} \overline{w_3} + \overline{w_2} \overline{w_3} + \overline{w_2} w_3) + \overline{w_1} (w_2 \overline{w_3}) = \\ &= \overline{w_1} (w_2 + \overline{w_3}) + \overline{w_1} (w_2 \overline{w_3}) \end{aligned}$$


BV 6.5

For the function

$$f(w_1, w_2, w_3) = \sum m(0, 2, 3, 6)$$

use Shannon's expansion to derive an implementation using a 2-to-1 multiplexer and any necessary gates.

$$\begin{aligned} f(w_1, w_2, w_3) &= \sum m(000, 010, 011, 110) = \\ &= \bar{w}_1 \bar{w}_2 \bar{w}_3 + \bar{w}_1 w_2 \bar{w}_3 + \bar{w}_1 w_2 w_3 + w_1 w_2 \bar{w}_3 = \\ &= \bar{w}_1 (\bar{w}_2 \bar{w}_3 + \bar{w}_2 w_3 + w_2 w_3) + w_1 (w_2 \bar{w}_3) = \\ &= \bar{w}_1 (w_2 + \bar{w}_3) + w_1 (w_2 \bar{w}_3) \end{aligned}$$

 



BV 6.5

For the function

$$f(w_1, w_2, w_3) = \sum m(0, 2, 3, 6)$$


use Shannon's expansion to derive an implementation using a 2-to-1 multiplexer and any necessary gates.

$$\begin{aligned} f(w_1, w_2, w_3) &= \sum m(000, 010, 011, 110) = \\ &= \bar{w}_1 \bar{w}_2 \bar{w}_3 + \bar{w}_1 w_2 \bar{w}_3 + \bar{w}_1 w_2 w_3 + w_1 w_2 \bar{w}_3 = \\ &= \bar{w}_1 (\bar{w}_2 \bar{w}_3 + w_2 \bar{w}_3 + w_2 w_3) + w_1 (w_2 \bar{w}_3) = \\ &= \bar{w}_1 (w_2 + \bar{w}_3) + w_1 (w_2 \bar{w}_3) \end{aligned}$$

  



(Ex 8.9)

 

Show how one four-input exorgate (XOR, odd parity function) is realized in an FPGA circuit. Show the contents of the SRAM cells (LUT, Lookup Table)



XOR

		$x_1 x_0$			
		00	01	11	10
x_3	x_2	00 0	01 1	11 3 0	10 2 1
	0				
x_3	x_2	01 4 1	10 5 0	11 7 1	10 6 0
	1				
x_3	x_2	11 12 0	10 13 1	11 15 0	10 14 1
	1				
x_3	x_2	10 8 1	11 9 0	11 11 1	10 10 0
	0				


XOR

$x_1 x_0$					
		00	01	11	10
x_3	x_2	0	1	3	2
		0	1	3	2
0	0	0	1	3	2
	1	4	5	7	6
1	1	12	13	15	14
	0	8	9	11	10

(8.9)

  


(8.9)

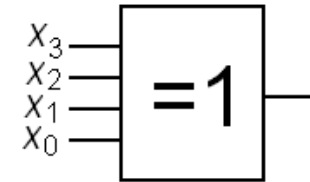


XOR

$x_3 \backslash x_2 \backslash x_1 x_0$	00	01	11	10
00	0	1	3	2
01	4	5	7	6
11	12	13	15	14
10	8	9	11	10

 


(8.9)

 


XOR

$x_3 \backslash x_1 x_0$	00	01	11	10
$x_2 \backslash$	00	11	30	21
0	0	1	3	2
1	4	5	7	6
0	0	1	3	2
1	4	5	7	6


 



(Ex 8.8)

 

Set up full adder truth table. Show how a full adder is implemented in an FPGA chip. Logic elements of an FPGA is able to cascade C_{OUT} and C_{IN} between "neighbors." Show the contents of the SRAM cells (LUT, Lookup Table).


(8.8)

  


 

(8.8)


x_2	x_1	x_0		
A	B	C_{IN}	Σ	C_{OUT}
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

 


 

x_2	x_1	x_0		
A	B	C_{IN}	Σ	C_{OUT}
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1


(8.8)

 

 

x_2	x_1	x_0		
A	B	C_{IN}	Σ	C_{OUT}
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

(8.8)

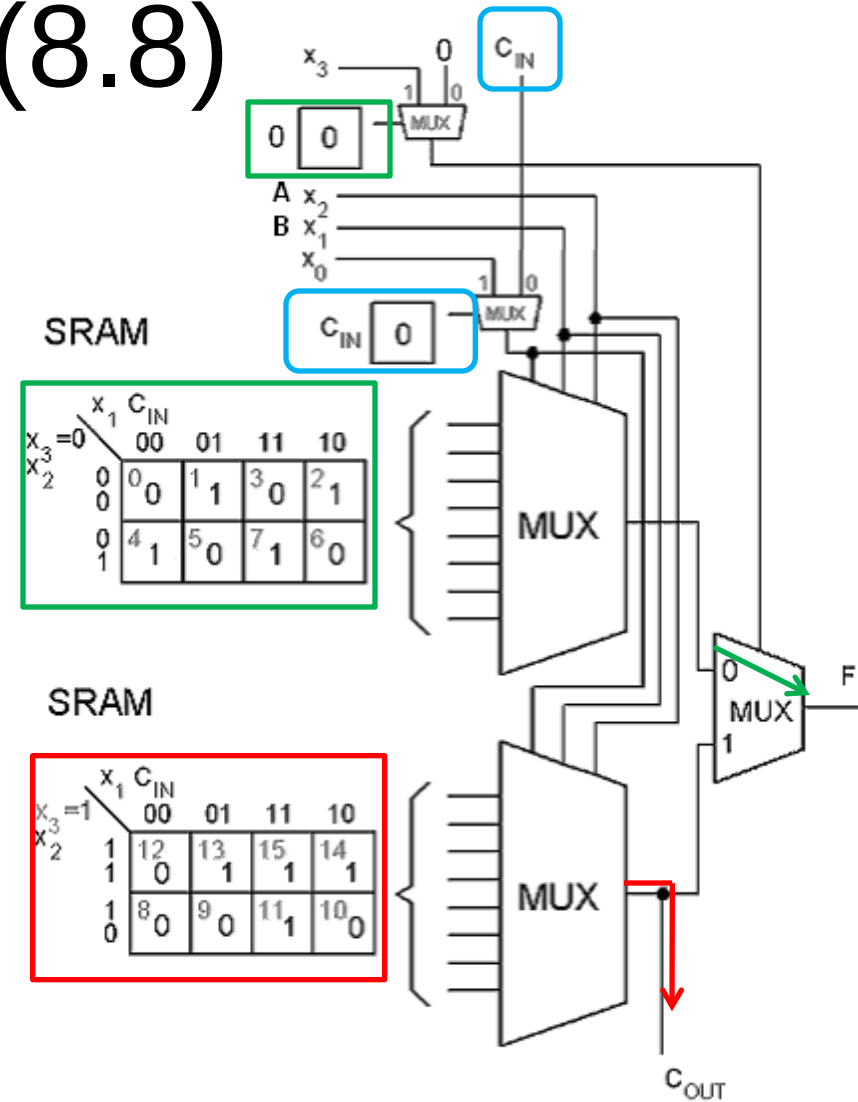


(BV ex 6.31)

In digital systems it is often necessary to have circuits that can shift the bits of a vector one or more bit positions to the left or right.


Design a circuit that can shift a four-bit vector $W = w_3w_2w_1w_0$ one bit position to the right when a control signal *Shift* is equal to 1.

 Let the outputs of the circuit be a four-bit vector $Y = y_3y_2y_1y_0$ and a signal k , such that if *Shift* = 1 then $y_3 = 0$, $y_2 = w_3$, $y_1 = w_2$, $y_0 = w_1$, and $k = w_0$. If *Shift* = 0 then $Y = W$ and $k = 0$.




(BV ex 6.31)

We use MUXes:

 

(BV ex 6.31)

We use MUXes:

 


BV ex. 6.32

Barrel shifter

The shifter in Example 6.31 shifts the bits of an input vector by one bit position to the right. It fills the vacated bit on the left side with 0. If the bits that are shifted out are placed into the vacated position on the left, then the circuit effectively rotates the bits of the input vector by a specified number of bit positions. Such a circuit is called a *barrel shifter*.

 Design a four-bit barrel shifter that rotates the bits by 0, 1, 2, or 3 bit positions as determined by the valuation of two control signals s_1 and s_0 .



A barrelshifter is used to speed up floating point operations.

Barrel shifter





William Sandqvist william@kth.se

BV ex. 6.32

Truth table:



S_1	S_0	y_3	y_2	y_1	y_0
0	0	w_3	w_2	w_1	w_0
0	1	w_0	w_3	w_2	w_1
1	0	w_1	w_0	w_3	w_2
1	1	w_2	w_1	w_0	w_3

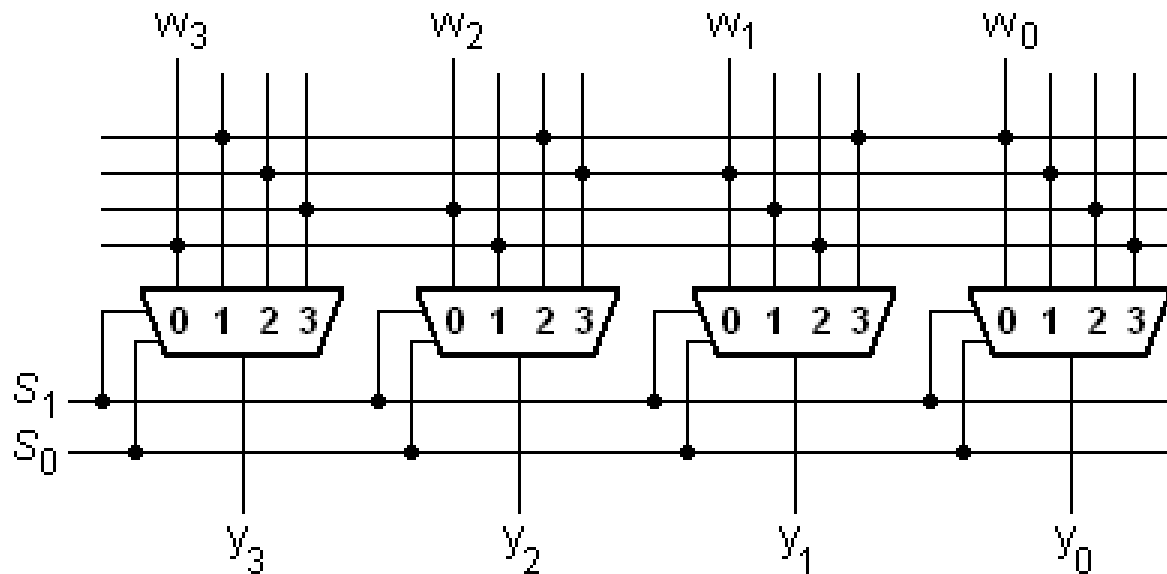 

BV ex. 6.32

Truth table:



S_1	S_0	y_3	y_2	y_1	y_0
0	0	w_3	w_2	w_1	w_0
0	1	w_0	w_3	w_2	w_1
1	0	w_1	w_0	w_3	w_2
1	1	w_2	w_1	w_0	w_3

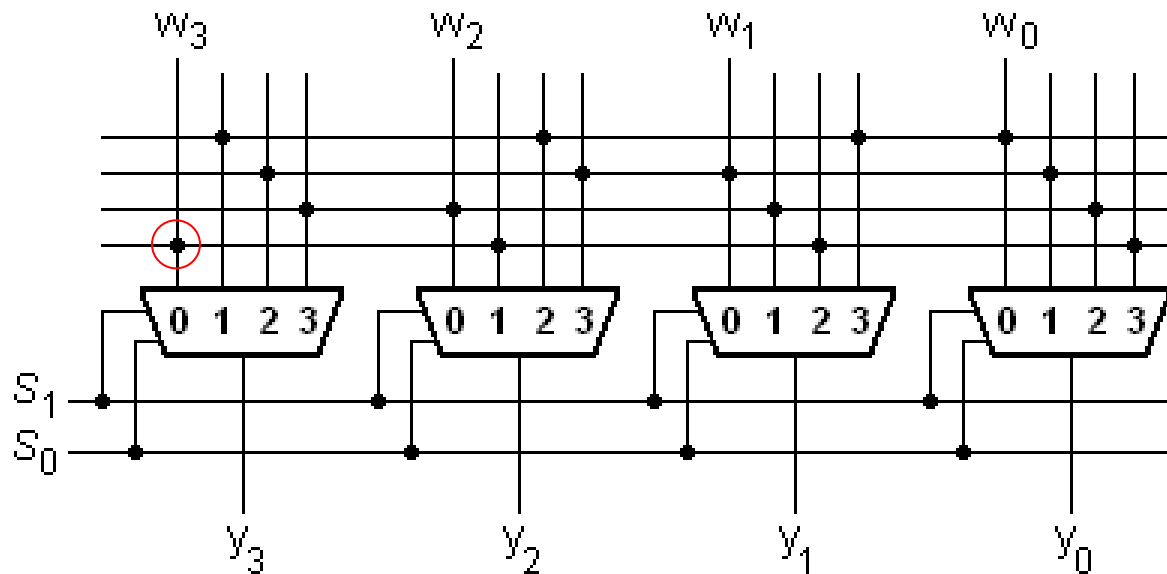 

BV ex. 6.32

Truth table:



S_1	S_0	y_3	y_2	y_1	y_0
0	0	w_3	w_2	w_1	w_0
0	1	w_0	w_3	w_2	w_1
1	0	w_1	w_0	w_3	w_2
1	1	w_2	w_1	w_0	w_3

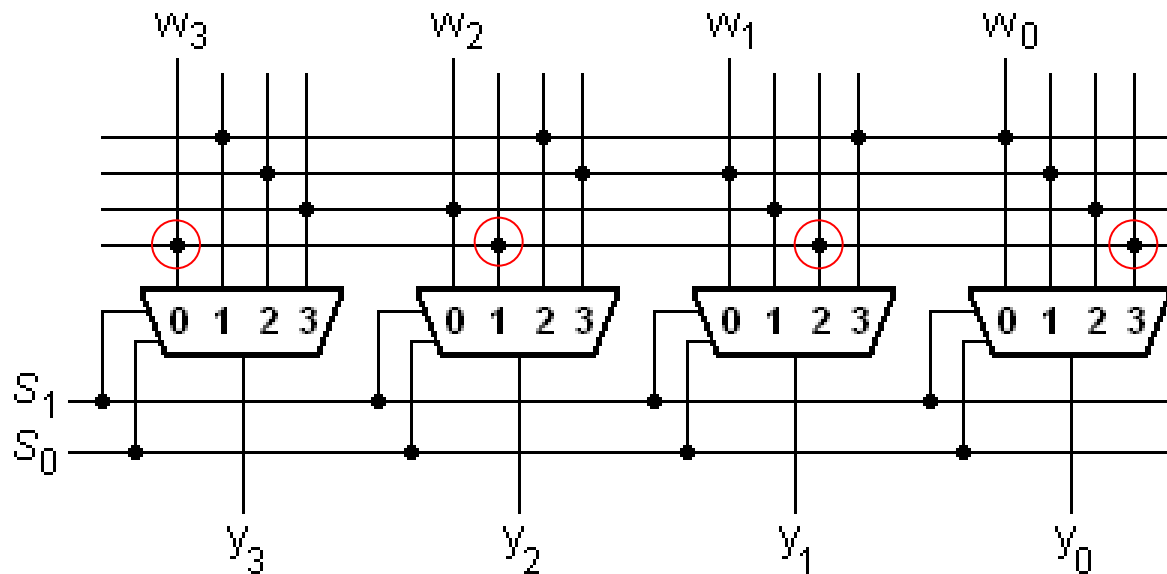 

BV ex. 6.32

Truth table:



S_1	S_0	y_3	y_2	y_1	y_0
0	0	w_3	w_2	w_1	w_0
0	1	w_0	w_3	w_2	w_1
1	0	w_1	w_0	w_3	w_2
1	1	w_2	w_1	w_0	w_3

  

BV ex. 6.32

Truth table:

S_1	S_0	y_3	y_2	y_1	y_0
0	0	w_3	w_2	w_1	w_0
0	1	w_0	w_3	w_2	w_1
1	0	w_1	w_0	w_3	w_2
1	1	w_2	w_1	w_0	w_3

 
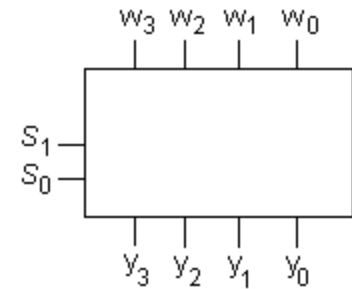


BV ex. 6.32

Truth table:

S_1	S_0	y_3	y_2	y_1	y_0
0	0	w_3	w_2	w_1	w_0
0	1	w_0	w_3	w_2	w_1
1	0	w_1	w_0	w_3	w_2
1	1	w_2	w_1	w_0	w_3

And so on ...

  


= Lowcost FPGA




Key Benefits

- Lowest FPGA unit cost starting at **\$0.49**
- Ultra-low power in Flash*Freeze mode, as low as 2 μ W
- Nonvolatile FPGA eliminates unnecessary parts from BOM
- Single-chip and ultra-low-power products simplify board design
- Variety of cost-optimized packages reduce assembly costs
- Low-power FPGAs reduce thermal management and cooling needs

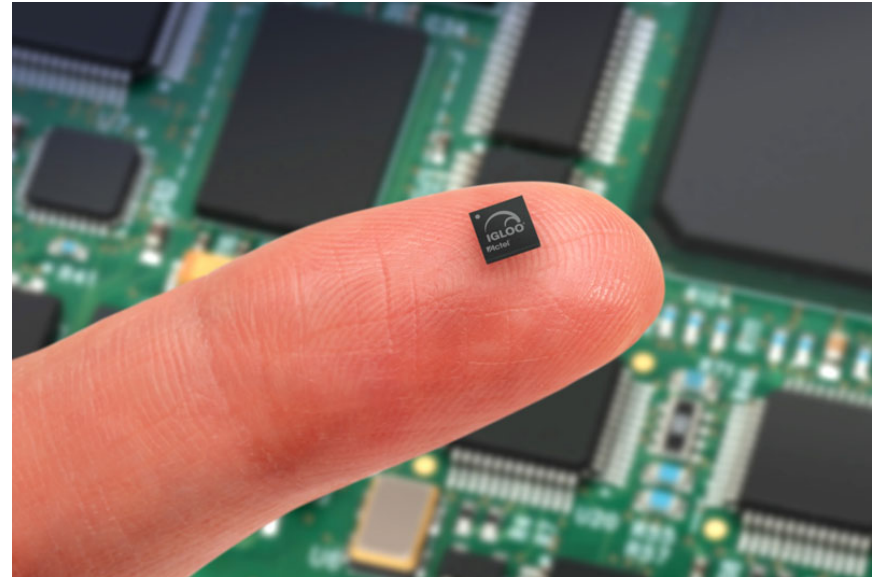

BV 6.16

 

Actel Corporation manufactures an FPGA family called Act 1, which uses multiplexer based logic blocks. Show how the function

$$f = w_2 \overline{w_3} + w_1 w_3 + \overline{w_2} w_3$$

can be implemented using only ACT 1 logic blocks.

BV 6.16

$$f = w_2 \overline{w_3} + w_1 w_3 + \overline{w_2} w_3$$

BV 6.16

$$f = w_2 \overline{w_3} + w_1 w_3 + \overline{w_2} w_3$$

$$f = \overline{w_3} (w_2) + w_3 (w_1 + \overline{w_2})$$

$$\overline{w_3} (w_2) = \overline{w_3} (\overline{w_2} \cdot 0 + w_2 \cdot 1)$$

$$w_3 (w_1 + \overline{w_2}) = w_3 (w_1 (w_2 + \overline{w_2}) + \overline{w_2}) = w_3 (w_2 w_1 + \overline{w_2} w_1 + \overline{w_2}) =$$

$$= w_3 (w_2 w_1 + \overline{w_2} (w_1 + 1)) = w_3 (\overline{w_2} \cdot 1 + w_2 \cdot w_1)$$

$$f = \overline{w_3} (\overline{w_2} \cdot 0 + w_2 \cdot 1) + w_3 (\overline{w_2} \cdot 1 + w_2 \cdot w_1)$$

BV 6.16

$$f = w_2 \overline{w_3} + w_1 w_3 + \overline{w_2} w_3$$


$$f = \overline{w_3} (w_2) + w_3 (w_1 + \overline{w_2})$$

$$\overline{w_3} (w_2) = \overline{w_3} (\overline{w_2} \cdot 0 + w_2 \cdot 1)$$

$$w_3 (w_1 + \overline{w_2}) = w_3 (w_1 (w_2 + \overline{w_2}) + \overline{w_2}) = w_3 (w_2 w_1 + \overline{w_2} w_1 + \overline{w_2}) =$$

$$= w_3 (w_2 w_1 + \overline{w_2} (w_1 + 1)) = w_3 (\overline{w_2} \cdot 1 + w_2 \cdot w_1)$$

$$f = \overline{w_3} (\overline{w_2} \cdot 0 + w_2 \cdot 1) + w_3 (\overline{w_2} \cdot 1 + w_2 \cdot w_1)$$

 

BV 6.16

$$f = w_2 \overline{w_3} + w_1 w_3 + \overline{w_2} w_3$$


$$f = \overline{w_3} (w_2) + w_3 (w_1 + \overline{w_2})$$

$$\overline{w_3} (w_2) = \overline{w_3} (\overline{w_2} \cdot 0 + w_2 \cdot 1)$$

$$w_3 (w_1 + \overline{w_2}) = w_3 (w_1 (w_2 + \overline{w_2}) + \overline{w_2}) = w_3 (w_2 w_1 + \overline{w_2} w_1 + \overline{w_2}) =$$

$$= w_3 (w_2 w_1 + \overline{w_2} (w_1 + 1)) = w_3 (\overline{w_2} \cdot 1 + w_2 \cdot w_1)$$
 
$$f = \overline{w_3} (\overline{w_2} \cdot \boxed{0} + w_2 \cdot \boxed{1}) + w_3 (\overline{w_2} \cdot \boxed{1} + w_2 \cdot \boxed{w_1})$$




VHDL BV 2.51a

Write VHDL code to describe the following functions

$$f_1 = x_1 \overline{x_3} + x_2 \overline{x_3} + \overline{x_3} \overline{x_4} + x_1 x_2 + x_1 \overline{x_4}$$
 
$$f_2 = (x_1 + \overline{x_3}) \cdot (x_1 + x_2 + \overline{x_4}) \cdot (\overline{x_2} + \overline{x_3} + \overline{x_4})$$




VHDL code is written with a text editor and saved in a file with the extension .vhd. The code always consists of two sections ENTITY and ARCHITECTURE.

Entity is a description of how the circuit "looks from the outside" (the interface), and Architecture how it "looks like inside."

VHDL BV 2.51a
 
$$f_1 = x_1 \overline{x_3} + x_2 \overline{x_3} + \overline{x_3} \overline{x_4} + x_1 x_2 + x_1 \overline{x_4}$$
$$f_2 = (x_1 + \overline{x_3}) \cdot (x_1 + x_2 + \overline{x_4}) \cdot (x_2 + \overline{x_3} + \overline{x_4})$$



Program code is written with a text editor. So we can only do text comments to the code. A fixed-width font is used (eg. Courier New).

Comments begin with

--


If you wish, you can "draw" clarification ASCII graphics in the comment lines..

One usually indent text blocks that belong together for greater clarity.

```
--
--
--
--      ->- |
--      ->- | Functions |
--      ->- | x1         |
--      ->- | x2         f1 | ->-
--      ->- | x3         f2 | ->-
--      ->- | x4         |
--      ->- |             |
--
```

VHDL BV 2.51a
 
$$f_1 = x_1 \overline{x_3} + x_2 \overline{x_3} + \overline{x_3} \overline{x_4} + x_1 x_2 + x_1 \overline{x_4}$$
$$f_2 = (x_1 + \overline{x_3}) \cdot (x_1 + x_2 + \overline{x_4}) \cdot (x_2 + \overline{x_3} + \overline{x_4})$$



ENTITY Functions **IS**

```
    PORT(x1, x2, x3, x4 :IN  STD_LOGIC;  
          f1, f2,       :OUT STD_LOGIC )
```

END Functions


ARCHITECTURE LogicFunc **OF** Functions **IS**
BEGIN

```
    f1 <= (x1 AND NOT x3)OR(x2 AND NOT x3)OR  
          (NOT x3 AND NOT x4)OR(x1 AND x2)OR  
          (x1 AND NOT x4);  
    f2 <= (x1 OR NOT x3)AND(x1 OR x2 OR NOT x4)AND  
          (x2 OR NOT x3 OR NOT x4);
```

END LogicFunc ;

VHDL BV 6.21

 Using a **selected** signal assignement, write VHDL code for a 4-to-2 binary encoder. Only one of w0 ...w3 is "1" at a time.




```
LIBRARY ieee;  
USE IEEE.std_logic_1164.all;  
ENTITY ENCODER IS  
    PORT( w :IN  STD_LOGIC_VECTOR( 3 DOWNTO 0 )  ;  
          y :OUT STD_LOGIC_VECTOR( 1 DOWNTO 0 ) );  
END ENCODER  
ARCHITECTURE Behavior OF ENCODER IS  
BEGIN  
    WITH w SELECT  
        y <= "00" WHEN "0001",  
            "01" WHEN "0010",  
            "10" WHEN "0100",  
            "11" WHEN OTHERS;  
END Behavior ;
```


(8.10) Additional if time permits

x_1x_0		Y			
		00	01	11	10
x_3 x_2	0	0 -	1 -	3 0	2 1
	0	-	-	0	1
	0	4 0	5 1	7 1	6 0
	1	0	1	1	0
	1	12 0	13 1	15 0	14 1
	1	0	1	0	1
	1	8 -	9 -	11 0	10 1
	0	-	-	0	1

$x_1 x_0$		Y			
		00	01	11	10
x_3	0	0	1	0	1
	0	-	-	0	1
x_2	0	4	5	7	6
	1	0	1	1	0
x_1	1	12	13	15	14
	1	0	1	0	1
x_0	1	8	9	11	10
	0	-	-	0	1
 
$$Y = \bar{x}_2 \bar{x}_0 + \bar{x}_1 x_0 + x_1 \bar{x}_0 x_3 + \bar{x}_3 x_2 x_0$$



$x_1 x_0$		Y			
		00	01	11	10
x_3	0	0	1	3	2
	0	-	-	0	1
x_2	0	4	5	7	6
	1	0	1	1	0
x_1	1	12	13	15	14
	1	0	1	0	1
x_0	1	8	9	11	10
	0	-	-	0	1

x_0		0	1
x_1	0		
	1		

$x_3 x_2(0,0) \Rightarrow$

x_0		0	1
x_1	0		
	1		


$x_3 x_2(0,1) \Rightarrow$

x_0		0	1
x_1	0		
	1		

$x_3 x_2(1,1) \Rightarrow$

x_0		0	1
x_1	0		
	1		

$x_3 x_2(1,0) \Rightarrow$

 

$x_1 x_0$		Y			
		00	01	11	10
x_3	0	0	1	3	2
	0	-	-	0	1
x_2	0	4	5	7	6
	1	0	1	1	0
x_1	1	12	13	15	14
	1	0	1	0	1
x_0	1	8	9	11	10
	0	-	-	0	1

x_0		0	1
x_1	0	-	-
	1	1	0

$x_3 x_2(0,0) \Rightarrow$

x_0		0	1
x_1	0	0	1
	1	0	1


$x_3 x_2(0,1) \Rightarrow$

x_0		0	1
x_1	0	0	1
	1	1	0

$x_3 x_2(1,1) \Rightarrow$


x_0		0	1
x_1	0	-	-
	1	1	0

$x_3 x_2(1,0) \Rightarrow$

 

$x_1 x_0$		Y			
x_3	x_2	00	01	11	10
0	0	0	1	3	2
0	1	4	5	7	6
1	1	12	13	15	14
1	0	8	9	11	10
		-	-	0	1
 
$$Y = \bar{x}_2 \bar{x}_0 + \bar{x}_1 x_0 + x_1 \bar{x}_0 x_3 + \bar{x}_3 x_2 x_0$$



x_1	x_0	0	1
0		-	-
1		1	0

$$x_3 x_2 (0,0) \Rightarrow$$

$$Y = \bar{x}_0$$

x_1	x_0	0	1
0		0	1
1		0	1

$$x_3 x_2 (0,1) \Rightarrow$$

$$Y = x_0$$

x_1	x_0	0	1
0		0	1
1		1	0

$$x_3 x_2 (1,1) \Rightarrow$$

$$Y = x_1 \oplus x_0$$


x_1	x_0	0	1
0		-	-
1		1	0

$$x_3 x_2 (1,0) \Rightarrow$$

$$Y = \bar{x}_0$$

$x_1 x_0$		Y			
x_3	x_2	00	01	11	10
0	0	0	1	3	2
0	1	4	5	7	6
1	1	12	13	15	14
1	0	8	9	11	10
		-	-	0	1
 
$$Y = \bar{x}_2 \bar{x}_0 + \bar{x}_1 x_0 + x_1 \bar{x}_0 x_3 + \bar{x}_3 x_2 x_0$$



Or ...

x_1	x_0	0	1
0		-	-
1		1	0

$$x_3 x_2 (0,0) \Rightarrow$$

$$Y = x_1 \oplus x_0$$

x_1	x_0	0	1
0		0	1
1		0	1

$$x_3 x_2 (0,1) \Rightarrow$$

$$Y = x_0$$

x_1	x_0	0	1
0		0	1
1		1	0

$$x_3 x_2 (1,1) \Rightarrow$$

$$Y = x_1 \oplus x_0$$

x_1	x_0	0	1
0		-	-
1		1	0

$$x_3 x_2 (1,0) \Rightarrow$$

$$Y = x_1 \oplus x_0$$

Or if you don't have access to the variable x_0 inverted ...

