
 


# VHDL testbänk

## Mall-programmets funktion


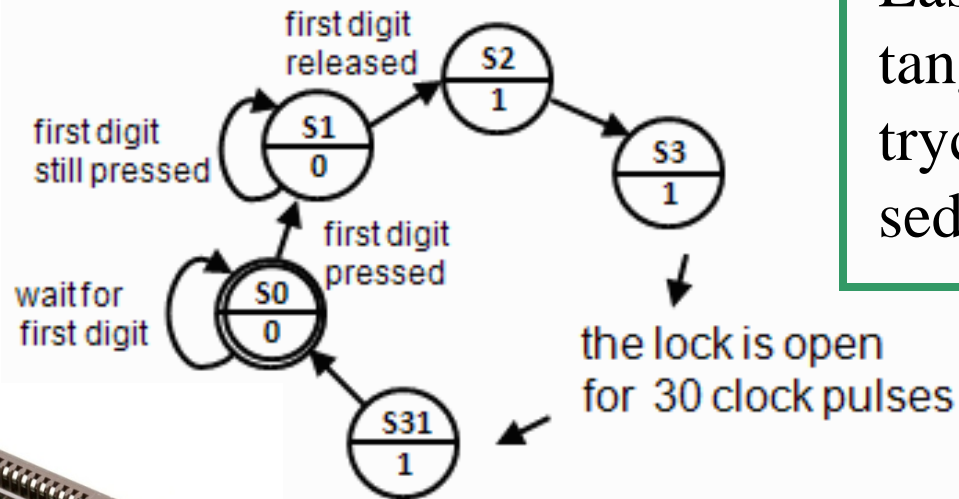


Låset öppnas när tangenten "1" trycks ned och sedan släpps.


  
# Keypad och Statecounter

*Bra val av datatyper gör koden självförklarande!*



`K: in std_logic_vector(1 to 3);`

`R: in std_logic_vector(1 to 4);`

`1 2 3`  
`K = "001" bitvector`

`K(3) = '1' bit`

`1 2 3 4`  
`R = "0001" bitvector`

`R(4) = '1' bit`

Statecounter: `4 3 2 1 0`  
`q = "00001" bitvektor`  
`q(0) = '1' bit`

# lockmall.vhd

This code is given



```
library IEEE;
use IEEE.std_logic_1164.all;
use IEEE.std_logic_arith.all;

entity codelock is
  port( clk:      in  std_logic;
        K:      in  std_logic_vector(1 to 3);
        R:      in  std_logic_vector(1 to 4);
        q:      out std_logic_vector(4 downto 0);
        UNLOCK: out std_logic );
end codelock;
```

```
architecture behavior of codelock is
  subtype state_type is integer range 0 to 31;
  signal state, nextstate: state_type;
```

```
begin
  nextstate_decoder: -- next state decoding part
  process(state, K, R)
  begin
```


```
    case state is
      when 0 => if (K = "100" and R ="0001")    then nextstate <= 1;
                else nextstate <= 0;
                end if;
      when 1 => if (K = "100" and R ="0001")    then nextstate <= 1;
                elsif (K = "000" and R = "0000") then nextstate <= 2;
                else nextstate <= 0;
                end if;
      when 2 to 30 => nextstate <= state + 1;
      when 31      => nextstate <= 0;
    end case;
  end process;
```

```
  debug_output: -- display the state
  q <= conv_std_logic_vector(state,5);
```

```
  output_decoder: -- output decoder part
  process(state)
  begin
    case state is
      when 0 to 1  => UNLOCK <= '0';
      when 2 to 31 => UNLOCK <= '1';
    end case;
  end process;
```

```
  state_register: -- the state register part (the flipflops)
  process(clk)
  begin
    if rising_edge(clk) then
      state <= nextstate;
    end if;
  end process;
end behavior;
```

*It's easy to see that this is correct!*

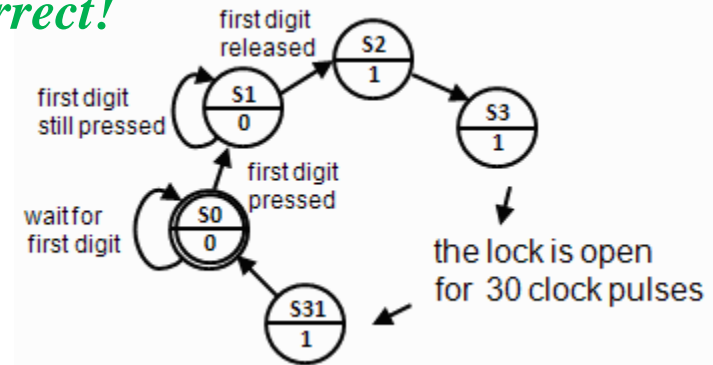

# lockmall\_with\_error.vhd

```
library IEEE;
use IEEE.std_logic_1164.all;
use IEEE.std_logic_arith.all;

entity codelock is
  port( clk:      in  std_logic;
        K:        in  std_logic_vector(1 to 3);
        R:        in  std_logic_vector(1 to 4);
        q:        out std_logic_vector(4 downto 0);
        UNLOCK:   out std_logic );
end codelock;

architecture behavior of codelock is
  subtype state_type is integer range 0 to 31;
  signal state, nextstate: state_type;

begin
  nextstate_decoder: -- next state decoding part
  begin
  nextstate_decoder: -- next state decoding part
  process(state, K, R)
  begin
    case state is
      when 0 => if(((R(2)='0') and (R(3)='0') and (K(2)='0') and (K(3)='1')) and
                  ( not (( not ((K(1)='0') and (R(1)='0') and (R(4)='1')) and
                              ( not ((K(1)='1') and (R(1)='1') and (R(4)='0'))))))))
                  then nextstate <= 1;
                  else nextstate <= 0;
                  end if;
      when 1 => if(((R(2)='0') and (R(3)='0') and (K(2)='0') and (K(3)='1')) and
                  ( not (( not ((K(1)='0') and (R(1)='0') and (R(4)='1')) and
                              ( not ((K(1)='1') and (R(1)='1') and (R(4)='0'))))))))
                  then nextstate <= 1;
                  elsif (K = "000" and R = "0000") then nextstate <= 2;
                  else nextstate <= 0;
                  end if;
      when 2 to 30 => nextstate <= state + 1;
      when 31      => nextstate <= 0;
    end case;
  end process;

  debug_output: -- display the state
  q <= conv_std_logic_vector(state,5);

  output_decoder: -- output decoder part
  process(state)
  begin
    case state is
      when 0 to 1 => UNLOCK <= '0';
      when 2 to 31 => UNLOCK <= '1';
    end case;
  end process;

  state_register: -- the state register part (the flipflops)
  process(clk)
  begin
    if rising_edge(clk) then
      state <= nextstate;
    end if;
  end process;
end behavior;
```

*Now it's hard to see if this is correct or not?*

# lockmall\_with\_error.vhd

*Betyder båda uttrycken samma sak?*

```
( K = "100" and R = "0001" )
```

*Är verkligen detta samma sak?*

```
((R(2)='0') and (R(3)='0') and (K(2)='0') and (K(3)='1')) and  
( not (( not ((K(1)='0') and (R(1)='0') and (R(4)='1')))) and  
( not ((K(1)='1') and (R(1)='1') and (R(4)='0'))))))
```

*Någon "lovar" att koden är korrekt – men hur kan man veta att detta är absolut sant?*

# Testbench

thank's to: *Francesco Robino*

**tb\_lockmall.vhd**

# tb\_lockmall.vhd

Vi behöver skriva en VHDL-testbench

Ett testbänksprogram kan testa alla möjliga tangentkombinationer och rapportera om det uppstår något problem ...

Det kan automatiskt loopa igenom all möjliga tangenttryckningar och rapportera om om låset försöker att öppna.

Det finns  $2^7 = 128$  möjliga tangentkombinationer och vi skulle bli helt uttröttade om vi försökte att prova dem alla för hand.

# **entity – en testbänk har inga portar**

```
entity tb_codelock is  
  -- entity tb_codelock has no ports  
  -- because it's for simulation only  
end tb_codelock;
```




# Några interna signaler behövs

```
signal          clk : std_logic := '0';
signal          K_test : std_logic_vector(1 to 3);
signal          R_test : std_logic_vector(1 to 4);
signal prev_K_test : std_logic_vector(1 to 3);
signal prev_R_test : std_logic_vector(1 to 4);
signal          q : std_logic_vector(4 downto 0);
signal          unlock : std_logic;
```

# Vårt codeLock används som component

```
-- we use our codeLock as a component
component codeLock
  port( clk : in std_logic;
        K : in std_logic_vector(1 to 3);
        R : in std_logic_vector(1 to 4);
        q : out std_logic_vector(4 downto 0);
        UNLOCK : out std_logic );
end component;
```

# Genera en simuleringsklocka

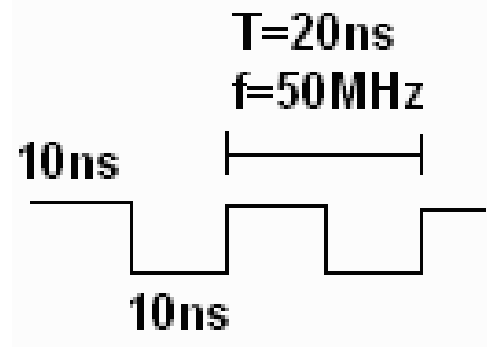


```
-- generate a simulation clock  
clk <= not clk after 10 ns;
```

# Instantiatiering och signal mapping

```
-- instantiation of the device under test,  
-- mapping of signals  
inst_codelock:  
  codelock  
  port map (  
      clk => clk,  
      K  => K_test,  
      R  => R_test,  
      q  => q,  
      UNLOCK => unlock );
```
 
# En nästlad slinga skapar tangentryckningarna



```
process
begin
  for k in 0 to 7 loop
    K_test <= conv_std_logic_vector(k,3);
16  for r in 0 to 15 loop
    prev_K_test <= K_test;
    prev_R_test <= R_test;
    R_test <= conv_std_logic_vector(r,4);
    wait until CLK='1';
  end loop;
end loop;
end process;
```



8·16=128 turns

# report, severity **note**, severity **error**

*Tests if state  $q = "00001"$  will be reached by any combination.*

check:

```
process(q)
begin if ((q = "00001") and
          (prev_K_test = conv_std_logic_vector(1,3)) and
          (prev_R_test = conv_std_logic_vector(1,4)))
  then assert false report
    "Lock tries to open for the right sequence!"
    severity note;
  else if ((q = "00001"))
  then
    assert false report
    "Lock tries to open with the wrong sequence!"
    severity error;
  else report "Lock closed!" severity note;
  end if;
end if;
end process check;
```

  

# *Simulera och hitta felet!*

Vad annat än att trycka på ”1” tangenten skulle kunna öppna låset?

?

