

Ex. 8.4 7-4-2-1 code

Codeconverter 7-4-2-1-code to BCD-code.

When encoding the digits 0 ... 9 sometimes in the past a code having weights 7-4-2-1 instead of the binary code weights 8-4-2-1 was used.

In the cases where a digit's code word can be expressed in various ways the code word that contains the least number of ones is selected

(A variation of the 7-4-2-1 code is used today to store the bar code)



	7	4	2	1		8	4	2	1
	x_7	x_4	x_2	x_1		y_8	y_4	y_2	y_1
(0)	0	0	0	0	0	0	0	0	0
(1)	0	0	0	1	1	0	0	0	1
(2)	0	0	1	0	2	0	0	1	0
(3)	0	0	1	1	3	0	0	1	1
(4)	0	1	0	0	4	0	1	0	0
(5)	0	1	0	1	5	0	1	0	1
(6)	0	1	1	0	6	0	1	1	0
					7	0	1	1	1
					8	1	0	0	0
					9	1	0	0	1

Ex. 8.4 7-4-2-1 code

Codeconverter 7-4-2-1-code to BCD-code.

When encoding the digits 0 ... 9 sometimes in the past a code having weights 7-4-2-1 instead of the binary code weights 8-4-2-1 was used.

In the cases where a digit's code word can be expressed in various ways the code word that contains the least number of ones is selected

(A variation of the 7-4-2-1 code is used today to store the bar code)



	7	4	2	1		8	4	2	1
	x_7	x_4	x_2	x_1		y_8	y_4	y_2	y_1
(0)	0	0	0	0	0	0	0	0	0
(1)	0	0	0	1	1	0	0	0	1
(2)	0	0	1	0	2	0	0	1	0
(3)	0	0	1	1	3	0	0	1	1
(4)	0	1	0	0	4	0	1	0	0
(5)	0	1	0	1	5	0	1	0	1
(6)	0	1	1	0	6	0	1	1	0
(8)	1	0	0	0	7	0	1	1	1
(9)	1	0	0	1	8	1	0	0	0
					9	1	0	0	1

Ex. 8.4 7-4-2-1 code

Codeconverter 7-4-2-1-code to BCD-code.

When encoding the digits 0 ... 9 sometimes in the past a code having weights 7-4-2-1 instead of the binary code weights 8-4-2-1 was used.

In the cases where a digit's code word can be expressed in various ways the code word that contains the least number of ones is selected

(A variation of the 7-4-2-1 code is used today to store the bar code)



	7	4	2	1		8	4	2	1
	x_7	x_4	x_2	x_1		y_8	y_4	y_2	y_1
(0)	0	0	0	0	0	0	0	0	0
(1)	0	0	0	1	1	0	0	0	1
(2)	0	0	1	0	2	0	0	1	0
(3)	0	0	1	1	3	0	0	1	1
(4)	0	1	0	0	4	0	1	0	0
(5)	0	1	0	1	5	0	1	0	1
(6)	0	1	1	0	6	0	1	1	0
(8)	1	0	0	0	7	0	1	1	1
(9)	1	0	0	1	8	1	0	0	0
(10)	1	0	1	0	9	1	0	0	1

8.4

	7	4	2	1		8	4	2	1
	x_7	x_4	x_2	x_1		y_8	y_4	y_2	y_1
(0)	0	0	0	0	0	0	0	0	0
(1)	0	0	0	1	1	0	0	0	1
(2)	0	0	1	0	2	0	0	1	0
(3)	0	0	1	1	3	0	0	1	1
(4)	0	1	0	0	4	0	1	0	0
(5)	0	1	0	1	5	0	1	0	1
(6)	0	1	1	0	6	0	1	1	0
(8)	1	0	0	0	7	0	1	1	1
(9)	1	0	0	1	8	1	0	0	0
(10)	1	0	1	0	9	1	0	0	1

y_8

x_7	x_4	x_2	x_1	
0	0	0	0	0
0	0	0	1	1
0	0	1	0	2
0	0	1	1	3
0	1	0	0	4
0	1	0	1	5
0	1	1	0	6
0	1	1	1	7
1	0	0	0	8
1	0	0	1	9
1	0	1	0	10
1	0	1	1	11
1	1	0	0	12
1	1	0	1	13
1	1	1	0	14
1	1	1	1	15

y_4

x_7	x_4	x_2	x_1	
0	0	0	0	0
0	0	0	1	1
0	0	1	0	2
0	0	1	1	3
0	1	0	0	4
0	1	0	1	5
0	1	1	0	6
0	1	1	1	7
1	0	0	0	8
1	0	0	1	9
1	0	1	0	10
1	0	1	1	11
1	1	0	0	12
1	1	0	1	13
1	1	1	0	14
1	1	1	1	15

y_2

x_7	x_4	x_2	x_1	
0	0	0	0	0
0	0	0	1	1
0	0	1	0	2
0	0	1	1	3
0	1	0	0	4
0	1	0	1	5
0	1	1	0	6
0	1	1	1	7
1	0	0	0	8
1	0	0	1	9
1	0	1	0	10
1	0	1	1	11
1	1	0	0	12
1	1	0	1	13
1	1	1	0	14
1	1	1	1	15

y_1

x_7	x_4	x_2	x_1	
0	0	0	0	0
0	0	0	1	1
0	0	1	0	2
0	0	1	1	3
0	1	0	0	4
0	1	0	1	5
0	1	1	0	6
0	1	1	1	7
1	0	0	0	8
1	0	0	1	9
1	0	1	0	10
1	0	1	1	11
1	1	0	0	12
1	1	0	1	13
1	1	1	0	14
1	1	1	1	15

8.4

	7	4	2	1		8	4	2	1
	x_7	x_4	x_2	x_1		y_8	y_4	y_2	y_1
(0)	0	0	0	0	0	0	0	0	0
(1)	0	0	0	1	1	0	0	0	1
(2)	0	0	1	0	2	0	0	1	0
(3)	0	0	1	1	3	0	0	1	1
(4)	0	1	0	0	4	0	1	0	0
(5)	0	1	0	1	5	0	1	0	1
(6)	0	1	1	0	6	0	1	1	0
(8)	1	0	0	0	7	0	1	1	1
(9)	1	0	0	1	8	1	0	0	0
(10)	1	0	1	0	9	1	0	0	1

y_8

x_7	x_4	x_2	x_1	
0	0	0	0	00
0	0	0	1	01
0	0	1	0	11
0	0	1	1	10
0	1	0	0	40
0	1	0	1	41
0	1	1	0	50
0	1	1	1	51
1	0	0	0	12
1	0	0	1	13
1	0	1	0	15
1	0	1	1	14
1	1	0	0	80
1	1	0	1	81
1	1	1	0	90
1	1	1	1	91

y_4

x_7	x_4	x_2	x_1	
0	0	0	0	00
0	0	0	1	01
0	0	1	0	11
0	0	1	1	10
0	1	0	0	40
0	1	0	1	41
0	1	1	0	50
0	1	1	1	51
1	0	0	0	12
1	0	0	1	13
1	0	1	0	15
1	0	1	1	14
1	1	0	0	80
1	1	0	1	81
1	1	1	0	90
1	1	1	1	91

y_2


x_7	x_4	x_2	x_1	
0	0	0	0	00
0	0	0	1	01
0	0	1	0	11
0	0	1	1	10
0	1	0	0	40
0	1	0	1	41
0	1	1	0	50
0	1	1	1	51
1	0	0	0	12
1	0	0	1	13
1	0	1	0	15
1	0	1	1	14
1	1	0	0	80
1	1	0	1	81
1	1	1	0	90
1	1	1	1	91

y_1

x_7	x_4	x_2	x_1	
0	0	0	0	00
0	0	0	1	01
0	0	1	0	11
0	0	1	1	10
0	1	0	0	40
0	1	0	1	41
0	1	1	0	50
0	1	1	1	51
1	0	0	0	12
1	0	0	1	13
1	0	1	0	15
1	0	1	1	14
1	1	0	0	80
1	1	0	1	81
1	1	1	0	90
1	1	1	1	91

8.4

	7	4	2	1		8	4	2	1
	x_7	x_4	x_2	x_1		y_8	y_4	y_2	y_1
(0)	0	0	0	0		0	0	0	0
(1)	0	0	0	1		1	0	0	1
(2)	0	0	1	0		2	0	0	1
(3)	0	0	1	1		3	0	0	1
(4)	0	1	0	0		4	0	1	0
(5)	0	1	0	1		5	0	1	0
(6)	0	1	1	0		6	0	1	1
(8)	1	0	0	0		7	0	1	1
(9)	1	0	0	1		8	1	0	0
(10)	1	0	1	0		9	1	0	1

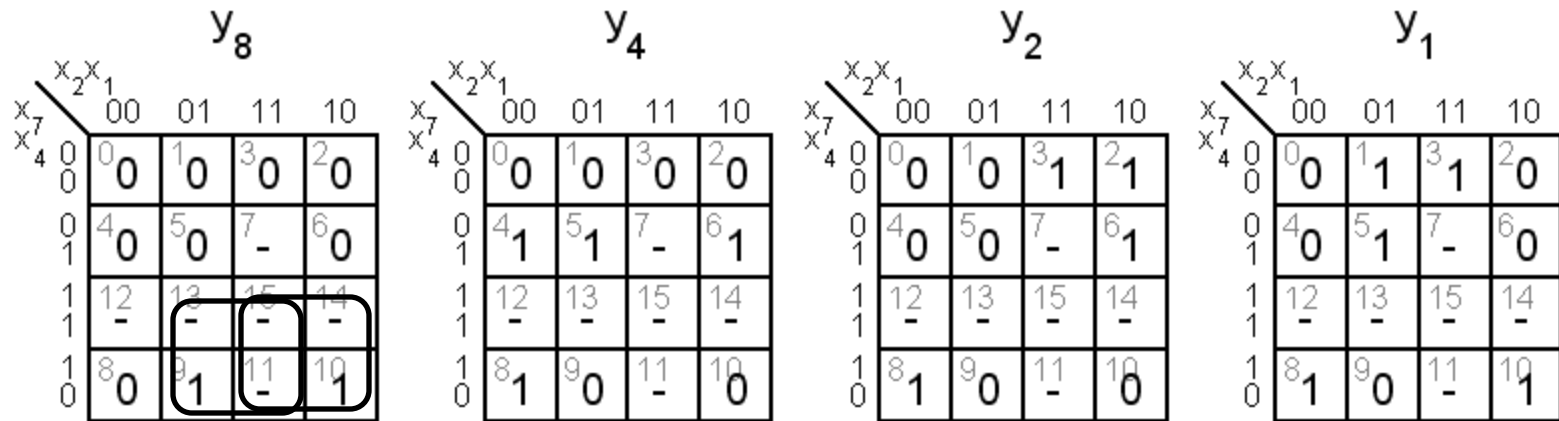

$$y_8 = x_7x_2 + x_7x_1$$

8.4

	7	4	2	1		8	4	2	1
	x_7	x_4	x_2	x_1		y_8	y_4	y_2	y_1
(0)	0	0	0	0	0	0	0	0	0
(1)	0	0	0	1	1	0	0	0	1
(2)	0	0	1	0	2	0	0	1	0
(3)	0	0	1	1	3	0	0	1	1
(4)	0	1	0	0	4	0	1	0	0
(5)	0	1	0	1	5	0	1	0	1
(6)	0	1	1	0	6	0	1	1	0
(8)	1	0	0	0	7	0	1	1	1
(9)	1	0	0	1	8	1	0	0	0
(10)	1	0	1	0	9	1	0	0	1

y_8

x_7	x_4	x_2	x_1	
0	0	01	11	10
0	0	0	0	0
0	0	1	0	0
1	4	5	7	6
1	0	0	-	0
1	12	13	15	14
1	-	-	-	-
1	8	9	11	10
0	0	1	-	1

y_4

x_7	x_4	x_2	x_1	
0	0	01	11	10
0	0	0	0	0
0	0	1	0	0
1	4	5	7	6
1	1	1	-	1
1	12	13	15	14
1	-	-	-	-
1	8	9	11	10
0	1	0	-	0

y_2

x_7	x_4	x_2	x_1	
0	0	01	11	10
0	0	0	0	0
0	0	1	0	0
1	4	5	7	6
1	0	0	-	1
1	12	13	15	14
1	-	-	-	-
1	8	9	11	10
0	1	0	-	0

y_1


x_7	x_4	x_2	x_1	
0	0	01	11	10
0	0	0	0	0
0	0	1	0	0
1	4	5	7	6
1	0	1	-	0
1	12	13	15	14
1	-	-	-	-
1	8	9	11	10
0	1	0	-	1

$$y_8 = x_7 x_2 + x_7 x_1$$


$$y_4 = x_4 + x_7 x_2 x_1$$

8.4


	7	4	2	1		8	4	2	1
	x_7	x_4	x_2	x_1		y_8	y_4	y_2	y_1
(0)	0	0	0	0	0	0	0	0	0
(1)	0	0	0	1	1	0	0	0	1
(2)	0	0	1	0	2	0	0	1	0
(3)	0	0	1	1	3	0	0	1	1
(4)	0	1	0	0	4	0	1	0	0
(5)	0	1	0	1	5	0	1	0	1
(6)	0	1	1	0	6	0	1	1	0
(8)	1	0	0	0	7	0	1	1	1
(9)	1	0	0	1	8	1	0	0	0
(10)	1	0	1	0	9	1	0	0	1

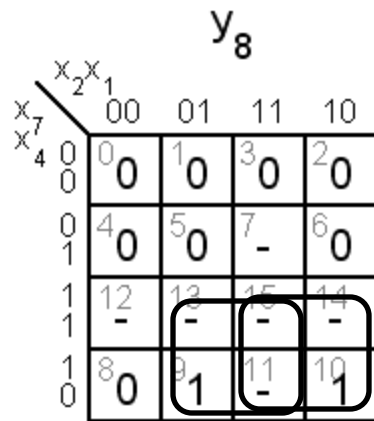


$$y_8 = x_7 x_2 + x_7 x_1$$

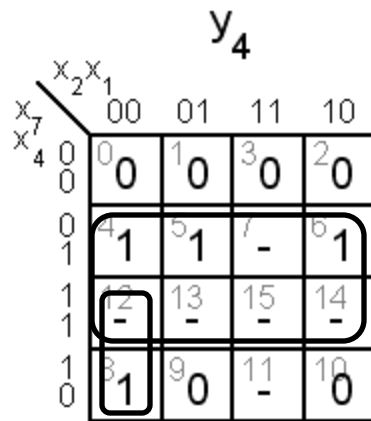

$$y_4 = x_4 + x_7 x_2 x_1$$

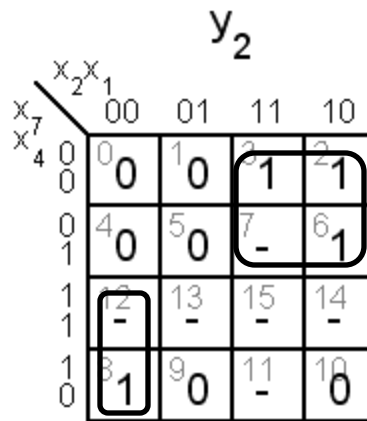

$$y_2 = x_7 x_2 + x_7 x_2 x_1$$

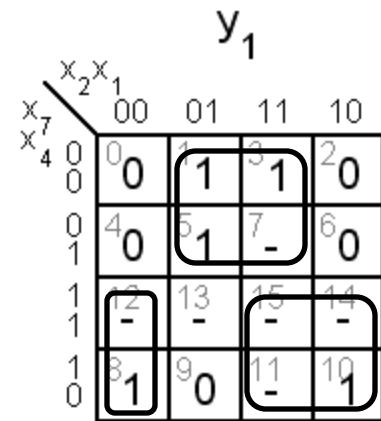


$$y_1 = x_7 x_1 + x_7 x_2 + x_7 x_2 x_1$$

8.4

Common groupings can provide for shared gates!

	7	4	2	1		8	4	2	1
	x_7	x_4	x_2	x_1		y_8	y_4	y_2	y_1
(0)	0	0	0	0	0	0	0	0	0
(1)	0	0	0	1	1	0	0	0	1
(2)	0	0	1	0	2	0	0	1	0
(3)	0	0	1	1	3	0	0	1	1
(4)	0	1	0	0	4	0	1	0	0
(5)	0	1	0	1	5	0	1	0	1
(6)	0	1	1	0	6	0	1	1	0
(8)	1	0	0	0	7	0	1	1	1
(9)	1	0	0	1	8	1	0	0	0
(10)	1	0	1	0	9	1	0	0	1

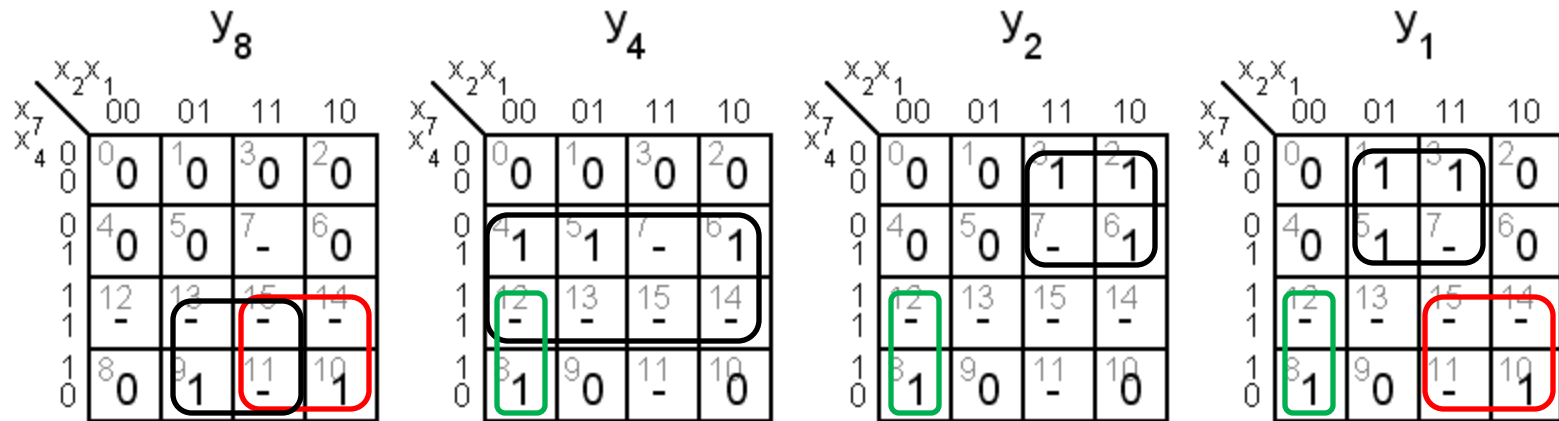

$$y_8 = x_7 x_2 + x_7 x_1$$


$$y_4 = x_4 + x_7 x_2 x_1$$

$$y_2 = x_7 x_2 + x_7 x_2 x_1$$

$$y_1 = x_7 x_1 + x_7 x_2 + x_7 x_2 x_1$$

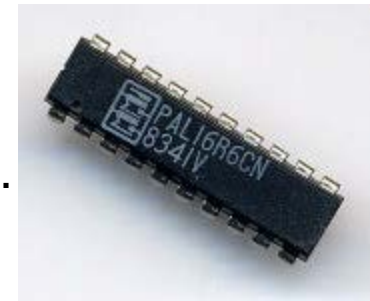
8.4

PLA circuits containing programmable AND and OR gates. (This turned out to be unnecessarily complex, so the common chips became PAL circuits with only the AND network programmable).




The gates have many programmable input connections. The many inputs are usually drawn in a "simplified" way.

Programmerbar logik

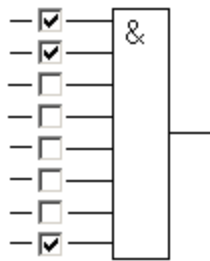

förenklat ritsätt för 8 ingångars grind

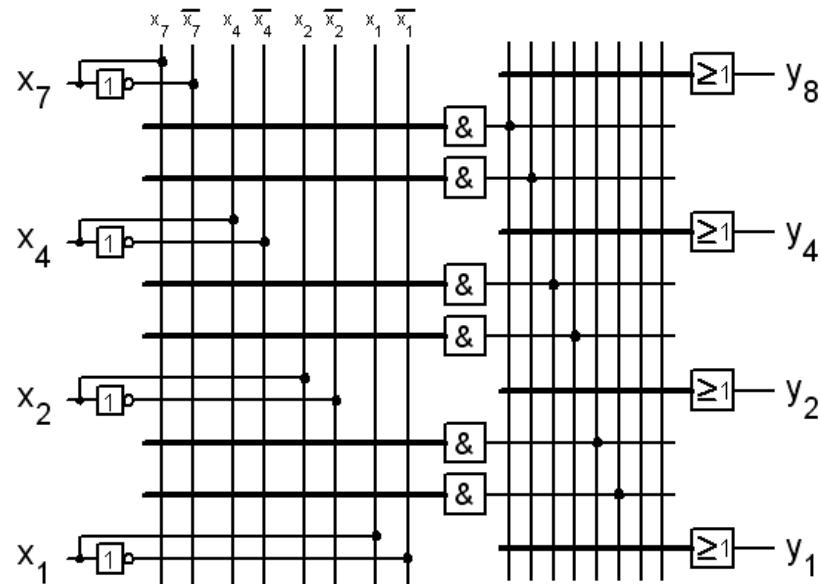

8.4


$$y_8 = x_7 x_2 + x_7 x_1$$

$$y_4 = x_4 + x_7 x_2 x_1$$

$$y_2 = \overline{x_7} x_2 + x_7 \overline{x_2} x_1$$

$$y_1 = \overline{x_7} x_1 + x_7 x_2 + x_7 \overline{x_2} x_1$$

Shared-gates!

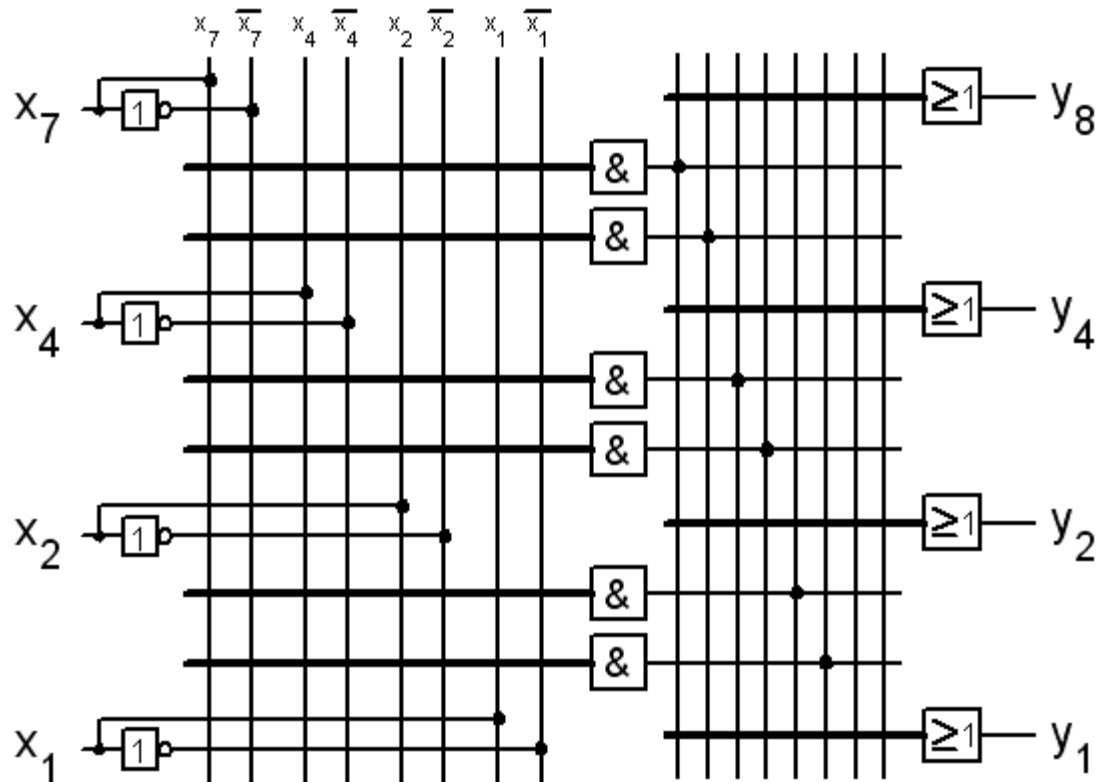

8.4


$$y_8 = x_7 x_2 + x_7 x_1$$

$$y_4 = x_4 + x_7 x_2 x_1$$

$$y_2 = \bar{x}_7 x_2 + x_7 \bar{x}_2 x_1$$

$$y_1 = \bar{x}_7 x_1 + x_7 x_2 + x_7 \bar{x}_2 x_1$$

Shared-gates!

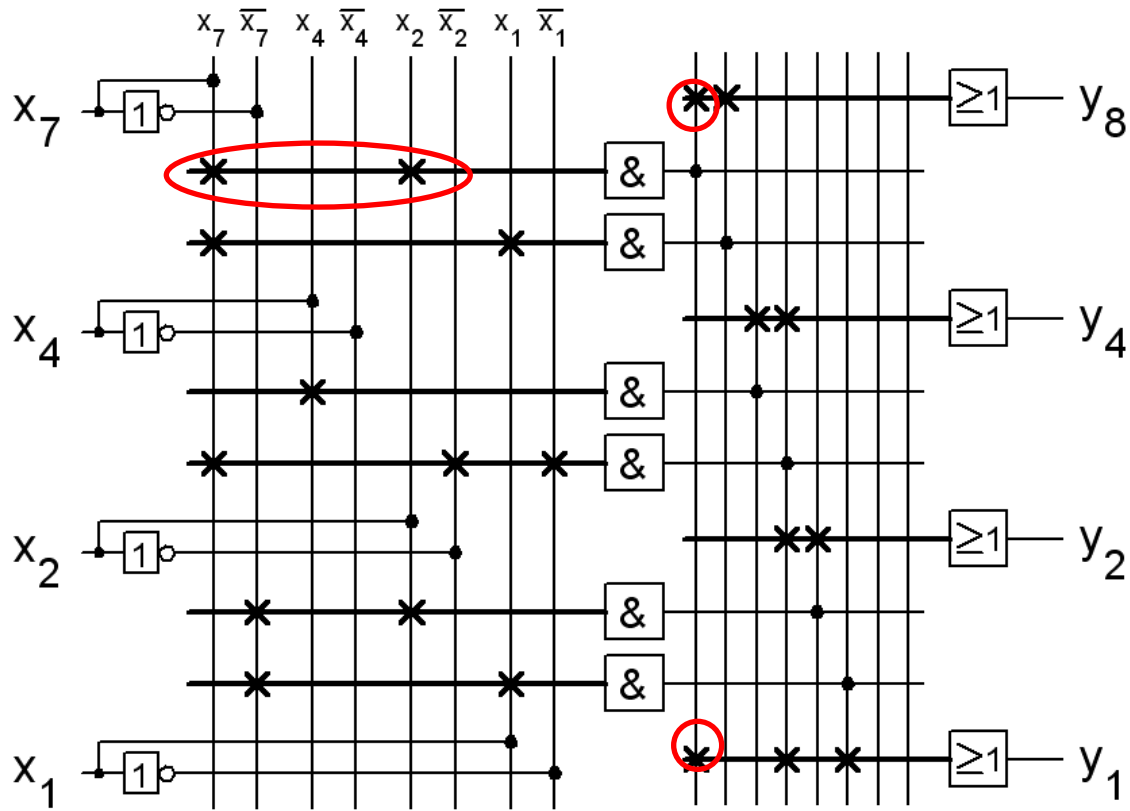

8.4


$$y_8 = x_7 x_2 + x_7 x_1$$

$$y_4 = x_4 + x_7 \overline{x_2} \overline{x_1}$$

$$y_2 = \overline{x_7} x_2 + x_7 \overline{x_2} \overline{x_1}$$

$$y_1 = \overline{x_7} x_1 + x_7 x_2 + x_7 \overline{x_2} \overline{x_1}$$

Shared-gates!

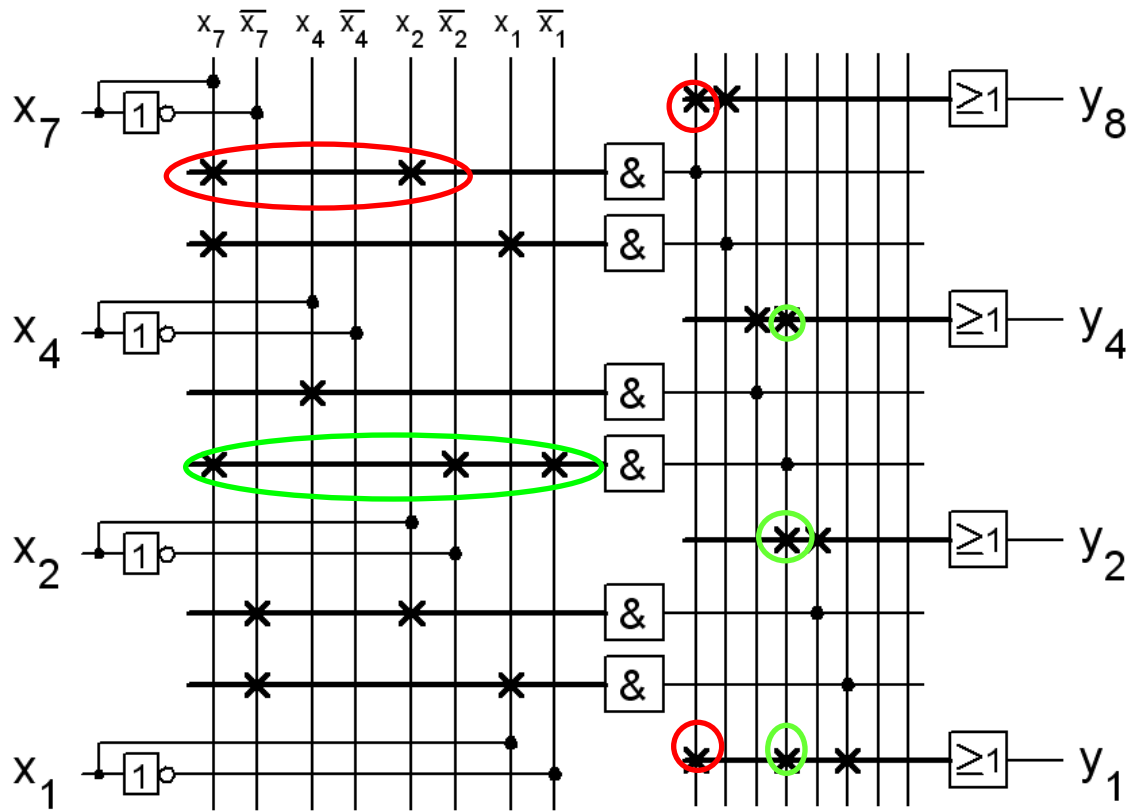

Real numbers

Decimal comma “,” and Binary point “.”

$$10,3125_{10} = 1010.0101_2$$

Bin \rightarrow Dec

1 0 1 0 . 0 1 0 1

2^3 2^2 2^1 2^0 . 2^{-1} 2^{-2} 2^{-3} 2^{-4}

8 4 2 1 0,5 0,25 0,125 0,0625

$$8 + 0 + 2 + 0 + 0 + 0,25 + 0 + 0,0625 = 10,3125$$

Ex. 1.2b


$$110100.010_2 =$$

Ex. 1.2b

$$\begin{aligned} 110100.010_2 &= \\ &= (2^5 + 2^4 + 2^2 + 2^{-2} = 32 + 16 + 4 + 0.25) = \\ &= 52,25_{10} \end{aligned}$$

Calculation with complement

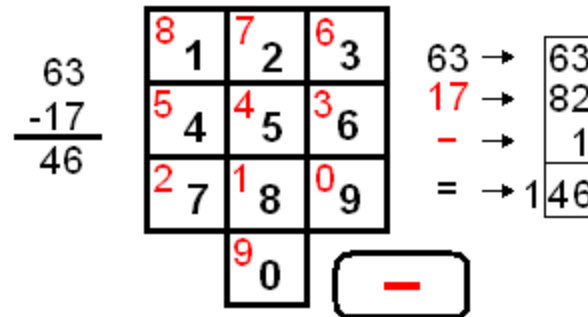Subtraction with an adding machine = counting with the complement




$$63 - 17 = 46$$

The number -17 is entered with red digits 17 and gets 82. When the - key is pressed 1 is added. The result is: $63 + 82 + 1 = 146$. If only two digits are shown: 46



2-complement

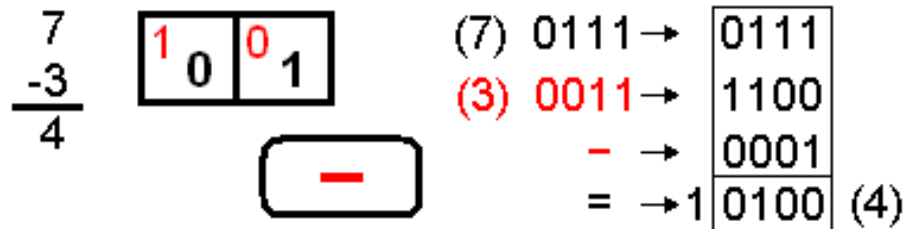

The binary number 3, 0011, gets negative -3 if one inverts the digits and adds one, 1101.

Register arithmetic


- Computer registers are "rings"



A four bit register could contain $2^4 = 16$ numbers.

Either 8 positive (+0...+7) and 8 negative (-1...-8) "signed integers", or 16 (0...F) "unsigned integers".

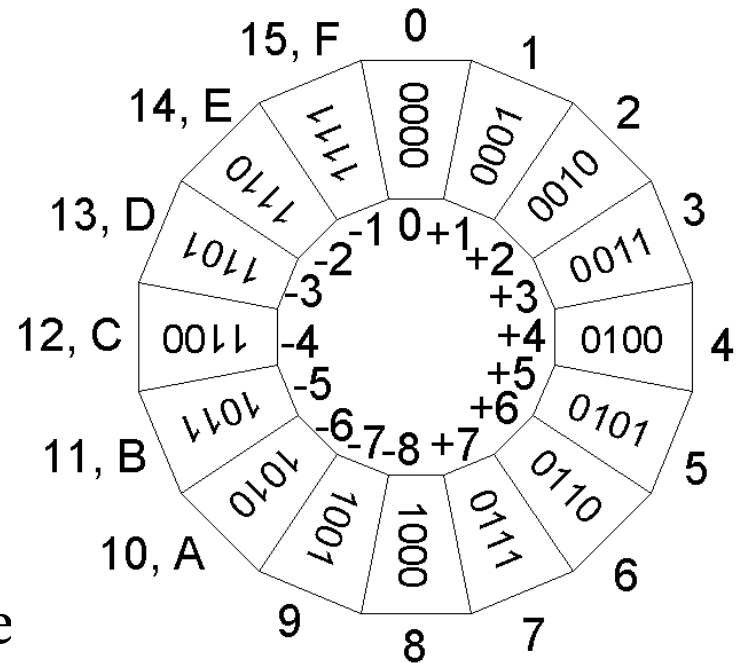If the register is full +1 makes the register to the "turn around".



Register width

- 4 bit is called a **Nibble**. The register contains $2^4 = 16$ numbers. $0 \dots 15$, $-8 \dots +7$
- 8 bit is called a **Byte**. The register contains $2^8 = 256$ numbers $0 \dots 255$, $-128 \dots +127$
- 16 bit is a **Word**. $2^{16} = 65536$ numbers.
 $0 \dots 65535$, $-32768 \dots +32767$

Today, general sizes are now 32 bits (Double Word) and 64 bits (Quad Word)..

Ex. 1.8

Write the following signed numbers with two's complement notation, $x = (x_6, x_5, x_4, x_3, x_2, x_1, x_0)$.

a) -23

b) -1 =

c) +38 =

d) -64 =

Ex. 1.8

Write the following signed numbers with two's complement notation, $x = (x_6, x_5, x_4, x_3, x_2, x_1, x_0)$.

a) $-23 = (+23_{10} = 0010111_2 \rightarrow -23_{10} = 1101000_2 + 1_2) = 1101001_2$
 $= 105_{10}$

b) $-1 =$

c) $+38 =$

d) $-64 =$

Ex. 1.8

Write the following signed numbers with two's complement notation, $x = (x_6, x_5, x_4, x_3, x_2, x_1, x_0)$.

$$\text{a) } -23 = (+23_{10} = 0010111_2 \rightarrow -23_{10} = 1101000_2 + 1_2) = 1101001_2 = 105_{10}$$

$$\text{b) } -1 = (+1_{10} = 0000001_2 \rightarrow -1_{10} = 1111110_2 + 1_2) = 1111111_2 = 127_{10}$$

$$\text{c) } +38 =$$

$$\text{d) } -64 =$$

Ex. 1.8

Write the following signed numbers with two's complement notation, $x = (x_6, x_5, x_4, x_3, x_2, x_1, x_0)$.

$$\text{a) } -23 = (+23_{10} = 0010111_2 \rightarrow -23_{10} = 1101000_2 + 1_2) = 1101001_2 = 105_{10}$$

$$\text{b) } -1 = (+1_{10} = 0000001_2 \rightarrow -1_{10} = 1111110_2 + 1_2) = 1111111_2 = 127_{10}$$

$$\text{c) } +38 = (32_{10} + 4_{10} + 2_{10}) = 0100110_2 = 38_{10}$$

$$\text{d) } -64 =$$

Ex. 1.8

Write the following signed numbers with two's complement notation, $x = (x_6, x_5, x_4, x_3, x_2, x_1, x_0)$.

$$\text{a) } -23 = (+23_{10} = 0010111_2 \rightarrow -23_{10} = 1101000_2 + 1_2) = 1101001_2 = 105_{10}$$

$$\text{b) } -1 = (+1_{10} = 0000001_2 \rightarrow -1_{10} = 1111110_2 + 1_2) = 1111111_2 = 127_{10}$$

$$\text{c) } +38 = (32_{10} + 4_{10} + 2_{10}) = 0100110_2 = 38_{10}$$

$$\text{d) } -64 = (+64_{10} = 1000000_2 \text{ är ett för stort positivt tal!} \\ \text{men fungerar ändå } -64_{10} \rightarrow 0111111_2 + 1_2) = 1000000_2 = 64_{10}$$

Ex. 2.1


a) $110 + 010$ b) $1110 + 1001$

c) $11\ 0011.01 + 111.1$ d) $0.1101 + 0.1110$


$$\begin{array}{r} \text{a)} \quad \begin{array}{r} \frac{1}{1} \frac{1}{1} 1 0 \\ + 0 1 0 \\ \hline 1 0 0 0 \end{array} \quad \text{b)} \quad \begin{array}{r} \frac{1}{1} 1 1 1 0 \\ + 1 0 0 1 \\ \hline 1 0 1 1 1 \end{array} \end{array}$$

$$\begin{array}{r} \text{c)} \quad \begin{array}{r} 1 1 \frac{1}{0} \frac{1}{0} \frac{1}{1} 1.0 1 \\ + \quad \quad \quad 1 1 1.1 \\ \hline 1 1 1 0 1 0.1 1 \end{array} \quad \text{d)} \quad \begin{array}{r} \frac{1}{0.1} \frac{1}{1} 1 0 1 \\ + 0.1 1 1 0 \\ \hline 1.1 0 1 1 \end{array} \end{array}$$

Full adder

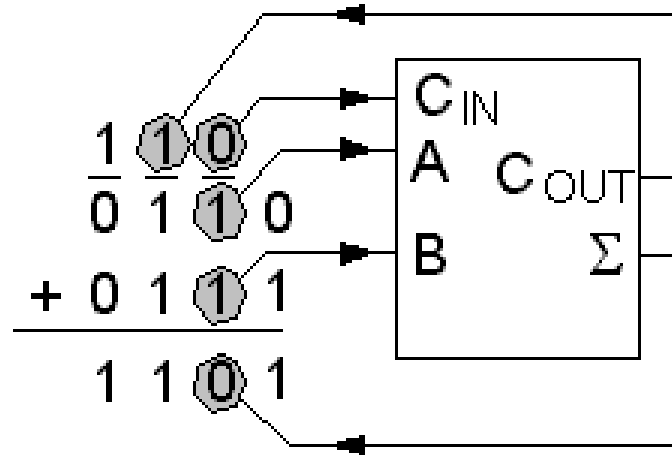


Full adder

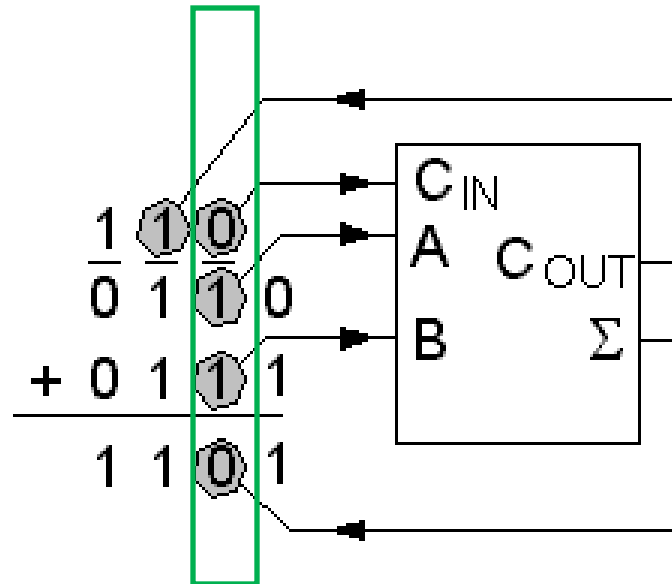


A logic circuit that makes a binary addition on any bit position with two binary numbers is called a full adder.

4-bit adder

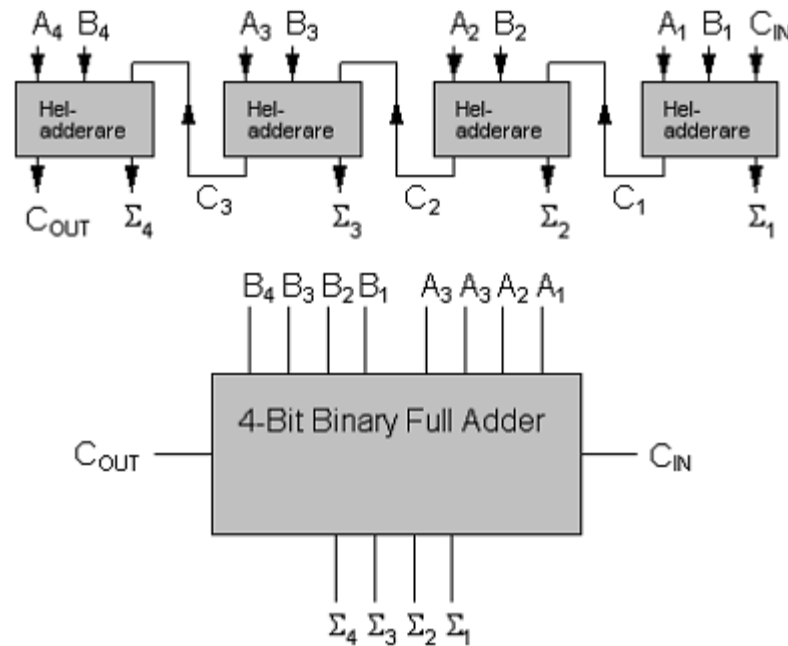An addition circuit for binary fourbitnumbers thus consists of four fulladdercircuits.




Subtraction?

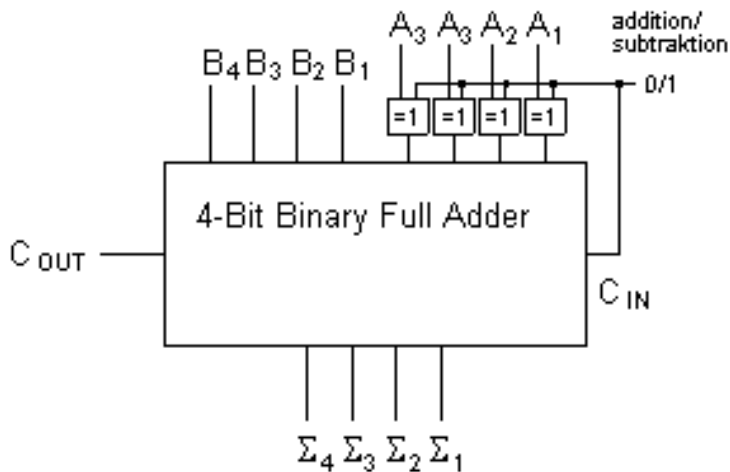

Subtracting the binary numbers can be done with the two-complement. Negative numbers are represented as the true complement, which means that all bits are inverted and a one is added. The adder is then used also for subtraction.

The inversion of the bits could be done with XOR-gates, and a one could then be added to the number by letting $C_{IN} = 1$.

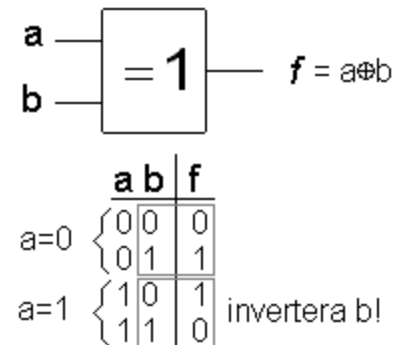


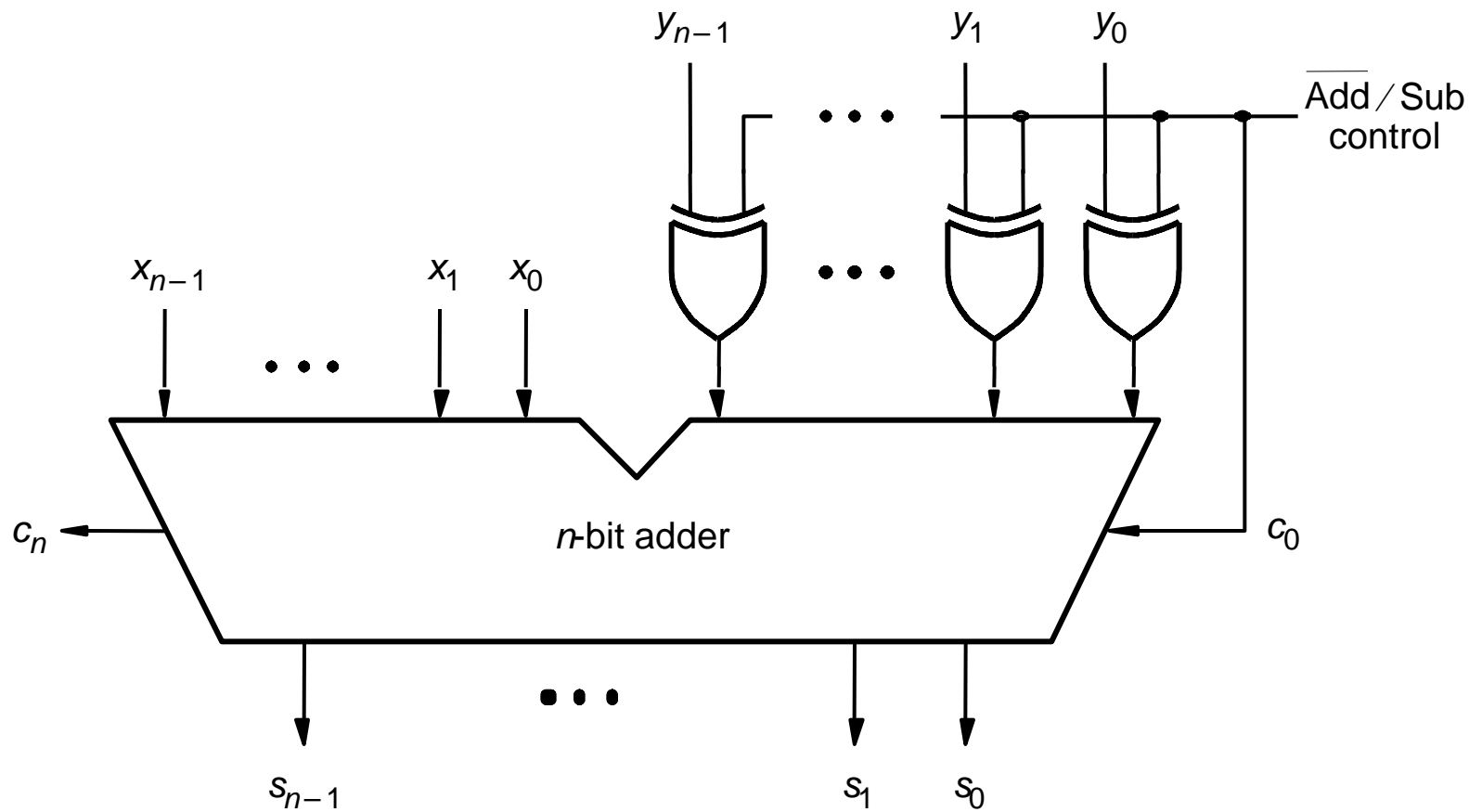


Figure 5.13. Adder/subtractor unit.

2-complement "fast"

- In order to easily produce 2's complement of a binary number, you can use the following procedure:
 - Start from right
 - Copy all bits from all zeroes to **the first 1**.
 - Invert all the rest of the bits

Example: 2-complement of

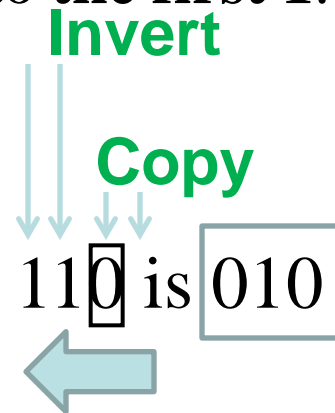

Ex. 2.2

Add or subtract (add with the corresponding negative number) the numbers below. The numbers are represented as binary 2-complement 4-bit numbers (nibble).

a) $1 + 2$ b) $4 - 1$ c) $7 - 8$ d) $-3 - 5$

The negative numbers that are used in the examples:

$$-1_{10} = (+1_{10} = 0001_2 \rightarrow -1_{10} = 1110_2 + 1_2) = 1111_2$$

$$-8_{10} = (+8_{10} = 1000_2 \rightarrow -8_{10} = 0111_2 + 1_2) = 1000_2$$

$$-3_{10} = (+3_{10} = 0011_2 \rightarrow -3_{10} = 1100_2 + 1_2) = 1101_2$$

$$-5_{10} = (+5_{10} = 0101_2 \rightarrow -5_{10} = 1010_2 + 1_2) = 1011_2$$

2.2

$$-1_{10} = 1111_2$$

$$-8_{10} = 1000_2$$

$$-3_{10} = 1101_2$$

$$-5_{10} = 1011_2$$

$$1+2=3$$

a)

$$\begin{array}{r|l} 0 & 0 & 0 & 1 & =1 \\ + & 0 & 0 & 1 & 0 & =2 \\ \hline & 0 & 0 & 1 & 1 & =3 \end{array}$$

$$4-1=3$$

b)

$$\begin{array}{r|l} 1 & 1 & & & & \\ + & 0 & 1 & 0 & 0 & =4 \\ + & 1 & 1 & 1 & 1 & =-1 \\ \hline \cancel{1} & 0 & 0 & 1 & 1 & =3 \end{array}$$

$$7-8=-1$$


c)

$$\begin{array}{r|l} 0 & 1 & 1 & 1 & =7 \\ + & 1 & 0 & 0 & 0 & =-8 \\ \hline & 1 & 1 & 1 & 1 & =-1 \end{array}$$

$$-3-5=-8$$

d)

$$\begin{array}{r|l} 1 & 1 & 1 & 1 & 1 & \\ + & 1 & 1 & 0 & 1 & =-3 \\ + & 1 & 0 & 1 & 1 & =-5 \\ \hline \cancel{1} & 1 & 0 & 0 & 0 & =-8 \end{array}$$

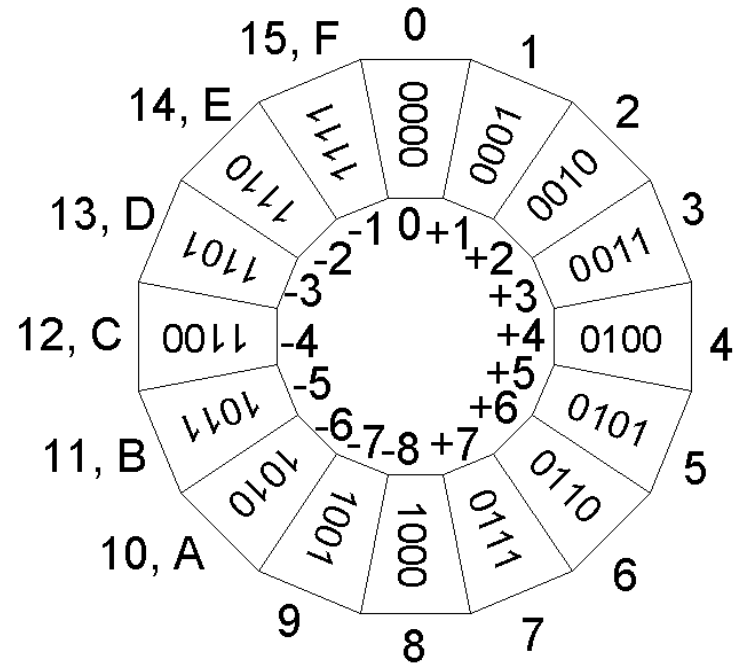

Ex. 2.3 a,b

Multiply by hand the following pairs of unsigned binary numbers.

a) $110 \cdot 010$ b) $1110 \cdot 1001$

$$110 \cdot 010 = (6 \cdot 2 = 12) = 1100$$

$$1110 \cdot 1001 = 1111110$$

a)

$$\begin{array}{r} 110 = 6 \\ \times 010 = 2 \\ \hline 000 \\ 110 \\ + 000 \\ \hline 01100 = 12 \end{array}$$

b)

$$\begin{array}{r} 1110 = 14 \\ \times 1001 = 9 \\ \hline 1110 \\ 0000 \\ 0000 \\ + 1110 \\ \hline 1111110 = 126 \end{array}$$

Ex. 2.3 c,d

Multiply by hand the following pairs of unsigned binary numbers.

$$\begin{array}{r}
 110011.01 \cdot 111.1 = \\
 = 110000000.011 \\
 \text{c) } \begin{array}{r}
 110011\boxed{01} \\
 \times \quad 111\boxed{1} \\
 \hline
 11001101 \\
 11001101 \\
 11001101 \\
 + 11001101 \\
 \hline
 110000000\boxed{011} \\
 \\
 = 110000000.011
 \end{array}
 \end{array}$$

$$(51,25 \cdot 7,5 = 384,375)$$

$$\begin{array}{r}
 0.1101 \cdot 0.1110 = \\
 = 0.10110110 \\
 \text{d) } \begin{array}{r}
 \quad \quad \boxed{1101} \\
 \times \quad \boxed{1110} \\
 \hline
 \quad \quad 0000 \\
 \quad \quad 1101 \\
 \quad 1101 \\
 + 1101 \\
 \hline
 \boxed{10110110} \\
 \\
 = 0.10110110
 \end{array}
 \end{array}$$

$$(0,8125 \cdot 0,875 = 0.7109375)$$

Fixpoint multiplication is an "integer multiplication", the binary point is inserted in the result.

Ex 2.4

Divide by hand the following pairs of unsigned binary numbers.

Method Short division:

a) $110/010=(6/2=3)=011$

$$\frac{\boxed{110}}{10} = \frac{110}{10} = 1 \quad \frac{\begin{array}{c} \boxed{1} \\ 110 \end{array}}{10} = 11$$

Ex 2.4

Divide by hand the following pairs of unsigned binary numbers.


Method Short division:

b) $1110/1001=(14/9=1,55\dots)=1.10\dots$

$$\frac{1110}{1001} = \frac{101}{1001} \frac{1110}{1001} = 1 \quad \frac{1010}{1001} \frac{1110.}{1001} = 1. \quad \frac{1}{1001} \frac{1110.}{1001} = 1.1 \quad \dots$$

If integer division the answer will be 1.

IEEE – 32 bit float

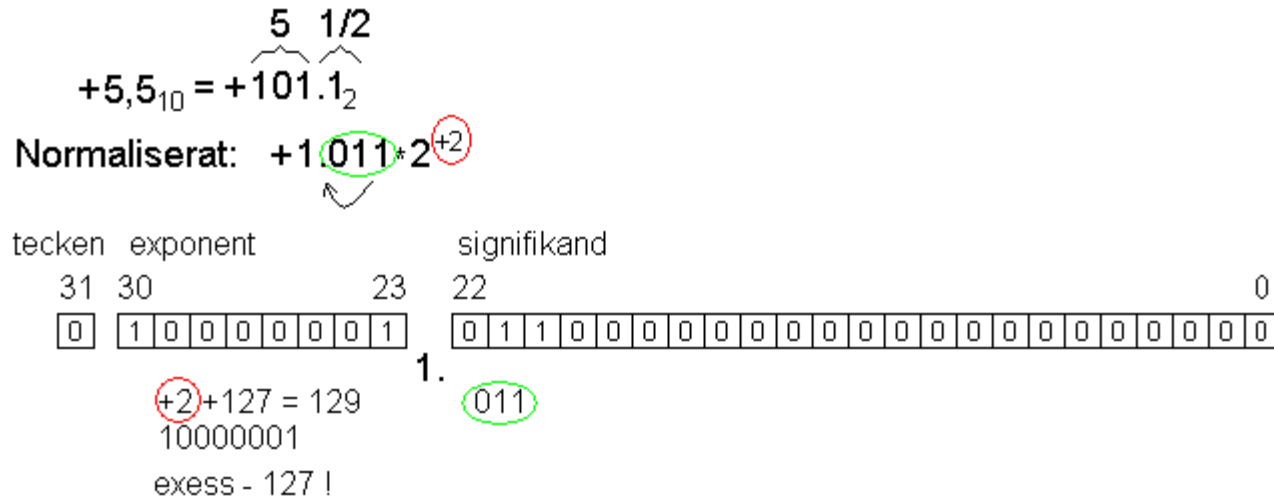

The exponent is written excess-127. It is then possible to sort float by size with ordinary integer arithmetic!

[Dec → IEEE-754](#)

2.5 Float format

IEEE 32 bit float

```
s  eeeeeeee  ffffffffffffffffffffffffffffffff
31 30      23 22                                0
```

2.5 Float format

IEEE 32 bit float

```
s  eeeeeeee  ffffffffffffffffffffffffffffffff
31 30      23 22                                0
```

What is:

```
    4    0    C    8    0    0    0    0
0100000011001000000000000000000000000000
```


IEEE-754 Floating-Point Conversion from 32-bit Hexadecimal to Floating-Point - Mozilla Firefox

Arkiv Redigera Visa Historik Bokmärken Verktyg Hjälp

http://babbage.cs.qc.cuny.edu/IEEE-754/32bit.html

IEEE-754 Floating-Point Conversion f...

IEEE-754 Floating-Point Conversion

From 32-bit Hexadecimal Representation To Decimal Floating-Point

Along with the Equivalent 64-bit Hexadecimal and Binary Patterns

Enter the 32-bit hexadecimal representation of a floating-point number here,
then click the **Compute** button.

Hexadecimal Representation:

Results:

Decimal Value Entered:


Single precision (32 bits):

Binary: Status:


Bit 31 Sign Bit <input type="text" value="0"/> 0: + 1: -	Bits 30 - 23 Exponent Field <input type="text" value="10000001"/> Decimal value of exponent field and exponent <input type="text" value="129"/> - 127 = <input type="text" value="2"/>	Bits 22 - 0 Significand <input type="text" value="1.100100000000000000000000"/> Decimal value of the significand <input type="text" value="1.5625000"/>
--	--	---

<http://babbage.cs.qc.cuny.edu/IEEE-754/32bit.html>

William Sandqvist william@kth.se

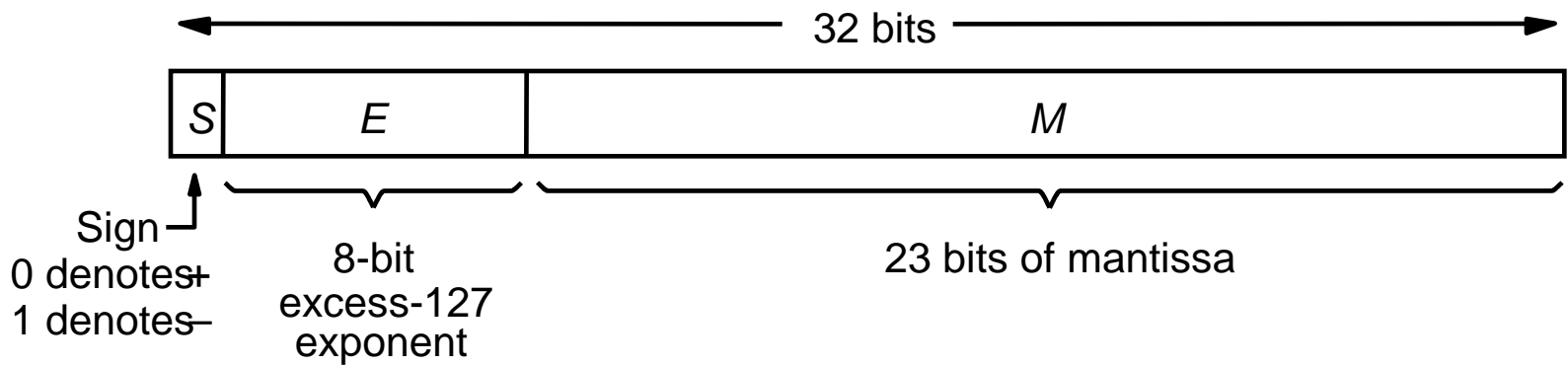


(a) Single precision

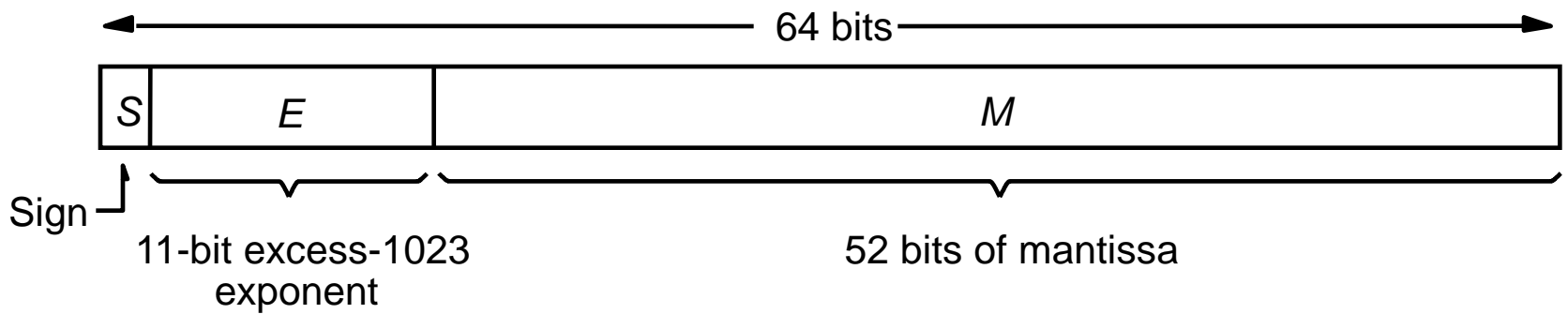

(b) Double precision

Figure 5.34. IEEE Standard floating-point formats.


Overflow

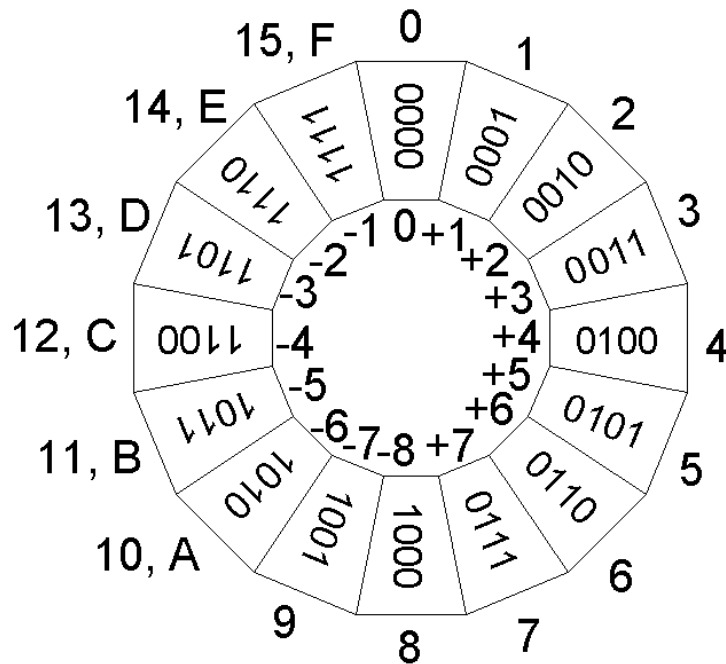

When using signed numbers the sum of two positive numbers could be incorrectly negative (eg. "+4" + "+5" = "-7"), in the same way the sum of two negative numbers could incorrectly be positive (eg. "-6" + "-7" = "+3").

This is called **Overflow**.

Logic to detect overflow

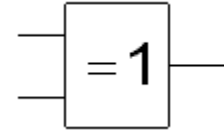

For 4-bit-numbers

Overflow if c_3 and c_4 are *different*

Otherwise it's not overflow

XOR detects

"not equal"

$$\text{Overflow} = c_3 \bar{c}_4 + \bar{c}_3 c_4 = c_3 \oplus c_4$$

For n -bit-numbers

$$\text{Overflow} = c_{n-1} \oplus c_n$$

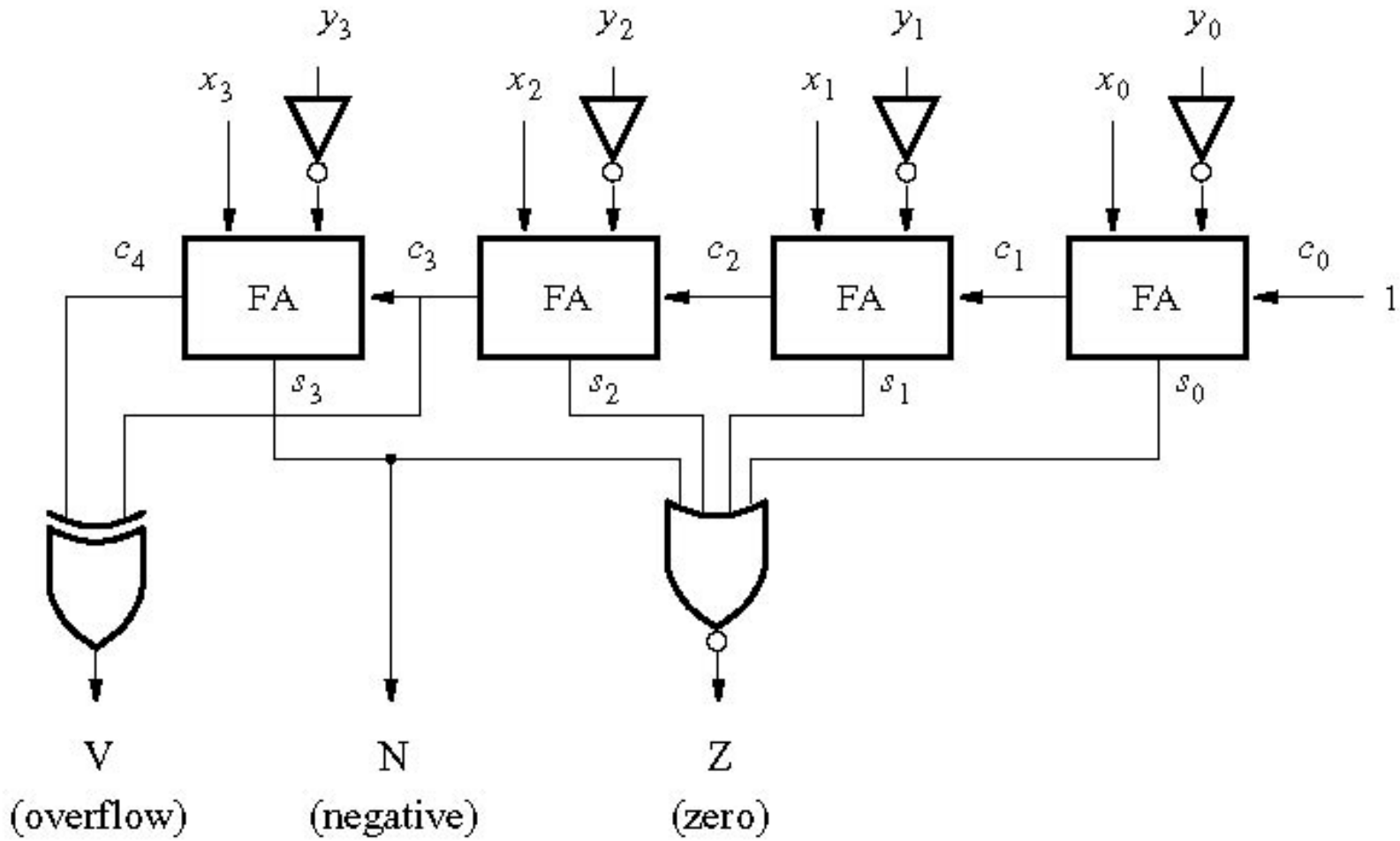



Figure 5.42. A comparator circuit.

BV ex 5.10, < > =

Flags, Comparator. Two four-bit signed numbers, $X = x_3x_2x_1x_0$ and $Y = y_3y_2y_1y_0$, can be compared by using a subtractor circuit, which performs the operation $X - Y$. The three Flag-outputs denote the following:


- $Z = 1$ if the result is 0; otherwise $Z = 0$
- $N = 1$ if the result is negative; otherwise $N = 0$
- $V = 1$ if arithmetic overflow occurs; otherwise $V = 0$

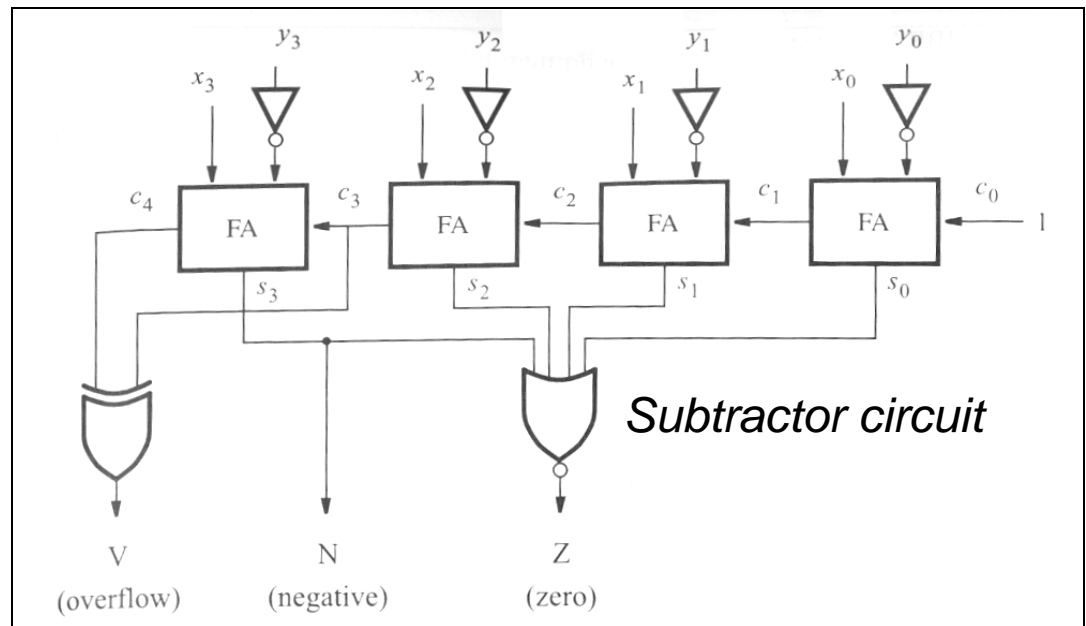Show how Z , N , and V can be used to determine the cases $X = Y$, $X < Y$, $X > Y$.



BV ex 5.10

$X = Y ?$

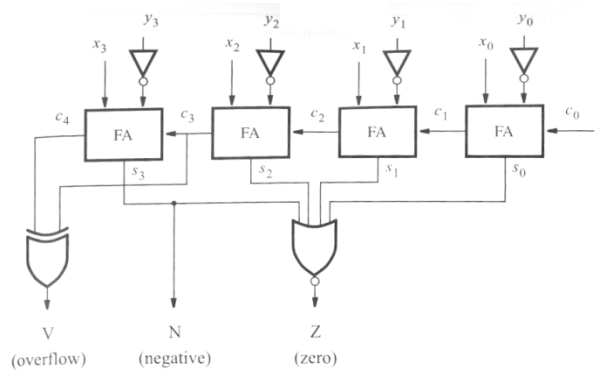


$X - Y$

$$V = c_4 \oplus c_3 \quad N = s_3$$


$$Z = \overline{(s_3 + s_2 + s_1 + s_0)}$$

$X = Y ?$

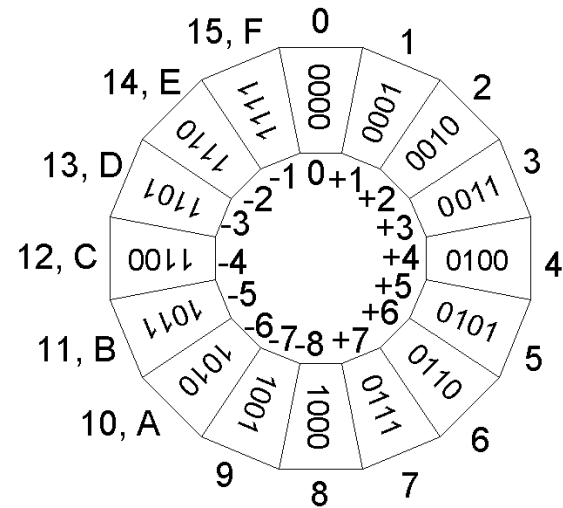

BV ex 5.10

$X = Y ?$

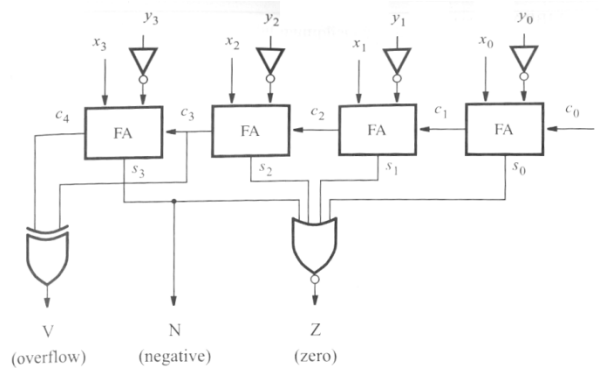


$X - Y$

$$V = c_4 \oplus c_3 \quad N = s_3$$


$$Z = (s_3 + s_2 + s_1 + s_0)$$

$X = Y ?$

$$X = Y \Rightarrow Z = 1$$

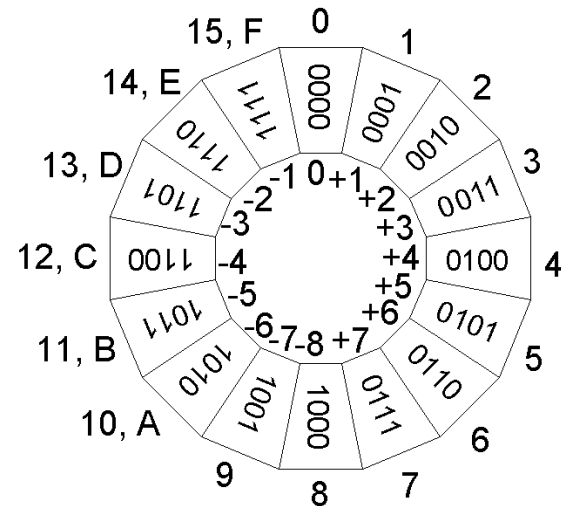

BV ex 5.10

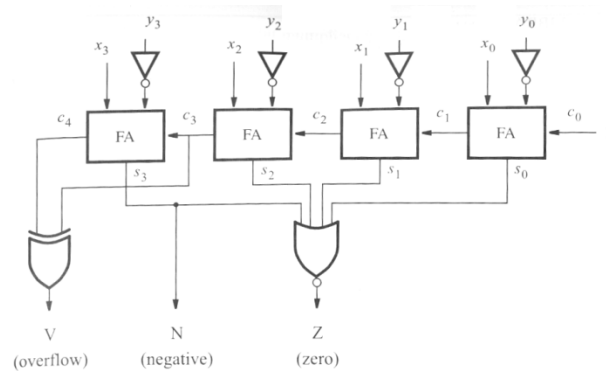

$$X - Y$$

$$V = c_4 \oplus c_3 \quad N = s_3$$


$$Z = (s_3 + s_2 + s_1 + s_0)$$

$X < Y$?

Some test numbers:

	$X < Y$	$X - Y$	V	N
3	4	$3 - 4 = -1$	0	1
-4	-3	$-4 - -3 = -1$	0	1
-3	4	$-3 - 4 = -7$	0	1
-5	4	$-5 - 4 = +7$	1	0

BV ex 5.10

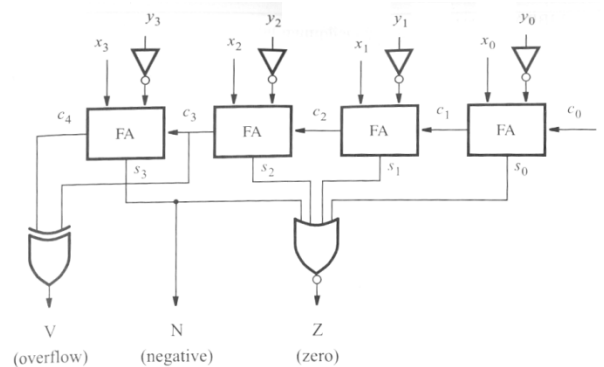

$$X - Y$$

$$V = c_4 \oplus c_3 \quad N = s_3$$

$$Z = \overline{(s_3 + s_2 + s_1 + s_0)}$$

$X < Y$?


If X and Y has the same sign $X - Y$ will always be correct and the flag $V = 0$. X, Y positive eg. $3 - 4$ $N = 1$. X, Y negative eg. $-4 - (-3)$ $N = 1$.

If X neg and Y pos and $X - Y$ has the correct sign, $V = 0$ and $N = 1$.
Tex. $-3 - 4$.

If X neg and Y but $X - Y$ gets the wrong sign, $V = 1$.
Then $N = 0$. Ex. $-5 - 4$.

- Summary: when $X < Y$ the flags V and N is always different. This could be indicated by a XOR gate.

BV ex 5.10

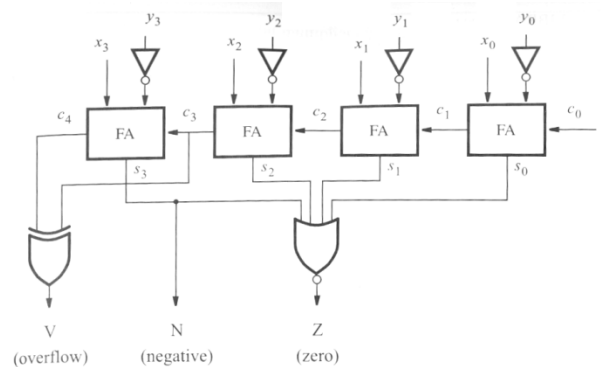

$$X - Y$$

$$V = c_4 \oplus c_3 \quad N = s_3$$

$$Z = \overline{(s_3 + s_2 + s_1 + s_0)}$$

$X < Y$?

If X and Y has the same sign $X - Y$ will always be correct and the flag $V = 0$. X, Y positive eg. $3 - 4$ $N = 1$. X, Y negative eg. $-4 - (-3)$ $N = 1$.


If X neg and Y pos and $X - Y$ has the correct sign, $V = 0$ and $N = 1$.
 Tex. $-3 - 4$.

If X neg and Y but $X - Y$ gets the wrong sign, $V = 1$.
 Then $N = 0$. Ex. $-5 - 4$.

- Summary: when $X < Y$ the flags V and N is always different. This could be indicated by a XOR gate.

$$X < Y \Rightarrow N \oplus V$$

BV ex 5.10

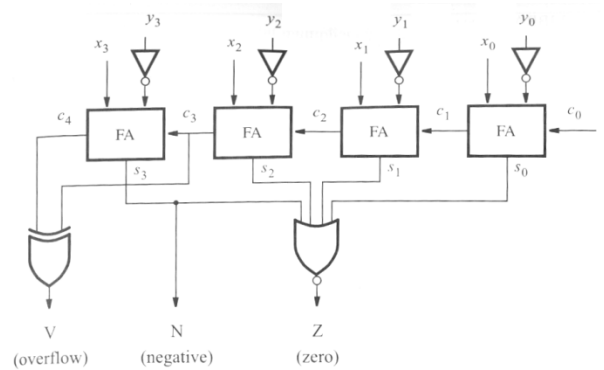

$$X - Y$$

$$V = c_4 \oplus c_3 \quad N = s_3$$

$$Z = \overline{(s_3 + s_2 + s_1 + s_0)}$$

$$X = Y \Rightarrow Z = 1$$


$$X < Y \Rightarrow N \oplus V$$

$$X \leq Y \Rightarrow$$

$$X > Y \Rightarrow$$

$$X \geq Y \Rightarrow$$

BV ex 5.10

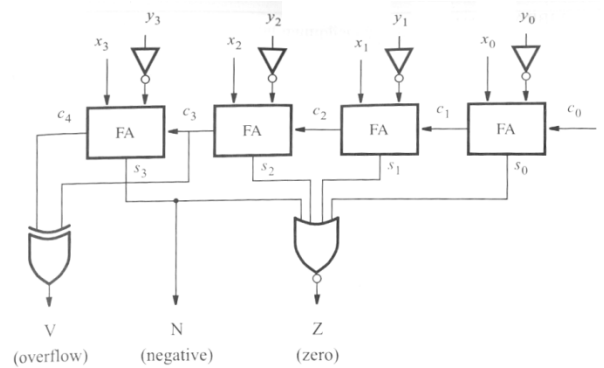

$$X - Y$$

$$V = c_4 \oplus c_3 \quad N = s_3$$

$$Z = \overline{(s_3 + s_2 + s_1 + s_0)}$$

$$X = Y \Rightarrow Z = 1$$


$$X < Y \Rightarrow N \oplus V$$

$$X \leq Y \Rightarrow Z + N \oplus V$$

$$X > Y \Rightarrow \overline{Z + N \oplus V} = \overline{Z} \cdot \overline{(N \oplus V)}$$

$$X \geq Y \Rightarrow \overline{N \oplus V}$$

BV ex 5.10

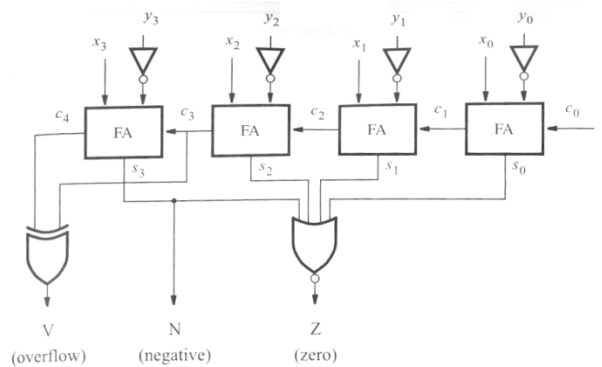

$$X - Y$$

$$V = c_4 \oplus c_3 \quad N = s_3$$

$$Z = \overline{(s_3 + s_2 + s_1 + s_0)}$$

$$X = Y \Rightarrow Z = 1$$

$$X < Y \Rightarrow N \oplus V$$

$$X \leq Y \Rightarrow Z + N \oplus V$$

$$X > Y \Rightarrow \overline{Z + N \oplus V} = \overline{\overline{Z}} \cdot \overline{(N \oplus V)}$$


$$X \geq Y \Rightarrow \overline{N \oplus V}$$

*This is how a computer
can perform the most
common comparisons*

William Sandqvist william@kth.se

Ex 8.11 Multiply with 6 ?

$$\begin{array}{cccc}
 x_3 & x_2 & x_1 & x_0 \\
 | & | & | & | \\
 \end{array}
 \qquad
 \begin{array}{cc}
 1 & 0 \\
 | & | \\
 \end{array}$$

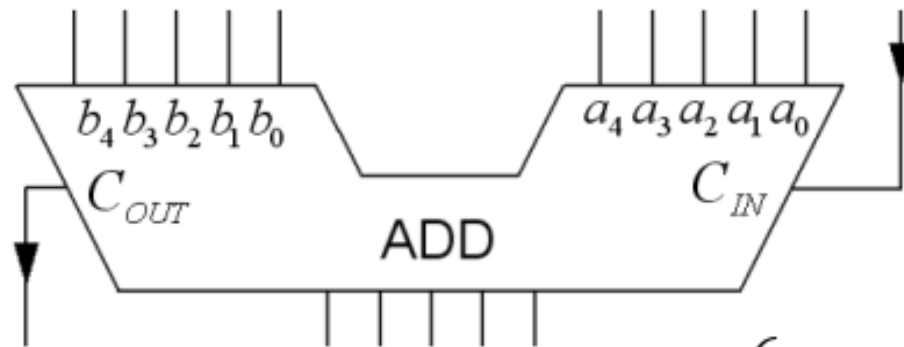


$$s = 6 \times x =$$


$$= 2 \times (2 \times x + 1 \times x)$$

$$\begin{array}{ccccccc}
 | & | & | & | & | & | & | \\
 s_6 & s_5 & s_4 & s_3 & s_2 & s_1 & s_0
 \end{array}$$


Ex 8.11 Multiply with 6 !

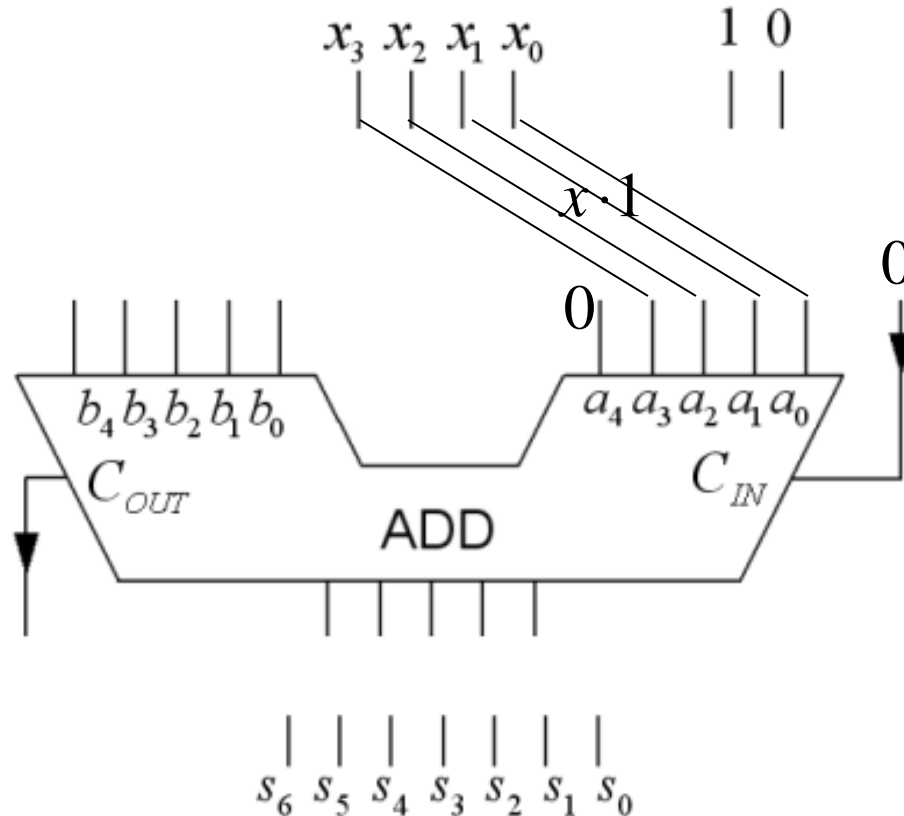

Ex 8.11 Multiply with 6 !

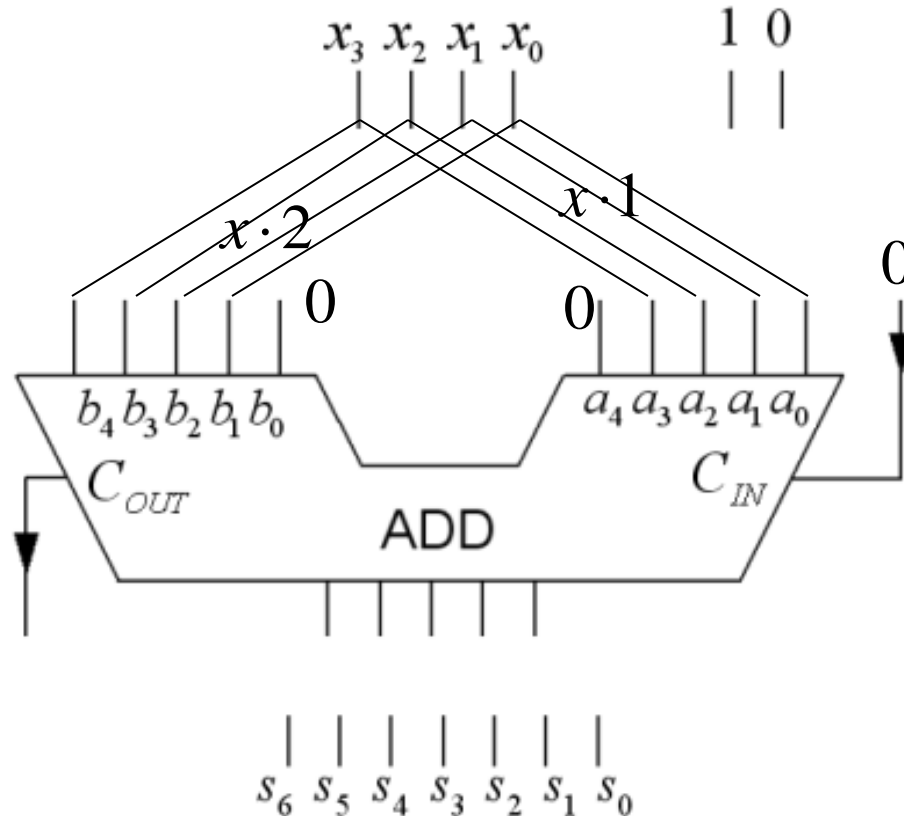

Ex 8.11 Multiply with 6 !

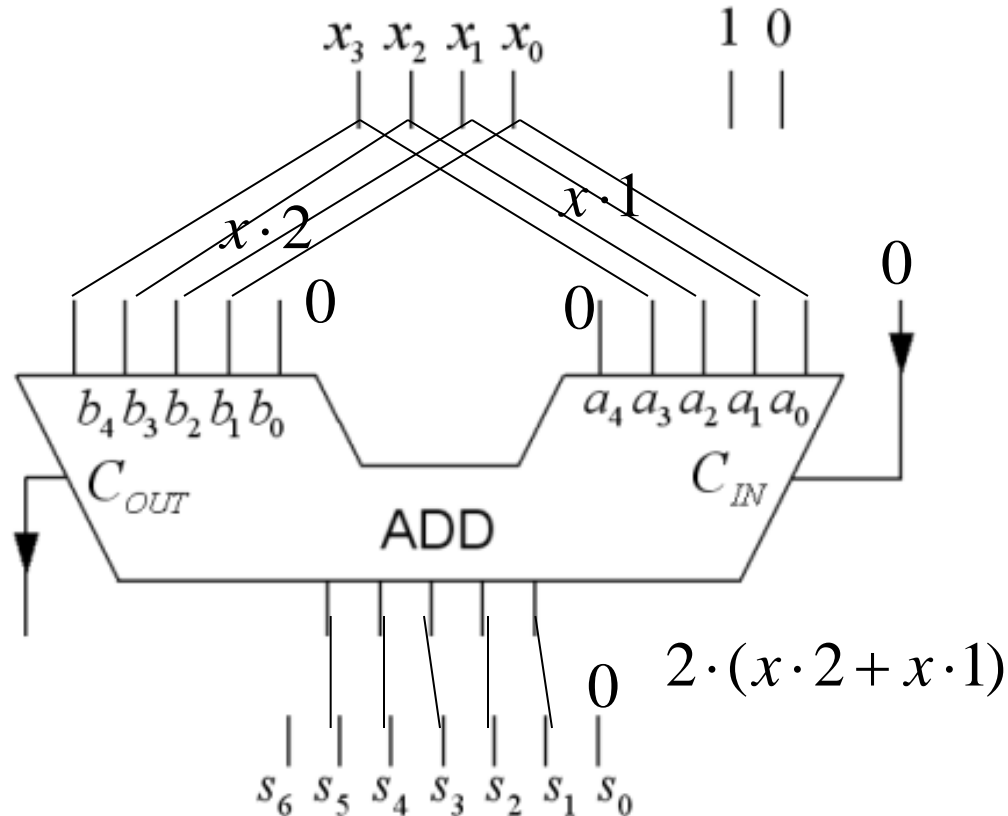


Ex 8.11 Multiply with 6 !

$$15 \cdot 6 = 90$$

$$1111 = 15$$

$x_3 \ x_2 \ x_1 \ x_0$
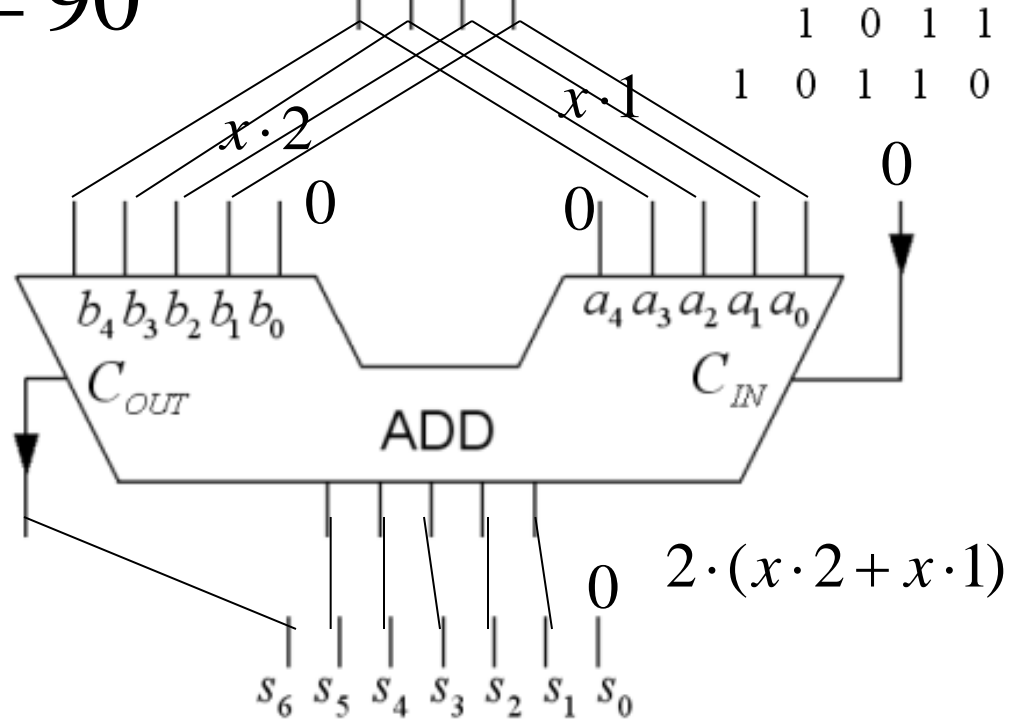
$$\begin{array}{r}
 \underline{1} \ \underline{1} \ \underline{1} \ \underline{1} \ \underline{0} \ \underline{0} \\
 0 \ \boxed{1 \ 1 \ 1 \ 1} \ 0 \quad 15 \times 2 \\
 + \ 0 \ 0 \ \boxed{1 \ 1 \ 1 \ 1} \quad 15 \times 1 \\
 \hline
 1 \ 0 \ 1 \ 1 \ 0 \ 1 \\
 1 \ 0 \ 1 \ 1 \ 0 \ 1 \ 0 \quad \times 2
 \end{array}$$



$$1011010 = 90$$

William Sandqvist william@kth.se