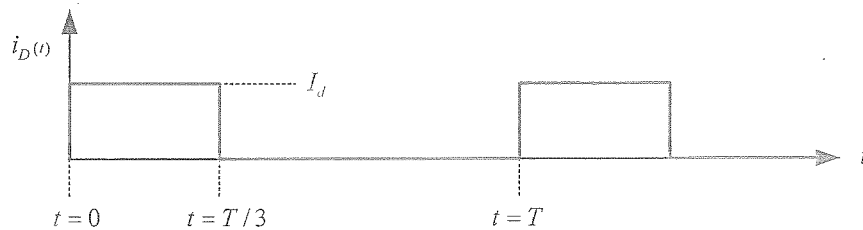


## Peer assessment #3 in Power Electronics, version A


A three-phase diode bridge rectifier has a totally smooth output current  $I_d$ . The waveform of the current through a diode is shown in the figure below.



1. Determine the mean value of  $i_D(t)$ .

$$I_D = \frac{1}{T} \int_0^T i_D(t) dt = \frac{I_d}{T} \int_0^{T/3} dt = \frac{I_d}{3}$$

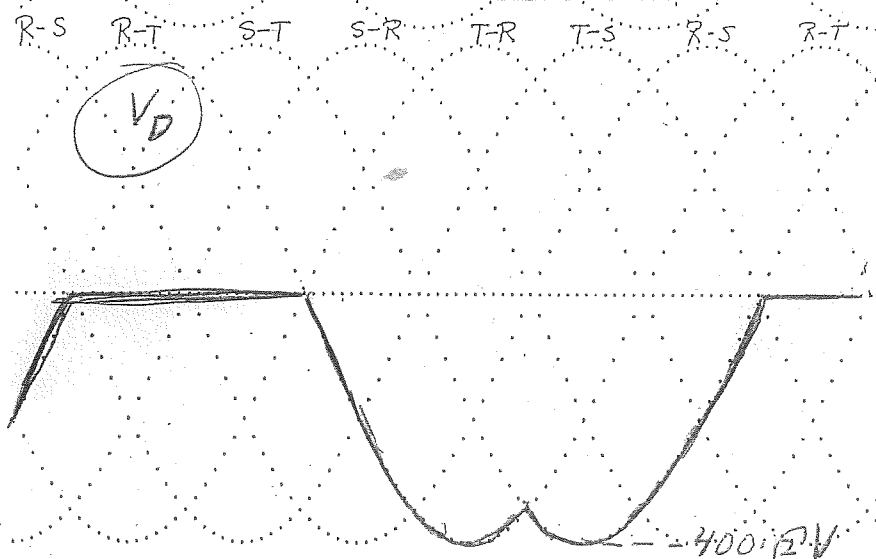2. Draw the voltage across one of the diodes during one cycle.




3. The same rectifier feeds a load consisting of a voltage source  $E$  in series with a resistance  $R$  and a large inductance. Calculate  $I_d$  if the line-to-line voltage of the grid is 400 V,  $E = 400$  V and  $R = 14 \Omega$ .

$$I_d = \frac{V_d - E}{R} = \frac{1,35 \cdot 400 - 400}{14} = \underline{\underline{10 \text{ A}}}$$
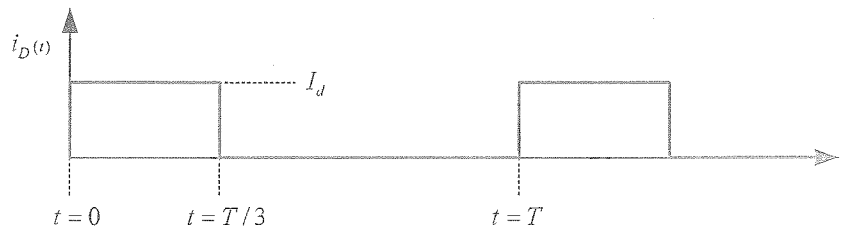
## Peer assessment #3 in Power Electronics, version B

A three-phase diode bridge rectifier has a totally smooth output current  $I_d$ . The waveform of the current through a diode is shown in the figure below.



1. Determine the RMS value of  $i_D(t)$ .


$$\begin{aligned} I_{DRMS} &= \sqrt{\frac{1}{T} \int_0^T [i_D(t)]^2 dt} = \sqrt{\frac{I_d^2}{T} \int_0^{T/3} dt} = \\ &= \sqrt{\frac{I_d^2}{3}} = \frac{I_d}{\sqrt{3}} \end{aligned}$$

2. The same rectifier feeds a load consisting of a voltage source  $E$  in series with a resistance  $R$  and an inductance. Calculate  $I_d$  if the line-to-line voltage of the grid is 200 V,  $E = 200$  V and  $R = 7 \Omega$ .

$$I_d = \frac{V_d - E}{R} = \frac{1,35 \cdot 200 - 200}{7} = \underline{\underline{10 \text{ A}}}$$
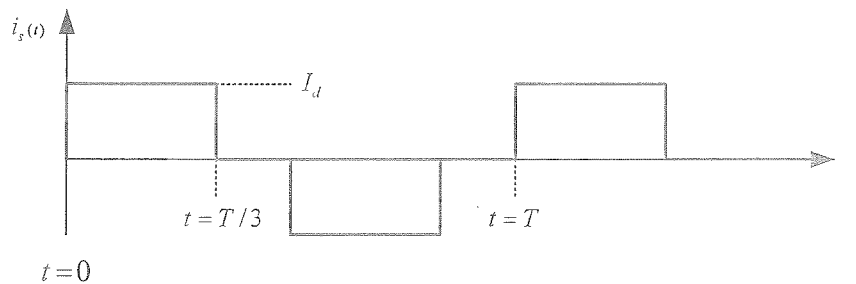
## Peer assessment #3 in Power Electronics, version C

A three-phase diode bridge rectifier has a totally smooth output current  $I_d$ . The waveform of one of the grid currents is shown in the figure below.



1. Determine the RMS value of  $i_s(t)$ .


$$\begin{aligned} I_{SRMS} &= \sqrt{\frac{1}{T} \int_0^T [i_s(t)]^2 dt} = \sqrt{\frac{1}{T} \left( \int_0^{T/3} I_d^2 dt + \int_0^{T/3} (-I_d)^2 dt \right)} = \\ &= \sqrt{\frac{1}{T} \left( I_d^2 \cdot \frac{T}{3} + I_d^2 \cdot \frac{T}{3} \right)} = \sqrt{I_d^2 \cdot \frac{2}{3}} = \sqrt{\frac{2}{3}} I_d \end{aligned}$$

2. The same rectifier feeds a load consisting of a voltage source  $E$  in series with a resistance  $R$  and an inductance. Calculate  $I_d$  if the line-to-line voltage of the grid is 300 V,  $E = 300$  V and  $R = 10,5 \Omega$ .

$$I_d = \frac{V_d - E}{R} = \frac{1,35 \cdot 300 - 300}{10,5} = \underline{\underline{10 \text{ A}}}$$
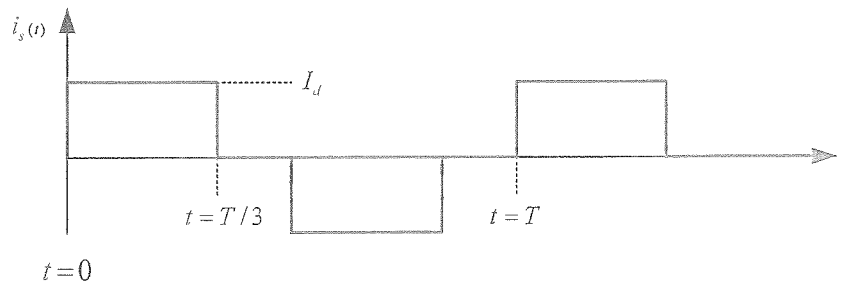
## Peer assessment #3 in Power Electronics, version D


A three-phase diode bridge rectifier has a totally smooth output current  $I_d$ . The waveform of one of the grid currents is shown in the figure below.



1. Determine the mean value of  $i_s(t)$ .

0

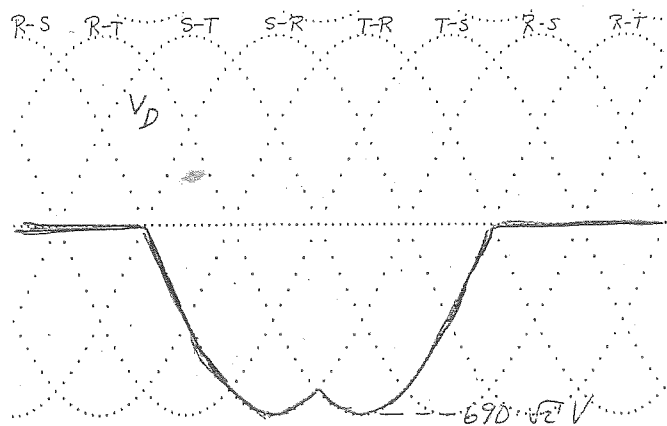2. Draw the voltage across one of the diodes during one cycle.



3. The same rectifier feeds a load consisting of a voltage source  $E$  in series with a resistance  $R$  and an inductance. Calculate  $I_d$  if the line-to-line voltage of the grid is  $690 \text{ V}$ ,  $E = 690 \text{ V}$  and  $R = 24,15 \Omega$ .

$$I_d = \frac{V_d - E}{R} = \frac{1,35 \cdot 690 - 690}{24,15} = \underline{\underline{10 \text{ A}}}$$