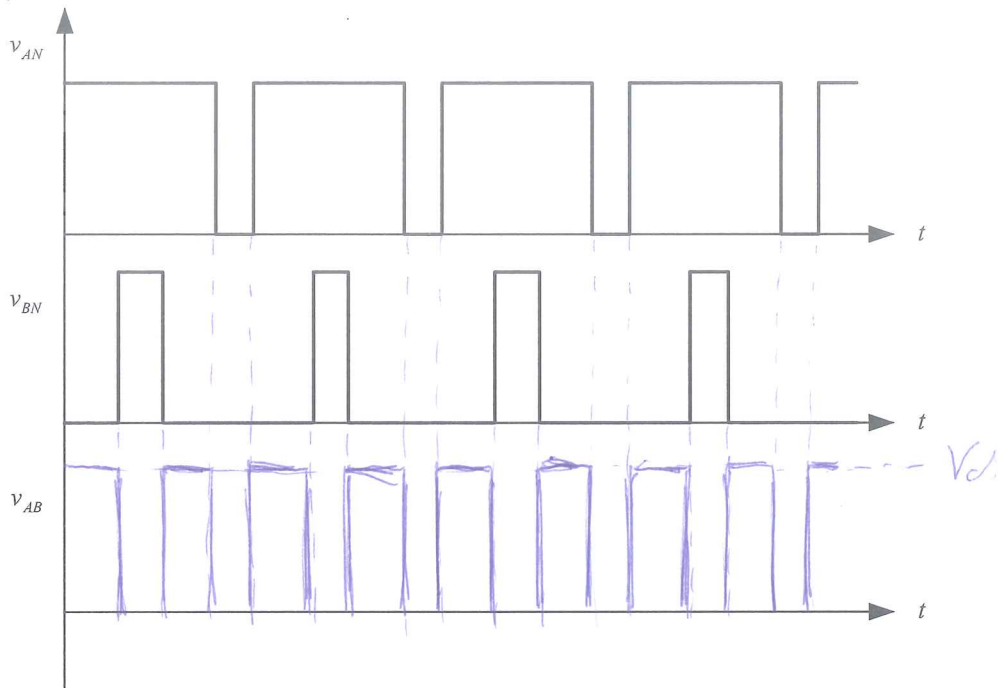


## Peer assessment #4 in Power Electronics, version A

1. In the figure below two output voltages from a three-phase switch-mode inverter are shown. The voltages are measured between the respective output terminal and the negative pole of the input direct voltage supply. Draw the waveform of  $v_{AB}$ .




2. Calculate the fundamental component of the line-to-line voltage at the output of the inverter if  $V_d = 540 \text{ V}$ ,  $m_a = 0,2$  and  $f_s = 11,4 \text{ kHz}$ .

$$V_{AN(1)} = m_a \cdot \frac{V_d}{2} \Rightarrow V_{AN(1)} = m_a \cdot \frac{V_d}{2 \cdot \sqrt{2}}$$

$$V_{AB(1)} = \sqrt{3} \cdot V_{AN(1)} = m_a \cdot \sqrt{\frac{3}{2}} \cdot \frac{V_d}{2} = 0,2 \cdot \sqrt{1,5} \cdot \frac{540}{2} = \underline{\underline{66 \text{ V}}}$$

## Peer assessment #4 in Power Electronics, version B

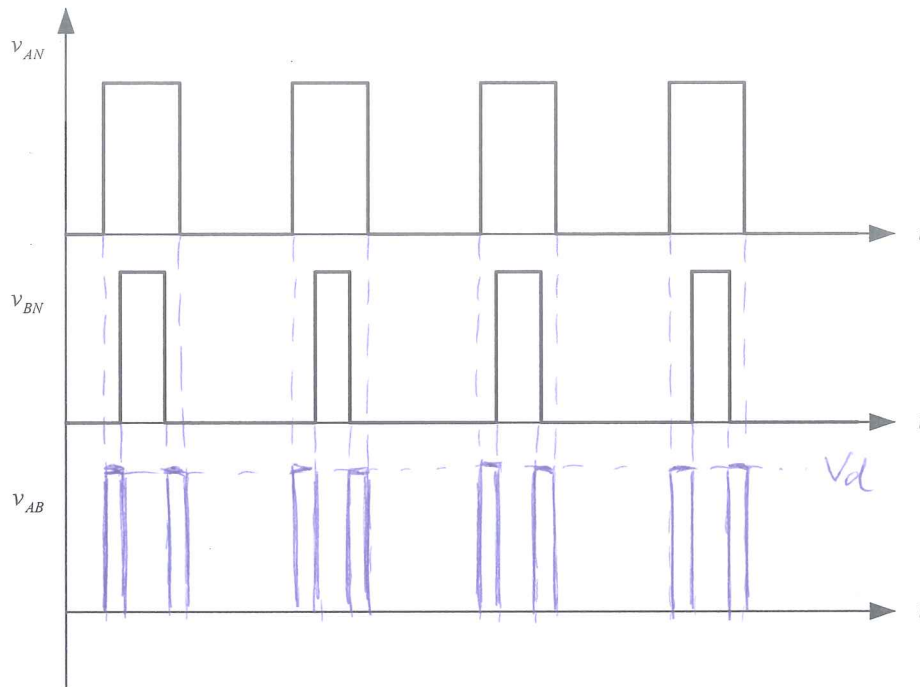1. In the figure below two output voltages from a three-phase switch-mode inverter are shown. The voltages are measured between the respective output terminal and the negative pole of the input direct voltage supply. Draw the waveform of  $v_{AB}$ .




2. Calculate the fundamental component of the line-to-line voltage at the output of the inverter if  $V_d = 540 \text{ V}$ ,  $m_a = 0,9$  and  $f_s = 4,7 \text{ kHz}$ .

$$\hat{V}_{AN(1)} = m_a \cdot \frac{V_d}{2} \Rightarrow V_{AN(1)} = m_a \cdot \frac{V_d}{2 \cdot \sqrt{2}}$$

$$V_{AB(1)} = \sqrt{3} \cdot V_{AN(1)} = m_a \cdot \sqrt{\frac{3}{2}} \cdot \frac{V_d}{2} = 0,9 \cdot \sqrt{1,5} \cdot \frac{540}{2} = \underline{\underline{298 \text{ V}}}$$

## Peer assessment #4 in Power Electronics, version C

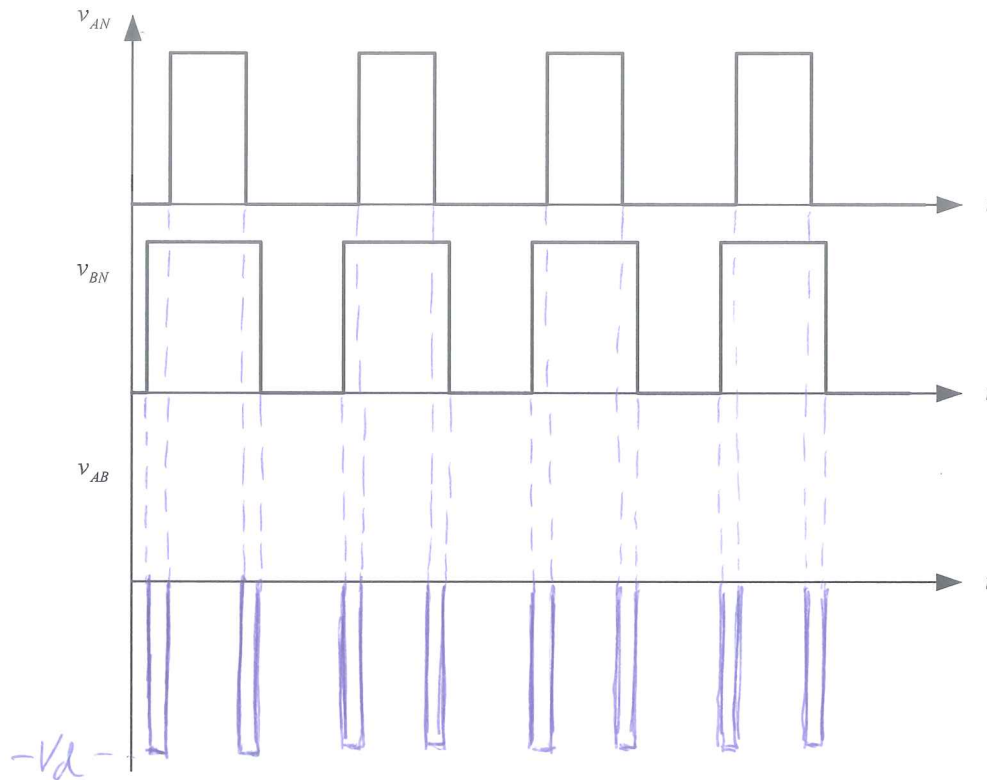1. In the figure below two output voltages from a three-phase switch-mode inverter are shown. The voltages are measured between the respective output terminal and the negative output terminal of the input direct voltage supply. Draw the waveform of  $v_{AB}$ .




2. Calculate the fundamental component of the line-to-line voltage at the output of the inverter if  $V_d = 540$  V,  $m_a = 0,4$  and  $f_s = 6,8$  kHz.

$$\hat{V}_{AN(1)} = m_a \cdot \frac{V_d}{2} \Rightarrow V_{AN(1)} = m_a \cdot \frac{V_d}{2 \cdot \sqrt{2}}$$

$$V_{AB(1)} = \sqrt{3} \cdot V_{AN(1)} = m_a \cdot \sqrt{\frac{3}{2}} \cdot \frac{V_d}{2} = 0,4 \cdot \sqrt{1,5} \cdot \frac{540}{2} = \underline{\underline{132 \text{ V}}}$$

## Peer assessment #4 in Power Electronics, version D

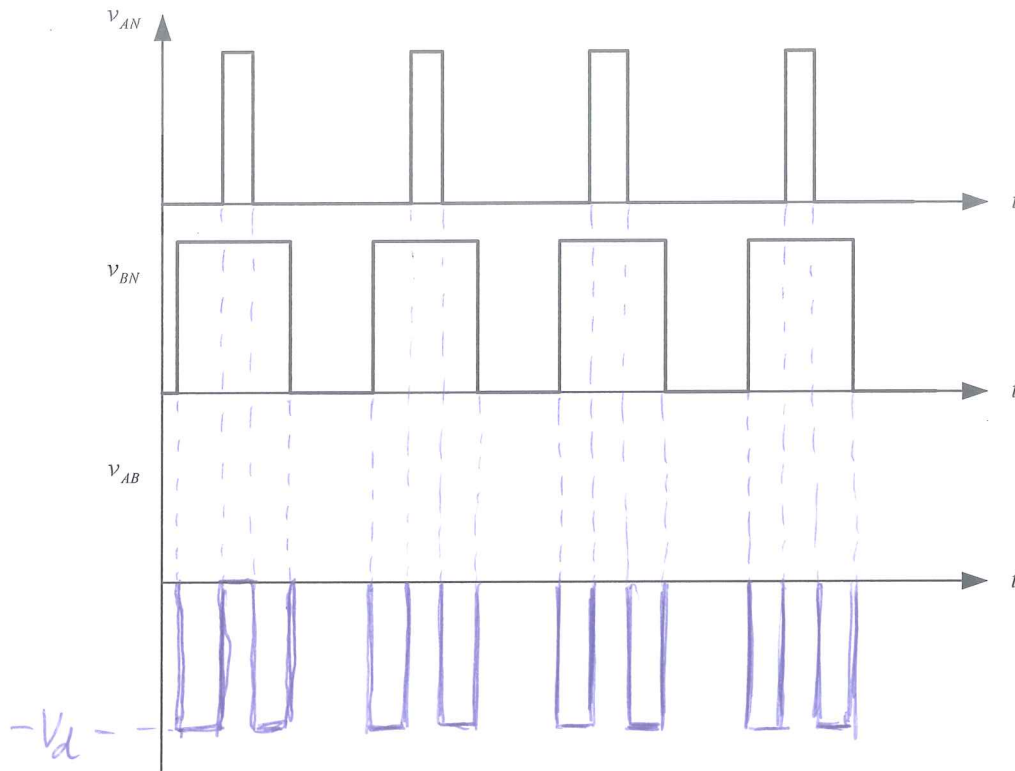1. In the figure below two output voltages from a three-phase switch-mode inverter are shown. The voltages are measured between the respective output terminal and the negative pole of the input direct voltage supply. Draw the waveform of  $v_{AB}$ .



2. Calculate the fundamental component of the line-to-line voltage at the output of the inverter if  $V_d = 540$  V,  $m_a = 0,6$  and  $f_s = 8,3$  kHz.

$$\hat{V}_{AN(1)} = m_a \cdot \frac{V_d}{2} \Rightarrow V_{AN(1)} = m_a \cdot \frac{V_d}{2 \cdot \sqrt{2}}$$

$$V_{AB(1)} = \sqrt{3} \cdot V_{AN(1)} = m_a \cdot \sqrt{\frac{3}{2}} \cdot \frac{V_d}{2} = 0,6 \cdot \sqrt{1,5} \cdot \frac{540}{2} = \underline{\underline{198 \text{ V}}}$$