
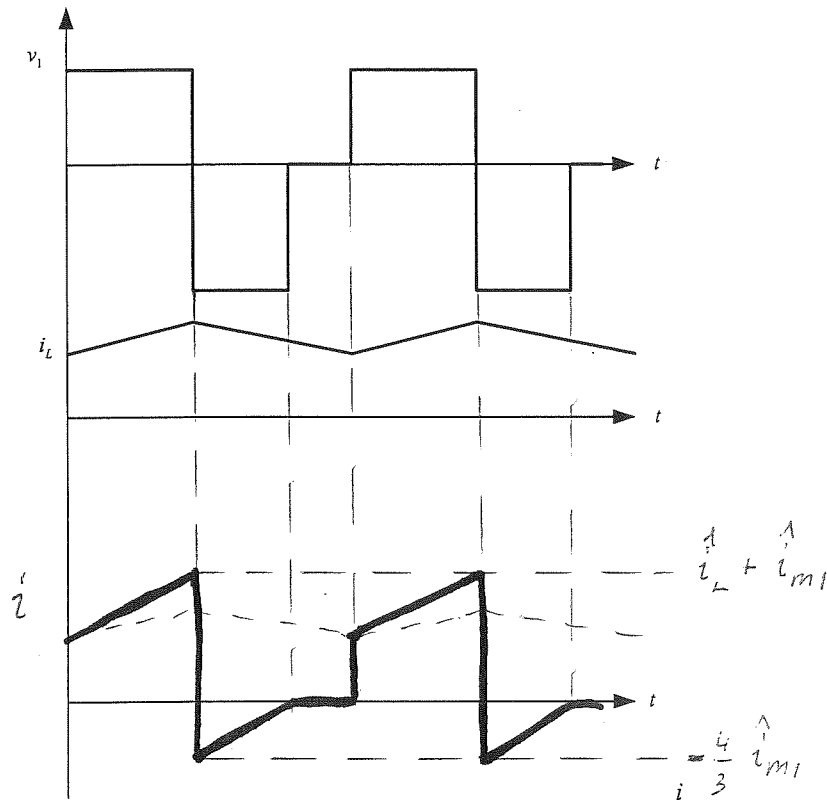


Peer assessment #5 in Power Electronics, version A

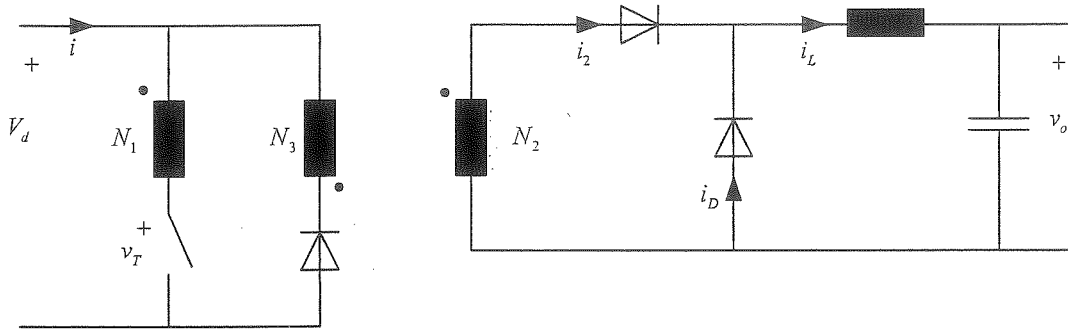1. Draw the waveform of i in the empty diagram below if v_1 is the voltage across Winding 1 and if $N_1 = N_2 = 40$ and $N_3 = 30$. The magnetizing current should be considered, but the magnitude can be chosen arbitrarily.





2. Estimate the average value of the output voltage if $V_d = 48$ V.

From the graph: $T_s = 38 \mu s$; $t_{on} = 17 \mu s \Rightarrow D = \frac{17}{38}$

$$V_o = V_d \cdot \frac{N_2}{N_1} \cdot D = 48 \cdot 1 \cdot \frac{17}{38} = \underline{\underline{21,5 \text{ V}}}$$

Peer assessment #5 in Power Electronics, version B

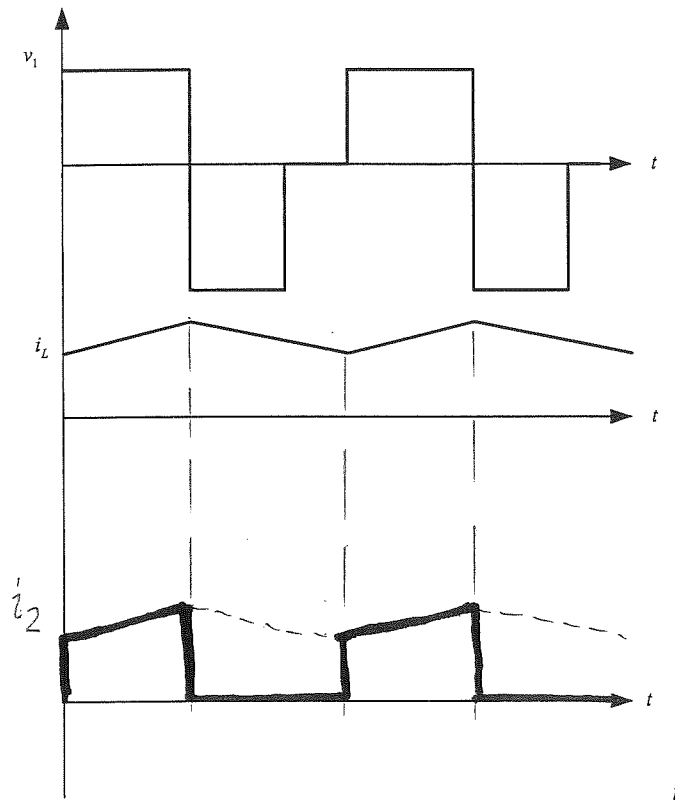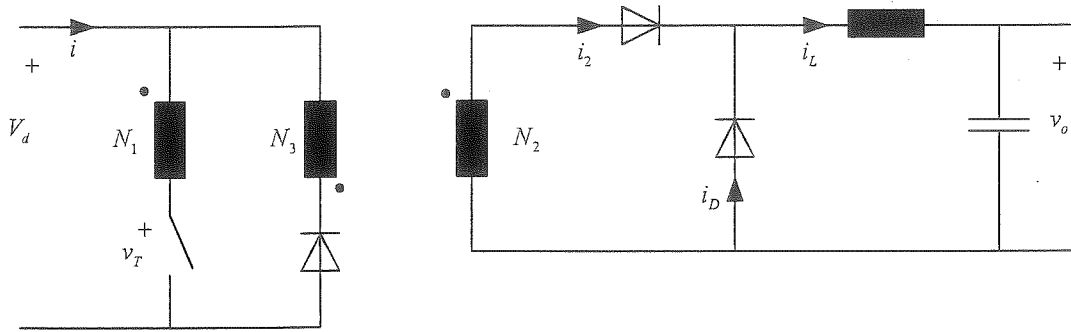1. Draw the waveform of i_2 in the empty diagram below if v_1 is the voltage across Winding 1 and if $N_1 = N_2 = 40$ and $N_3 = 30$.





2. Estimate the average value of the output voltage if $V_d = 24$ V.

From the graph: $T_s = 38 \mu\text{s}$; $t_{ON} = 17 \mu\text{s} \Rightarrow D = \frac{17}{38}$

$$V_o = V_d \cdot \frac{N_2}{N_1} \cdot D = 24 \cdot 1 \cdot \frac{17}{38} = \underline{\underline{10,7 \text{ V}}}$$

Peer assessment #5 in Power Electronics, version C

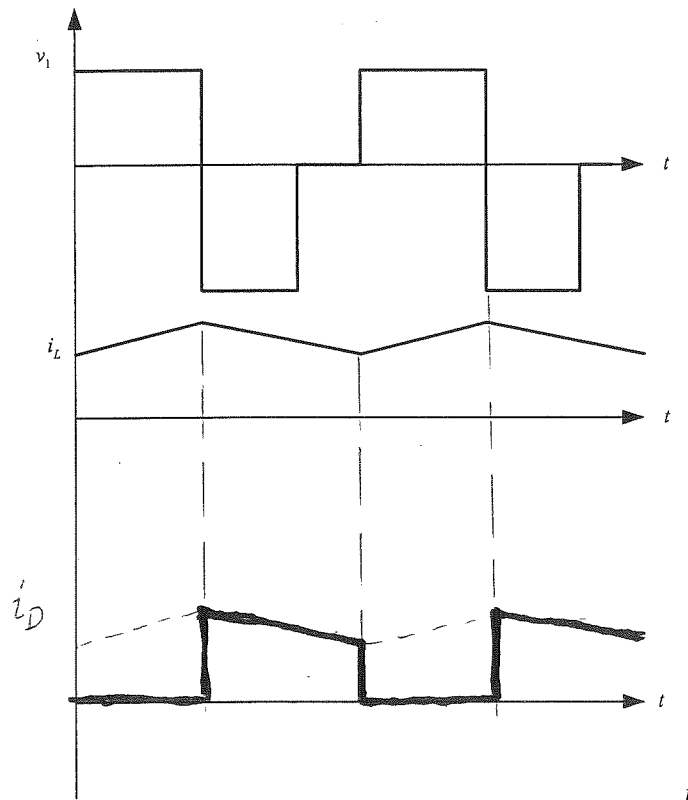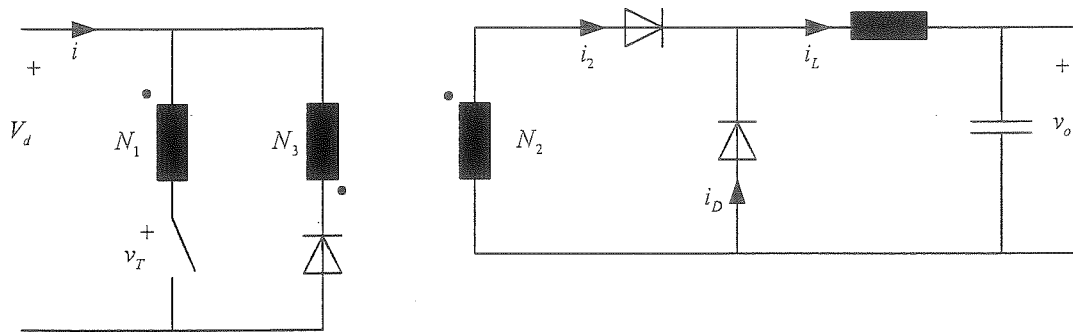1. Draw the waveform of i_D in the empty diagram below if v_1 is the voltage across Winding 1 and if $N_1 = N_2 = 40$ and $N_3 = 30$.





2. Estimate the average value of the output voltage if $V_d = 36$ V.

From the graph: $T_s = 38 \mu\text{s}$; $t_{ON} = 17 \mu\text{s} \Rightarrow D = \frac{17}{38}$

$$V_o = V_d \cdot \frac{N_2}{N_1} \cdot D = 36 \cdot 1 \cdot \frac{17}{38} = \underline{\underline{16,1 \text{ V}}}$$

Peer assessment #5 in Power Electronics, version D

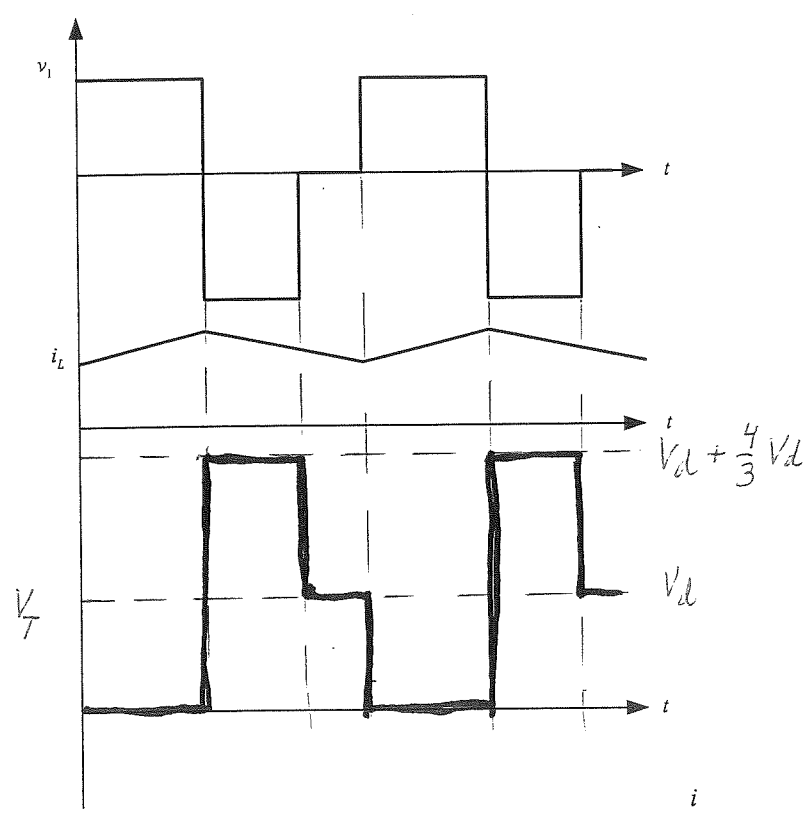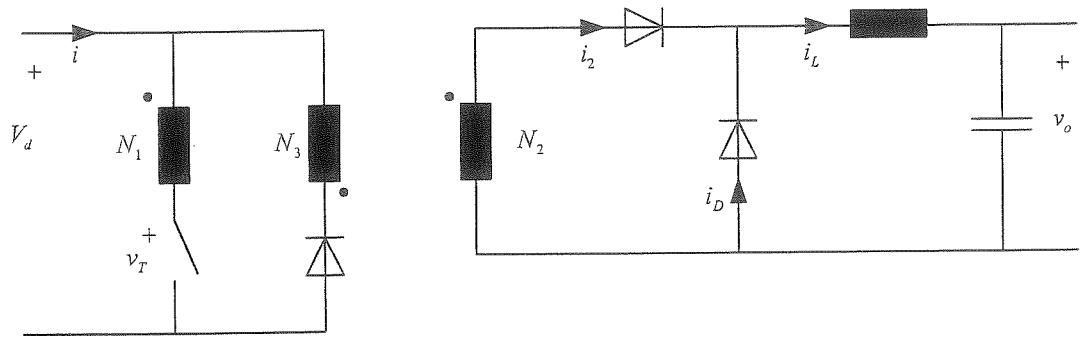1. Draw the waveform of v_r in the empty diagram below if v_1 is the voltage across Winding 1 and if $N_1 = N_2 = 40$ and $N_3 = 30$.



2. Estimate the average value of the output voltage if $V_d = 72$ V.

From the graph: $T_s = 38 \mu s$; $t_{on} = 17 \mu s \Rightarrow D = \frac{17}{38}$

$$V_o = V_d \cdot \frac{N_2}{N_1} \cdot D = 72 \cdot 1 \cdot \frac{17}{38} = \underline{\underline{32,2 \text{ V}}}$$