
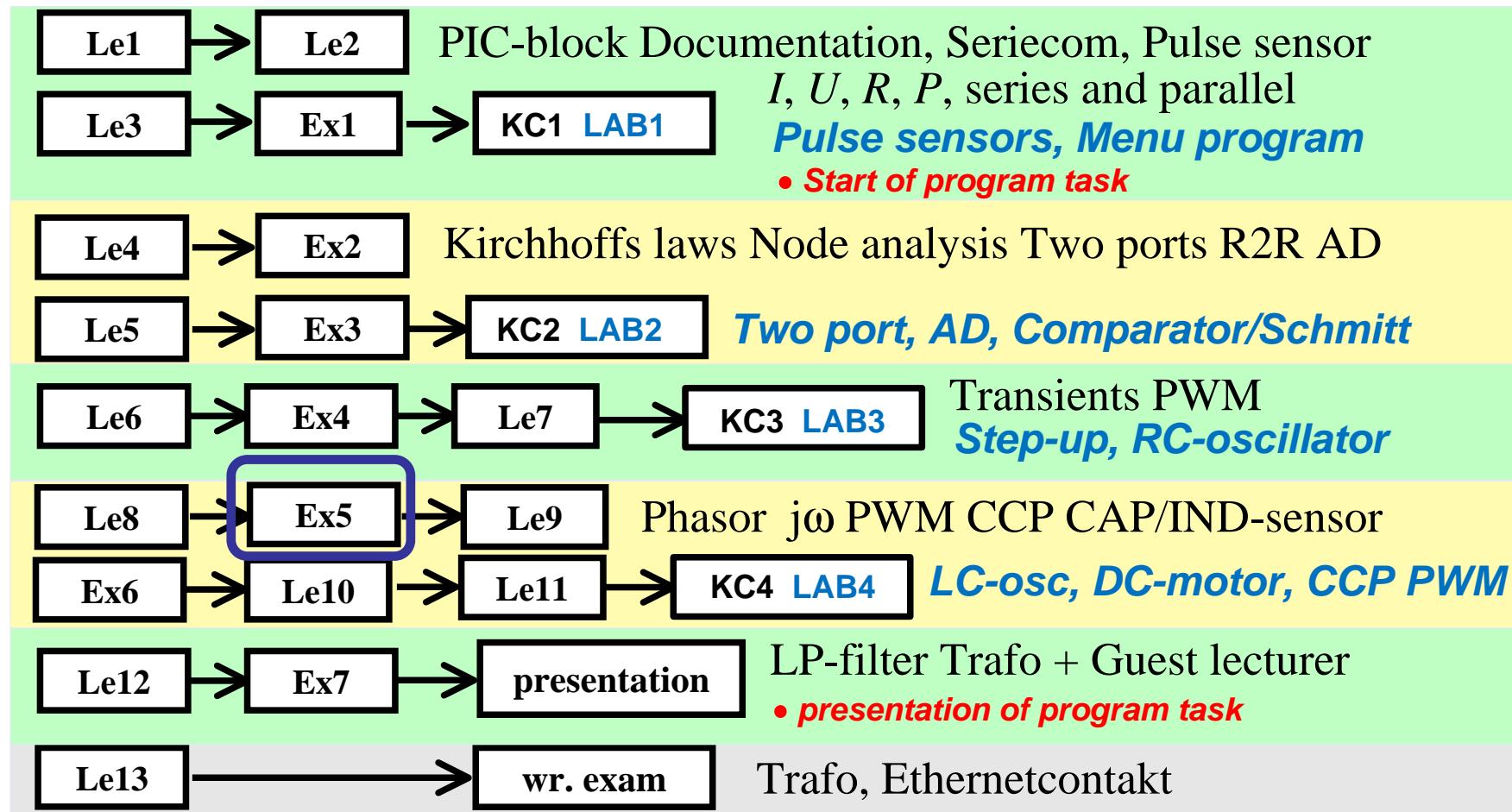


IE1206 Embedded Electronics

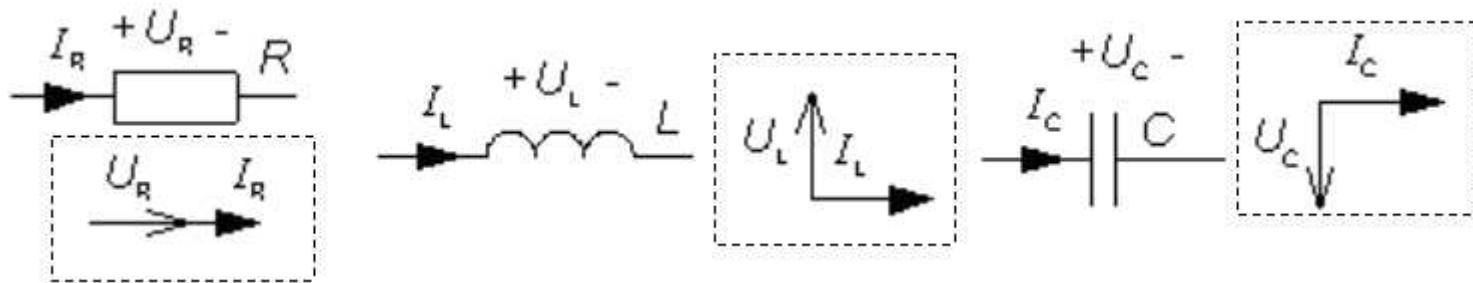

Phasor - vector




$$\omega = 2\pi f \quad |X_L| = \omega \cdot L \quad |X_C| = \frac{1}{\omega \cdot C}$$


$$Z = \frac{U}{I}$$

William Sandqvist william@kth.se

What's inside the circuit? (11.4)

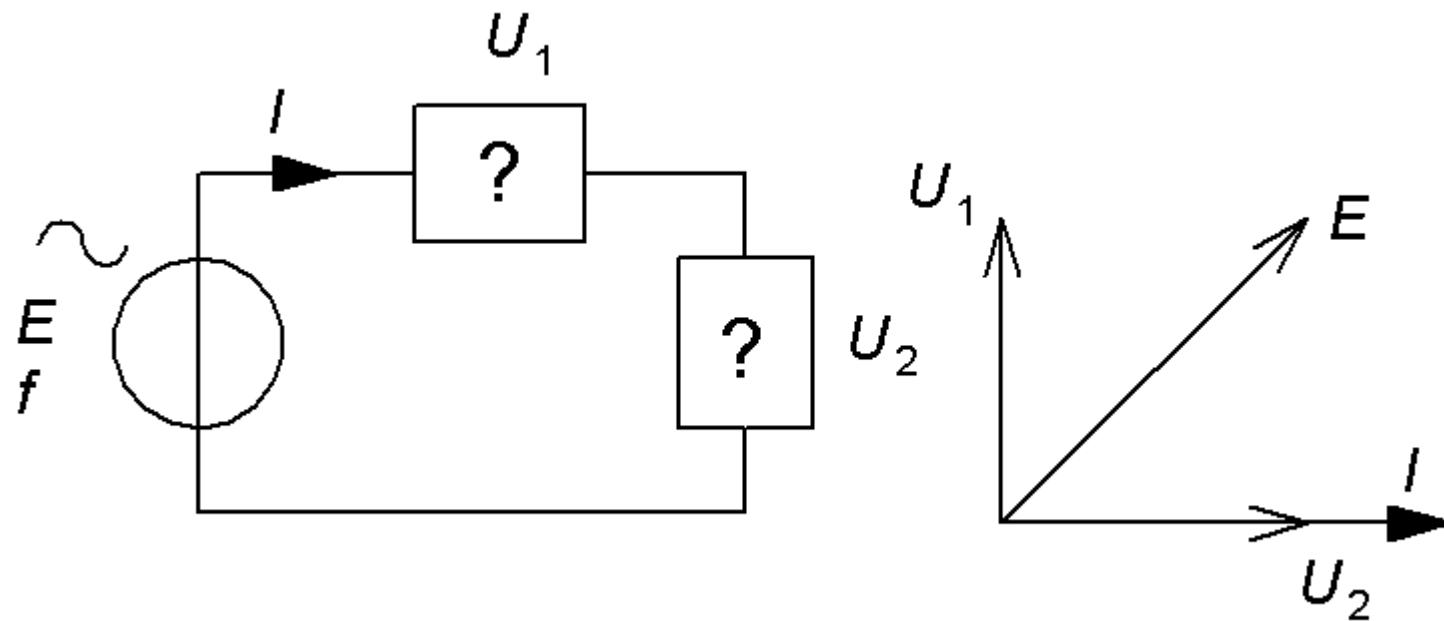


What's inside the circuit? (11.4)


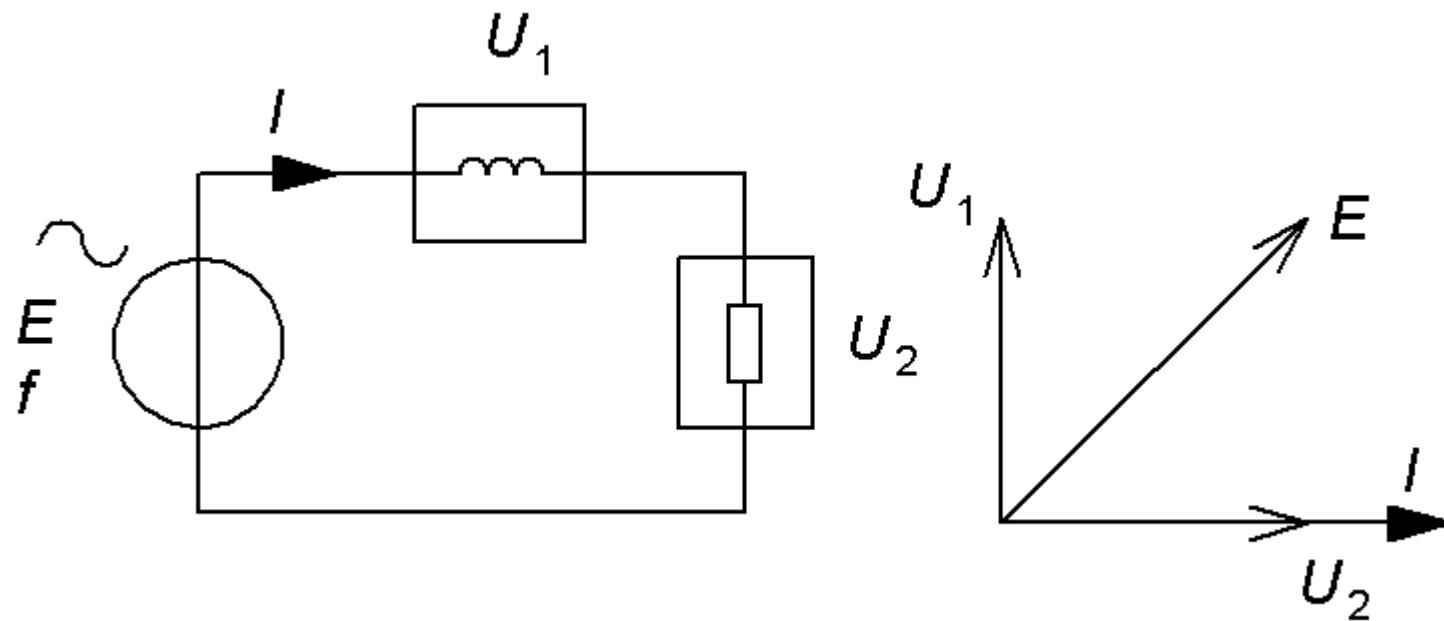


William Sandqvist william@kth.se

Phasor chart

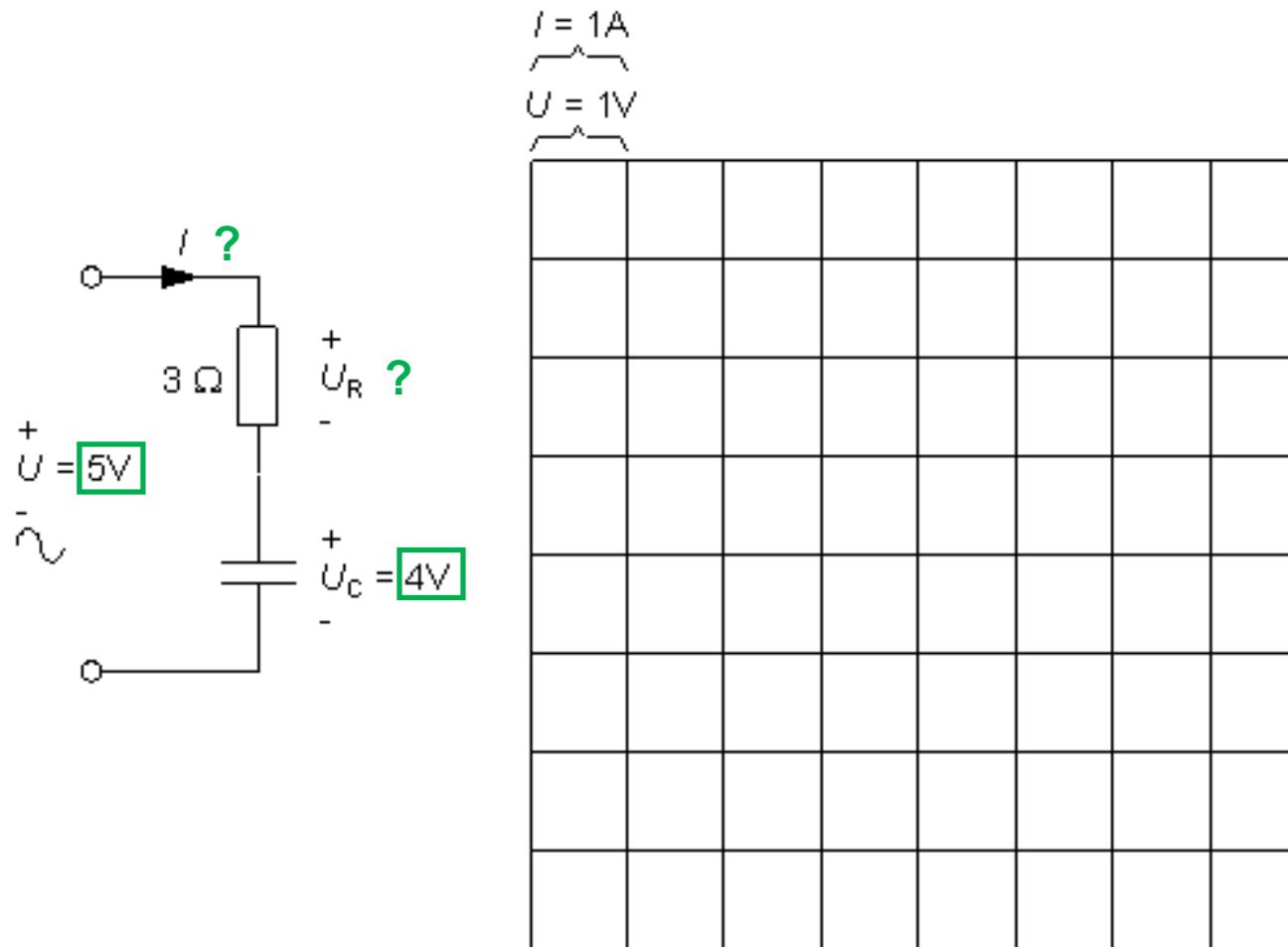


Phasor chart

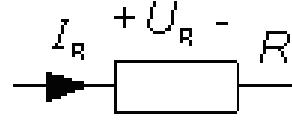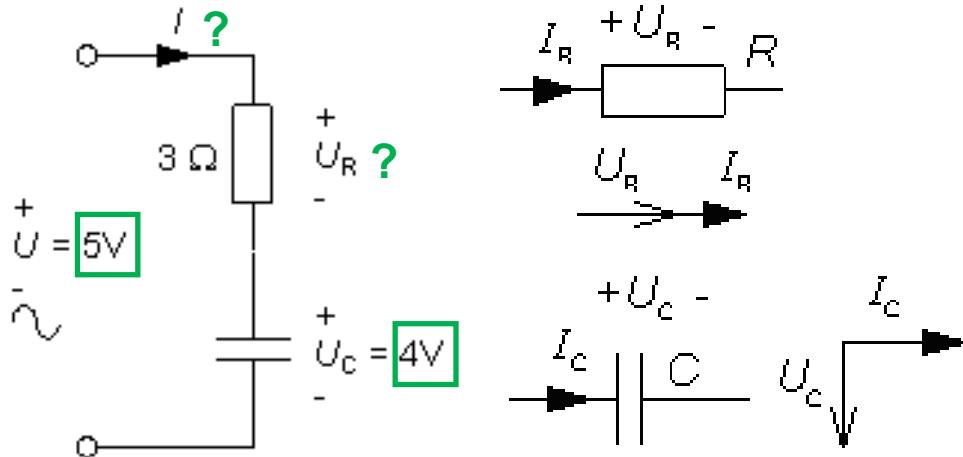

$$\underline{I}_R = \underline{I}_C = \underline{I}$$

$$\underline{U}_R \perp \underline{U}_C$$

$$U^2 = U_R^2 + U_C^2$$

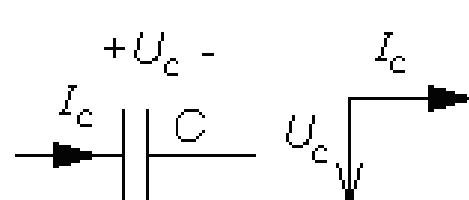


The two voltages have 90° phase angle. Pythagorean theorem applies!

$$U_R = \sqrt{U^2 - U_C^2} = \sqrt{5^2 - 4^2} = 3 \quad I = \frac{U_R}{R} = \frac{3}{3} = 1$$

Now all values are known!


Phasor chart

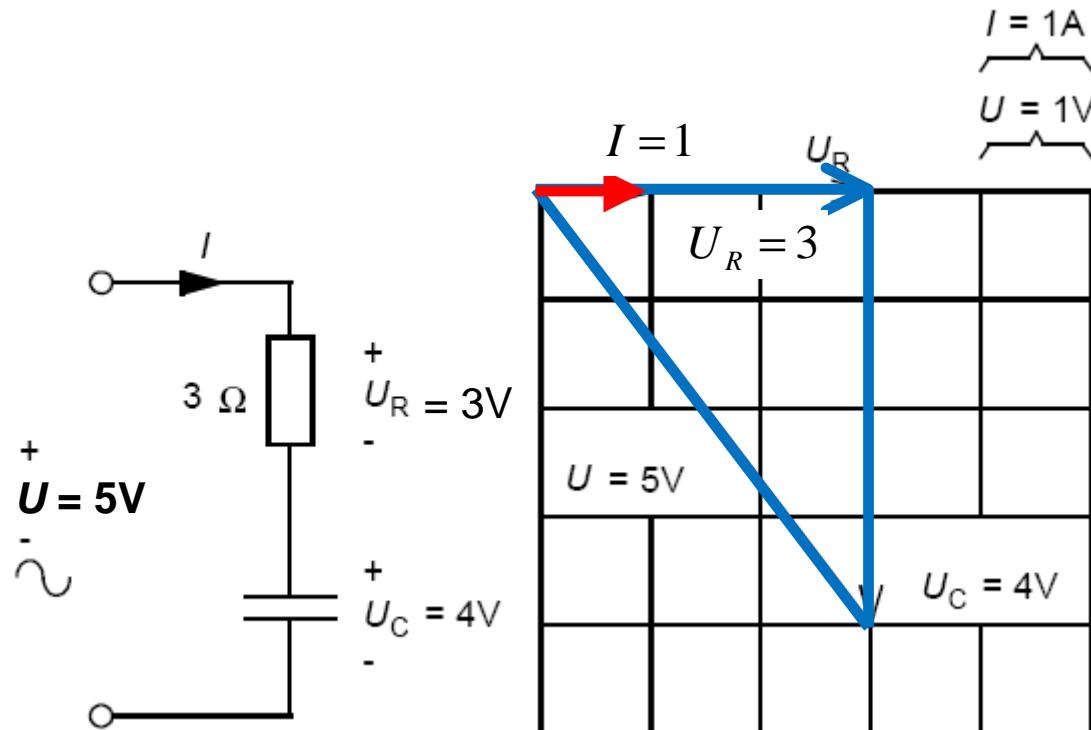

William Sandqvist william@kth.se

Phasor chart (11.6)

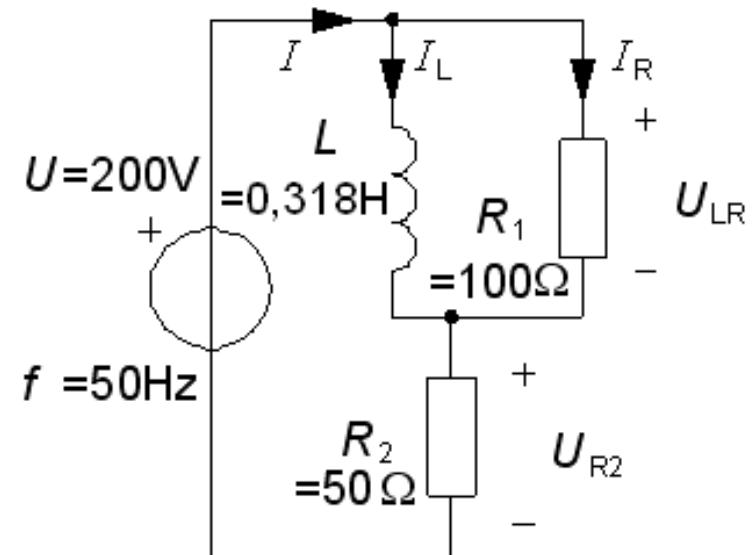
$U = 200 \text{ V}$, $f = 50 \text{ Hz}$,
 $L = 0,318 \text{ H}$, $R_1 = 100 \Omega$,
 $R_2 = 50 \Omega$.




Phasor chart (11.6)

$U = 200 \text{ V}$, $f = 50 \text{ Hz}$,
 $L = 0,318 \text{ H}$, $R_1 = 100 \Omega$,
 $R_2 = 50 \Omega$.

$$|X_L| = \omega \cdot L = 2\pi \cdot 50 \cdot 0,318 \\ = 100 \Omega$$

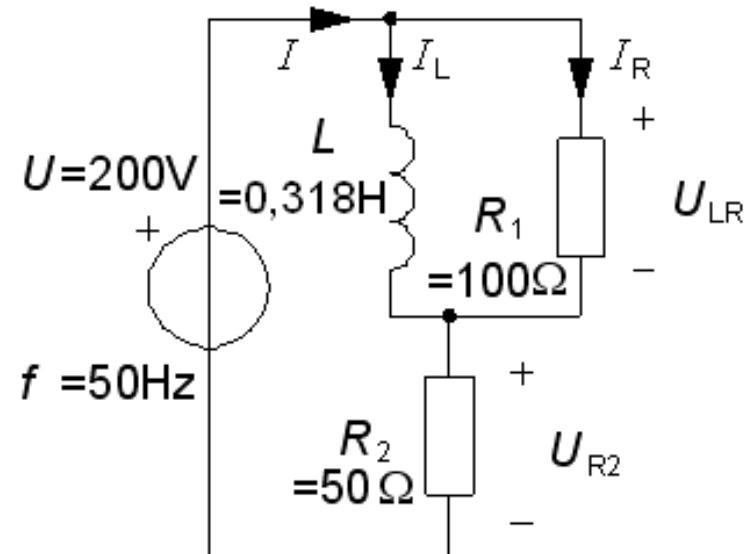

Phasor chart (11.6)

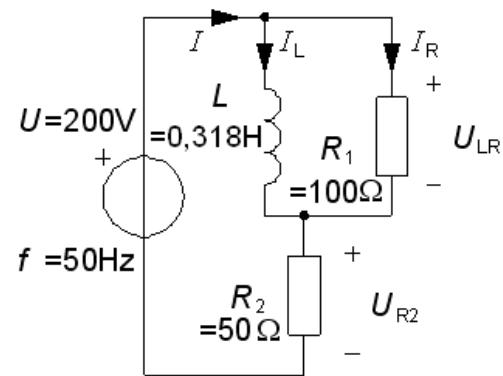

Phasor chart (11.6)




Choose U_{LR} as reference phase (= horizontal).

Phasor chart (11.6)




The current I_R has the same direction as U_{LR} .

Phasor chart (11.6)

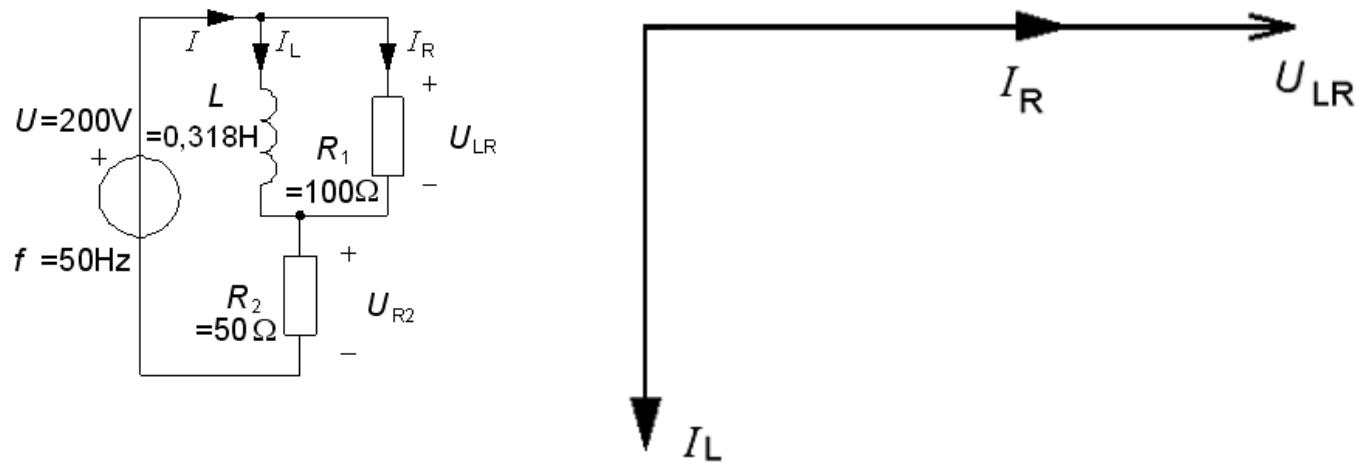


The current I_L lags 90° behind U_{LR} and has an equally long pointer as I_R because R_1 and L has the same impedance.
($|X_L| = 100 \Omega$, $R_1 = 100 \Omega$)

Phasor chart (11.6)

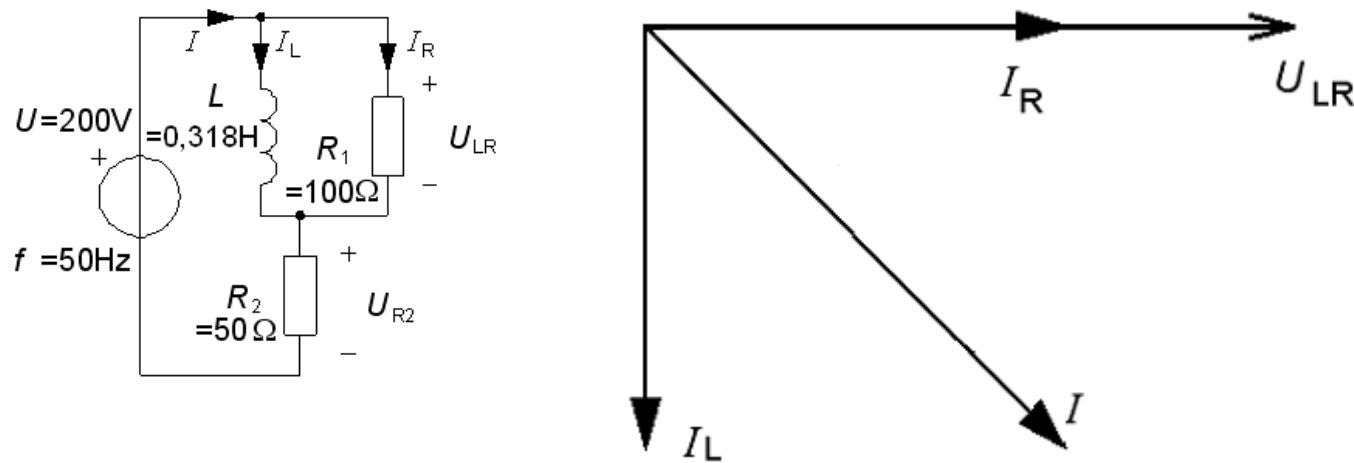

The two currents I_R and I_L can be added as vectors to the current I . I is $\sqrt{2}$ longer than I_R and I_L
(Pythagorean theorem applies!).

Phasor chart (11.6)


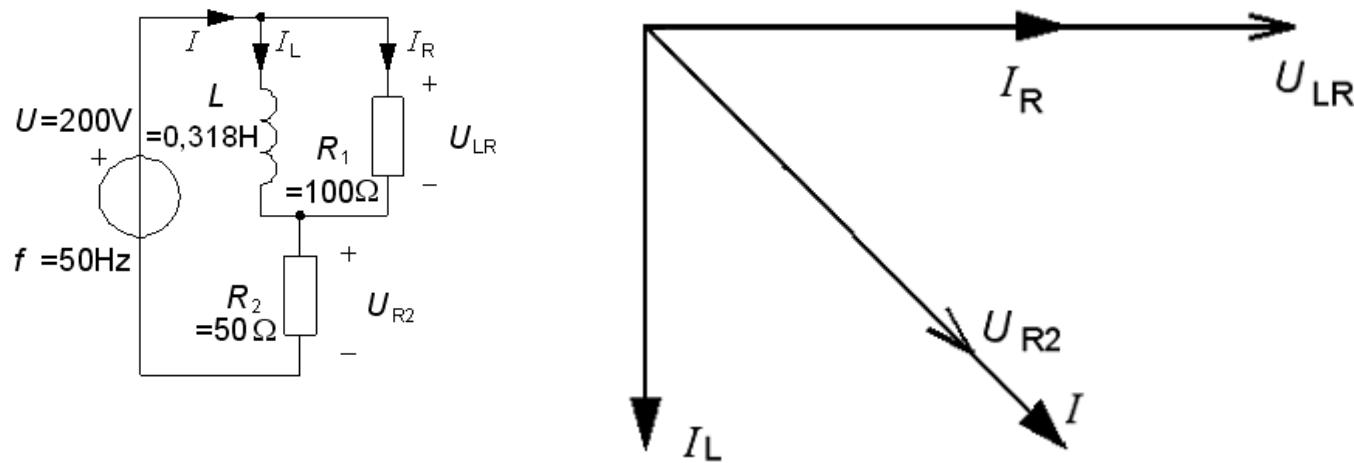


Current I passes through the lower resistor R_2 . The voltage drop U_{R2} gets the same direction as I .

U_{LR} has the length $I_R \cdot 100$, U_{R2} has length $I \cdot 50$.

Because $I = I_R \cdot \sqrt{2}$ we get $U_{R2} = U_{LR} / \sqrt{2}$.

Phasor chart (11.6)

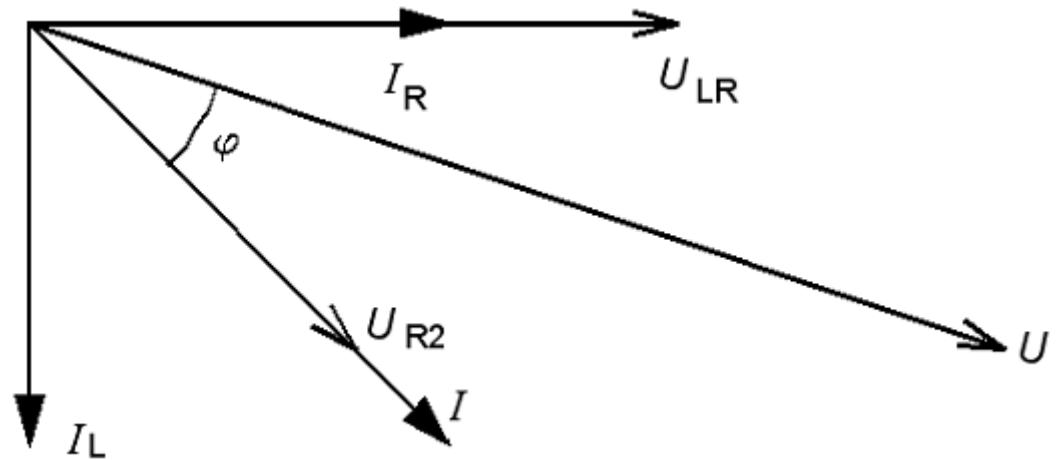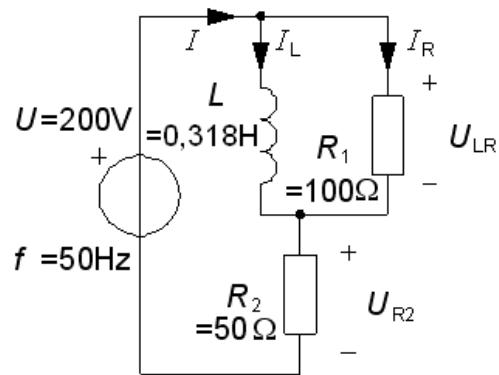

Voltage U can finally be determined as the vector sum of U_{LR} and U_{R2} .

- Phase φ is the angle between U and I .
- Z is the ratio between lengths of U and I .


The current after the voltage - inductive character

William Sandqvist william@kth.se

Phasor chart (11.7)

Draw the phasor chart for this circuit. At the frequency f applies that $|X_C| = R$ and $|X_L| = R/2$.

U_2 is a suitable reference phase.

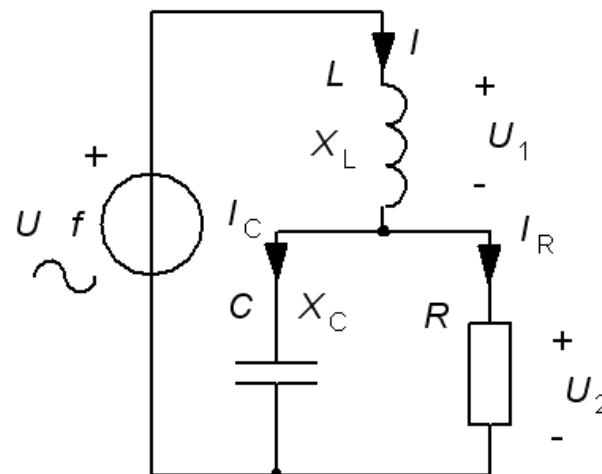

Phasor chart (11.7)





Start with U_2 as reference phase (= horizontal).

Phasor chart (11.7)





Current I_R has the same direction as U_2 .

Phasor chart (11.7)

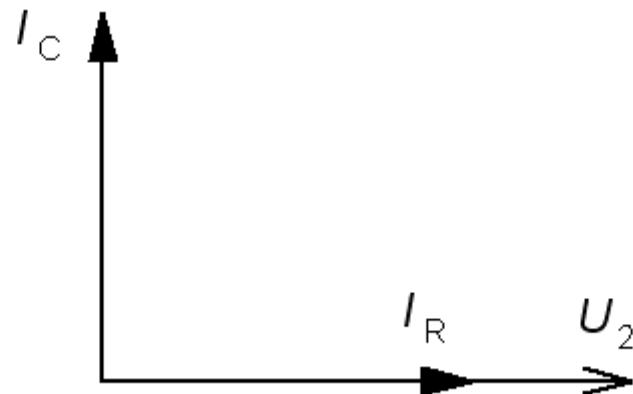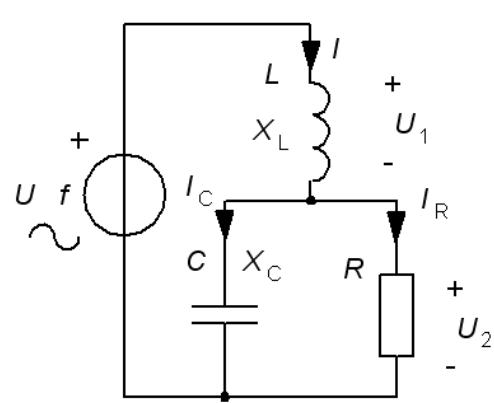

Current I_C leads 90° before U_2 and is equally long as I_R because $X_C = R$.


Phasor chart (11.7)

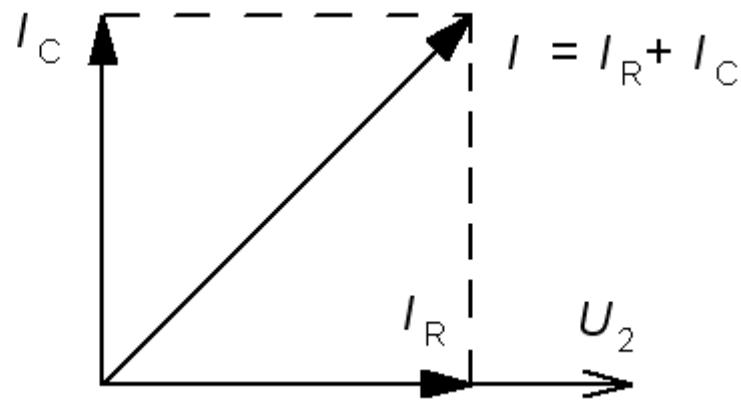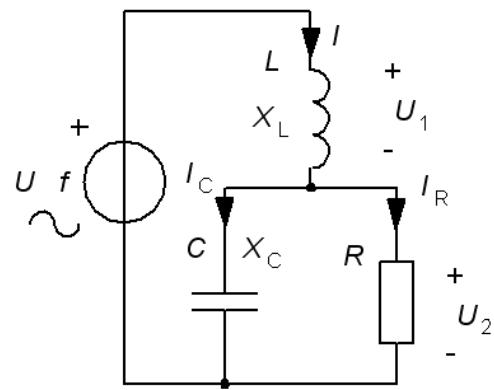

Current I_C and I_R are summed to I .

I is $\sqrt{2}$ times longer than I_C and I_R (Pythagorean theorem applies).


Phasor chart (11.7)

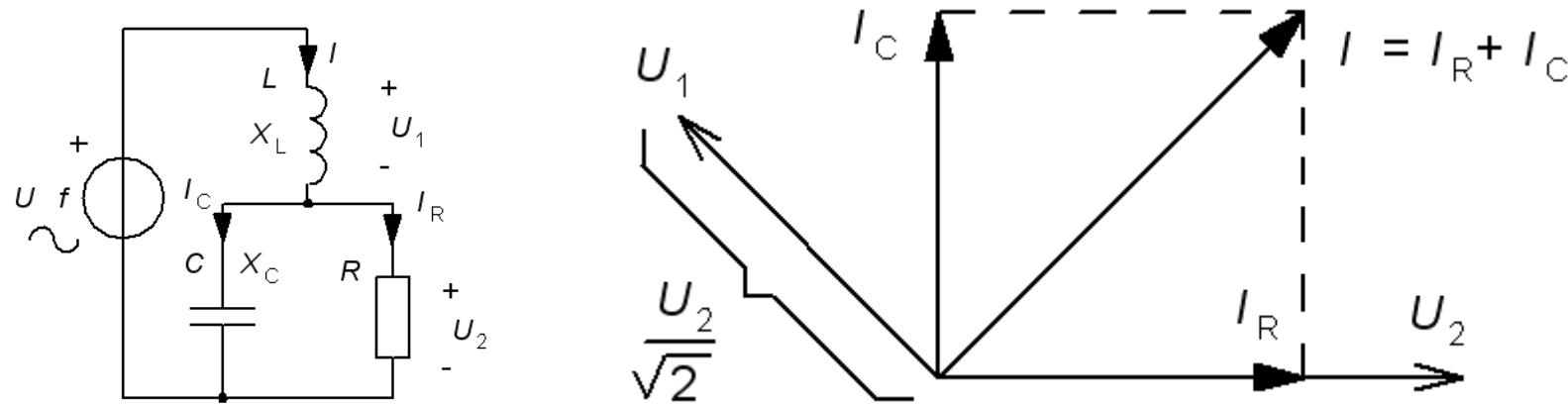

U_1 leads 90° before I .


The length is $U_1 = I \cdot X_L = \sqrt{2} \cdot I_R \cdot R / 2 = I_R \cdot R / \sqrt{2}$

Phasor chart (11.7)

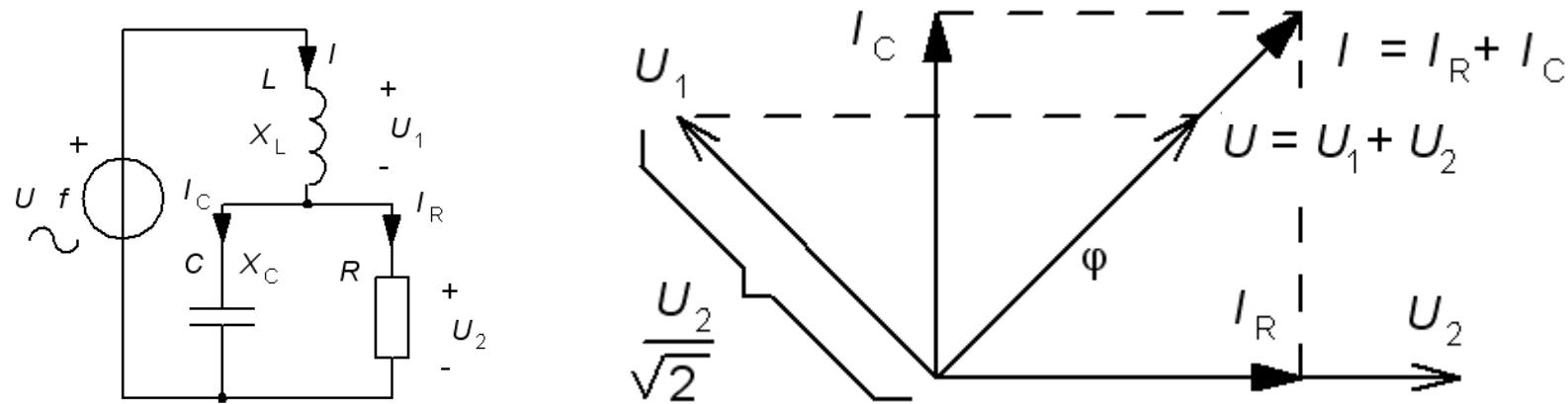

Voltage U_1 and U_2 are summed to voltage U .

Phasor chart (11.7)

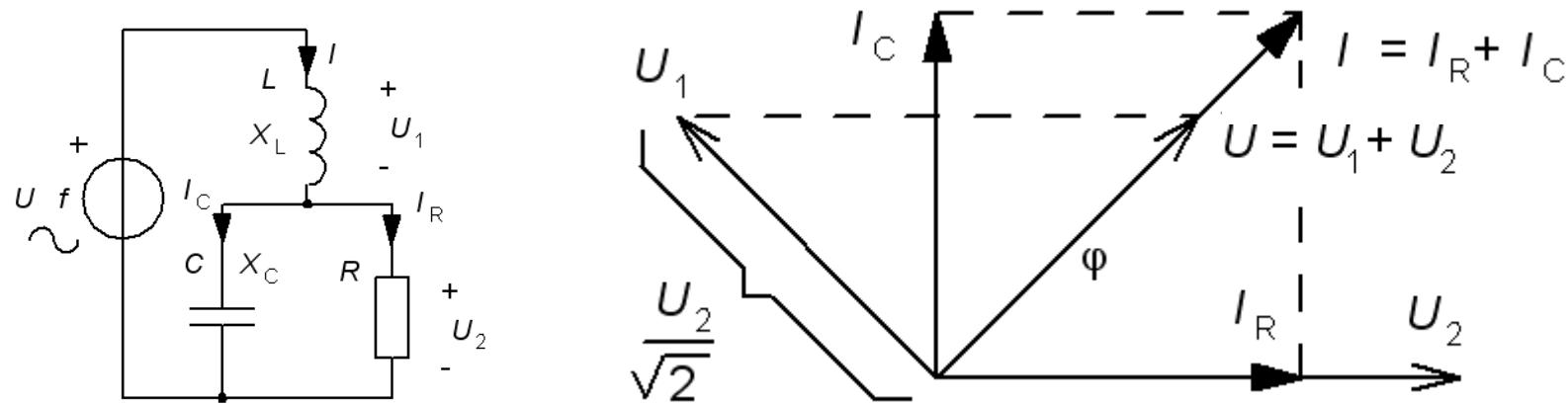

One can see from the chart that U becomes equal long to U_1 .
The angle $\varphi = 0$ and thereby U and I are in phase.

Inductive or capacitive character?

William Sandqvist william@kth.se

Complex numbers, $j\omega$ -method

Complex OHM's law for R L and C .

$$\underline{U}_R = \underline{I}_R \cdot R$$

$$\underline{U}_L = \underline{I}_L \cdot jX_L = \underline{I}_L \cdot j\omega L \quad X_L = \omega L$$

$$\underline{U}_C = \underline{I}_C \cdot jX_C = \underline{I}_C \cdot \frac{1}{j\omega C} \quad X_C = -\frac{1}{\omega C} \quad \omega = 2\pi \cdot f$$

Complex OHM's law for Z .


$$\boxed{\underline{U} = \underline{I} \cdot \underline{Z}}$$

$$Z = \frac{\underline{U}}{\underline{I}}$$


$$\varphi = \arg(\underline{Z}) = \arctan\left(\frac{\text{Im}[\underline{Z}]}{\text{Re}[\underline{Z}]}\right)$$

William Sandqvist william@kth.se

$j\omega$ Impedance (12.2)

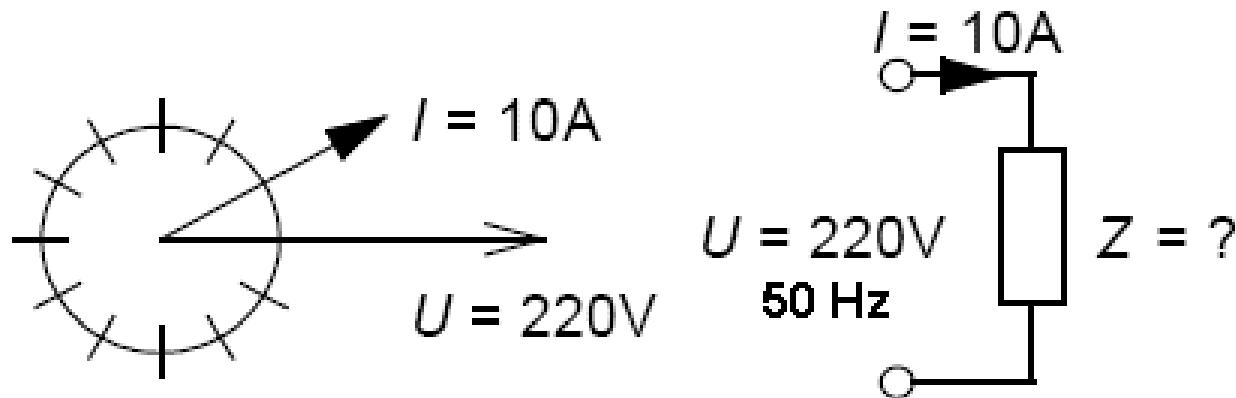


$j\omega$ Impedance (12.2)

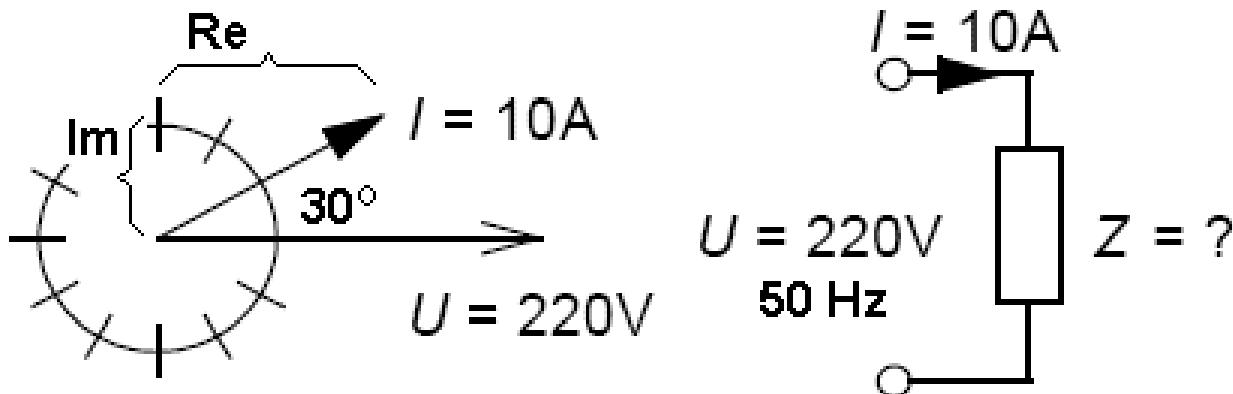


One can imagine that the phasor chart shows the complex plane, and then splitting the current phasor in real part and imaginary part:

$j\omega$ Impedance (12.2)

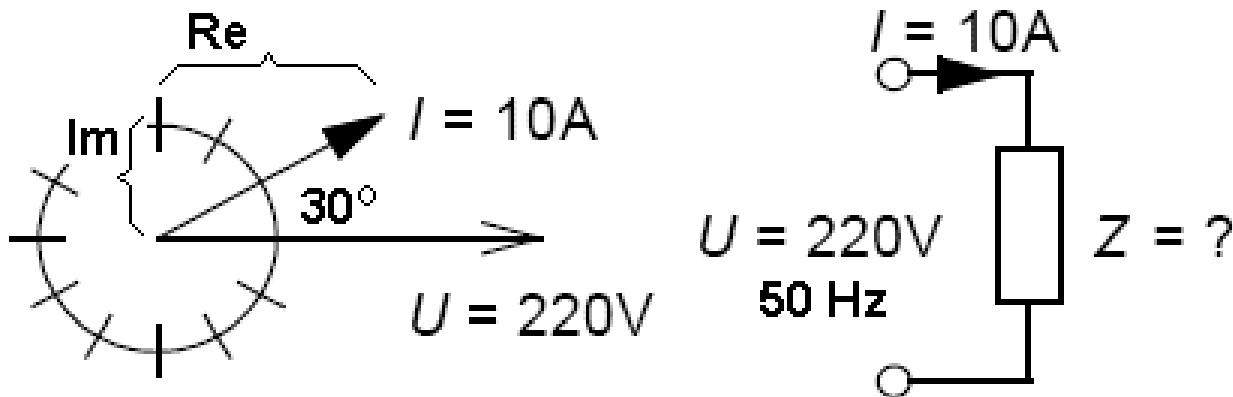

$$\begin{aligned} Z &= \frac{U}{I} = \frac{220}{10 \cdot (\cos(30^\circ) + j \cdot \sin(30^\circ))} = \\ &= \frac{220}{8,6 + 5j} \cdot \frac{(8,6 - 5j)}{(8,6 - 5j)} = \frac{1892 - 1100j}{99} = 19,1 - 11,1j \end{aligned}$$

$j\omega$ Impedance (12.2)

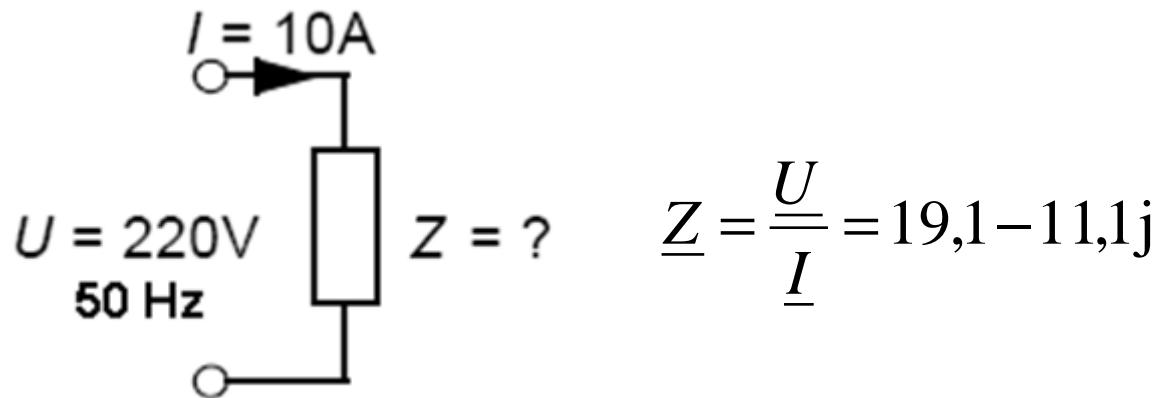


- One possible solution is then a series circuit with R and C


$$R = 19,1 \Omega \quad X_C = -\frac{1}{\omega C} = -11,1$$

$$C = -\frac{1}{2\pi \cdot 50 \cdot (-11,1)} = 287 \mu\text{F}$$


Capacitor has negative
reactance.

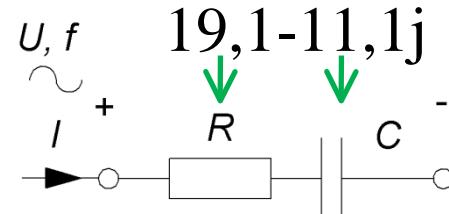



$j\omega$ Impedance (12.2)

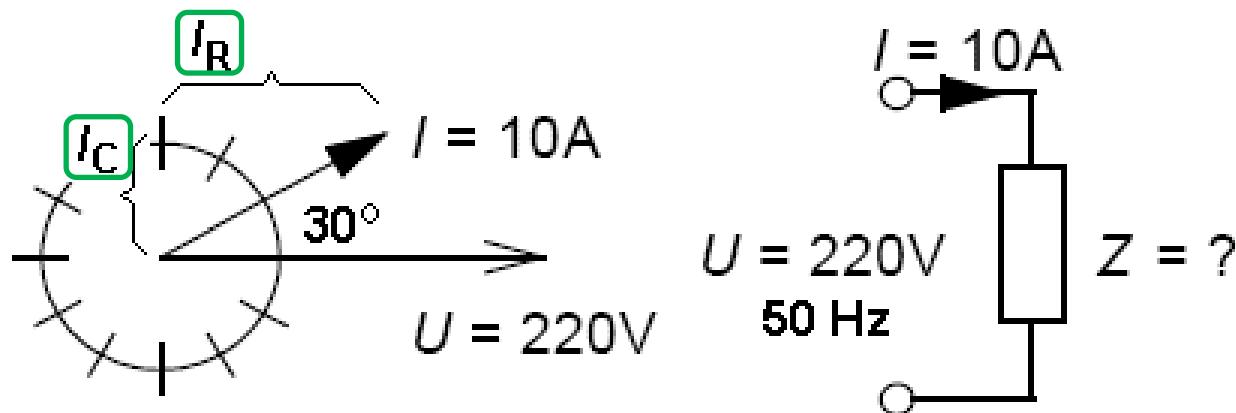

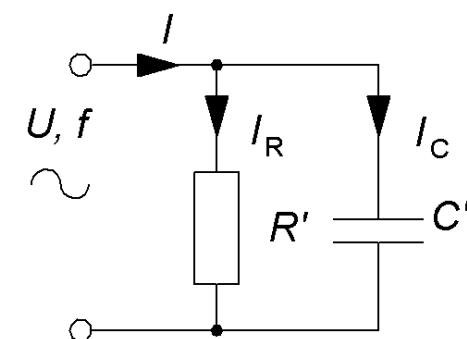- Another possible solution is a parallel circuit with R' and C' one then thinks on I as divided in to **current composants** I_R and I_C which are perpendicular to each other.



$j\omega$ Impedance (12.2)

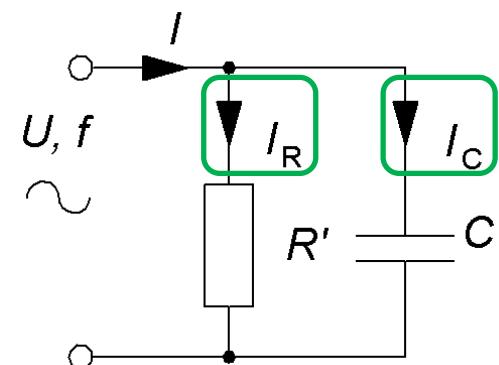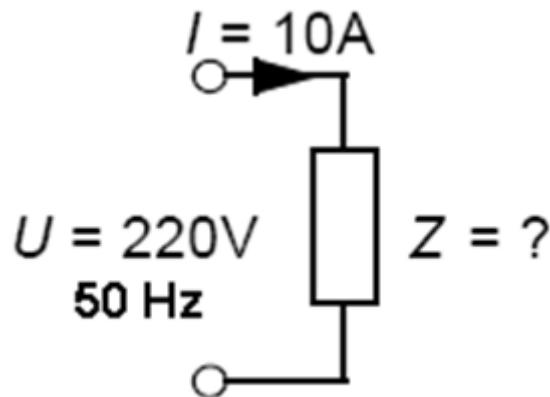


$$R' = \frac{U}{I_R} = \frac{U}{I \cos 30^\circ} = \frac{220}{10 \cdot 0,87} = 25,3 \Omega$$



$$|X'_C| = \frac{U}{I_C} = \frac{U}{I \sin 30^\circ} = \frac{220}{10 \cdot 0,5} = 44 \Omega$$

$$|X'_C| = \frac{1}{\omega C'} \Rightarrow C' = \frac{1}{2\pi \cdot 50 \cdot 44} = 72,6 \mu\text{F}$$

$j\omega$ Impedance (12.2)

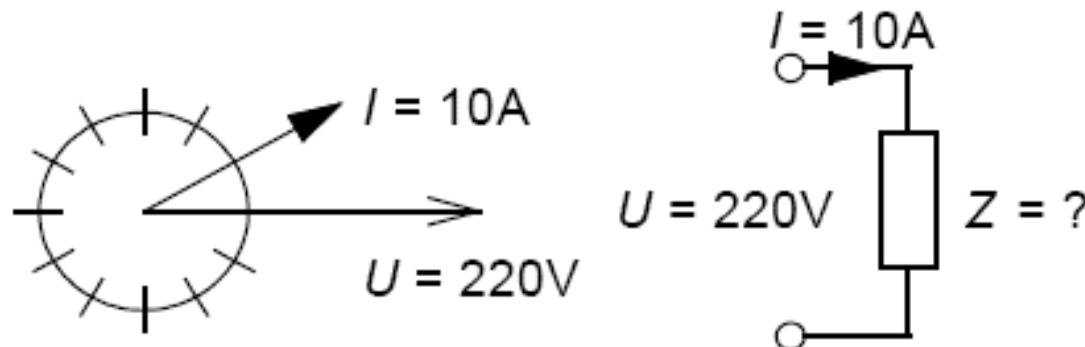

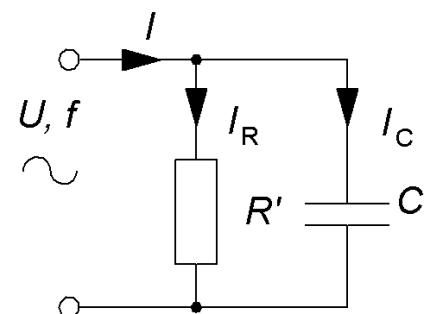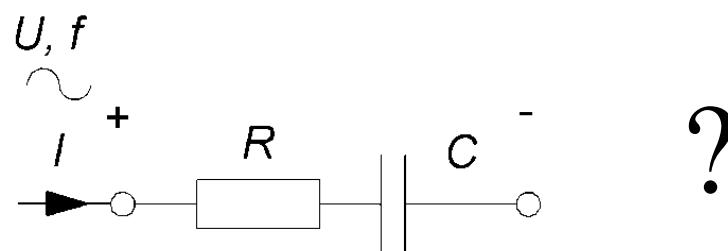
Is there any way to find out which of the two proposed circuits Z actually contain?



William Sandqvist william@kth.se


Complex impedance (12.6)

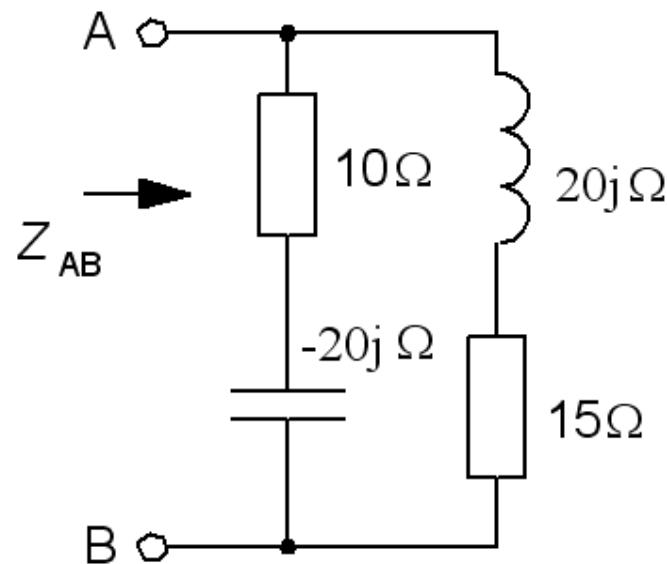Determine the complex impedance Z_{AB} of this circuit.



Complex numbers calculation


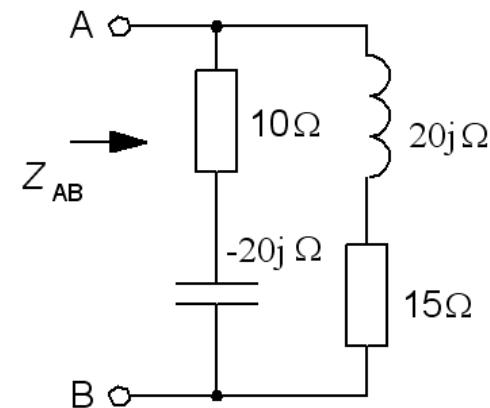
$$\begin{aligned} Z_{AB} &= \frac{(15 + j20) \cdot (10 - j20)}{15 + j20 + 10 - j20} = \\ &= \frac{550 - j100}{25} = \\ &= 22 - j4 \text{ } [\Omega] \end{aligned}$$



Here the denominator directly was a real number so there no need to multiply with the complex conjugate of the denominator, otherwise the calculations had been moore extensive...

Complex numbers calculation
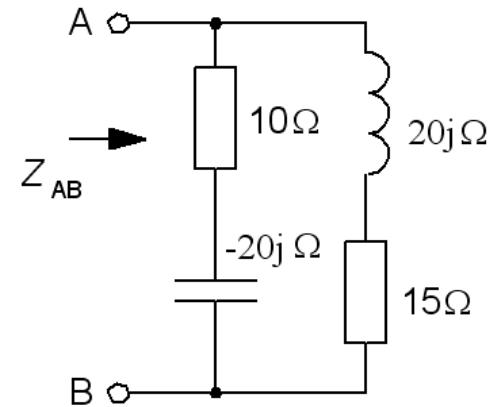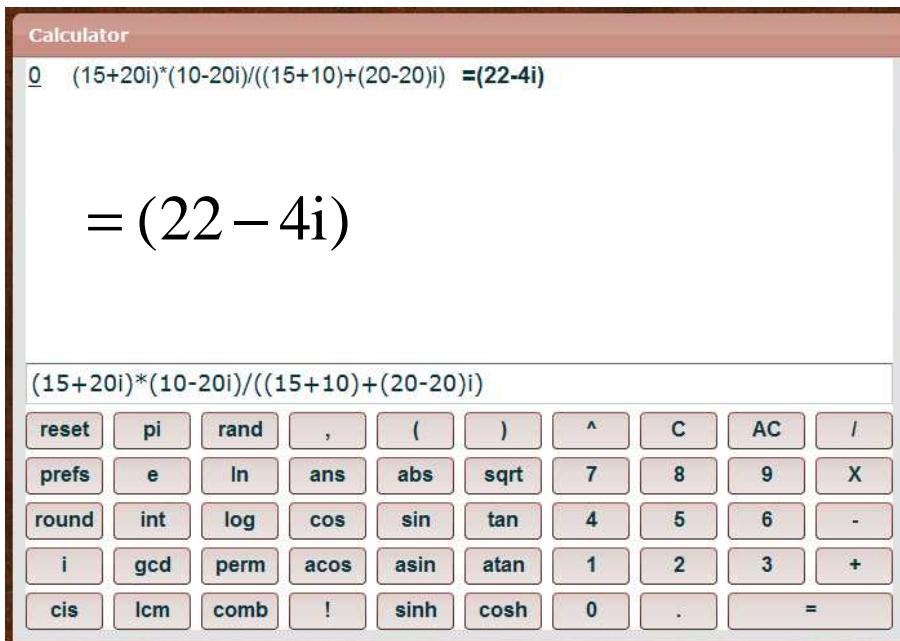
$$Z_{AB} = \frac{(15 + j20) \cdot (10 - j20)}{15 + j20 + 10 - j20} =$$




[Online Scientific
Calculator](#)

William Sandqvist william@kth.se

"heavy" calculations! (12.9)

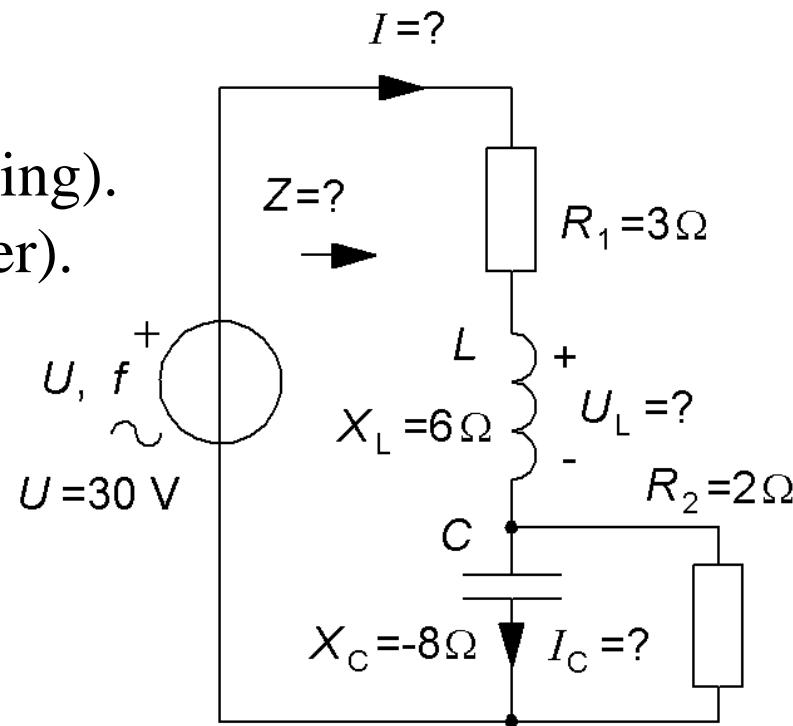
- Calculate impedance Z .
- Calculate current I .
- Calculate I_C (current branching).
- Calculate U_L (voltage divider).



Calculate impedance Z

$$\underline{Z}_{R||C} = \frac{2 \cdot (-8j)}{2 - 8j} \cdot \frac{(2 + 8j)}{2 + 8j} = \\ = 1,88 - 0,47j$$

$$\underline{Z} = R_1 + jX_L + \underline{Z}_{R||C} = \\ = 3 + 6j + (1,88 - 0,47j) = 4,88 + 5,53j$$

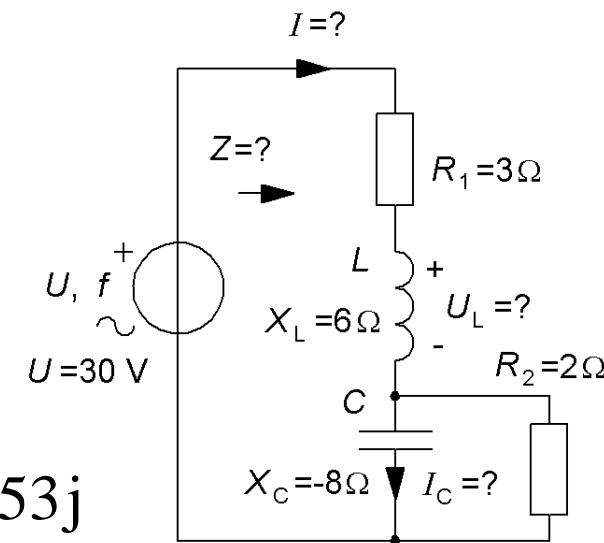


$$Z = \sqrt{4,88^2 + 5,53^2} = 7,38 \Omega$$

Calculate current I

U is reference phase, real.

$$\underline{I} = \frac{\underline{U}}{\underline{Z}} = \frac{30}{4,88 + 5,53j} \cdot \frac{(4,88 - 5,53j)}{(4,88 - 5,53j)} =$$
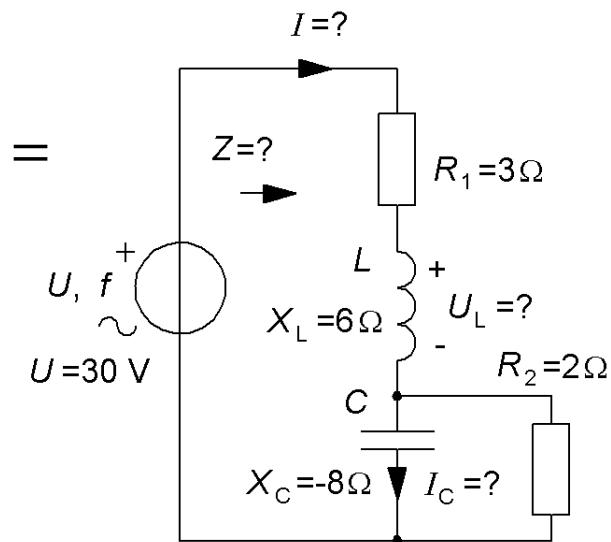
$$= \frac{146,5 - 165,9j}{4,88^2 + 5,53^2} = 2,7 - 3j$$




$$I = \sqrt{2,7^2 + 3^2} = 4 \text{ A}$$

Calculate current I_C

$$I_C = \frac{R_2}{R_2 + jX_C} = (2,7 - 3j) \cdot \frac{2}{2 - 8j} =$$

$$= \frac{(2,7 - 3j) \cdot 2}{2 - 8j} \cdot \frac{(2 + 8j)}{(2 + 8j)} = 0,86 + 0,46j$$
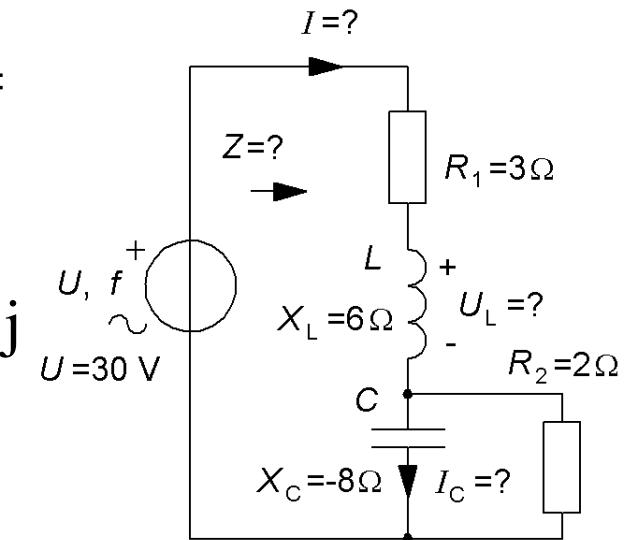
$$I_C = \sqrt{0,86^2 + 0,46^2} = 0,98 \text{ A}$$




U_L complex conjugate method?

$$\underline{U}_L = U \frac{jX_L}{jX_L + Z_{R||C} + R_1} = \\ = 30 \frac{6j}{6j + (1,88 - 0,47j) + 3} =$$

$$= 30 \frac{6j}{4,88 + 5,53j} \cdot \frac{(4,88 - 5,53j)}{(4,88 - 5,53j)} = 18,3 + 16,2j$$
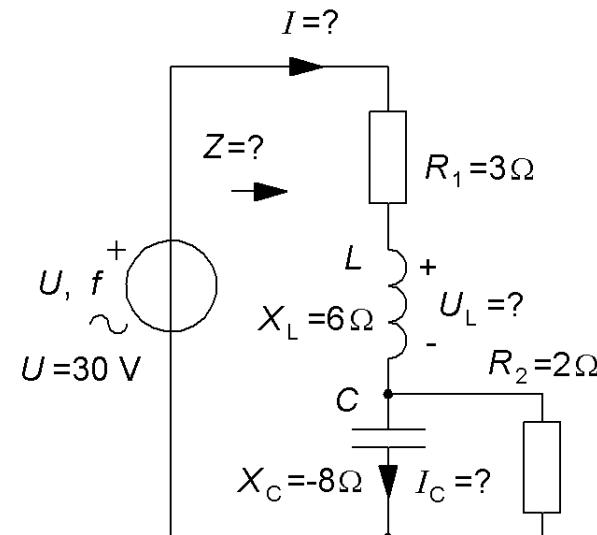
$$U_L = \sqrt{18,3^2 + 16,2^2} = 24,4 \text{ V}$$



Amount and phase

$$\underline{Z} = \underline{Z}_1 \cdot \underline{Z}_2 \quad |\underline{Z}| = |\underline{Z}_1 \cdot \underline{Z}_2| = |\underline{Z}_1| \cdot |\underline{Z}_2|$$

$$\arg(\underline{Z}) = \arg(\underline{Z}_1) + \arg(\underline{Z}_2)$$

$$\underline{Z} = \frac{\underline{Z}_1}{\underline{Z}_2} \quad |\underline{Z}| = \left| \frac{\underline{Z}_1}{\underline{Z}_2} \right| = \frac{|\underline{Z}_1|}{|\underline{Z}_2|}$$

$$\arg(\underline{Z}) = \arg(\underline{Z}_1) - \arg(\underline{Z}_2)$$

U_L amount \angle phase method?

Amount \angle phase method, the polar form, often gives simpler calculations, but nowadays most math programs and pocket calculators handles complex numbers directly ...

$$\begin{aligned} \underline{U}_L &= U \frac{jX_L}{jX_L + Z_{R||C} + R_1} = 30 \frac{6j}{6j + (1,88 - 0,47j) + 3} = \\ &= 30 \frac{6j}{4,88 + 5,53j} = 30 \frac{6}{\sqrt{4,88^2 + 5,53^2}} \angle \arctan\left(\frac{5,53}{4,88}\right) = \\ &= 30 \frac{6}{7,38} \angle (90^\circ - 48,6^\circ) = 24,4 \angle 41,4^\circ \end{aligned}$$


$$U_L = 24,4 \text{ V}$$

William Sandqvist william@kth.se

Derive the complex current I (12.7)

Set up the complex current I (with U as reference phase).

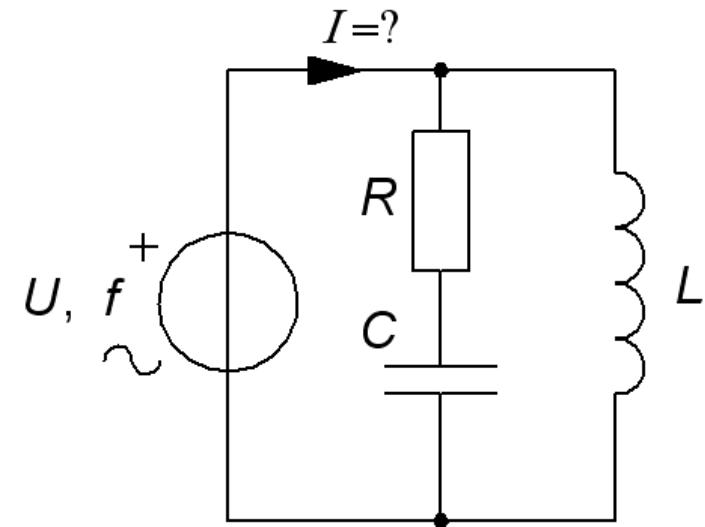
Note! One does not always have to give the answer of the form $a+jb$. The same information, but with less effort, one gets if the answer is expressed as a ratio of complex numbers. Amount and phase can if necessary be taken from the numerator and the denominator directly.



Derive the complex current I (12.7)

Set up the complex current I (with U as reference phase).

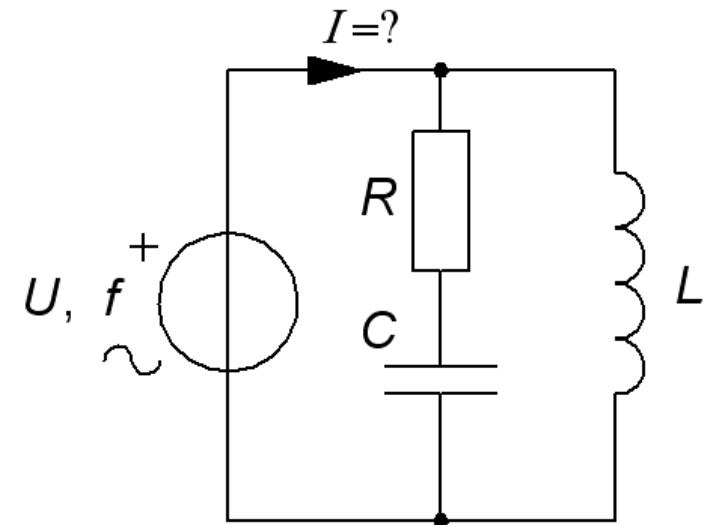Note! One does not always have to give the answer of the form $a+jb$. The same information, but with less effort, one gets if the answer is expressed as a ratio of complex numbers. Amount and phase can if necessary be taken from the numerator and the denominator directly.




$$\underline{I} = \frac{a + jb}{c + jd} \quad I = \frac{|a + jb|}{|c + jd|} \quad \arg(\underline{I}) = \arg(a + jb) - \arg(c + jd)$$

Note!

Derive the complex current I (12.7)

Set up the complex current I (With U as the reference phase).
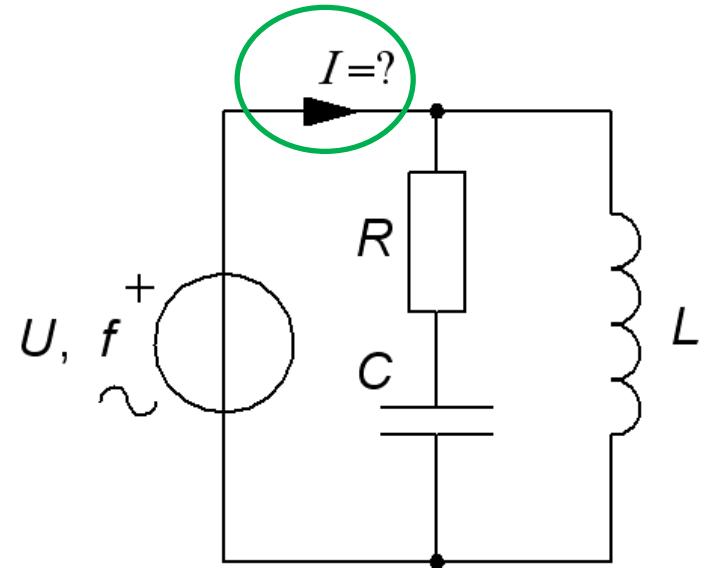
$$\underline{Z} = \frac{(R + \frac{1}{j\omega C}) \cdot j\omega L}{R + j\omega L + \frac{1}{j\omega C}} = \frac{\frac{L}{C} + j\omega LR}{R + j(\omega L - \frac{1}{\omega C})}$$



$$I = \frac{U}{\underline{Z}} = U \frac{R + j(\omega L - \frac{1}{\omega C})}{\frac{L}{C} + j\omega LR}$$


Sufficiently simplified!

That it is U which is the reference phase can be seen that we let the voltage be a real number!

William Sandqvist william@kth.se

Derive the complex current I (12.8)

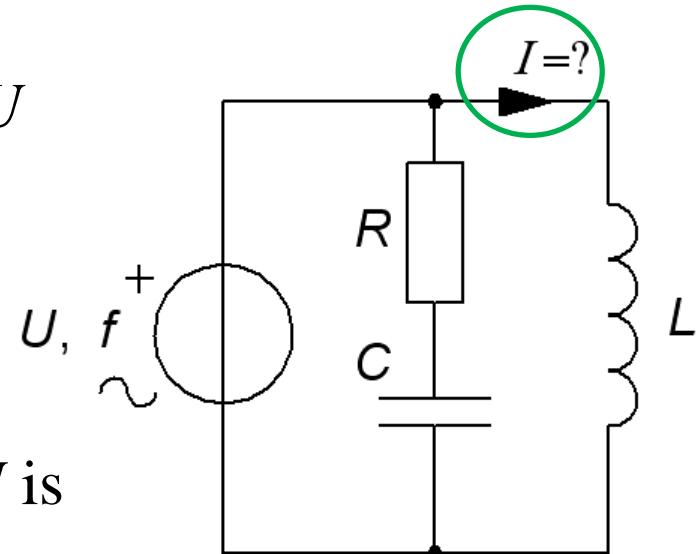Set up the complex current I (With U as the reference phase).



Now it will be easier! The voltage U is located directly across the parallel branch with the inductance L . (We need not concern ourselves with R and C)

$$\underline{I} = \frac{U}{j\omega L} = -j \frac{U}{\omega L}$$

William Sandqvist william@kth.se