 



# Digital or Analog

1 1/2 1/4 1/8 1/16 1/32 1/64 1/128  
 binary coded funnels

- digitally:  
 $q$  0 ... 255



- Digital style*

 

- or analog?




- Old school*

# Digital→Analog converter?

$b_7b_6b_5b_4b_3b_2b_1b_0$

- Binary coded resistor values


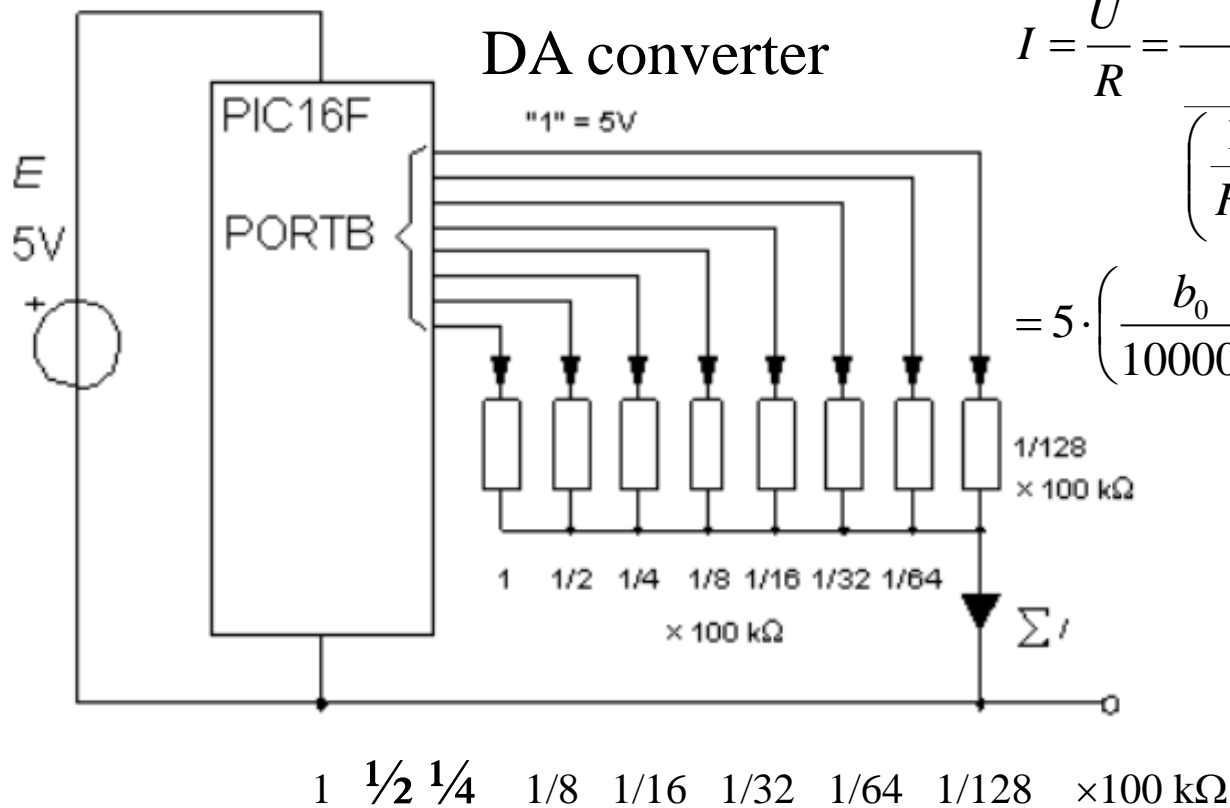


$$I = \frac{U}{R} = \frac{U}{\frac{1}{\left(\frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_n}\right)}}$$

$$= 5 \cdot \left( \frac{b_0}{100000} + \frac{b_1}{50000} + \frac{b_2}{25000} + \dots + \frac{b_7}{781} \right)$$

The current  $I$  is the **sum** of the currents from the "binary coded" resistors.

# Digital→Analog converter?

 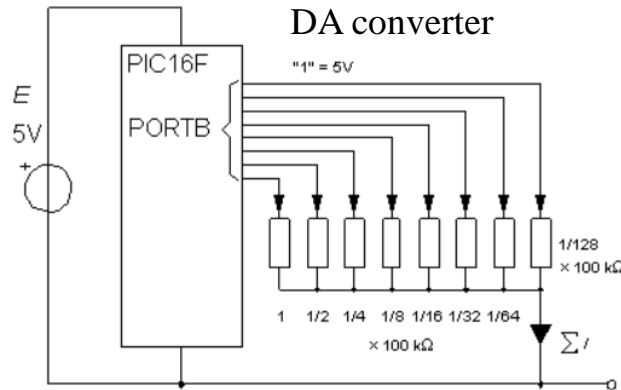

$$I = \frac{U}{R} = 5 \cdot \left( \frac{b_0}{100000} + \frac{b_1}{50000} + \frac{b_2}{25000} + \frac{b_3}{12500} + \frac{b_4}{6250} + \frac{b_5}{3125} + \frac{b_6}{1563} + \frac{b_7}{781} \right)$$

$$I_{\max} = 5 \cdot \left( \frac{1}{100000} + \frac{1}{50000} + \frac{1}{25000} + \frac{1}{12500} + \frac{1}{6250} + \frac{1}{3125} + \frac{1}{1563} + \frac{1}{781} \right) = 128 \mu\text{A}$$

# Problems with tolerances


Binary coded resistors for 8 bit.

Biggest resistor *exactly* **100000  $\Omega$**  and  
smallest resistor *exactly* **781  $\Omega$**  (preferably  
781,25 )?


**It is difficult to manufacture such various resistors with tight tolerances.**

- There is a better solution!


**R2R- method.**

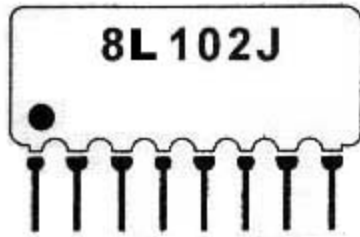

# R-2R-ladder

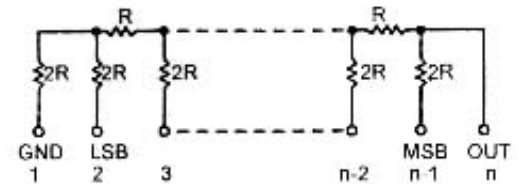

$$b_4 b_3 b_2 b_1 b_0$$

 


Just one resistance value needs to be manufactured,  $R$ , and then  $R+R=2R$ . One must be able to produce many "equal" resistors - the exact value is no longer important.

# Two-terminal equivalent $R_I$

The R2R-ladder is not that easy to understand ...

Repeated use of two-terminal equivalents and the superposition rule is what is required.


R-2R  $b_0=0$   $R_I=?$

 

$R_I = ?$

$$R_I = \frac{2 \cdot 2}{2 + 2} = 1 \text{ k}\Omega$$

R-2R  $b_0=1$   $R_I=?$

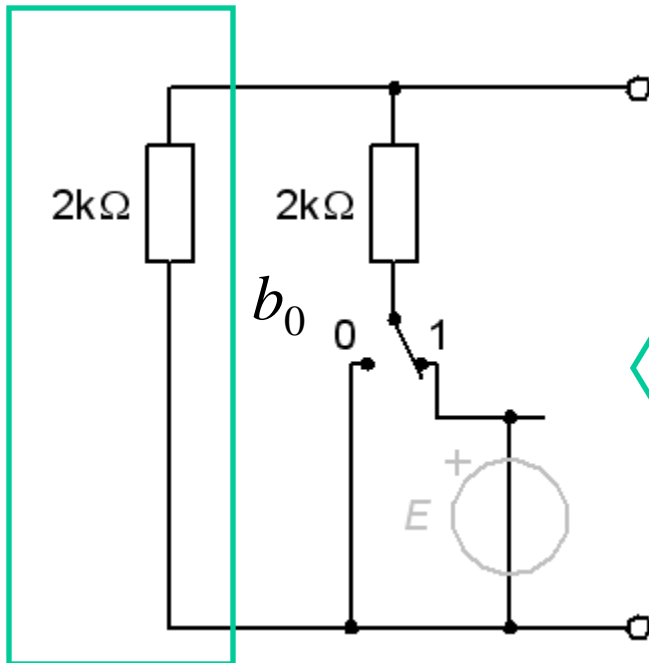


$R_I = ?$

$$R_I = \frac{2 \cdot 2}{2 + 2} = 1 \text{ k}\Omega$$

$b_0$  1 or 0, same internal resistance!




R-2R  $b_0$   $R_I = ?$

 

$$R_I = 1 + 1 = 2 \text{ k}\Omega$$

**The total resistance of one stage becomes 2 kΩ.**


R-2R  $b_1=0$   $R_I=?$

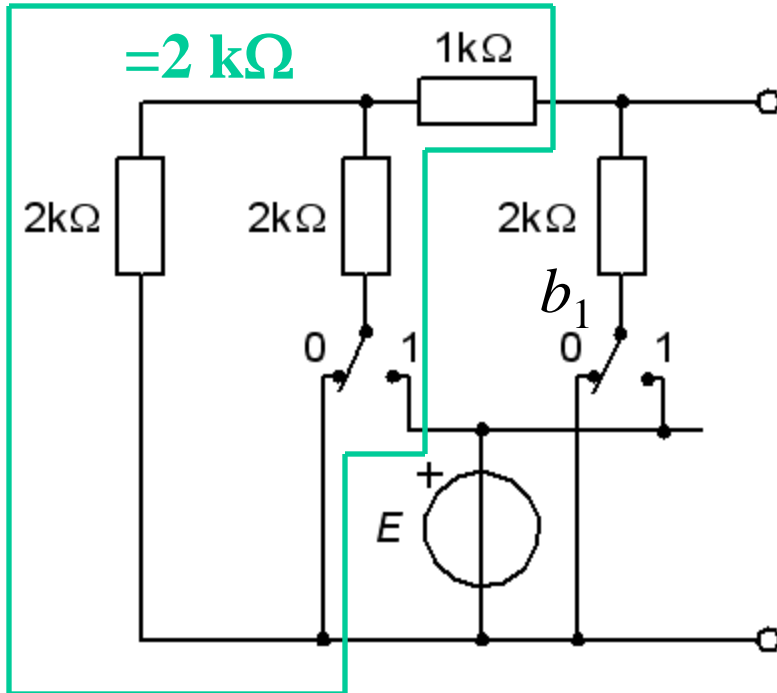

$R_I = ?$

$$R_I = \frac{2 \cdot 2}{2 + 2} = 1\text{ k}\Omega$$

R-2R  $b_1=1$   $R_I=?$

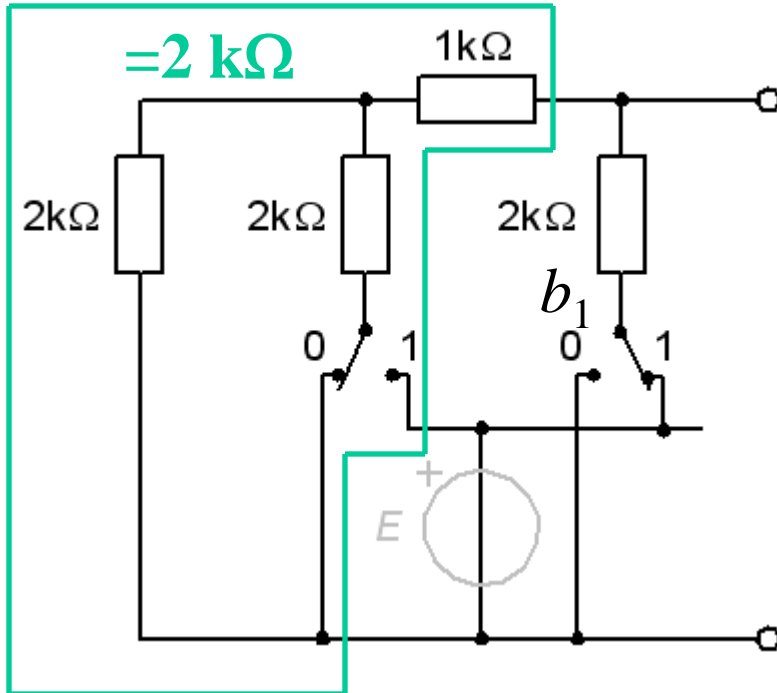


$R_I = ?$

$$R_I = \frac{2 \cdot 2}{2 + 2} = 1 \text{ k}\Omega$$

$b_1$  1 or 0, same  
internal resistance!

# R-2R $b_1$ $R_I = ?$

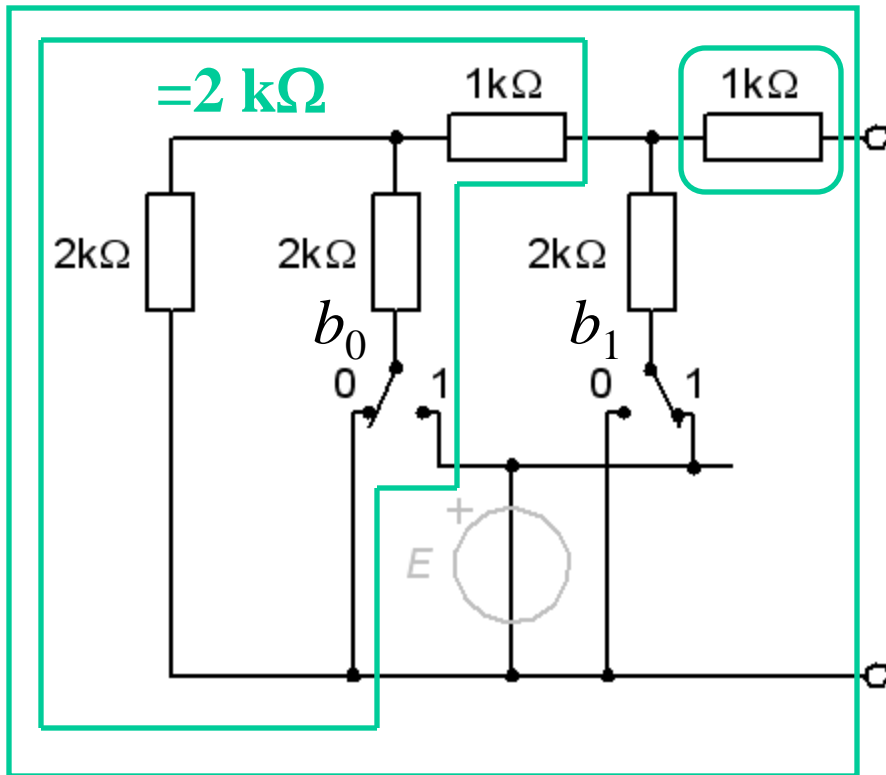


• Conclusion:

$$R_I = 1 + 1 = 2 \text{ k}\Omega$$


Regardless 1's or 0's is the total input resistance from the previous stages always  $2 \text{ k}\Omega$

# Two-terminal equivalent $E_0$

R-2R  $b_4=1$   $E_0=?$

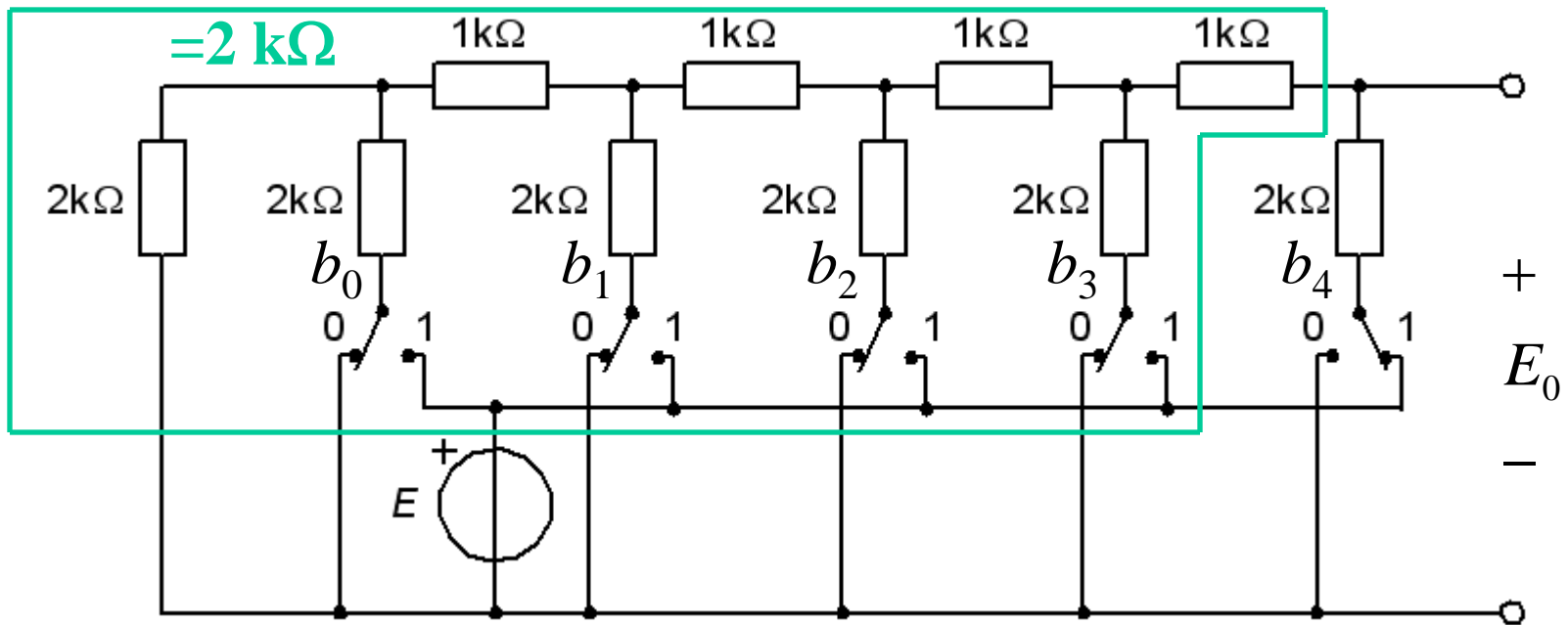


R-2R  $b_4=1$   $E_0=?$

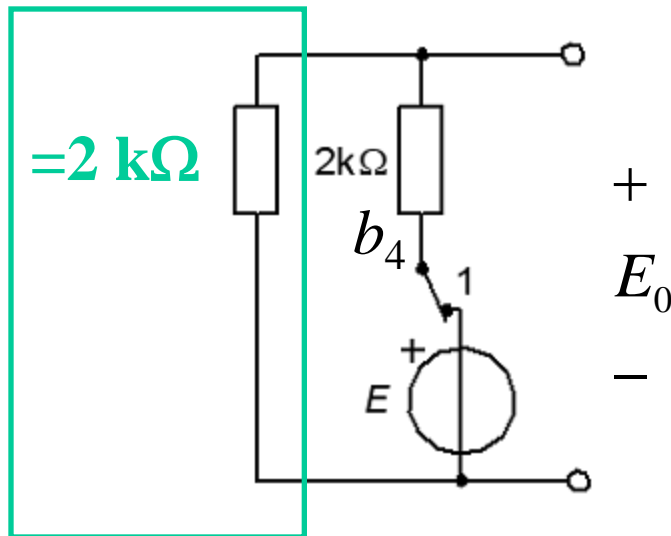

Voltage divider:





$$E_0 = E \frac{2}{2+2} = \frac{E}{2}$$

R-2R  $b_3=1$   $E_0=?$

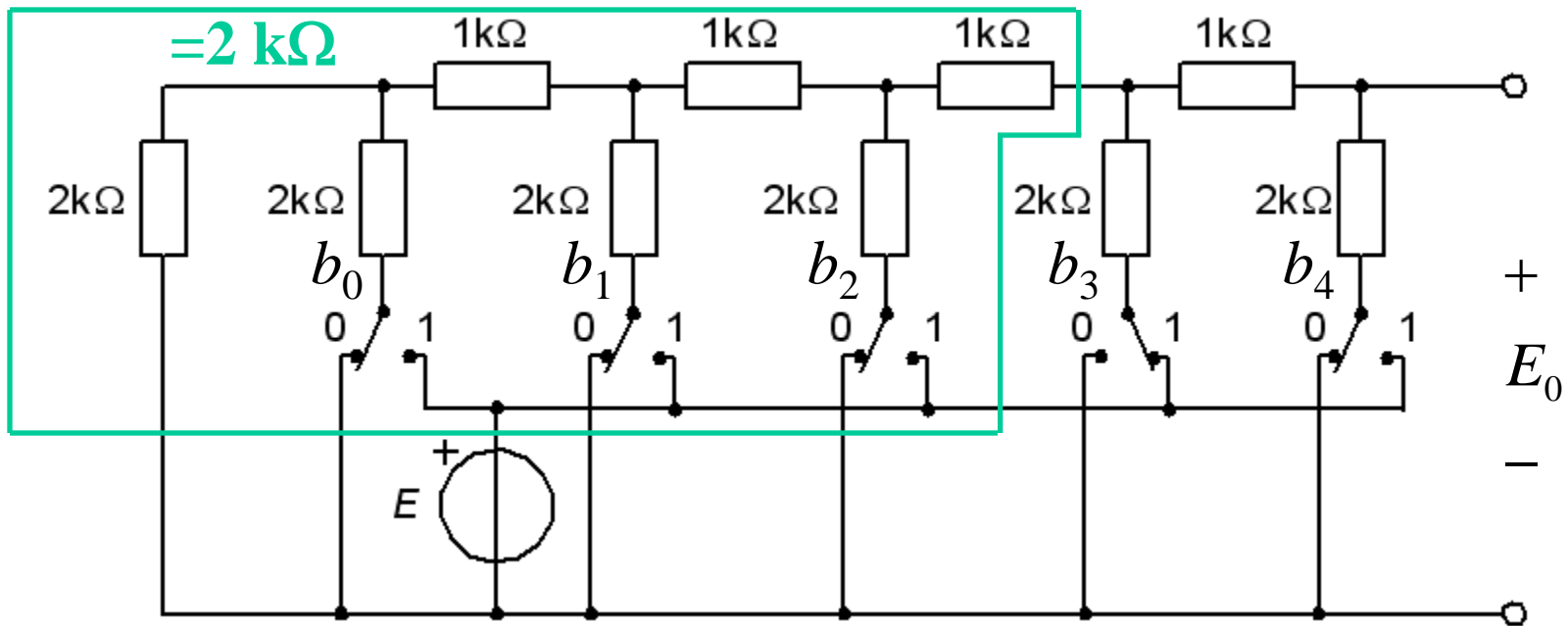




# R-2R $b_3=1$ $E_0=?$

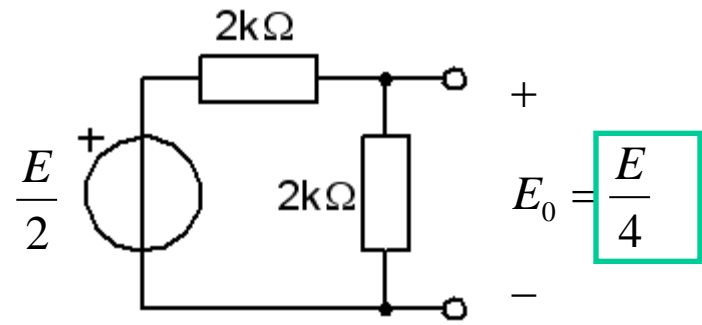 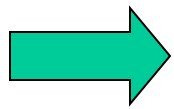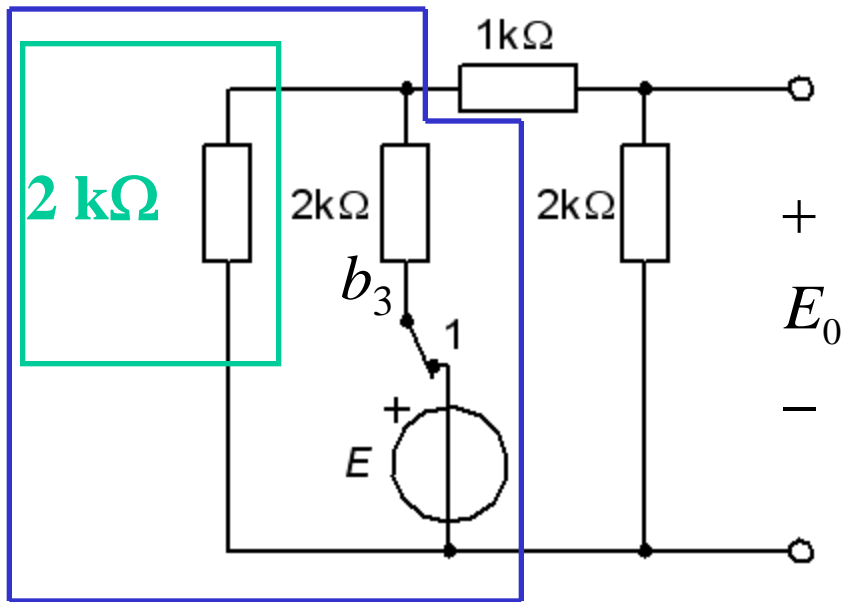


# R-2R conclusion $E_0 \dots$

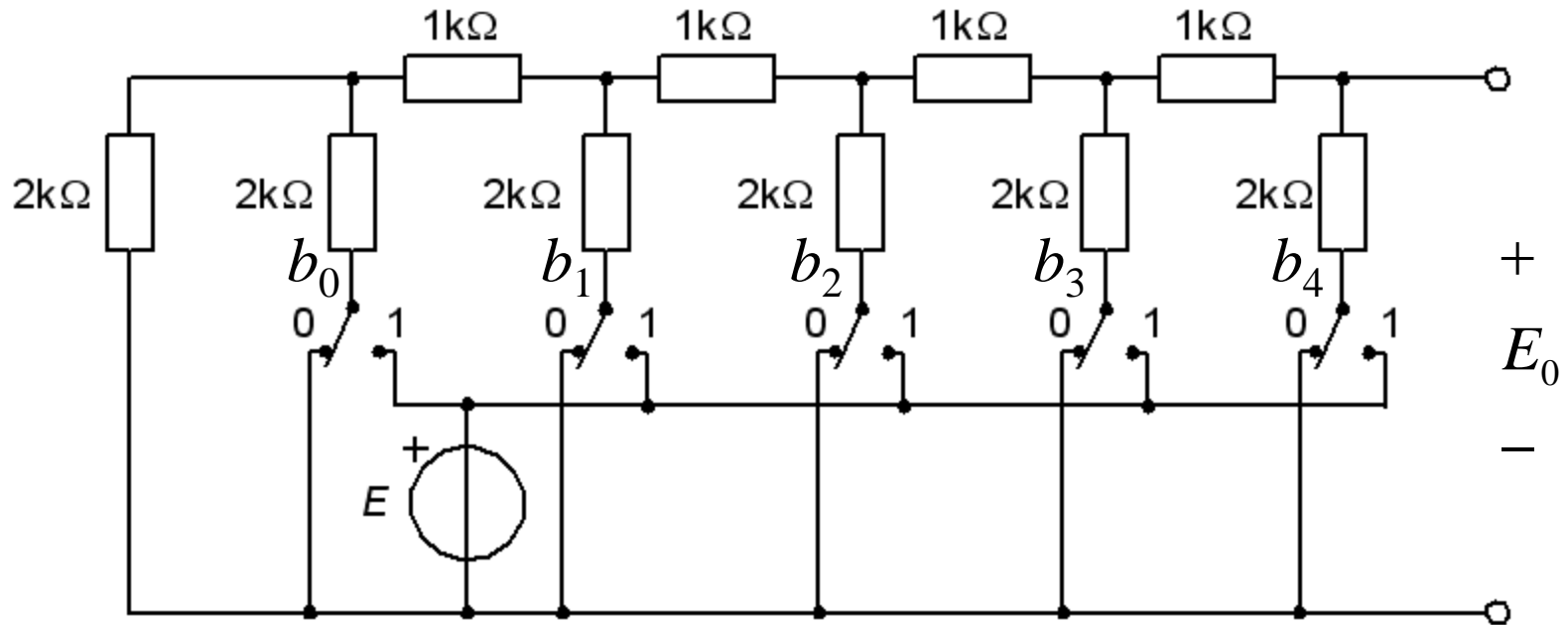

$$b_4 = 1 \Rightarrow \frac{E}{2} \quad b_3 = 1 \Rightarrow \frac{E}{4} \quad b_2 = 1 \Rightarrow \frac{E}{8} \quad \dots$$

- Reasonable guess – is it not?

# R-2R superposition

 


- According to the **superposition** principle, the contributions of  $b_4 b_3 b_2 \dots b_0$  can be added individually:

$$b_4 b_3 b_2 b_1 b_0 \longrightarrow E_0 = E \cdot \left( \frac{b_4}{2} + \frac{b_3}{4} + \frac{b_2}{8} + \frac{b_1}{16} + \frac{b_0}{32} \right)$$

*We have a  
DA-converter!*

# R-2R simulation

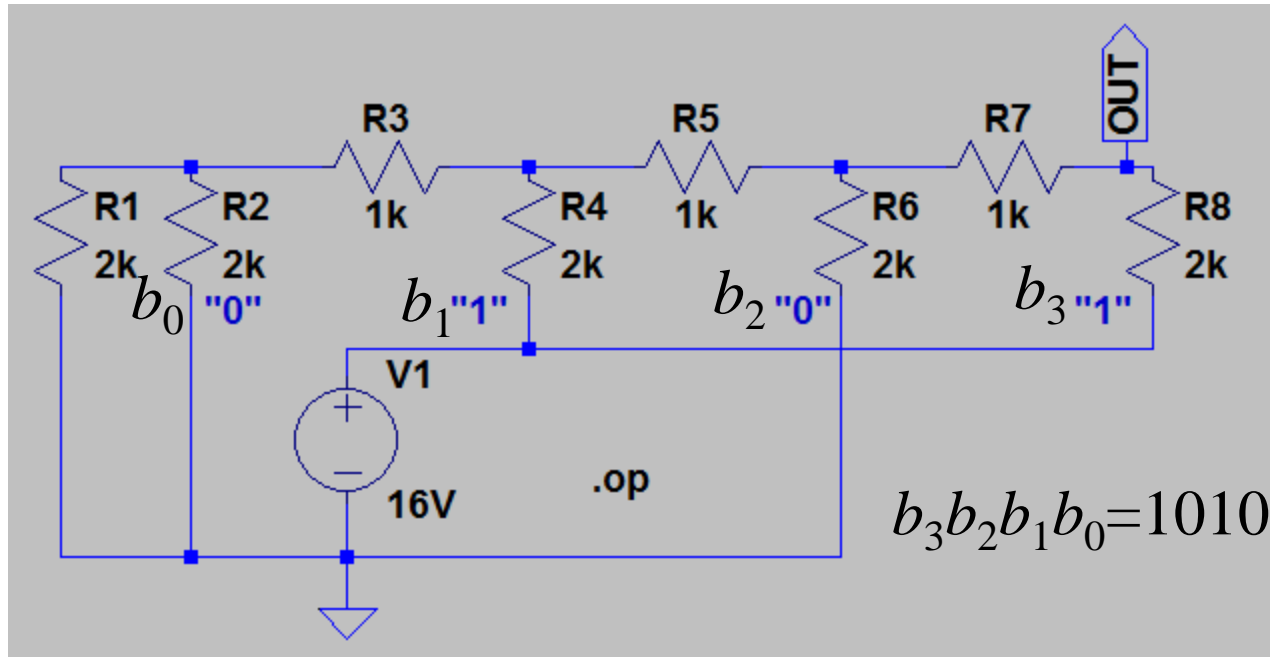


Guess value of voltage OUT?


William Sandqvist [william@kth.se](mailto:william@kth.se)

# AD-converter?






# Successive approximations

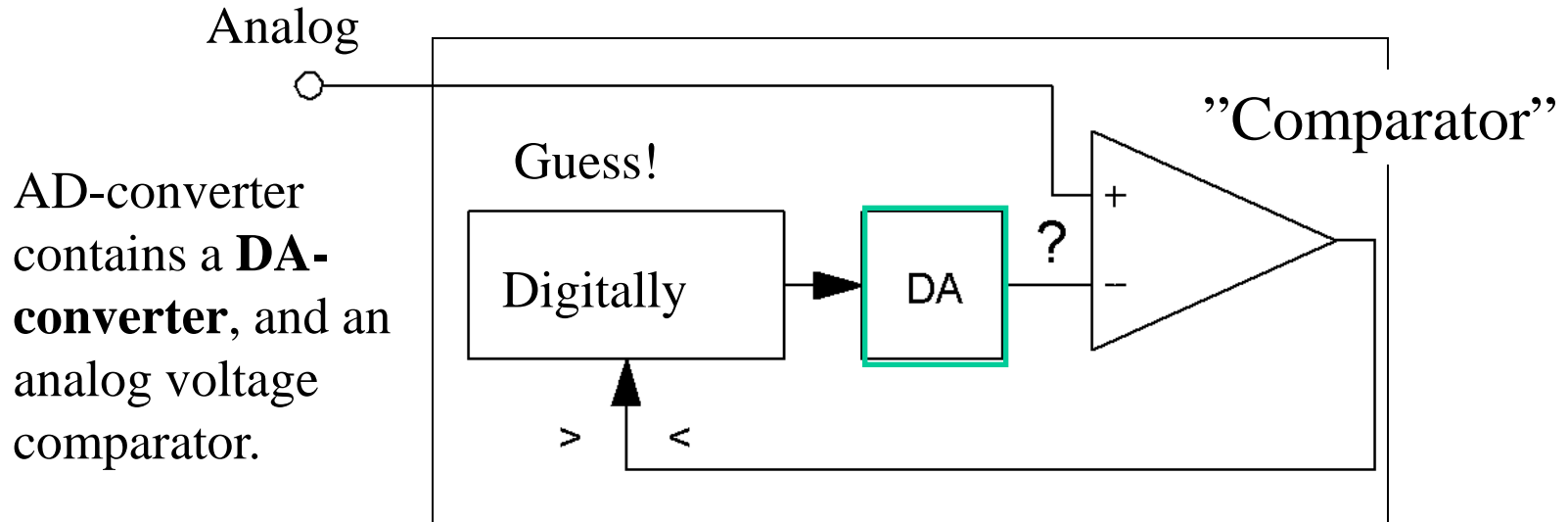

 *AD conversion according to the method of successive approximations is comparable to weigh an unknown mass with binary weights on a balance. We try step by step to adding binary "weight" if "<" or remove "weight" if ">".*




# Binary weights 8 4 2 1 ...

     

AD conversion takes time. For each bit higher resolution a comparison one step further is required.




# An AD-converter, 14 channels

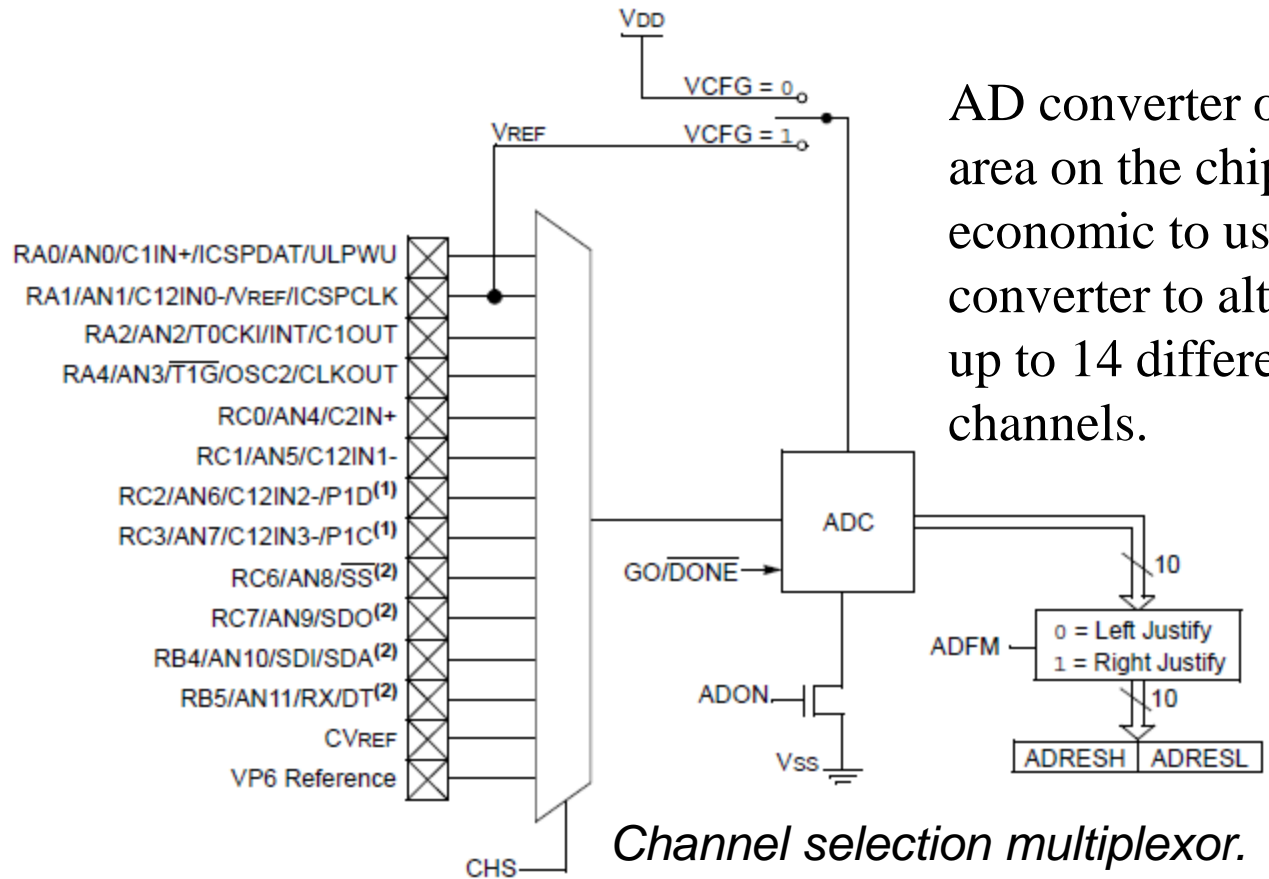

AD converter occupies a large area on the chip - so it is economic to use the same converter to alternately measure up to 14 different sources, channels.

The PIC-processor has a 10-bits AD-converter


# Supply voltage as reference

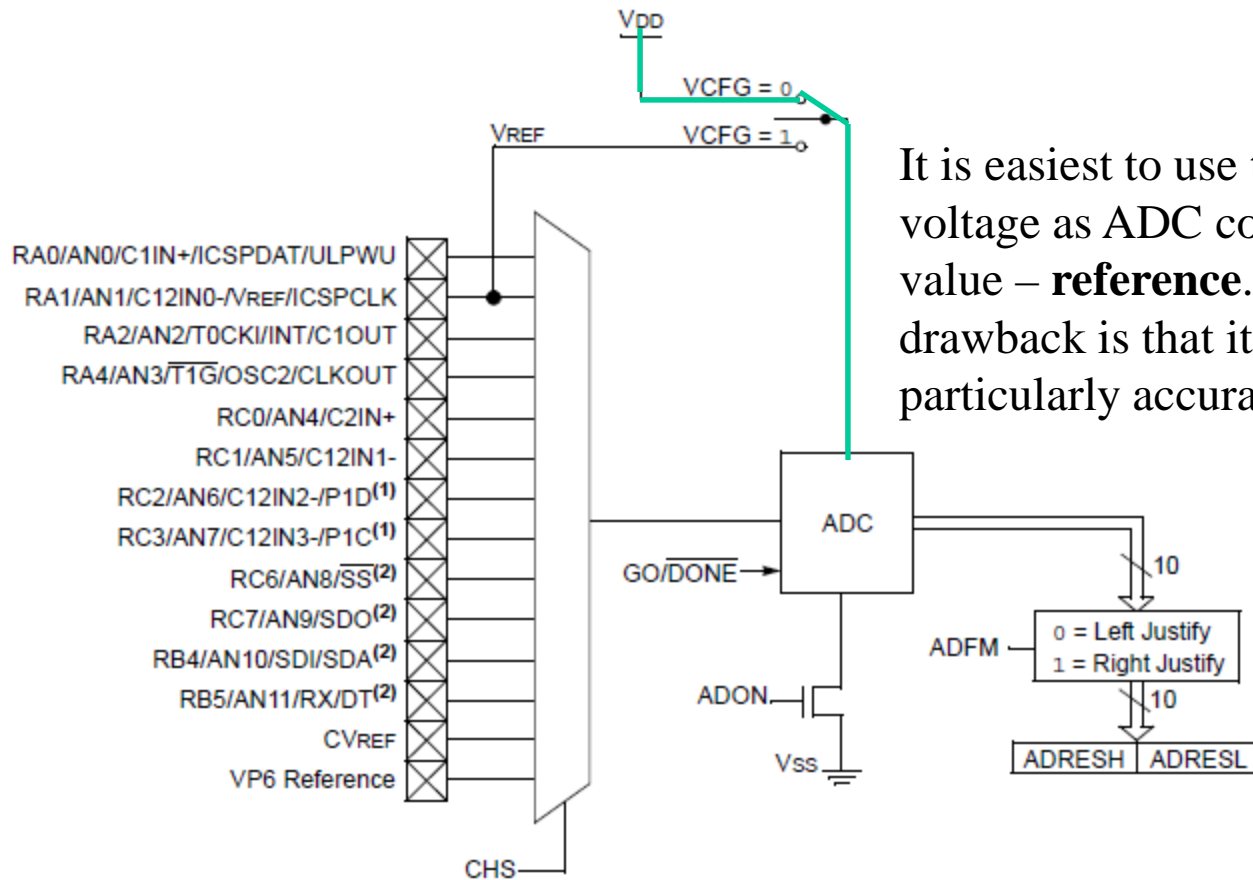


It is easiest to use the supply voltage as ADC comparison value – **reference**. The drawback is that it is not particularly accurate.

# Internal or external reference?


Why external reference?

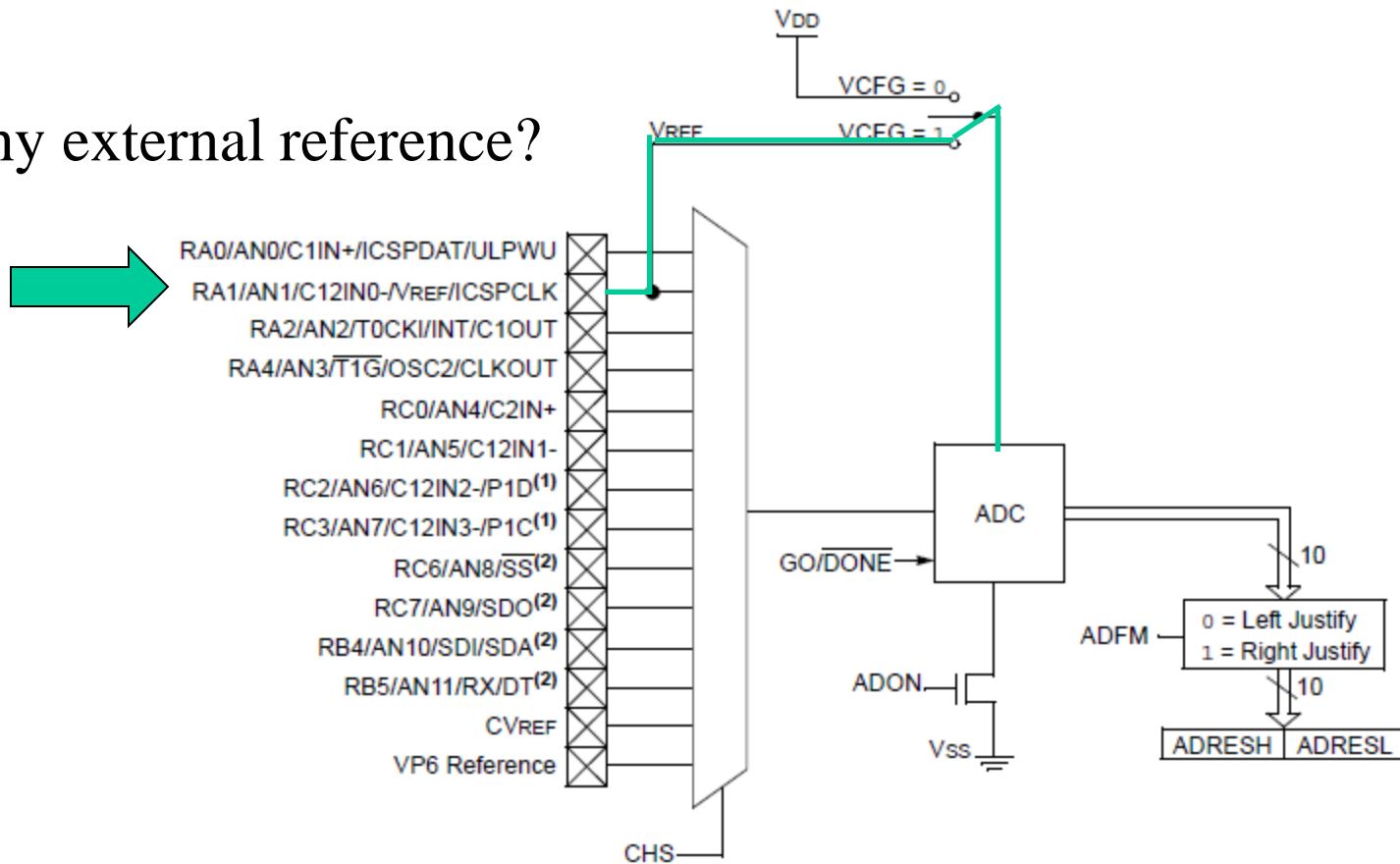


# Stabilized reference 4,096 V

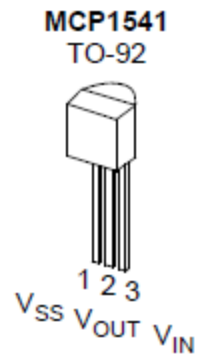

## MCP1541

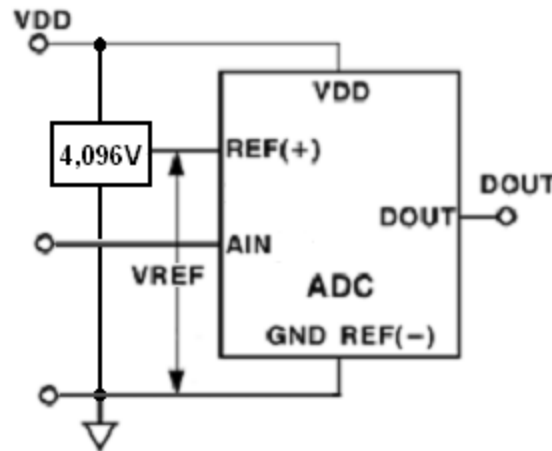


## Temperature Drift

 

If you buy a stabilized reference circuit you can perhaps choose the value 4,096 V ( $4096=2^{12}$ ) which gives a 10-bit AD-converter exact 4 mV-steps, *without* the need to scale the measured result with multiplications and divisions.


# Ratiometric connection

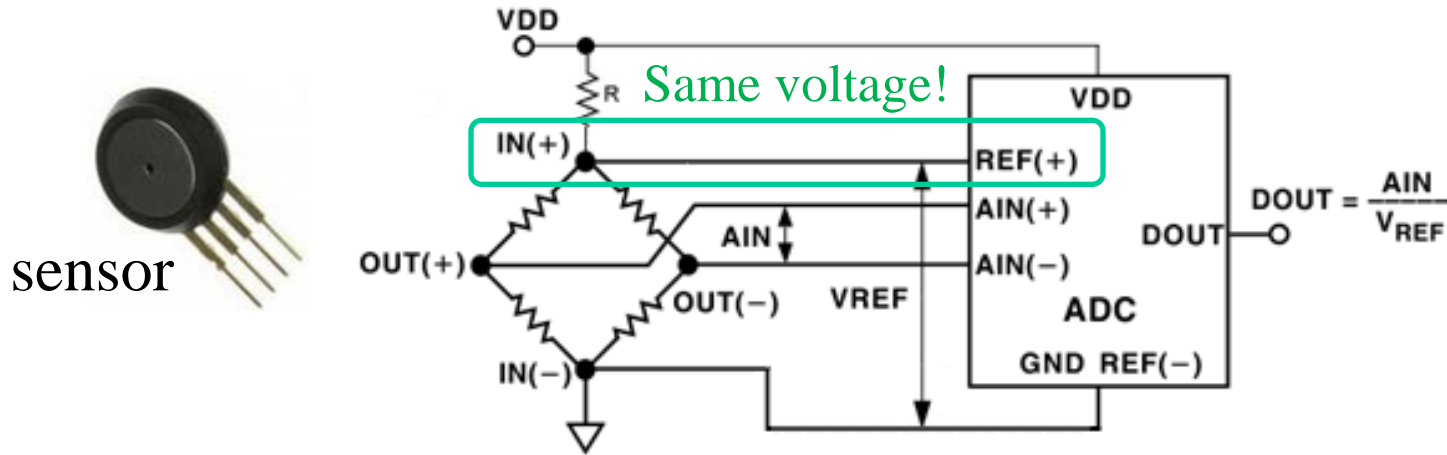


If a sensor measurement value depends on its supply voltage, you can either have stabilized supply (expensive) – or easier, use so-called ratiometric connection. If the sensor supply voltage and AD converter reference voltage **are the same**, then changes in this voltage will be the same for both, and the AD converted measured value will remain intact!
 
# Adapt measuring range

An NTC thermistor has a high sensitivity but a non-linear temperature relationship.



 We can linearize with a resistor – and then get the measuring range  $0 \dots 3,5$  V. If the reference is  $3,5$  V instead of  $5$  V then one utilizes the entire ADC range for the measurement.



# Or we program the linearization

```
test5.c
1  /* test5.c float NTC linearization */
2  /* No hardware needed */
3  /* B Knudsen Cc5x C-compiler - not ANSI-C */
4
5  #include "16F690.h"
6  #include "math24f.h"
7  #include "math24lb.h"
8  #pragma config |= 0x00D4
9
10 void main( void)
11 {
12     unsigned long int R_T;
13     float T, temp1, temp2;
14     const float A0 = 123.456;
15     const float A1 = 345.678;
16     // T=1/(A0+A1*log(R_T))
17     temp1=log((float) R_T);
18     temp2=A1*temp1;
19     temp1=A0+temp2;
20     T=1/temp1;
21 }
22
```



$$T = \frac{1}{a_0 + a_1 \cdot \ln(R_T)}$$



```
Console
NPP_SAVE: H:\PK2proj\Work\test5.c
CD: H:\PK2proj\npp
Current directory: H:\PK2proj\npp
CD: ..\Work\
Current directory: H:\PK2proj\Work
..\Cc5x\Cc5x.exe test5.c -a
Process started >>>
CC5X Version 3.4H, Copyright (c) B Knudsen Data, Norway 1992-2012
--> FREE edition, 8-16 bit int, 24 bit float, 32k code, reduced optim.
test5.c:
Chip = 16F690
RAM : -----
40h: =====, * *****
80h: -----
C0h: -----
100h: -----
140h: -----
RAM usage: 39 bytes (38 local), 217 bytes free
Optimizing - removed 69 instructions (-6 %)
File 'test5.asm'
File 'test5.occ'
File 'test5.hex'
Codepage 0 has 901 word(s) : 43 %
Codepage 1 has 0 word(s) : 0 %
Total of 901 code words (21 %)
* Estimated CODE SIZE of full optimization: 689 code words (-23 %)
<<< Process finished.
```
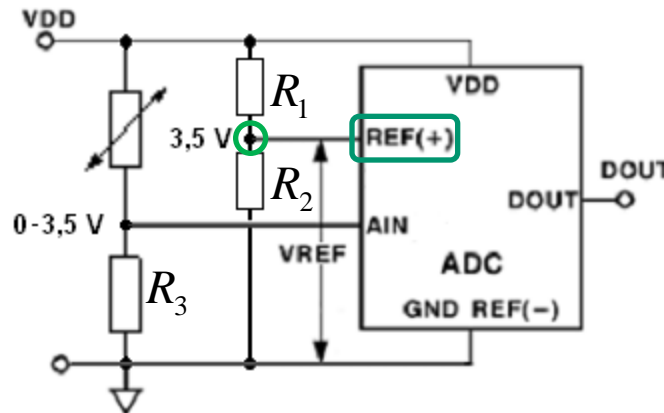 
# There exists a choice ... ??

There is apparently a choice between buying **three resistors** – or to use an **900 instruction** program.



*For those of you who knows about Embedded Electronics ...*





# Are 10-bit resolution required?

$b_9 b_8 b_7 b_6 b_5 b_4 b_3 b_2 b_1 b_0$

AD converter is 10 bits.

What does a sensor cost that has 10-bit resolution?

100 \$ ?

  

10 bits

1024 steps

5 mV/step


resolution  $\approx 0,1\%$

More common is that you can afford an 8-bit sensor. ( PIC processor itself costs 2 \$ ).


The picture shows a resistive position sensor that can take advantage of 10-bit resolution.
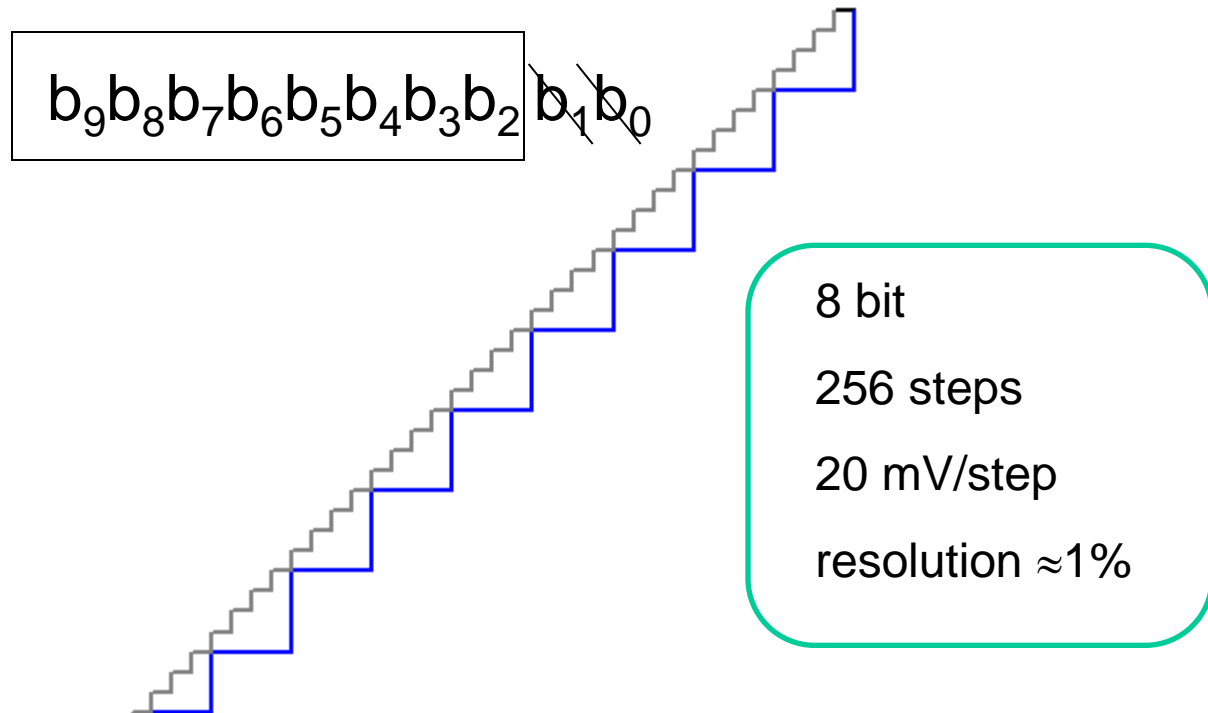
# 8-bit program

If one need only 8 bit resolution one can ignore the two least significant bits and handle the result as a byte.



# 8-bit program

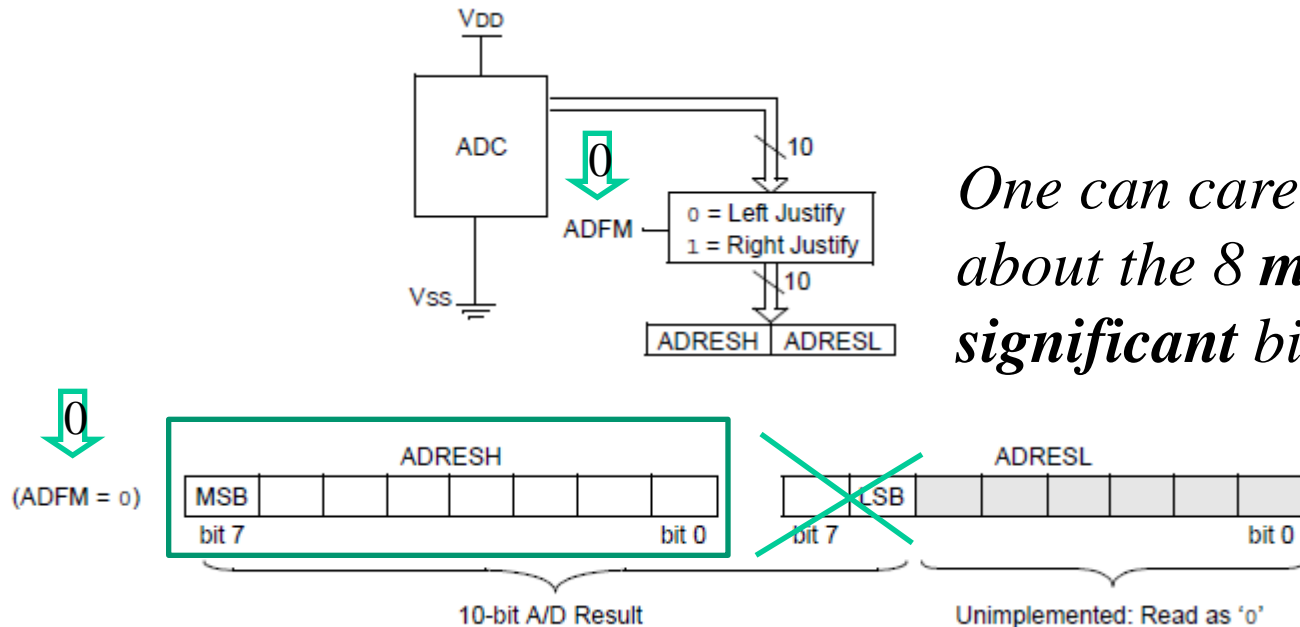


```
ADFM=0;  
char value;  
value = ADRESH; /* 8-bit measurement */
```

# Avoid amplifier


If one only need 8 bit resolution one can still use the 10-bit resolution to avoid the need to amplify the sensor signal, the two most significant bits becomes constant. One can therefore ignore to read them.

~~1~~ ~~0~~  $b_7 b_6 b_5 b_4 b_3 b_2 b_1 b_0$

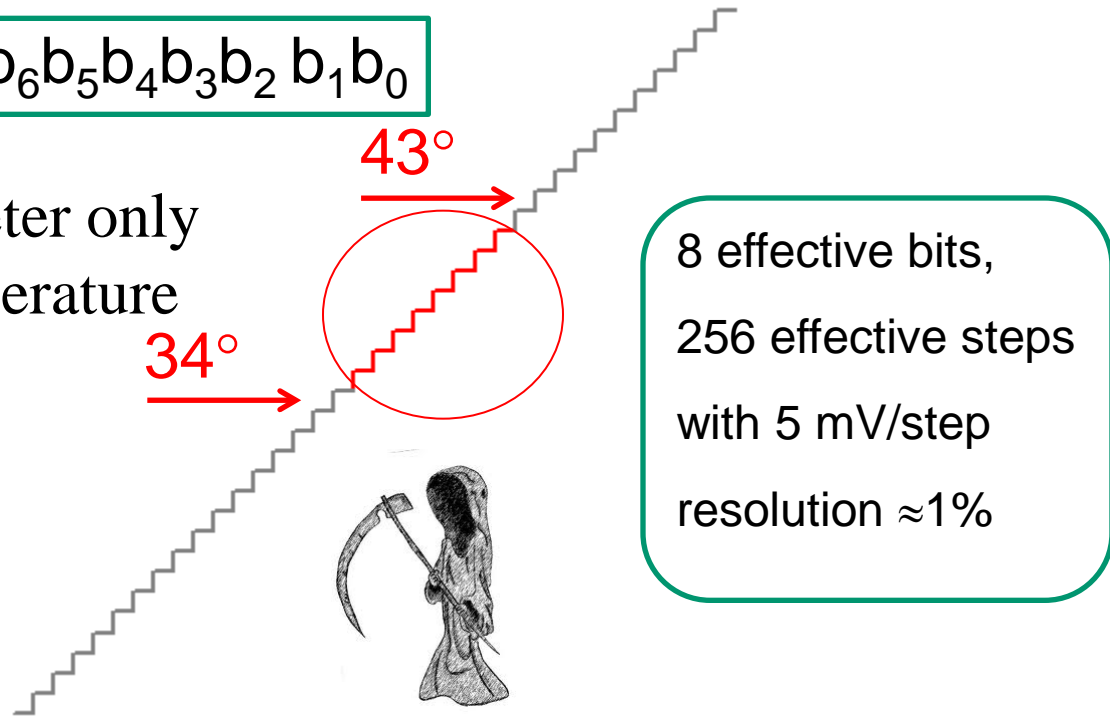A fever thermometer only need a small temperature range  $34^\circ \dots 43^\circ$  (right?)




# 8-bit program (10 bit)

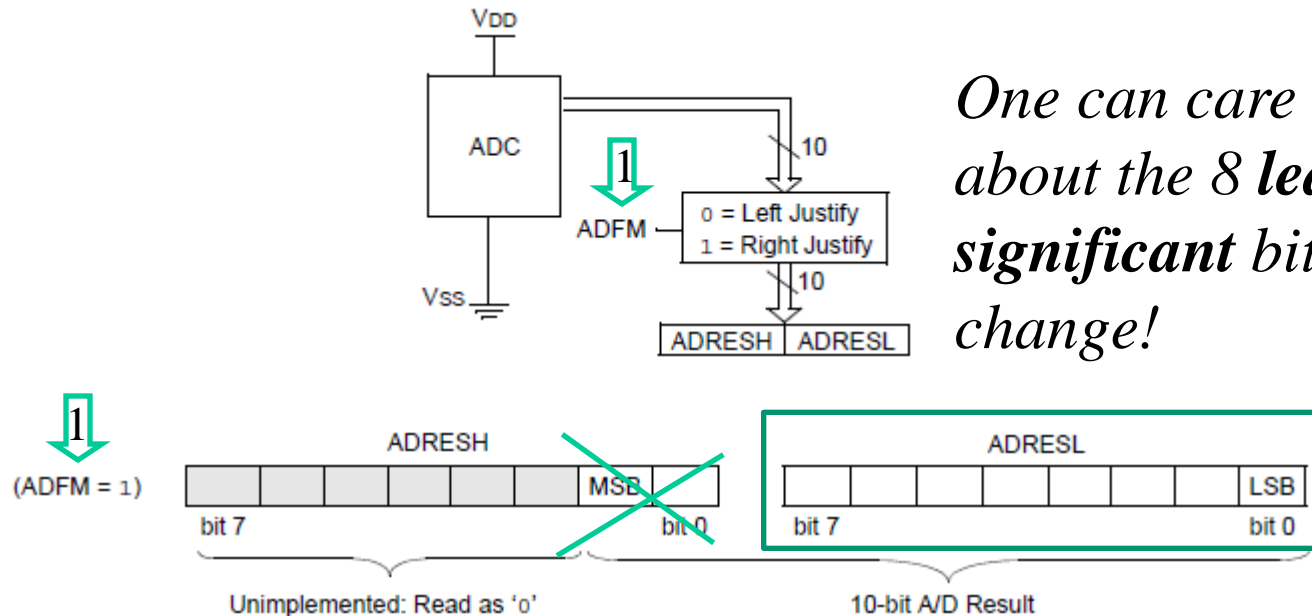


```
ADFM=1;  
char value;  
value = ADRESL; /* 8-bit measurement */
```
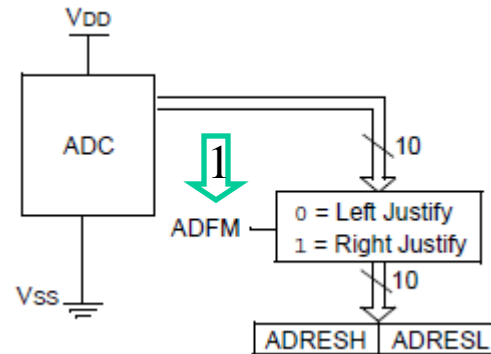
# 16-bit program

10-bits  
1024 steps  
5 mV/step  
resolution  $\approx 0,1\%$



 *When you really need  
10 bits in a 16-bit  
variable.*




```
ADFM=1;  
unsigned long value;  
value = ADRESH * 256;  
value += ADRESL; /* 10-bit measurement */
```

William Sandqvist [william@kth.se](mailto:william@kth.se)

 
# What happens if the signal changes during conversion?

AD converter can not "undo" a previously determined bit!



 The result is a value that has occurred during the conversion, but at an unspecified time!






## The problem

The time for the sampling is indeterminate!
 
# Sample & Hold - circuit

The solution is that the analog signal is "frozen" during the conversion.

At the AD conversion start a switch is taking a "sample" of the signal and stores it in a capacitor.




The course PIC processor, the sampling capacitor has capacitance  $\approx 10\text{pF}$ .


# Acquisition time $t_{ACQ}$

Every time one has **chosen/changed channel** the **sampling capacitor**  $C_{HOLD}$  must have time to recharge to the analog voltage. **This will take about 5  $\mu$ s.**

## ANALOG INPUT MODEL

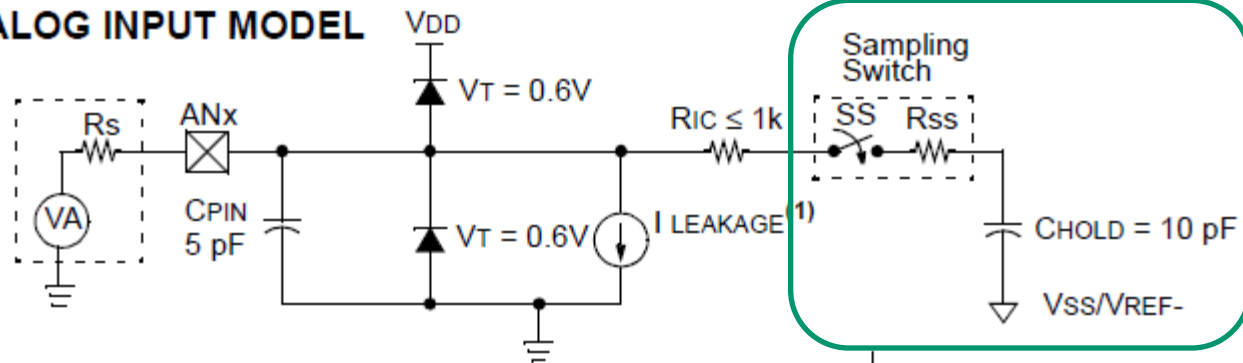

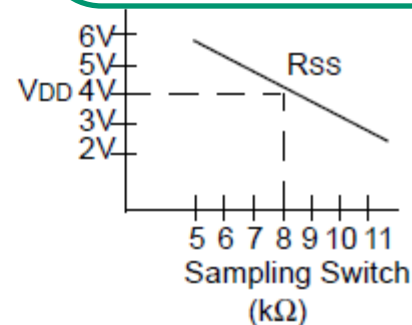**Legend:** CPIN = Input Capacitance  
VT = Threshold Voltage  
I LEAKAGE = Leakage current at the pin due to various junctions  
RIC = Interconnect Resistance  
SS = Sampling Switch  
CHOLD = Sample/Hold Capacitance



A 5  $\mu$ s delay can simply be programmed as:

```
nop2(); nop2(); nop(); /* 5 us 4 MHz clock */;
```

# AD-clock pulses

AD-converter can use a maximum clock frequency of 250 kHz. If the PIC processor clock is 4 MHz this must first be divided 16 times before it can be used as AD-clock. This frequency divider is provided.

REGISTER 9-2: ADCON1: A/D CONTROL REGISTER 1

U-0	RW-0	RW-0	RW-0	U-0	U-0	U-0	U-0
—	ADCS2	ADCS1	ADCS0	—	—	—	—
bit 7							bit 0

**ADCS<2:0>**: A/D Conversion Clock Select bits

000 = FOSC/2

001 = FOSC/8

010 = FOSC/32

x11 = FRC (clock derived from a dedicated internal oscillator = 500 kHz max)

100 = FOSC/4

101 = FOSC/16

110 = FOSC/64

**ADCON1=0b0.101.0000;**

$$1010000_2 = 80_{10} \quad T_{AD} = 4\mu\text{s} \quad f_{AD} = 500\text{kHz}$$

# Start AD and wait for done

REGISTER 9-1: ADCON0: A/D CONTROL REGISTER 0

R/W-0	R/W-0	R/W-0	R/W-0	R/W-0	R/W-0	R/W-0	R/W-0
ADFM	VCFG	CHS3	CHS2	CHS1	CHS0	GO/DONE	ADON
bit 7							bit 0

Start AD-  
conversion:


```
GO = 1;
```

Wait for AD-  
conversion done:

```
while(GO) ;
```

# AD-conversion takes time

FIGURE 9-2: ANALOG-TO-DIGITAL CONVERSION  $T_{AD}$  CYCLES

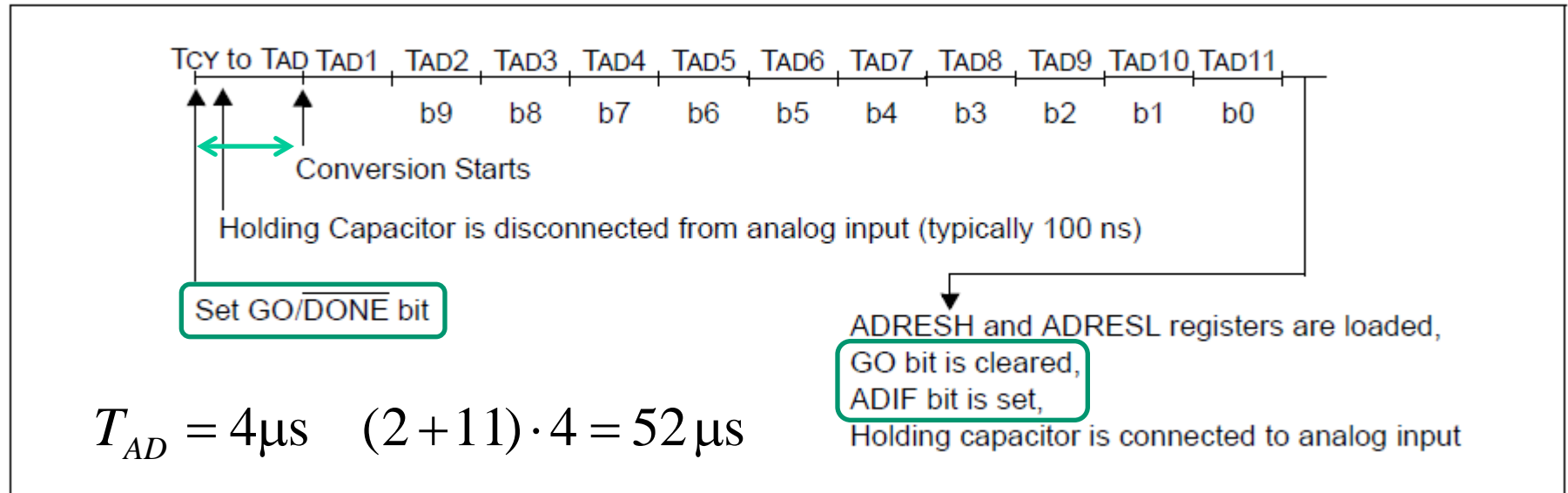

The conversion takes approximately 2 + 11 AD clock pulses. If one ignores the fact that the PIC processor must do something (?) With the AD-converted value (which also takes time), then the theoretically maximum sampling rate becomes:

$$f_{S \max} = \frac{1}{52\mu\text{s}} = 19,2 \text{ kHz}$$

# AD-conversion takes time

If one converts alternating two channels (stereo?) then there will also be the setting time of sampling capacitor  $T_{ACQ} = 5 \mu\text{s}$ .

$$f_{S_{\max}} = \frac{1}{52 + 5 + 52 + 5 [\mu\text{s}]} = 8,8 \text{ kHz}$$

The PIC processor can handle most industrial control processes - but it is of course totally inadequate as a "signal processor" for sound effects!

# Many setup possibilities

**TABLE 9-2: SUMMARY OF ASSOCIATED ADC REGISTERS**

Name	Bit 7	Bit 6	Bit 5	Bit 4	Bit 3	Bit 2	Bit 1	Bit 0	Value on POR, BOR	Value on all other Resets
ADCON0	ADFM	VCFG	CHS3	CHS2	CHS1	CHS0	GO/DONE	ADON	0000 0000	0000 0000
ADCON1	—	ADCS2	ADCS1	ADCS0	—	—	—	—	-000 ----	-000 ----
ANSEL	ANS7	ANS6	ANS5	ANS4	ANS3	ANS2	ANS1	ANS0	1111 1111	1111 1111
ANSELH	—	—	—	—	ANS11	ANS10	ANS9	ANS8	---- 1111	---- 1111
ADRESH	A/D Result Register High Byte								xxxx xxxx	uuuu uuuu
ADRESL	A/D Result Register Low Byte								xxxx xxxx	uuuu uuuu
INTCON	GIE	PEIE	T0IE	INTE	RABIE	T0IF	INTF	RABIF	0000 000x	0000 000x
PIE1	—	ADIE	RCIE	TXIE	SSPIE	CCP1IE	TMR2IE	TMR1IE	-000 0000	-000 0000
PIR1	—	ADIF	RCIF	TXIF	SSPIF	CCP1IF	TMR2IF	TMR1IF	-000 0000	-000 0000
PORTA	—	—	RA5	RA4	RA3	RA2	RA1	RA0	--xx xxxx	--uu uuuu
PORTB	RB7	RB6	RB5	RB4	—	—	—	—	xxxx ----	uuuu ----
PORTC	RC7	RC6	RC5	RC4	RC3	RC2	RC1	RC0	xxxx xxxx	uuuu uuuu
TRISA	—	—	TRISA5	TRISA4	TRISA3	TRISA2	TRISA1	TRISA0	--11 1111	--11 1111
TRISB	TRISB7	TRISB6	TRISB5	TRISB4	—	—	—	—	1111 ----	1111 ----
TRISC	TRISC7	TRISC6	TRISC5	TRISC4	TRISC3	TRISC2	TRISC1	TRISC0	1111 1111	1111 1111

**Legend:** x = unknown, u = unchanged, – = unimplemented read as '0'. Shaded cells are not used for ADC module.



# AD-conversion – step by step

1. Configure Port:
  - Disable pin output driver (See TRIS register)
  - Configure pin as analog (See ANSEL register).
2. Configure the ADC module:
  - Select ADC conversion clock (ADCON1, ADCS<2:0>).
  - Configure voltage reference (ADCON0, VCFG).
  - Select ADC input channel (ADCON0, CHS<3:0>).
  - Select result format (ADCON0, ADFM).
  - Turn on ADC module (ADCON0, ADON)
3. Start conversion set the GO/DONE bit. (ADCON0, GO)
4. Wait for ADC conversion to complete, polling the GO/DONE bit. (ADCON0, GO)
5. Read ADC Result (ADRESH, ADRESL)

William Sandqvist [william@kth.se](mailto:william@kth.se)