
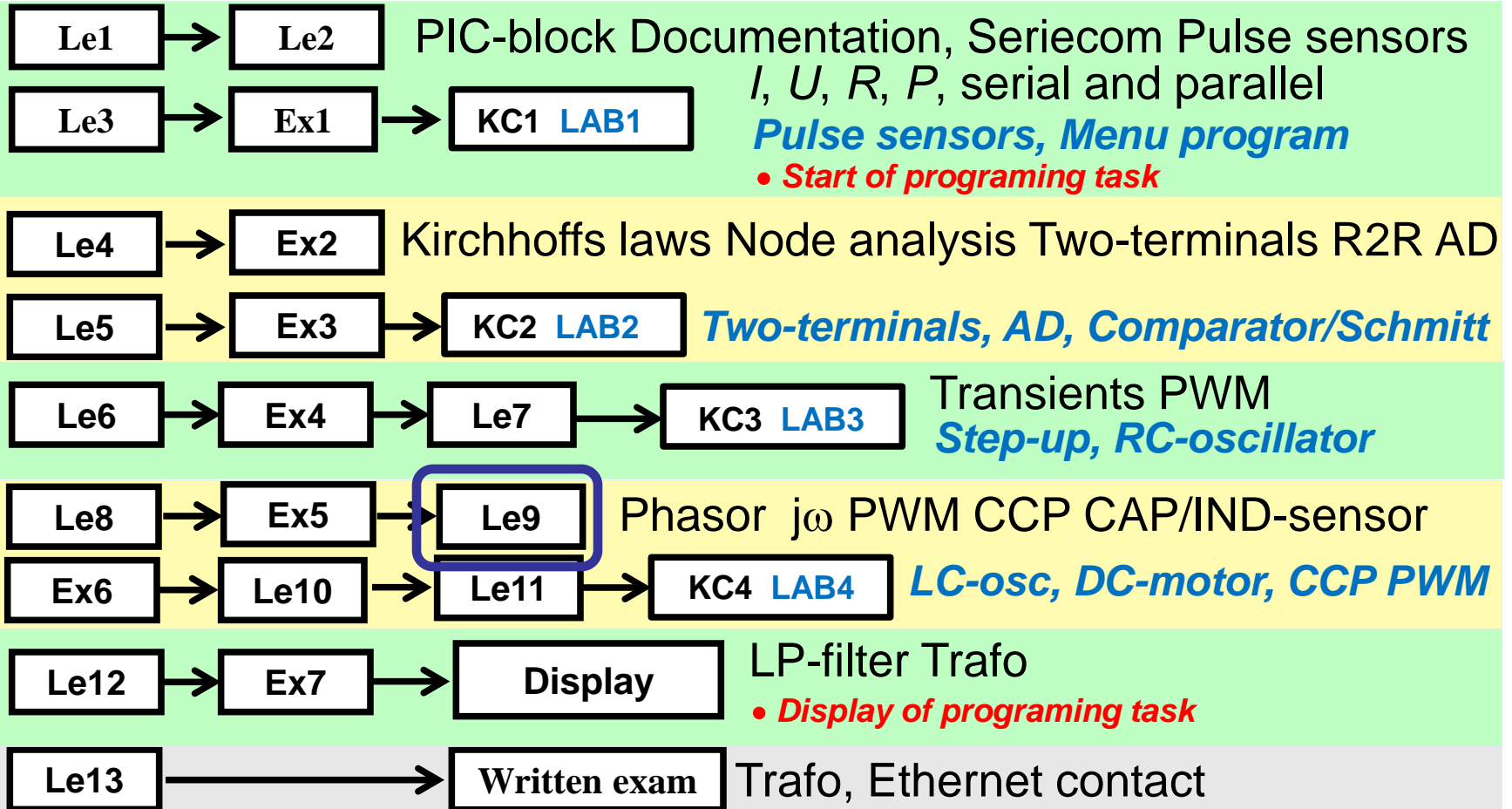


IE1206 Embedded Electronics

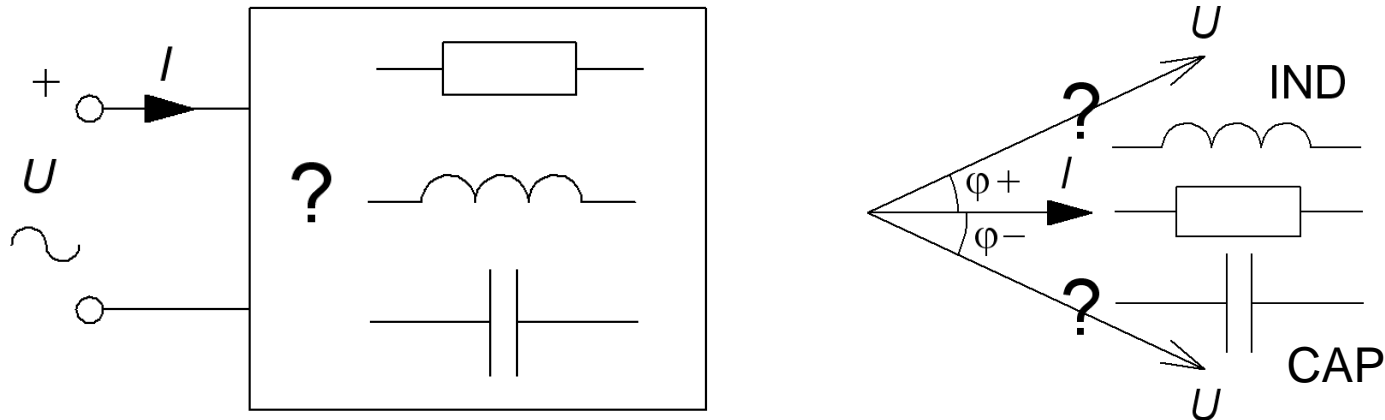



R L C



An impedance which contains inductors and capacitors has, depending on the frequency, either inductive character **IND**, or capacitive character **CAP**.

An important special case occurs at the frequency where capacitances and inductances are equally strong, and their effects cancel each other out. The impedance becomes purely resistive. The phenomenon is called the **resonance** and the frequency on which this occurs is the **resonant frequency**.


Reactance frequency dependency

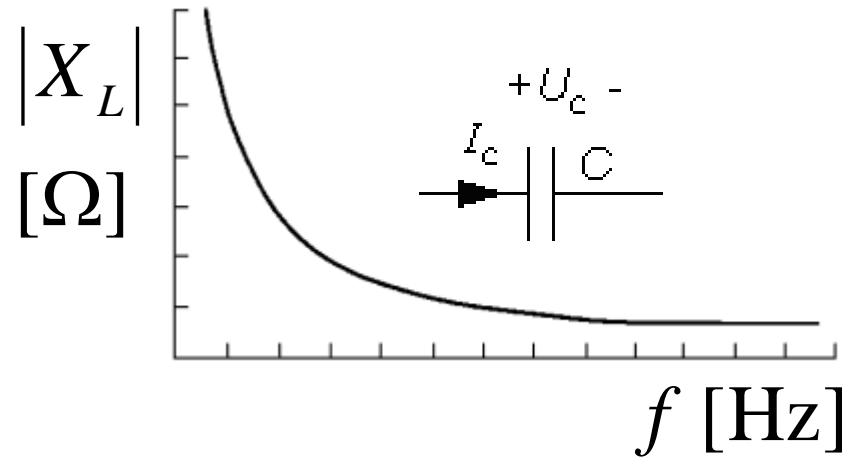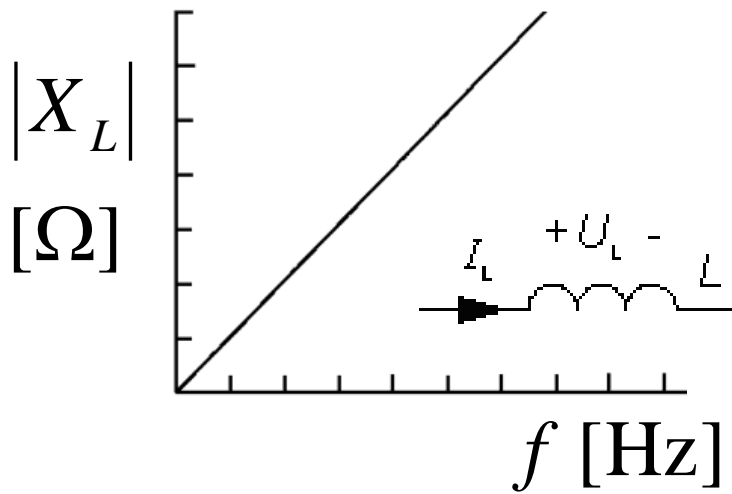

$$|X_L| = \omega \cdot L \quad |X_C| = \frac{1}{\omega \cdot C}$$

$$\omega = 2\pi f$$

$R L C$ impedances

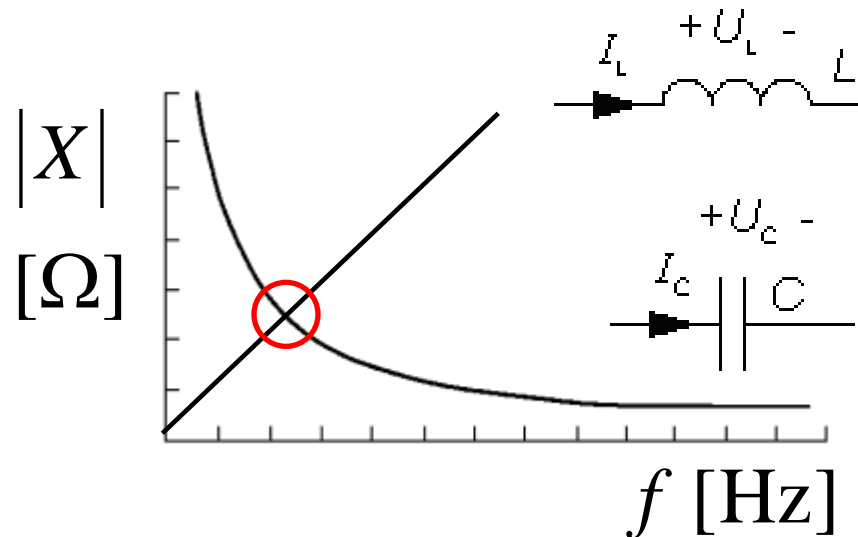

- At a certain frequency X_L and X_C has the same amount.


$$|X_L| = \omega \cdot L \quad |X_C| = \frac{1}{\omega \cdot C}$$

$$\omega = 2\pi f$$

William Sandqvist william@kth.se


How big is U ? (13.1)

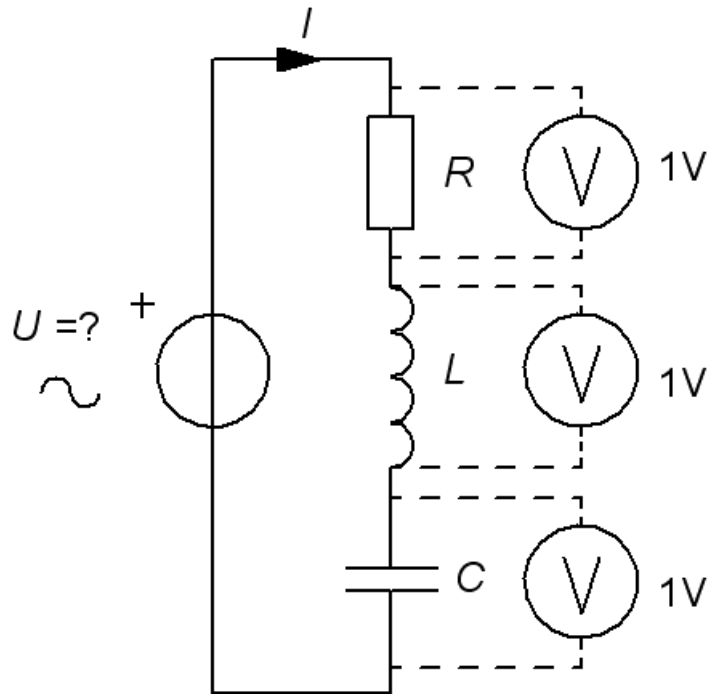The three volt meters show the same, 1V, how much is the alternating supply voltage U ? (*Warning, teaser*)




How big is U ? (13.1)

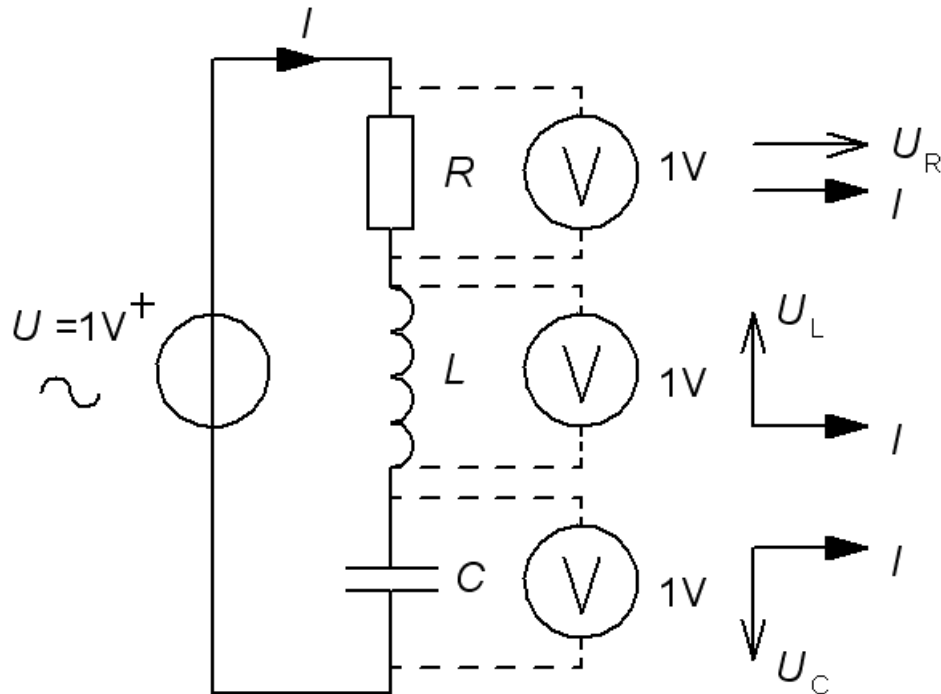The three volt meters show the same, 1V, how much is the alternating supply voltage U ? (*Warning, teaser*)



How big is U ? (13.1)

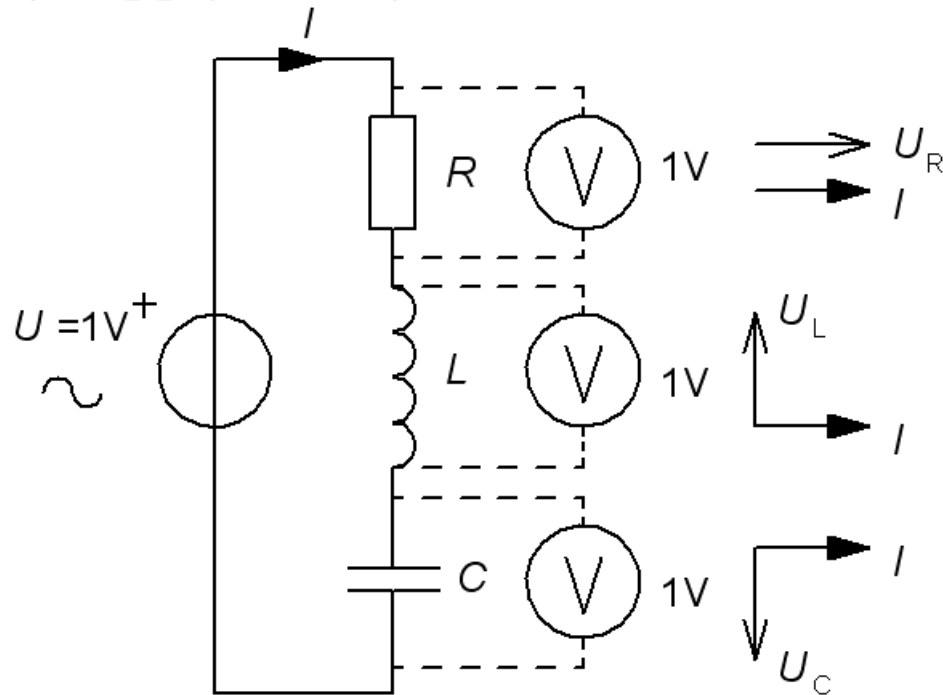The three volt meters show the same, 1V, how much is the alternating supply voltage U ? (*Warning, teaser*)




Since volt meters show the "same" and the current I is common:

$$R = |X_L| = |X_C| \quad R = \omega L = \frac{1}{\omega C}$$

If $|X_L| = |X_C| = 2R$?

Suppose the AC voltage U still 1 V, but the reactances are *twice* as big.
What will the voltmeters show?

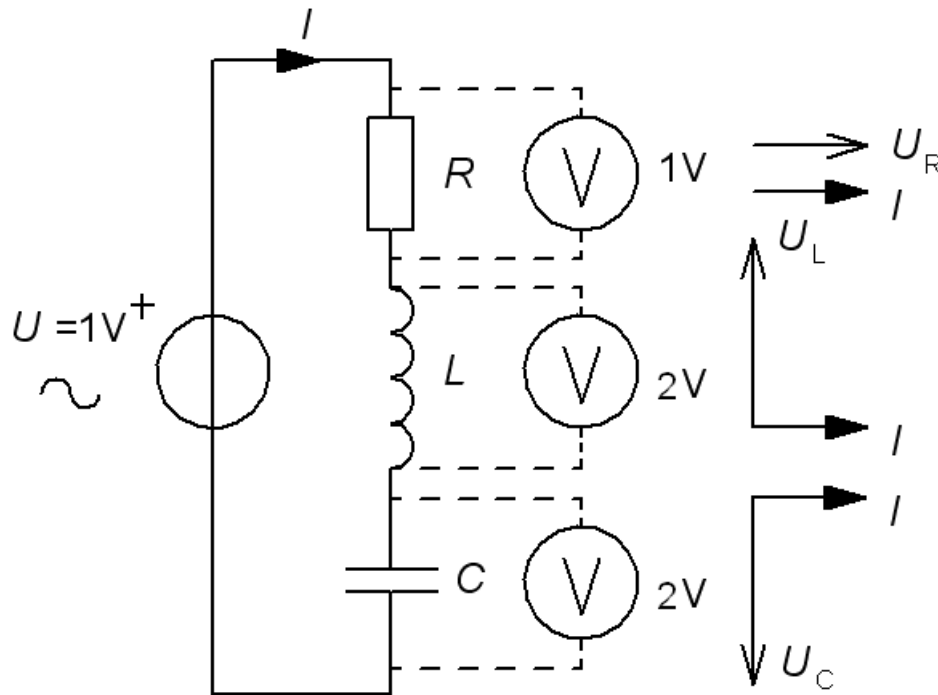
$$\omega L = \frac{1}{\omega C} = 2 \cdot R$$



If $|X_L| = |X_C| = 2R$?

Suppose the AC voltage U still 1 V, but the reactances are *twice* as big.
What will the voltmeters show?

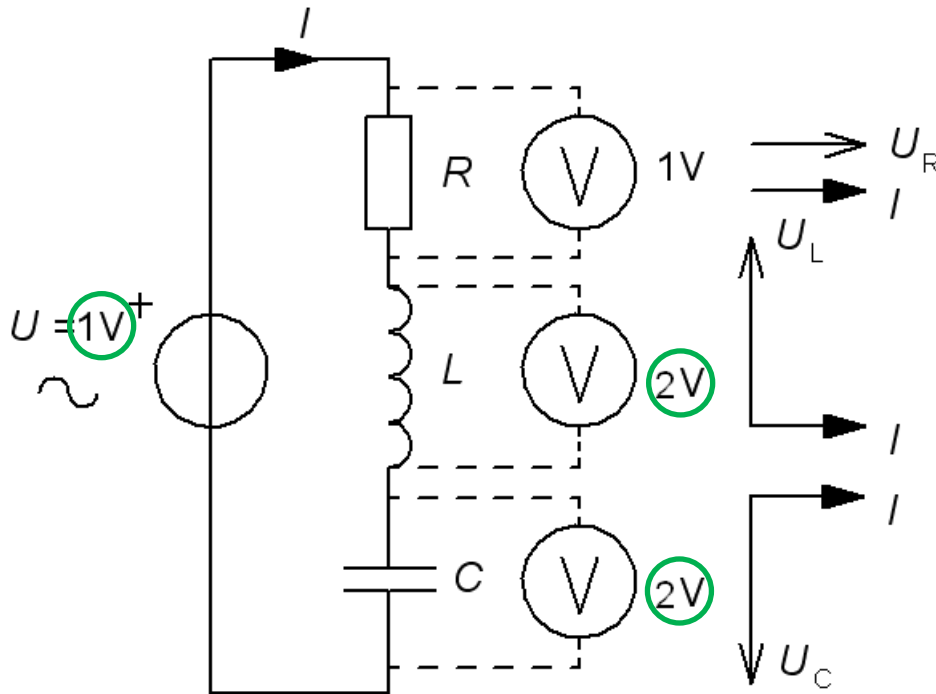
$$\omega L = \frac{1}{\omega C} = 2 \cdot R$$



If $|X_L| = |X_C| = 2R$?

Suppose the AC voltage U still 1 V, but the reactances are *twice* as big.
What will the voltmeters show?


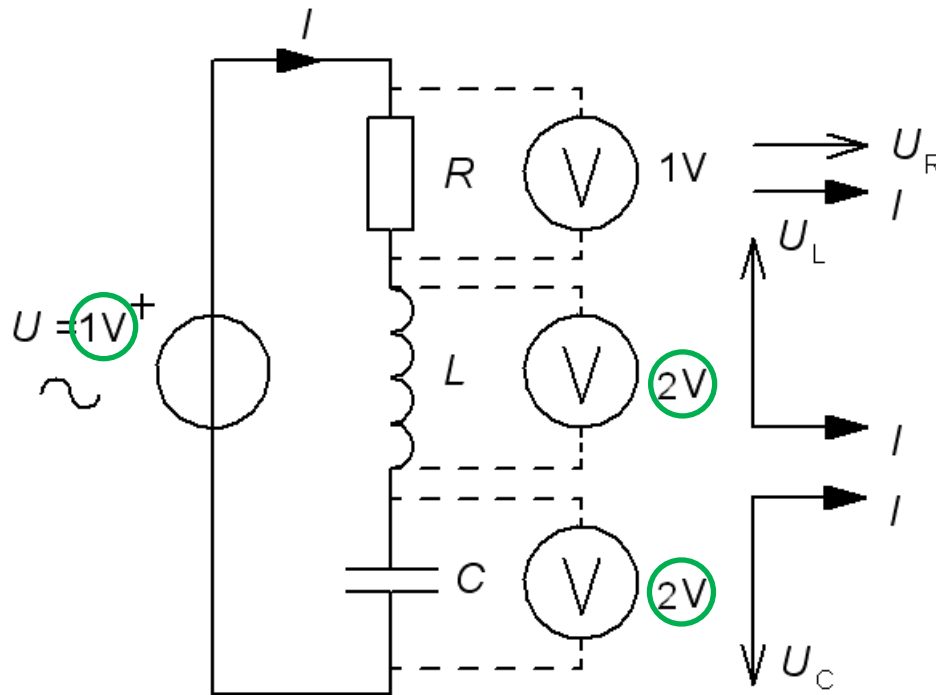
$$\omega L = \frac{1}{\omega C} = 2 \cdot R$$



At resonance, the voltage over the reactances can be many times higher than the AC supply voltage.

Tesla coil

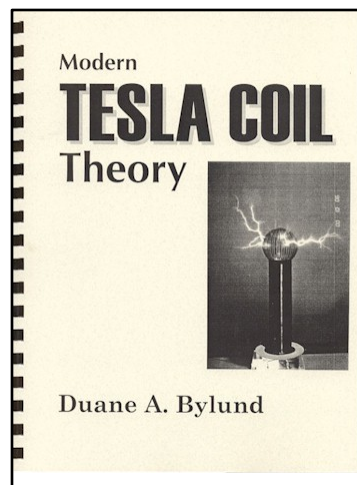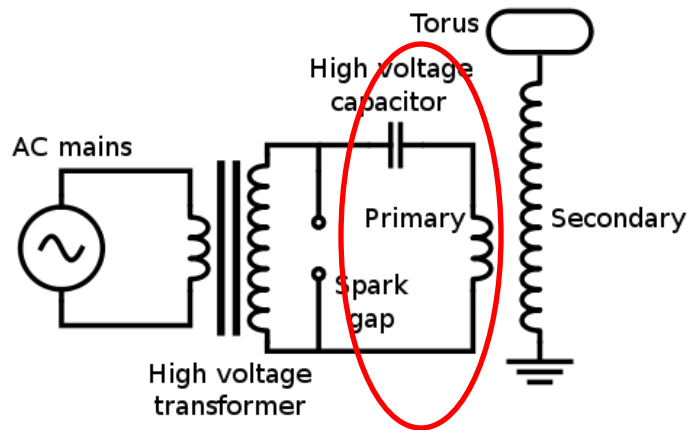
Many builds "Tesla" coils to gain some excitement in life...



William Sandqvist william@kth.se

Inductor quality factor Q

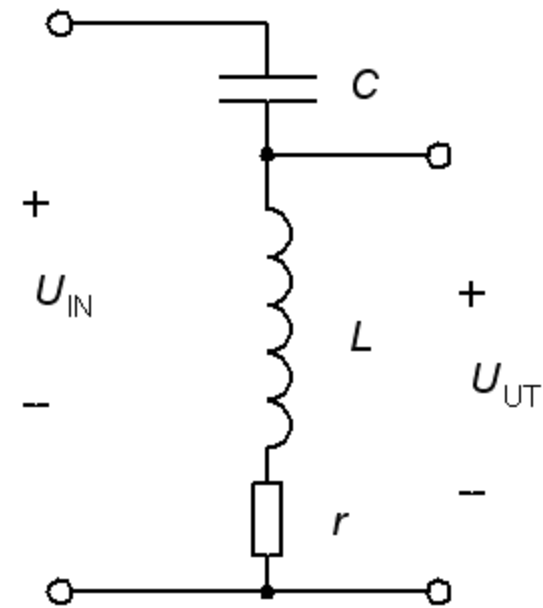
Usually it is the internal resistance of the coil which is the resistor in the RLC circuit. The higher the coil AC resistance ωL is in relation to the DC resistance r , the larger the voltage across the coil at a resonance get. This ratio is called the coil quality factor Q . (or Q-factor).



$$Q = \frac{X_L}{r} = \frac{\omega L}{r} \Rightarrow U_{UT} \approx Q \cdot U_{IN}$$

Series resonance

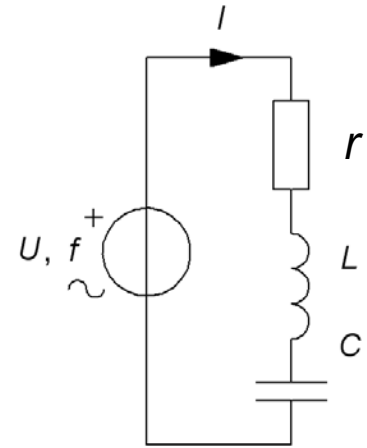
$$\underline{U} = \underline{I} \cdot \left(r + j\omega L + \frac{1}{j\omega C} \right) = \underline{I} \cdot \left(r + j\left(\omega L - \frac{1}{\omega C}\right) \right)$$



Series resonance

$$\underline{U} = \underline{I} \cdot \left(r + j\omega L + \frac{1}{j\omega C} \right) = \underline{I} \cdot \left(r + j \left(\omega L - \frac{1}{\omega C} \right) \right)$$

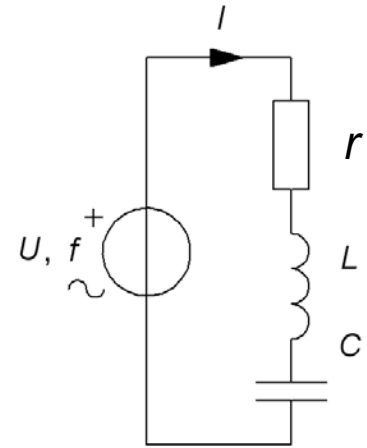The Impedance is real when the imaginary part is "0". This will happen at angular frequency ω_0 (frequency f_0).




Series resonance

$$\underline{U} = \underline{I} \cdot \left(r + j\omega L + \frac{1}{j\omega C} \right) = \underline{I} \cdot \left(r + j \left(\omega L - \frac{1}{\omega C} \right) \right)$$



The Impedance is real when the imaginary part is "0".
This will happen at angular frequency ω_0 (frequency f_0).
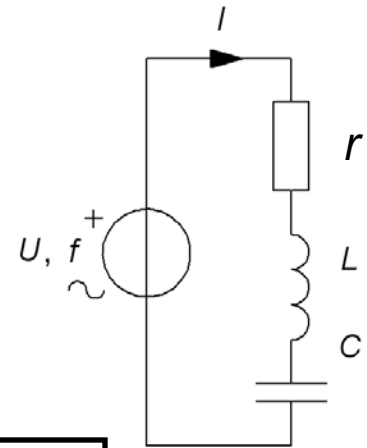
$$\text{Im}[\underline{Z}] = \omega L - \frac{1}{\omega C} = 0 \quad \Rightarrow \quad \omega_0 = \frac{1}{\sqrt{LC}} \quad \boxed{f_0 = \frac{1}{2\pi\sqrt{LC}}}$$





Series resonance phasor diagram
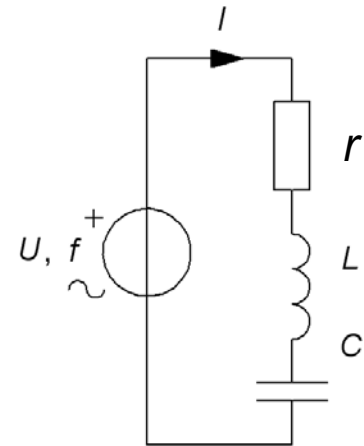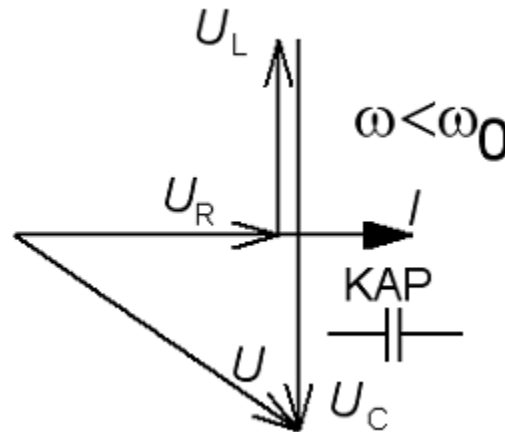
$$\underline{U} = \underline{I} \cdot \left(r + j\left(\omega L - \frac{1}{\omega C}\right) \right)$$





Series resonance phasor diagram
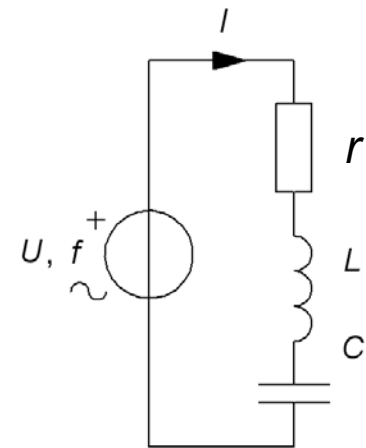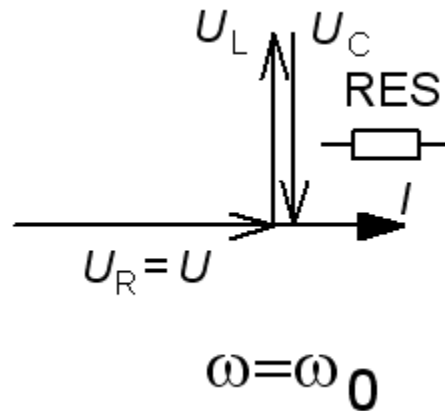
$$\underline{U} = \underline{I} \cdot \left(r + j\left(\omega L - \frac{1}{\omega C}\right) \right)$$



Series resonance phasor diagram
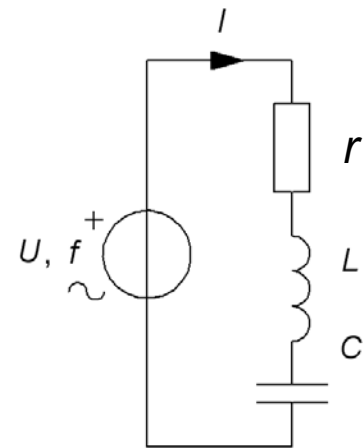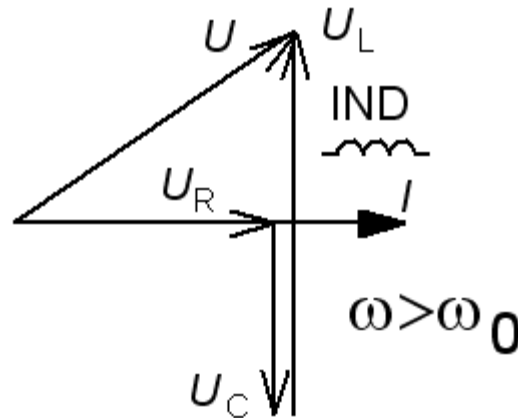
$$\underline{U} = \underline{I} \cdot \left(r + j\left(\omega L - \frac{1}{\omega C}\right) \right)$$





Series resonance circuit Q

It is the resistance of the resonant circuit, usually coil internal resistance, which determines how pronounced resonance phenomenon becomes. It is customary to "normalize" the relationship between the different variables by introducing the resonance angular frequency ω_0 together with the peak current I_{\max} in the function $I(\omega)$ with parameter Q :

$$\omega_0 = \frac{1}{\sqrt{LC}} \quad Q = \frac{\omega_0 L}{r}$$

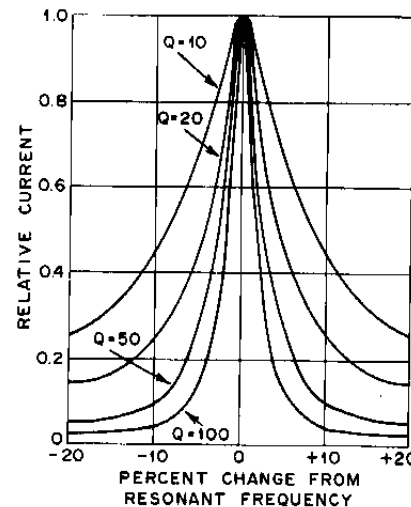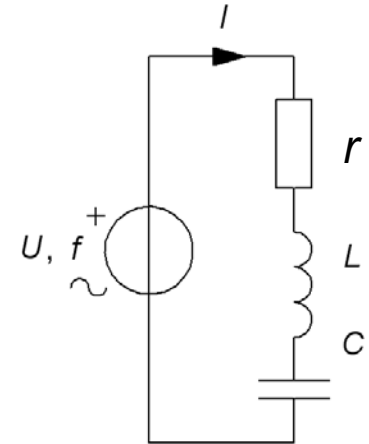
$$\underline{I} = \frac{I_{\max}}{\left(1 + jQ \left(\frac{\omega}{\omega_0} - \frac{\omega_0}{\omega} \right) \right)}$$



Normalized chart of the series resonant circuit. A high Q corresponds to a narrow resonance peak.

Bandwidth BW

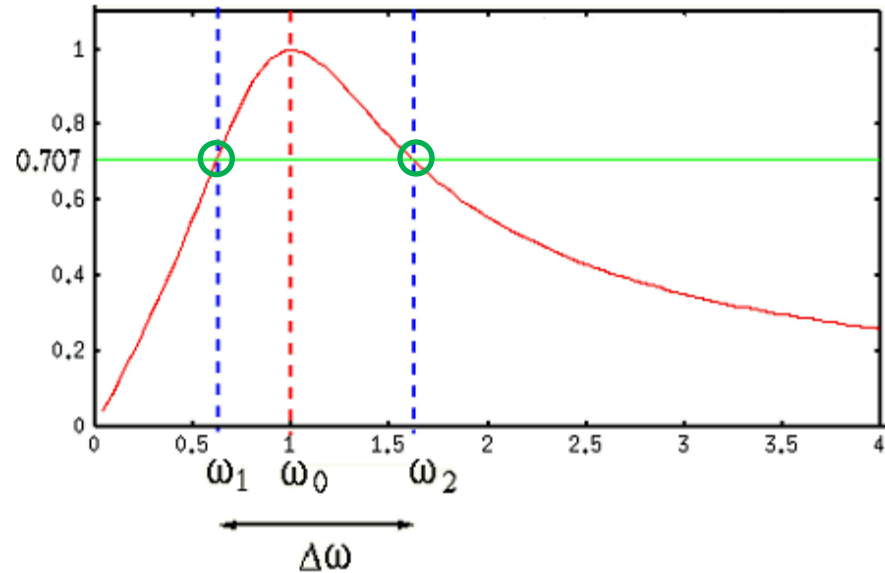At two different angular frequencies becomes imaginary Im and real part Re in the denominator equal. I is then $I_{\max}/\sqrt{2}$ ($\approx 71\%$).
 The **Bandwidth** $BW = \Delta\omega$ is the distance between those two angular frequencies.




$$\underline{I} = \frac{I_{\max}}{\left(\boxed{1} + \boxed{jQ\left(\frac{\omega}{\omega_0} - \frac{\omega_0}{\omega}\right)} \right)}$$

Re = Im

The equations give :

$$BW [\text{rad/s}] = \Delta\omega = \omega_2 - \omega_1 = \frac{\omega_0}{Q} \quad \omega_0^2 = \omega_2 \cdot \omega_1 \quad \omega_2, \omega_1 = \omega_0 \left(\pm \frac{1}{2Q} + \sqrt{\frac{1}{(2Q)^2} + 1} \right)$$

- More convenient formulas

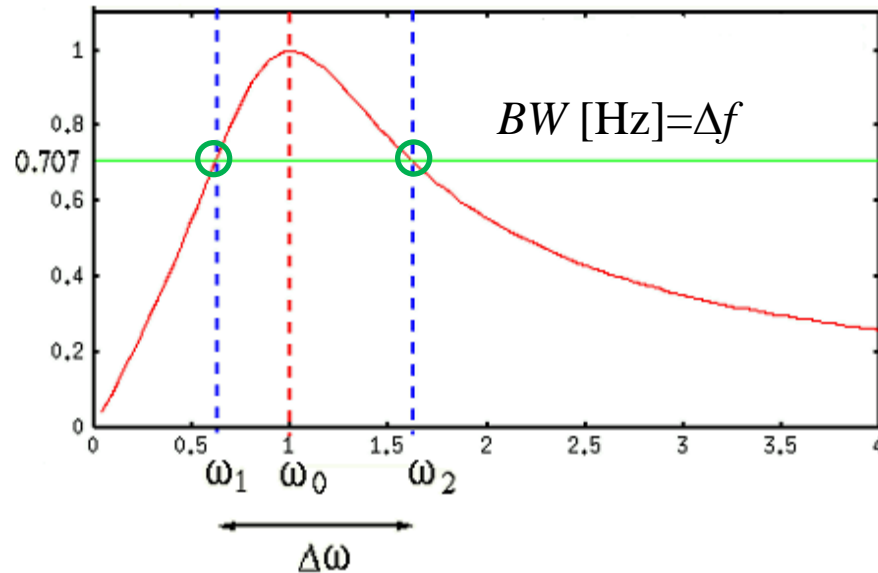

$$f_0 = \frac{1}{2\pi\sqrt{LC}}$$

$$Q = \frac{2\pi f_0 L}{r}$$

$$\frac{\Delta\omega}{\omega_0} = \frac{1}{Q} \Rightarrow$$

$$\frac{\Delta f}{f_0} = \frac{1}{Q}$$

If Q is high, no significant error is done if the bandwidth is divided equally on both sides of f_0 .

$$f_2, f_1 \approx f_0 \pm \frac{\Delta f}{2}$$

William Sandqvist william@kth.se



Example, series resonance circuit

$$C = 25 \text{ nF}$$

$$f_0 = 100 \text{ kHz}$$

$$BW = \Delta f = 12,5 \text{ kHz}$$

$$Q = ? \quad L = ? \quad r = ?$$

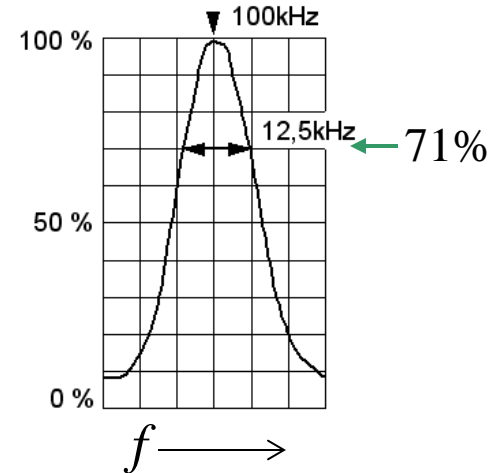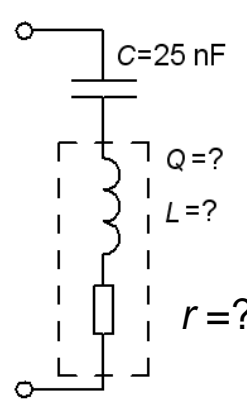

Example, series resonance circuit



$$C = 25 \text{ nF}$$

$$f_0 = 100 \text{ kHz}$$

$$BW = \Delta f = 12,5 \text{ kHz}$$

$$Q = ? \quad L = ? \quad r = ?$$
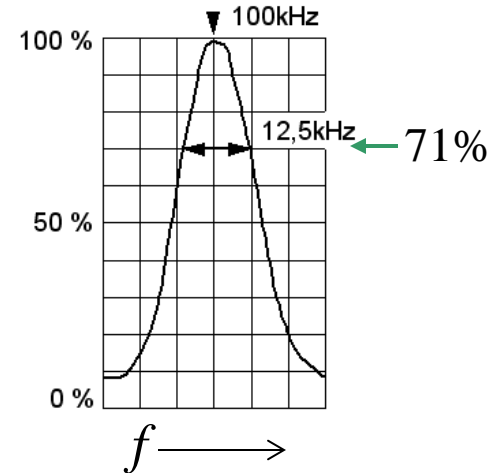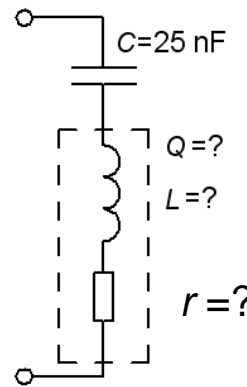
$$Q = \frac{f_0}{\Delta f} = \frac{100}{12,5} = 8$$



Example, series resonance circuit

$$C = 25 \text{ nF}$$


$$f_0 = 100 \text{ kHz}$$

$$BW = \Delta f = 12,5 \text{ kHz}$$

$$Q = ? \quad L = ? \quad r = ?$$

$$Q = \frac{f_0}{\Delta f} = \frac{100}{12,5} = 8$$
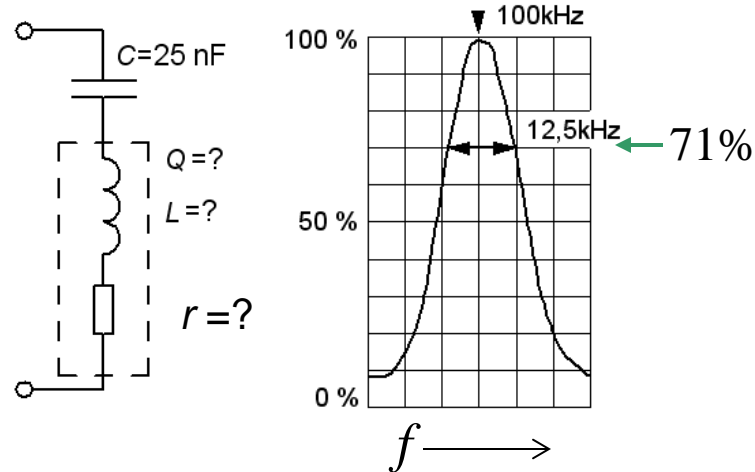
$$f_0 = \frac{1}{2\pi\sqrt{LC}} \Rightarrow L = \frac{1}{(2\pi f_0)^2 C} = \frac{1}{(2\pi \cdot 100 \cdot 10^3)^2 \cdot 25 \cdot 10^{-9}} = 0,1 \text{ mH}$$



Example, series resonance circuit

$$C = 25 \text{ nF}$$

$$f_0 = 100 \text{ kHz}$$


$$BW = \Delta f = 12,5 \text{ kHz}$$

$$Q = ? \quad L = ? \quad r = ?$$

$$Q = \frac{f_0}{\Delta f} = \frac{100}{12,5} = 8$$

$$f_0 = \frac{1}{2\pi\sqrt{LC}} \Rightarrow L = \frac{1}{(2\pi f_0)^2 C} = \frac{1}{(2\pi \cdot 100 \cdot 10^3)^2 \cdot 25 \cdot 10^{-9}} = 0,1 \text{ mH}$$

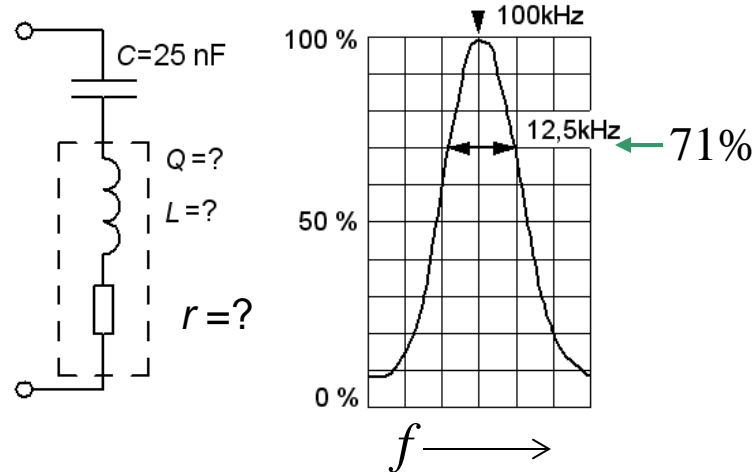
$$Q = \frac{X_L}{r} = \frac{2\pi f_0 \cdot L}{r} \Rightarrow r = \frac{2\pi f_0 \cdot L}{Q} = \frac{2\pi \cdot 100 \cdot 10^3 \cdot 0,1 \cdot 10^{-3}}{8} \approx 8 \Omega$$



William Sandqvist william@kth.se


How big is I ? (13.2)

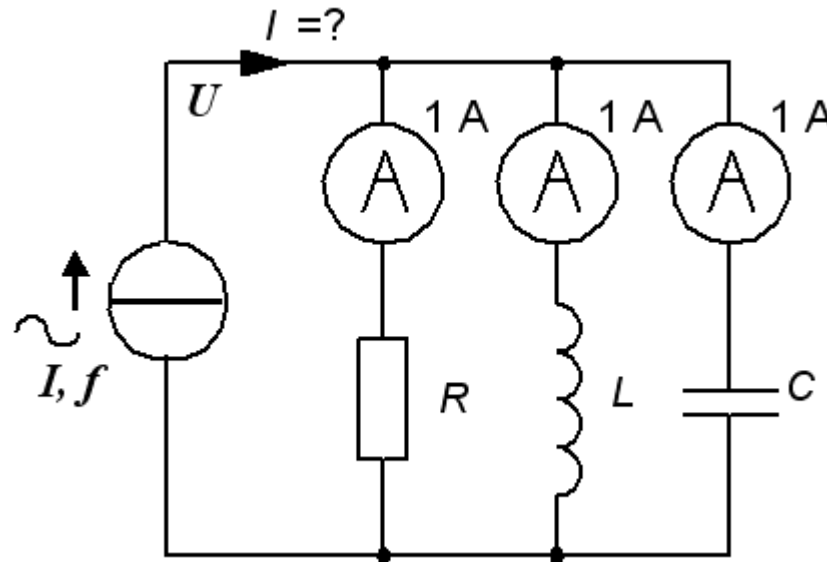The three ammeters show the same, 1 A, how much is the AC supply current I ? (*Warning, teaser*)




How big is I ? (13.2)

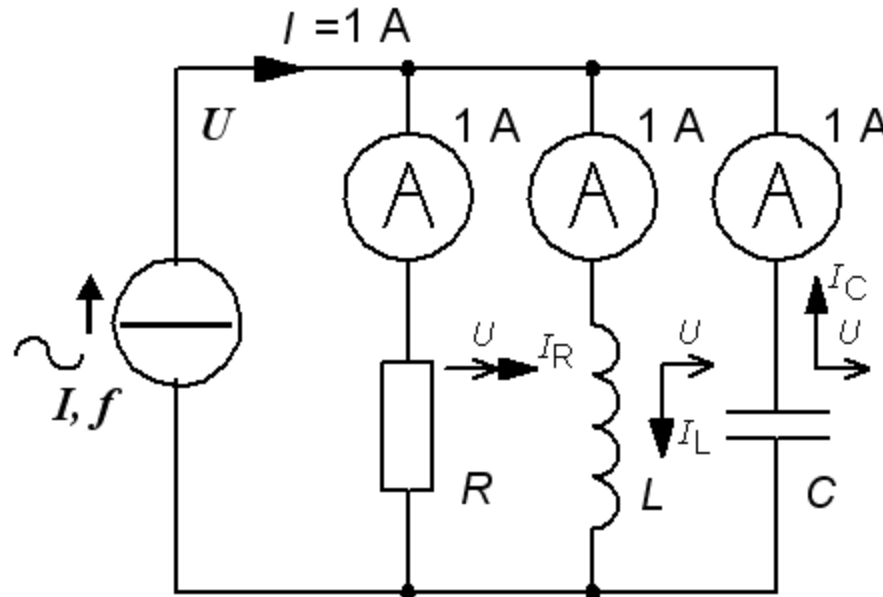The three ammeters show the same, 1 A, how much is the AC supply current I ? (*Warning, teaser*)



How big is I ? (13.2)

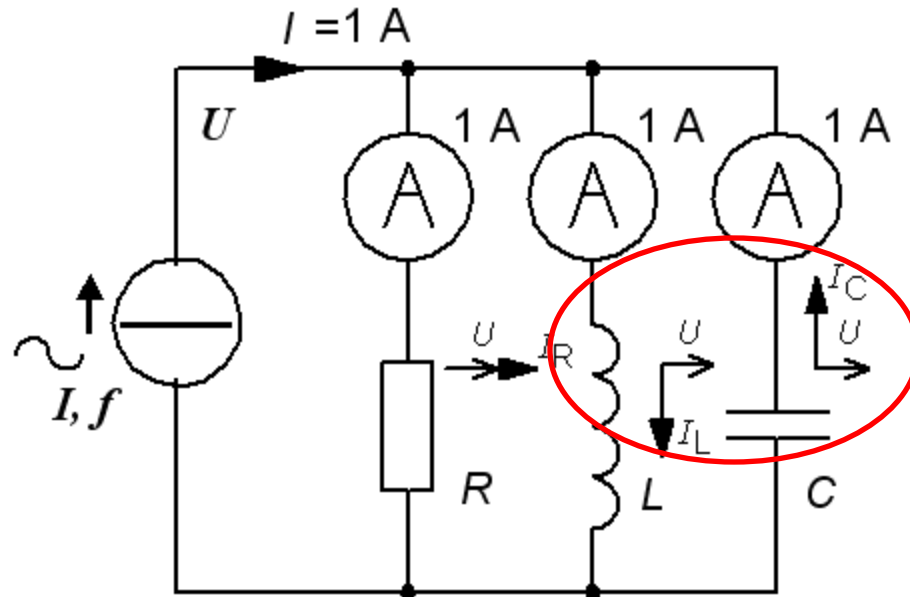The three ammeters show the same, 1A, how much is the AC supply current I ? (*Warning, teaser*)




I_L and I_C becomes a **circulating current** decoupled from I_R . I_L , I_C can be *many times bigger* than the supply current $I = I_R$. This is parallel resonance.

Ideal parallel resonance circuit

$$\underline{Z} = R \parallel L \parallel C = \frac{1}{\frac{1}{R} + \frac{1}{j\omega L} + j\omega C} = \frac{1}{\frac{1}{R} + j\left(\omega C - \frac{1}{\omega L}\right)}$$

$\omega C - \frac{1}{\omega L}$
=0

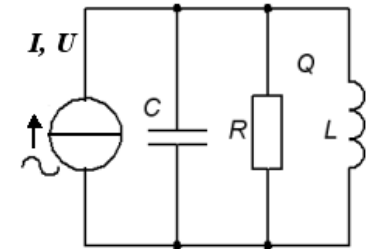


The resonance frequency has exactly the same expression as for the series resonant circuit, but otherwise the circuit has **reverse character**, **IND** at low frequencies and **CAP** at high. At resonance, the impedance is real = R .

$$f_0 = \frac{1}{2\pi\sqrt{LC}}$$

Ideal parallel resonance circuit

$$\underline{Z} = R \parallel L \parallel C = \frac{1}{\frac{1}{R} + \frac{1}{j\omega L} + j\omega C} = \frac{1}{\frac{1}{R} + j\left(\omega C - \frac{1}{\omega L}\right)}$$

=0

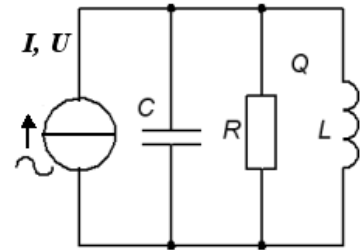


The resonance frequency has exactly the same expression as for the series resonant circuit, but otherwise the circuit has **reverse character, IND** at low frequencies and **CAP** at high. At resonance, the impedance is real = R .

$$f_0 = \frac{1}{2\pi\sqrt{LC}}$$

Actual parallel resonant circuit

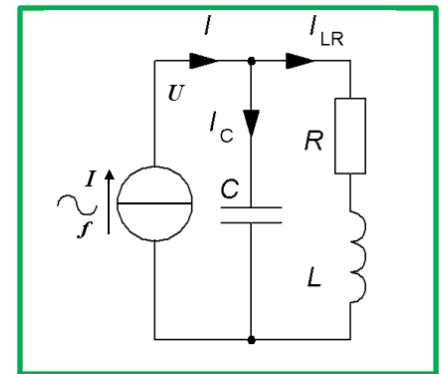Actual parallel resonant circuits has a series resistance inside the coil. The calculations become more complicated and the resonance frequency will also differ slightly from our formula.




William Sandqvist william@kth.se

Example, actual circuit (13.3)

$$\underline{I} = \underline{I}_C + \underline{I}_{LR} = \frac{U}{\frac{1}{j\omega C}} + \frac{U}{r + j\omega L} \cdot \frac{(r - j\omega L)}{(r - j\omega L)} = U \cdot \left(j\omega C + \frac{r - j\omega L}{r^2 + (\omega L)^2} \right) =$$

$$= U \cdot \left(\frac{r}{r^2 + (\omega L)^2} + j \left(\omega C - \frac{\omega L}{r^2 + (\omega L)^2} \right) \right)$$

=0

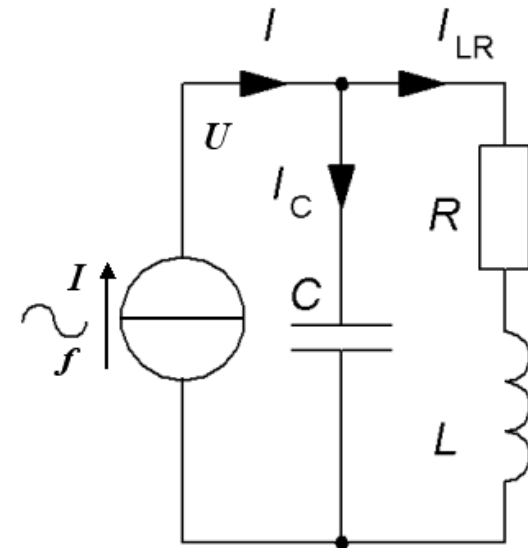


Example, actual circuit (13.3)

$$\underline{I} = \underline{I}_C + \underline{I}_{LR} = \frac{U}{\frac{1}{j\omega C}} + \frac{U}{r + j\omega L} \cdot \frac{(r - j\omega L)}{(r - j\omega L)} = U \cdot \left(j\omega C + \frac{r - j\omega L}{r^2 + (\omega L)^2} \right) =$$

$$= U \cdot \left(\frac{r}{r^2 + (\omega L)^2} + j \left(\omega C - \frac{\omega L}{r^2 + (\omega L)^2} \right) \right)$$

=0

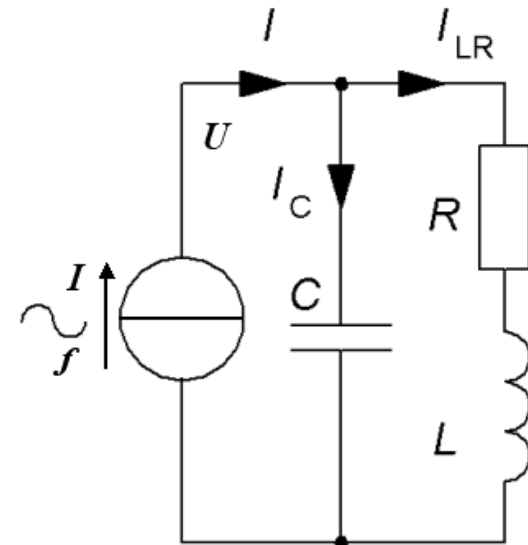

$$\omega_0 C = \frac{\omega_0 L}{r^2 + (\omega_0 L)^2} \Rightarrow \omega_0^2 = \frac{1}{LC} - \frac{r^2}{L^2} \quad \omega_0 = 2\pi f \Rightarrow f_0 = \frac{1}{2\pi} \sqrt{\left(\frac{1}{LC} - \frac{r^2}{L^2} \right)}$$


William Sandqvist william@kth.se

Metal Detector


$$f_0 = \frac{1}{2\pi} \sqrt{\left(\frac{1}{LC} - \frac{r^2}{L^2} \right)}$$

Any "losses" (even eddy-current losses in all kinds of metals) are summarized by the symbol r !

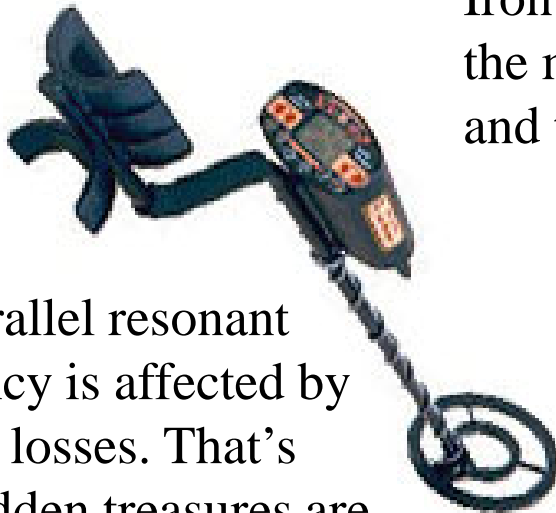Iron objects affects the magnetic field and thus also L !



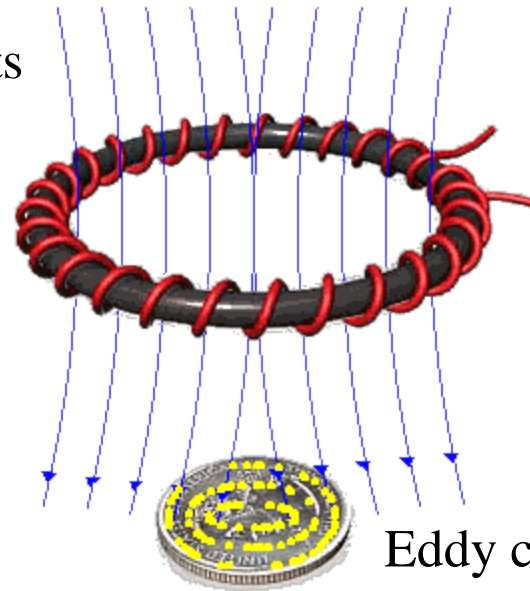The parallel resonant frequency is affected by the coil losses. That's how hidden treasures are found!



Eddy current losses


William Sandqvist william@kth.se

Series or parallel resistor

In manual computation for simplicity one usually uses the formulas of the ideal resonant circuit. At high Q and close to the resonance frequency f_0 the deviations becomes insignificant.

At $Q > 10$ are the two circuits "interchangeable".

$$\omega_0 \approx \frac{1}{\sqrt{LC}}$$

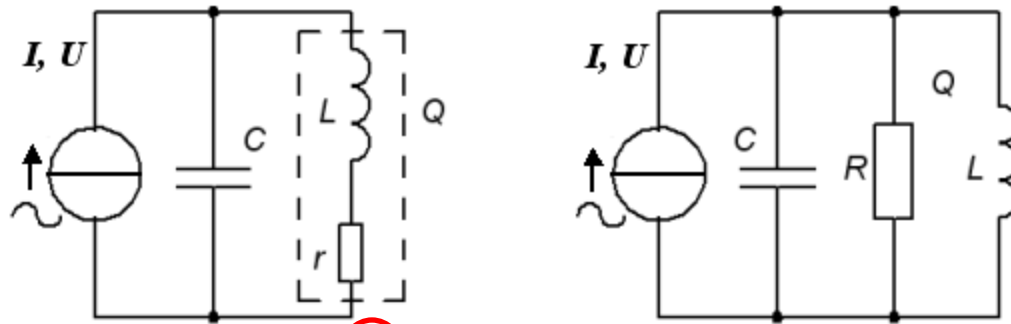

Alternative
definition of Q
with R_p

$$Q = \frac{\omega_0 L}{r_s} = \frac{R_p}{\omega_0 L} \Rightarrow R_p = Q^2 \cdot r_s$$

(applies approximately for $Q > 10$)

Example, parallel circuit

Parallel circuit.

$$C = 25 \text{ nF}$$

$$f_0 = 100 \text{ kHz}$$

$$BW = 1250 \text{ Hz}$$

$$L = ? \quad r = ?$$

Example, parallel circuit

Parallel circuit.

$$C = 25 \text{ nF}$$

$$f_0 = 100 \text{ kHz}$$

$$BW = 1250 \text{ Hz}$$

$$L = ? \quad r = ?$$

$$Q = \frac{f_0}{\Delta f} = \frac{100 \cdot 10^3}{1250} = 80$$

Example, parallel circuit

Parallel circuit.

$$C = 25 \text{ nF}$$


$$f_0 = 100 \text{ kHz}$$

$$BW = 1250 \text{ Hz}$$

$$L = ? \quad r = ?$$

$$Q = \frac{f_0}{\Delta f} = \frac{100 \cdot 10^3}{1250} = 80$$

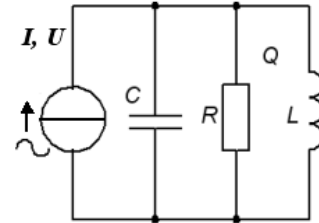80 > 10 justifying
counting with the ideal
model.



Example, parallel circuit

Parallel circuit.

$$C = 25 \text{ nF}$$

$$f_0 = 100 \text{ kHz}$$


$$BW = 1250 \text{ Hz}$$

$$L = ? \quad r = ?$$

$$Q = \frac{f_0}{\Delta f} = \frac{100 \cdot 10^3}{1250} = 80$$

80 > 10 justifying
counting with the ideal
model.
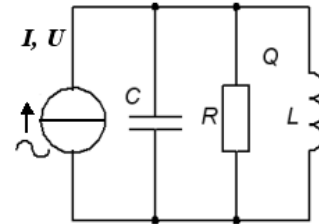
$$f_0 = \frac{1}{2\pi\sqrt{LC}} \Rightarrow L = \frac{1}{(2\pi f_0)^2 C} = \frac{1}{(2\pi \cdot 100 \cdot 10^3)^2 \cdot 25 \cdot 10^{-9}} = 0,1 \text{ mH}$$



Example, parallel circuit

Parallel circuit.

$$C = 25 \text{ nF}$$

$$f_0 = 100 \text{ kHz}$$

$$BW = 1250 \text{ Hz}$$


$$L = ? \quad r = ?$$

$$Q = \frac{f_0}{\Delta f} = \frac{100 \cdot 10^3}{1250} = 80$$

80 > 10 justifying
counting with the ideal
model.

$$f_0 = \frac{1}{2\pi\sqrt{LC}} \Rightarrow L = \frac{1}{(2\pi f_0)^2 C} = \frac{1}{(2\pi \cdot 100 \cdot 10^3)^2 \cdot 25 \cdot 10^{-9}} = 0,1 \text{ mH}$$
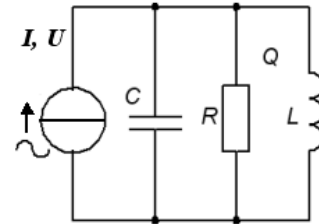
$$Q = \frac{R_p}{X_L} = \frac{R_p}{2\pi f_0 \cdot L} \Rightarrow R_p = 2\pi f_0 \cdot L \cdot Q = 2\pi \cdot 100 \cdot 10^3 \cdot 0,1 \cdot 10^{-3} \cdot 80 \approx 5027 \Omega$$



Example, parallel circuit


Parallel circuit.

$$C = 25 \text{ nF}$$

$$f_0 = 100 \text{ kHz}$$

$$BW = 1250 \text{ Hz}$$

Answer with a series resistor!

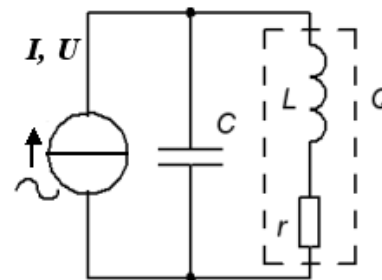

$$L = ? \quad r = ?$$

$$Q = \frac{f_0}{\Delta f} = \frac{100 \cdot 10^3}{1250} = 80$$

80 > 10 justifying counting with the ideal model.

$$f_0 = \frac{1}{2\pi\sqrt{LC}} \Rightarrow L = \frac{1}{(2\pi f_0)^2 C} = \frac{1}{(2\pi \cdot 100 \cdot 10^3)^2 \cdot 25 \cdot 10^{-9}} = 0,1 \text{ mH}$$

$$Q = \frac{R_P}{X_L} = \frac{R_P}{2\pi f_0 \cdot L} \Rightarrow R_P = 2\pi f_0 \cdot L \cdot Q = 2\pi \cdot 100 \cdot 10^3 \cdot 0,1 \cdot 10^{-3} \cdot 80 \approx 5027 \Omega$$

$$r_s = \frac{1}{Q^2} R_P = \frac{1}{80^2} 5027 \approx 0,8 \Omega$$

Example, parallel circuit


Parallel circuit.

$$C = 25 \text{ nF}$$

$$f_0 = 100 \text{ kHz}$$

$$BW = 1250 \text{ Hz}$$

Answer with a series resistor!

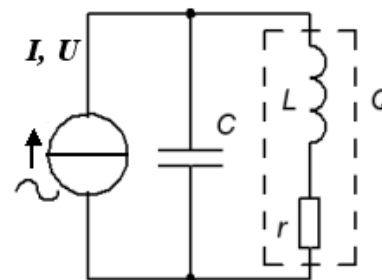

$$L = ? \quad r = ?$$

$$Q = \frac{f_0}{\Delta f} = \frac{100 \cdot 10^3}{1250} = 80$$

80 > 10 justifying counting with the ideal model.

$$f_0 = \frac{1}{2\pi\sqrt{LC}} \Rightarrow L = \frac{1}{(2\pi f_0)^2 C} = \frac{1}{(2\pi \cdot 100 \cdot 10^3)^2 \cdot 25 \cdot 10^{-9}} = 0,1 \text{ mH}$$

$$Q = \frac{R_P}{X_L} = \frac{R_P}{2\pi f_0 \cdot L} \Rightarrow R_P = 2\pi f_0 \cdot L \cdot Q = 2\pi \cdot 100 \cdot 10^3 \cdot 0,1 \cdot 10^{-3} \cdot 80 \approx 5027 \Omega$$

$$r_s = \frac{1}{Q^2} R_P = \frac{1}{80^2} 5027 \approx 0,8 \Omega$$

Luckily we did not have to use this formula to calculate the L

$$f_0 = \frac{1}{2\pi} \sqrt{\left(\frac{1}{LC} - \frac{r^2}{L^2} \right)}$$

Nowdays there are help ...



solve $L f = (1/(2\pi)) \sqrt{1/(LC) - r^2/L^2}$

Input interpretation:

solve	$f = \frac{1}{2\pi} \sqrt{\frac{1}{LC} - \frac{r^2}{L^2}}$	for	L
-------	--	-----	-----

Results:

$L = \frac{1 - \sqrt{1 - 16\pi^2 C^2 f^2 r^2}}{8\pi^2 C f^2}$

$L = \frac{\sqrt{1 - 16\pi^2 C^2 f^2 r^2} + 1}{8\pi^2 C f^2}$

Even if the transformation of R to r is not necessary, by computational reasons, anymore – so these are still important concepts when engineers "reason".


We chose the positive solution ...

Nowdays there are help ...


$$\begin{aligned} L &= \frac{\sqrt{1 - 16\pi^2 C^2 f_0^2 r^2} + 1}{8\pi^2 C f_0^2} = \\ &= \frac{\sqrt{1 - 16\pi^2 (25 \cdot 10^{-9})^2 \cdot (100 \cdot 10^3)^2 \cdot 0,8^2} + 1}{8\pi^2 \cdot 25 \cdot 10^{-9} \cdot (100 \cdot 10^3)^2} = 0,1 \text{ mH} \end{aligned}$$

William Sandqvist william@kth.se


Loaded resonance circuit

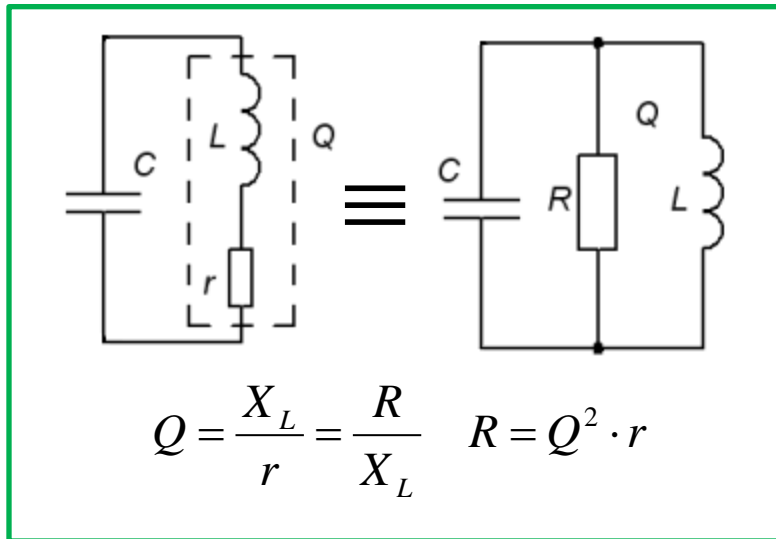

Usually the resonance circuit is loaded!

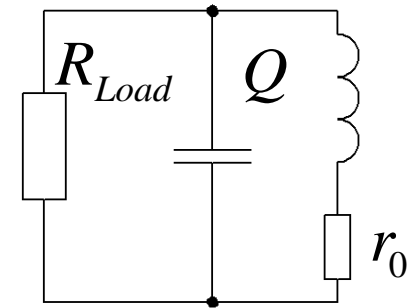


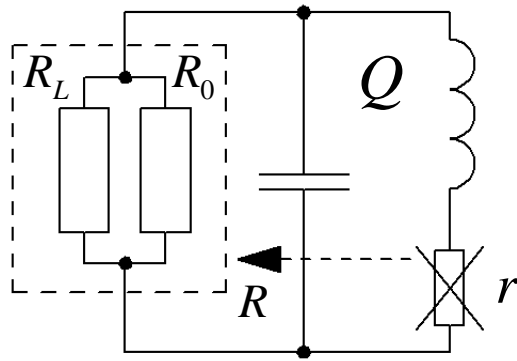If the loaded resonance circuit is to become the wanted Q value one has to have an inductor with a much better Q_0 !




$$R_L \parallel R_0 = R$$

$$R = Q^2 \cdot r$$


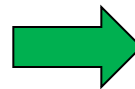


- Q_0 unloaded Q-value

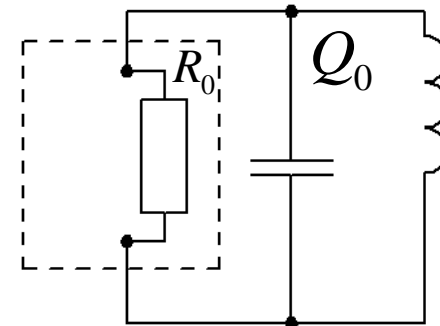

$$Q_0 = \frac{R_0}{X_L} > Q$$

Loaded resonance circuit

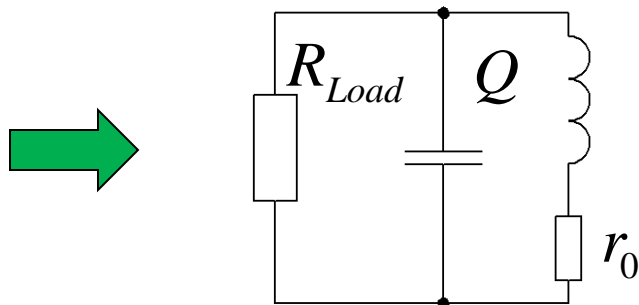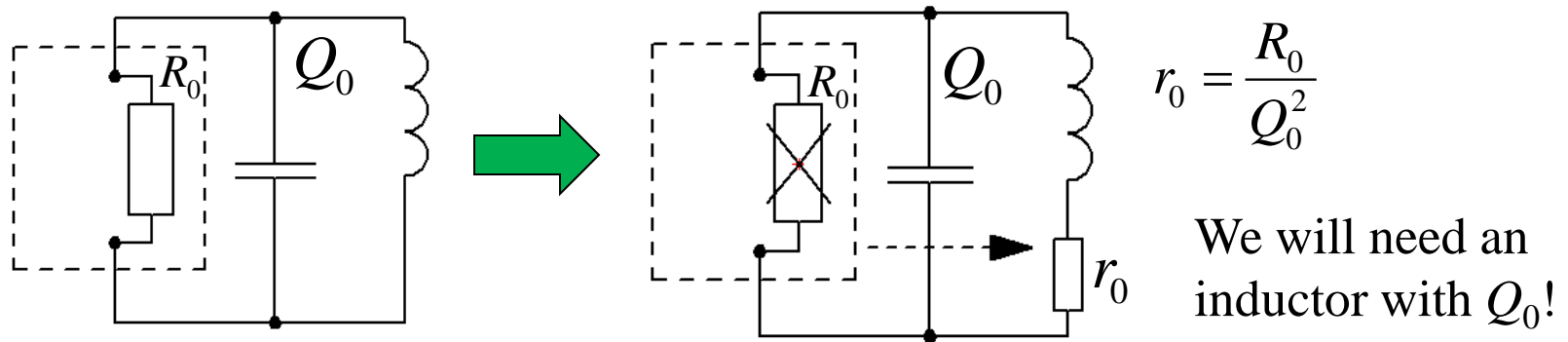


- When the circuit is loaded with R_{Load} the Q -value will change from Q_0 to Q !


William Sandqvist william@kth.se

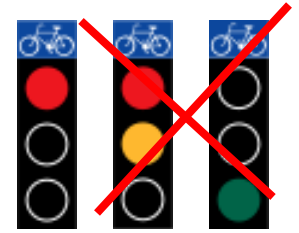The inductive sensor is a rugged sensor type available in many types.





Cyclists who request green?

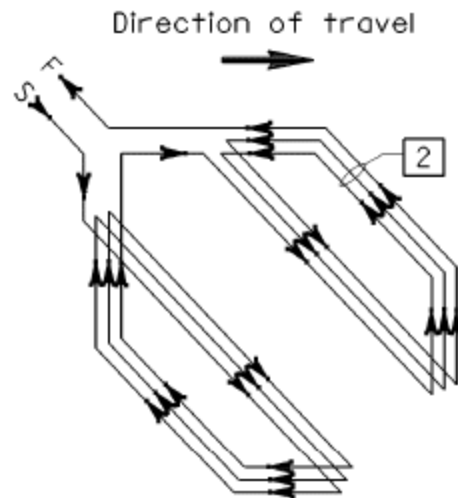

Inductive sensor
for bicycle



*Sorry! The
Sensor does not
work for **all**
bicycles?*

William Sandqvist william@kth.se

