

# IE1204 Digital Design

## F12: Asynchronous Sequential Circuits (Part 1)



**KTH Informations- och  
kommunikationsteknik**

Elena Dubrova  
KTH / ICT / ES  
dubrova@kth.se

# This lecture

- BV pp. 584-640

# Asynchronous Sequential Machines


- An asynchronous sequential machine is a sequential machine without flip-flops
- Asynchronous sequential machines are constructed by analyzing combinational logic circuits with feedback
- **Assumption: Only one signal in a circuit can change its value at any time**

# Asynchronous state machines

- Asynchronous state machines are used when it is necessary to keep the information about a state, but no clock is available
    - All flip-flops and latches are asynchronous state machines
    - Useful to synchronize events in situations where metastability is/can be a problem
-

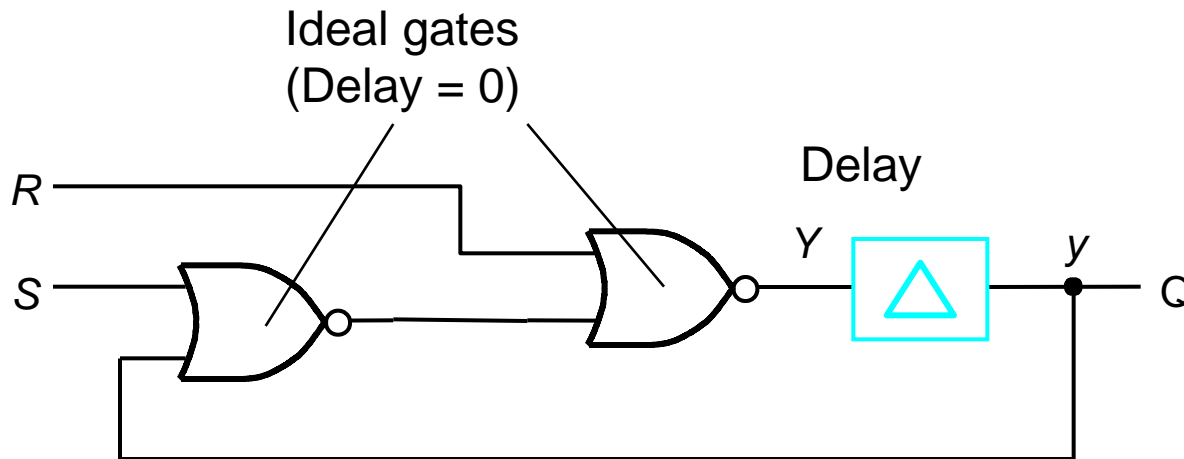
# Asynchronous sequential circuit: SR-latch with NOR gates

- To analyze the behavior of an asynchronous circuit, we use ideal gates and summarize their delays to a single block with delay  $\Delta$



 
# Analysis of a sequential asynchronous circuit

- By using a delay block, we can treat
  - $y$  as the current state
  - $Y$  as the next state


 
# State table

- Thus, we can produce a state table where the next state  $Y$  depends on the inputs and the current state  $y$



$$Y = \overline{R + (S + y)}$$

# State table

Present state $y$	Next state			
	$SR = 00$	01	10	11
	$Y$	$Y$	$Y$	$Y$
0	0	0	1	0
1	1	0	1	0

$$Y = R + \overline{\overline{S + y}}$$



# Stable states

Present state $y$	Next state			
	$SR = 00$	01	10	11
0	0	0	1	0
1	1	0	1	0

- Since we do not have flip-flops, but only combinational circuits, a state change can cause additional state changes
- A state is
  - stable if  $Y(t) = y(t + \Delta)$
  - unstable if  $Y(t) \neq y(t + \Delta)$


# Excitation table

- The state-assigned state table is called *excitation table*
- Stable states (next state = present state) are circled

Present state $y$	Next state			
	$SR = 00$	01	10	11
	$Y$	$Y$	$Y$	$Y$
0	0	0	1	0
1	1	0	1	0


# Flow table (Moore)

Present state	Next state				Output Q
	SR = 00	01	10	11	
A	(A)	(A)	B	(A)	0
B	(B)	A	(B)	A	1

 

# Flow Table (Mealy)

Present state	Next state				Output, Q			
	SR = 00	01	10	11	00	01	10	11
A	(A)	(A)	B	(A)	0	0	-	0
B	(B)	A	(B)	A	1	-	1	-

 

Do not care ('-') has been chosen for output decoder, since output changes directly after the state transition (basic implementation)

# Terminology

- When dealing with asynchronous sequential circuits, a different terminology is used
  - The state table called *flow table*
  - The state-assigned state table is called *excitation table*


# Analysis of Asynchronous Circuits

- The analysis is done using the following steps:
  - 1) Replace the feedbacks in the circuit with a delay element  $\Delta$ . The input of the delay element represents the next state  $Y$ , while the output  $y$  represents the current state.
  - 2) Find out the next-state and output expressions
  - 3) Set up the corresponding excitation table
  - 4) Create a flow table and replace the encoded states with symbolic states
  - 5) Draw a state diagram if necessary

# Example
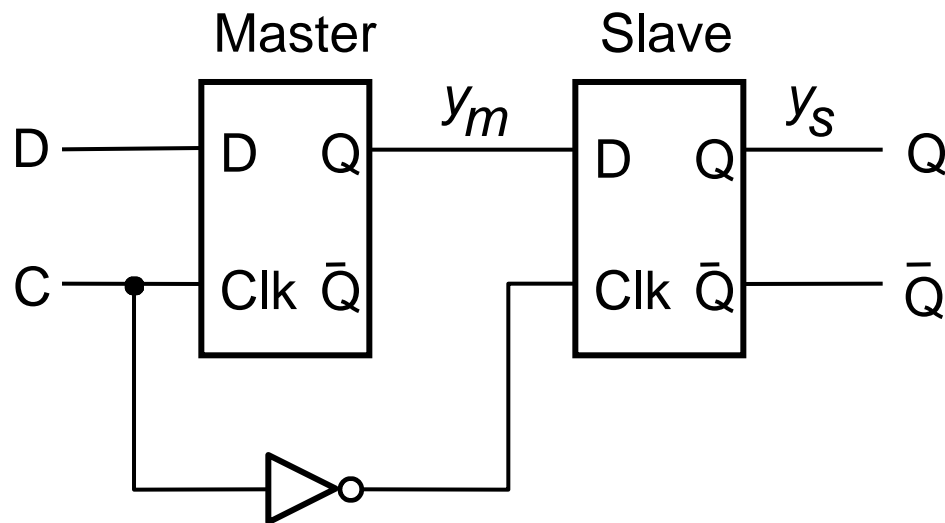
## Master-slave D flip-flop

- Master-slave D flip-flop is designed using two D-latches



The equations for the next state:

$$Y_m = CD + \bar{C}y_m$$
$$Y_s = \bar{C}y_m + Cy_s$$

# Excitation table

- From these equations, we can directly deduce the excitation table

$$Y_m = CD + \bar{C}y_m$$

$$Y_s = \bar{C}y_m + Cy_s$$

Present state $y_m y_s$	Nextstate				Output Q
	$CD = 00$	01	10	11	
	$Y_m Y_s$				
00	⓪⓪	⓪⓪	⓪⓪	10	0
01	00	00	⓪1	11	1
10	11	11	00	⓪10	0
11	⓪11	⓪11	01	⓪11	1



# Flow table

- We define four states S1, S2, S3, S4 and get the following flow table

Present state	Nextstate				Output Q
	CD = 00	01	10	11	
S1	(S1)	(S1)	(S1)	S3	0
S2	S1	S1	(S2)	S4	1
S3	S4	S4	S1	(S3)	0
S4	(S4)	(S4)	S2	(S4)	1

# Flow table

Present state	Nextstate				Output Q
	$CD = 00$	01	10	11	
S1	(S1)	(S1)	(S1)	S3	0
S2	S1	S1	(S2)	S4	1
S3	S4	S4	S1	(S3)	0
S4	(S4)	(S4)	S2	(S4)	1

- Remember: Only one input can be changed simultaneously
- Thus, some transitions never occur!

# Flow table

## (Impossible transitions)

Present state	Nextstate				Output Q
	<i>CD</i> = 00	01	10	11	
S1	(S1)	(S1)	(S1)	S3	0
S2	S1	S1	(S2)	S4	1
S3	<del>S4</del>	S4	S1	(S3)	0
S4	(S4)	(S4)	S2	(S4)	1

- State S3
  - The only stable state is S3 with input combination 11
  - Only one input can be changed => possible transitions are (11 => 01, 11 => 10)
    - These transitions originate in S3!
    - The input combination 00 in S3 is not possible!
    - The input combination 00 is set to don't care!


# Flow table (Impossible transitions)

Present state	Nextstate				Output Q
	$CD = 00$	01	10	11	
S1	(S1)	(S1)	(S1)	S3	0
S2	S1	<del>S1</del>	(S2)	S4	1
S3	-	S4	S1	(S3)	0
S4	(S4)	(S4)	S2	(S4)	1

- State S2
  - The only stable state is S2 with input combination 10
  - Only one entry can be changed => possible transitions are (10 => 11, 10 => 00)
    - These transitions originate in S2!
    - The input combination 01 in S2 is not possible!
    - The input combination 01 is set to don't care!

# State Diagram

## Master-slave D flip-flop

 


# Synthesis of asynchronous circuits

- The synthesis is carried out using the following steps:
  - 1) Create a state diagram according to the functional description
  - 2) Create a flow table and reduce the number of states if possible
  - 3) Assign codes to the states and create excitations table
  - 4) Determine expressions (transfer functions) for the next state and outputs
  - 5) Construct a circuit that implements the above expressions

# Example: Serial Parity Generator
 
## Step 1: Create a state diagram

- Input  $x$
- Output  $z$
- $z = 1$  if the number of pulses applied to  $x$  is odd
- $z = 0$  if the number of pulses applied to  $x$  is even



# Step 2: Flow chart

Pres state	Next State		z
	x=0	x=1	
A	(A)	B	0
B	C	(B)	1
C	(C)	D	1
D	A	(D)	0



# Step 3: Assign state codes

## Which encoding is good?

Pres state $y_2y_1$	Next State		z
	x=0	x=1	
	$Y_2Y_1$		
00	00	01	0
01	10	01	1
10	10	11	1
11	00	11	0

Poor encoding (HD = 2)

If we are in 11 under input  $x = 1$  and input change to  $x = 0$ , the circuit should change to 00

Pres state $y_2y_1$	Next State		z
	x=0	x=1	
	$Y_2Y_1$		
00	00	01	0
01	11	01	1
11	11	10	1
10	00	10	0

Good encoding (HD = 1)

# State encoding


- In asynchronous sequential circuits, it is impossible to guarantee that the two state variables change value simultaneously
  - Thus, a transition  $00 \Rightarrow 11$  results in
    - a transition  $00 \Rightarrow 01 \Rightarrow ???$
    - a transition  $00 \Rightarrow 10 \Rightarrow ???$
- To ensure correct operation, all state transitions **MUST** have Hamming distance 1
  - The **Hamming distance** is the number of bits in which two binary numbers differ
    - Hamming distance between 00 and 11 is 2
    - Hamming distance between 00 and 01 is 1

# State encoding

- Procedure to obtain good codes:
  - 1) Draw the transition diagram along the edges of the hypercube defined by the codes
  - 2) Remove any crossing lines by
    - a) swapping two adjacent nodes
    - b) exploiting available unused states
    - c) introducing more dimensions in the hypercube

# Example: Serial Parity Generator


Pres state $y_2y_1$	Next State		z
	x=0	x=1	
	$Y_2Y_1$		
00	00	01	0
01	10	01	1
10	10	11	1
11	00	11	0

 

Poor coding -  
Hamming Distance = 2  
(Intersecting lines)

# Example: Serial Parity Generator

Pres state $y_2y_1$	Next State		z
	x=0	x=1	
	$Y_2Y_1$		
00	00	01	0
01	11	01	1
11	11	10	1
10	00	10	0

 


Good coding  
Hamming Distance = 1  
(No intersecting lines)

# Exploiting unused states

Flow table from Fig. 9.21a of BV textbook

Present state	Nextstate				Output $g_2g_1$
	$r_2r_1 = 00$	01	10	11	
A	(A)	B	C	-	00
B	A	(B)	C	(B)	01
C	A	B	(C)	(C)	10

 


Poor coding

In the transition from B to C (or C to B) has the Hamming distance 2!  
 Danger to get stuck in an unspecified state (with code 11)!
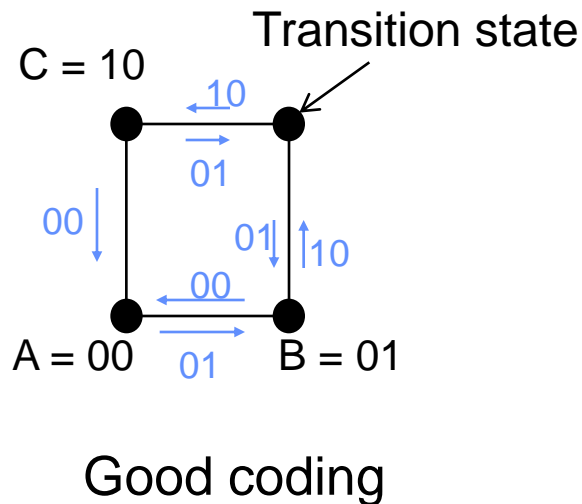
# Exploiting unused states




- Solution: Introduce a transition state that ensures that you do not end up in an unspecified state!



	Present state $y_2 y_1$	Nextstate				Output $g_2 g_1$
		$r_2 r_1 = 00$	01	11	10	
		$Y_2 Y_1$				
A	00	⊙00	01	-	10	00
B	01	00	⊙01	⊙01	11	01
D	11	-	01	-	10	dd
C	10	00	11	⊙10	⊙10	10
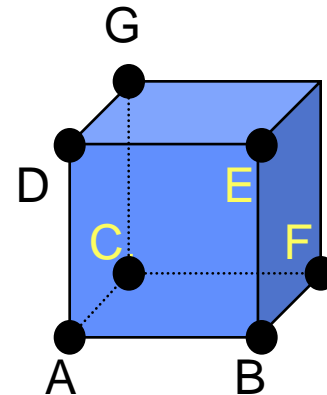  
# Additional states (more dimensions)

- One can increase the number of dimensions in order to implement stable state transitions



If it is not possible to redraw a diagram for  $HD = 1$ , we can add more states by adding extra dimensions. We take the nearest largest hypercube and draw the transitions through the available non steady states.



# Step 4: Draw Karnaugh maps

Pres state	Next State		z
	x=0	x=1	
	$Y_2Y_1$		
$y_2y_1$			
00	00	01	0
01	11	01	1
11	11	10	1
10	00	10	0

		$y_2y_1$			
		00	01	11	10
x	0	0	1	1	0
	1	0	0	1	1

		$y_2y_1$			
		00	01	11	10
x	0	0	1	1	0
	1	1	1	0	0

$$Y_2 = \bar{x}y_1 + y_2y_1 + xy_2$$

$$Y_1 = x\bar{y}_2 + \bar{y}_2y_1 + \bar{x}y_1$$

		$y_1$	
		0	1
$y_2$	0	0	1
	1	0	1

$$z = y_1$$

They red circles are needed to avoid hazards (see later Section)!

# Final circuit

		$y_2y_1$			
		00	01	11	10
$x$	0	0	1	1	0
	1	0	0	1	1


$$Y_2 = \bar{x}y_1 + y_2y_1 + xy_2$$

		$y_1$	
		0	1
$y_2$	0	0	1
	1	0	1

$$z = y_1$$

		$y_2y_1$			
		00	01	11	10
$x$	0	0	1	1	0
	1	1	1	0	0
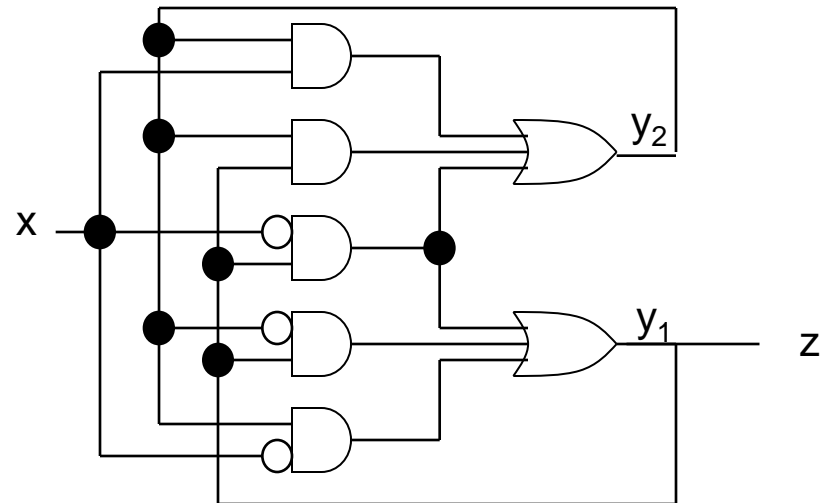
$$Y_1 = x\bar{y}_2 + \bar{y}_2y_1 + \bar{x}y_1$$





# What is a Hazard?

- Hazard is a term that means that there is a danger that the output value is not stable, but it can have glitches at certain input combinations
- Hazard occurs when paths from different inputs to the output have different lengths
- To avoid this, we must add implicants to cover the "dangerous" transitions

# Examples of hazard: MUX

x \ y <sub>2</sub> y <sub>1</sub>	00	01	11	10
0	0	1	1	0
1	0	0	1	1

$$Y_2 = \bar{x}y_1 + y_2y_1 + xy_2$$

  

During the transition from the  $(xy_2y_1) = (111)$  to  $(011)$ , the output  $Q$  has a glitch, as the path from  $x$  to  $Q$  is longer through the upper AND gate than through the lower AND gate (racing).

MORE ABOUT hazard in the next lecture!

# Step 5: Complete circuit

		$y_2y_1$			
	$x$	00	01	11	10
0		0	1	1	0
1		0	0	1	1


$$Y_2 = \bar{x}y_1 + y_2y_1 + xy_2$$

		$y_1$	
	$y_2$	0	1
0		0	1
1		0	1

$$z = y_1$$

		$y_2y_1$			
	$x$	00	01	11	10
0		0	1	1	0
1		1	1	0	0
 
$$Y_1 = x\bar{y}_2 + \bar{y}_2y_1 + \bar{x}y_1$$



# State minimization

- Procedure for minimizing the number of states
  1. Form equivalence classes.
  2. Minimize equivalence classes (state reduction)
  3. Form state diagrams either for Mealy or Moore.
  4. Merge compatible states in classes. Minimize the number of classes simultaneously. Each state can only belong to one classes.
  5. Construct the reduced flow table by merging rows in the selected classes
  6. Repeat steps 4-5 to see if more minimizations can be done


# Example

## Candy Machine (BV page 610)

- Candy machine has two inputs:
  - N: nickel (5 cents)
  - D: dime (10 cents)
- A candy bar costs 10 cents
- The machine will not return any change if there is 15 cents in the vending machine (a candy bar returned)
- The output  $z$  is active if there is enough money for a piece of candy
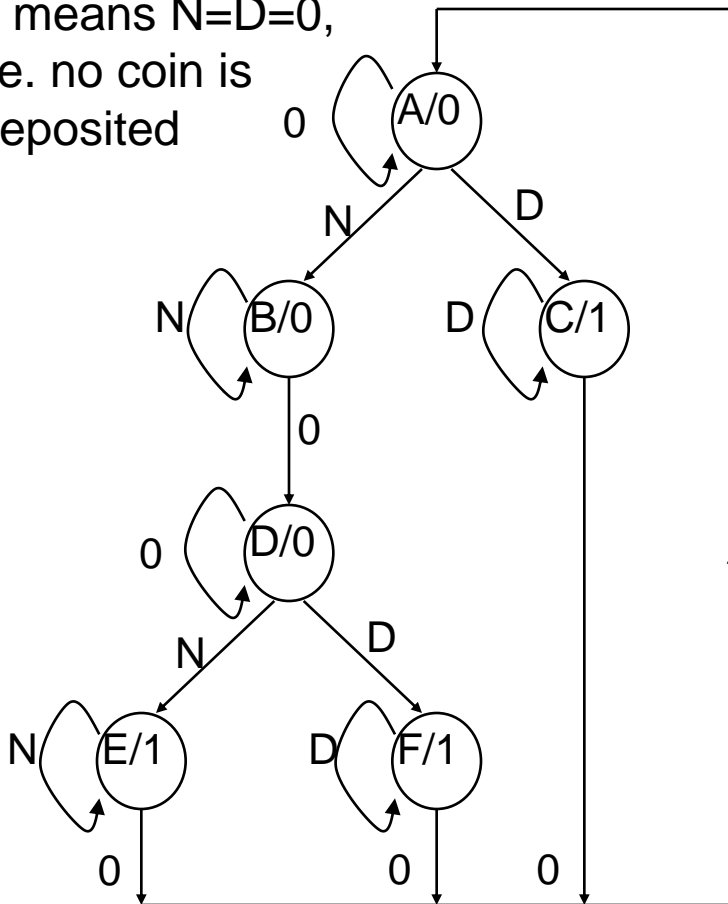
# State Diagram and Flow Chart

0 means  $N=D=0$ ,  
i.e. no coin is  
deposited



Pres state	Next State				z
	X=00	01	10	11	
A	(A)	B	C	-	0
B	D	(B)	-	-	0
C	A	-	(C)	-	1
D	(D)	E	F	-	0
E	A	(E)	-	-	1
F	A	-	(F)	-	1

(X = DN)

A flow table that contains only one stable state per row is called *primitive* flow table.



# Step 1: Form and minimize equivalence classes

1. Forming equivalence classes. To be in the same class, the following should hold for states:
  - Outputs must have the same value
  - Successors must be in the same classes
  - Stable states must be at the same positions
  - Don't cares for next state must be in the same positions
2. Minimize equivalence classes (state-reduction)

# State reduction

## Equivalence classes

$p_1 = (AD) (B) (CF) (E)$

$p_2 = (A) (D) (B) (CF) (E)$  ←

$p_3 = p_2$

A and D's successors fall into different classes for the input combination 01

Primitive flow table

Pres state	Next State				Q
	X=00	01	10	11	
A	(A)	B	C	-	0
B	D	(B)	-	-	0
C	A	-	(C)	-	1
D	(D)	E	F	-	0
E	A	(E)	-	-	1
F	A	-	(F)	-	1

Resulting flow table

Pres state	Next State				Q
	X=00	01	10	11	
A	(A)	B	C	-	0
B	D	(B)	-	-	0
C	A	-	(C)	-	1
D	(D)	E	C	-	0
E	A	(E)	-	-	1

## Step 2: Merging states

3. Construct state diagram either for Mealy or Moore
4. Merge compatible states in groups. Minimize the number of groups simultaneously. Each state may belong to one group only.
5. Construct the reduced flow table by merging rows in the selected groups
6. Repeat steps 3-5 to see if more minimizations can be done

# Merging states

- Two states are compatible and can be merged if the following applies
  1. at least one of the following conditions apply to all input combinations
    - both  $S_i$  and  $S_j$  have the same successor, or
    - both  $S_i$  and  $S_j$  are stable, or
    - the successor of  $S_i$  or  $S_j$ , or both, is unspecified
  2. For a Moore machine, in addition the following should hold
    - both  $S_i$  and  $S_j$  have the same output values whenever specified (not necessary for a Mealy machine)


# Merging states

Resulting flow table

Pres state	Next State				Q
	X=00	01	10	11	
A	Ⓐ	B	C	-	0
B	D	Ⓑ	-	-	0
C	A	-	Ⓒ	-	1
D	Ⓓ	E	C	-	0
E	A	Ⓔ	-	-	1

Each row will be a point in a compatibility graph

Compatibility graph

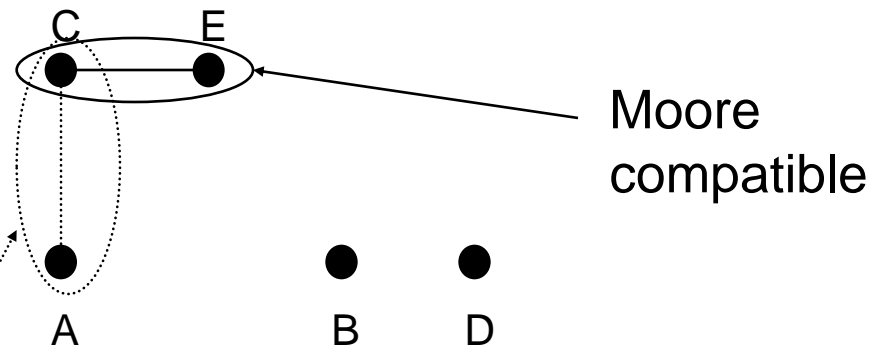

Mealy-compatible: In state A ( $X = 00$ ) the output is 0, in state C the output is 1

# An illustrative example

## Equivalence classes

$P_1 = (AG) (BL) (C) (D) (E) (F) (HK) (J)$

$P_2 = (A) (G) (BL) (C) (D) (E) (F) (HK) (J)$

$P_3 = P_2$

## Primitive flow table

Pres state	Next State				Q
	X=00	01	10	11	
A	Ⓐ F	C	-	-	0
B	A Ⓑ	-	H	-	1
C	G	-	Ⓒ	-	0
D	-	F	-	Ⓓ	1
E	G	-	Ⓔ	D	1
F	-	Ⓕ	-	K	0
G	Ⓖ	B	J	-	0
H	-	L	E	Ⓗ	1
J	G	-	Ⓙ	-	0
K	-	B	E	Ⓚ	1
L	A	Ⓛ	-	K	1


## Reduced flow table

Pres state	Next State				Q
	X=00	01	10	11	
A	Ⓐ F	C	-	-	0
B	A Ⓑ	-	H	-	1
C	G	-	Ⓒ	D	0
D	-	F	-	Ⓓ	1
E	G	-	Ⓔ	D	1
F	-	Ⓕ	-	H	0
G	Ⓖ	B	J	-	0
H	-	B	E	Ⓗ	1
J	G	-	Ⓙ	-	0

# An illustrative example (cont'd)

Reduced flow table

Pres state	Next State				Q
	X=00	01	10	11	
A	(A) F C -	0			
B	A (B) - H	1			
C	G - (C) D	0			
D	- F - (D)	1			
E	G - (E) D	1			
F	- (F) - H	0			
G	(G) B J -	0			
H	- B E (H)	1			
J	G - (J) -	0			

 


Pres state	Next State				Q
	X=00	01	10	11	
A	A A C B	0			
B	A B D B	1			
C	G - C D	0			
D	G A D D	1			
G	G B G -	0			

# An illustrative example (cont'd)

Reduced flow table

Pres state	Next State				Q
	X=00	01	10	11	
A	Ⓐ	Ⓐ	C	B	0
B	A	Ⓑ	D	Ⓑ	1
C	G	-	Ⓒ	D	0
D	G	A	Ⓓ	Ⓓ	1
G	Ⓔ	B	Ⓔ	-	0

 

Final flow table

Pres state	Next State				Q
	X=00	01	10	11	
A	Ⓐ	Ⓐ	C	B	0
B	A	Ⓑ	D	Ⓑ	1
C	Ⓒ	B	Ⓒ	D	0
D	C	A	Ⓓ	Ⓓ	1



# Summary

- Asynchronous state machines
  - Based on analysis of combinational circuits with feedback
  - All flip-flops and latches are asynchronous state machines
- A similar theory as for synchronous state machines can be applied
  - Only one input or state variable can be changed at a time!
  - We must also take into account the problem with hazards
- Next lecture: BV pp. 640-648, 723-724