
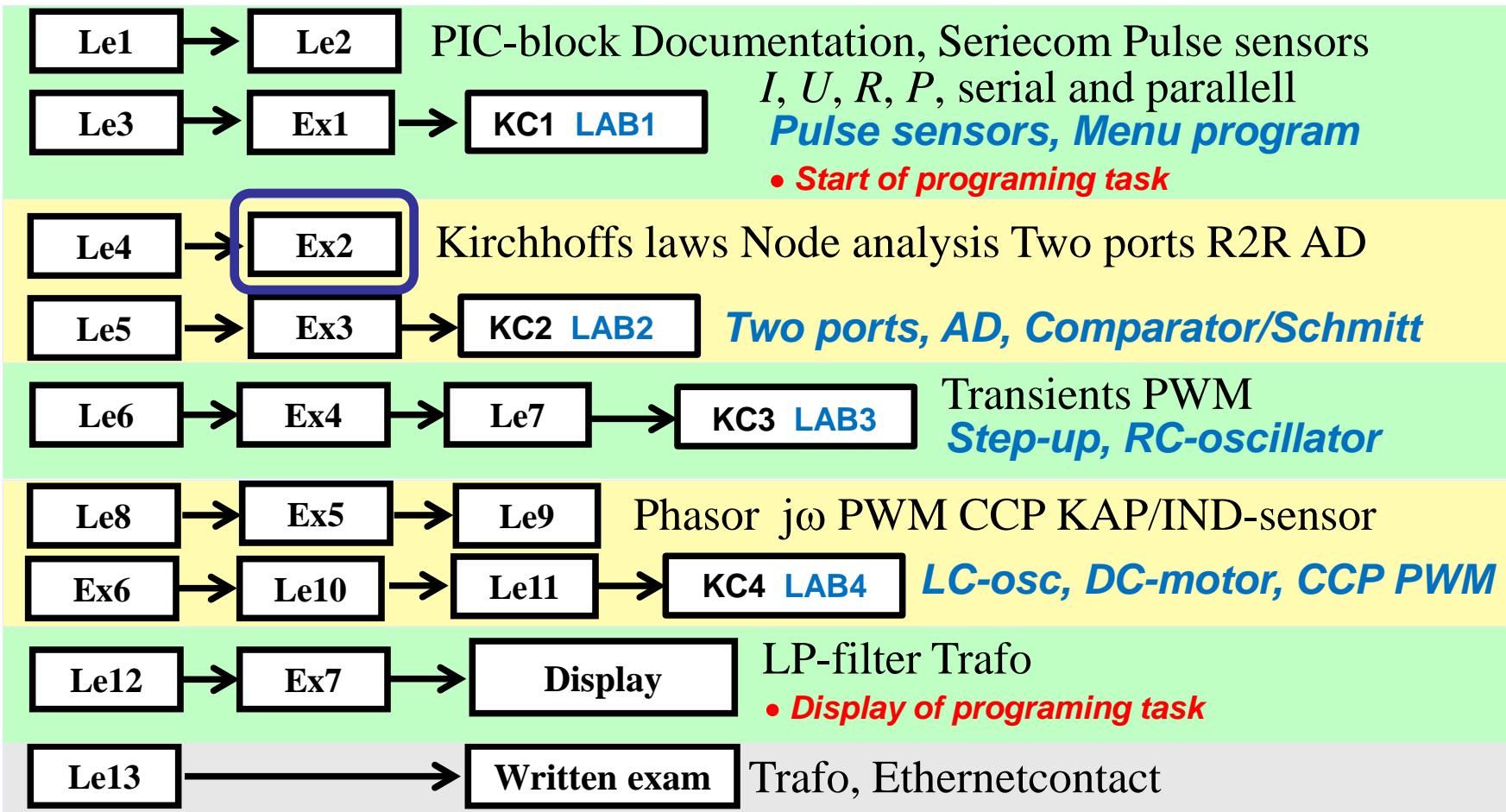


# IE1206 Embedded Electronics

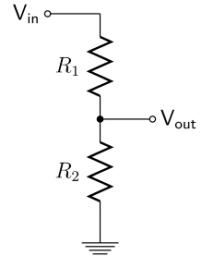



# Voltage divider formula

Voltage  
division  
factor



	Divided Total Voltage Voltage	$U_1 = U \times \frac{R_1}{R_1 + R_2} = 12 \frac{100}{100+200} = 4V$
	$U_2 = U \times \frac{R_2}{R_1 + R_2} = 12 \frac{200}{100+200} = 8V$	


According to the voltage divider formula you get a divided voltage, for example  $U_1$  across the resistor  $R_1$ , by multiplying the total voltage  $U$  with a voltage division factor. This voltage division factor is the resistance  $R_1$  divided by the sum of all the resistors that are in the series connection.

William Sandqvist william@kth.se
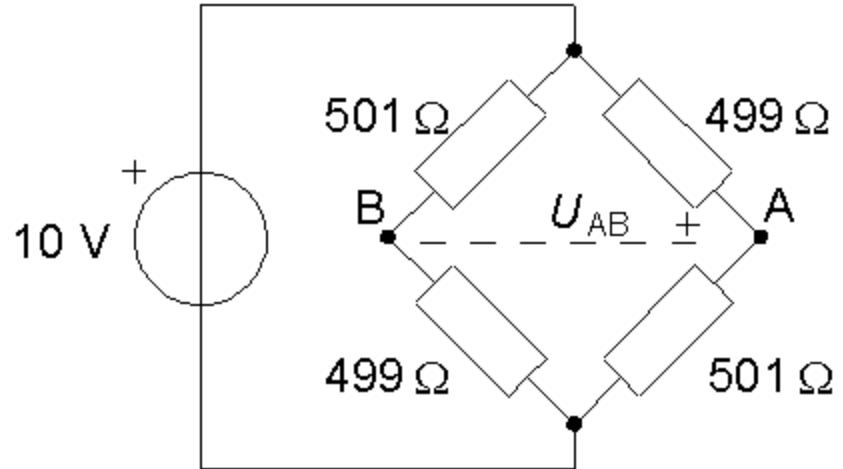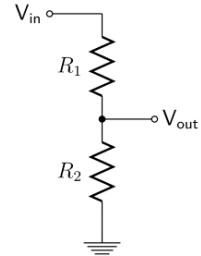
# Unbalanced Wheatstone bridge

Points A and B are approximately at half the battery voltage. A is closer to "+ pole" and B is closer to "-pole." The difference  $U_{AB}$  can be measured with a sensitive millivoltmeter connected between A and B.




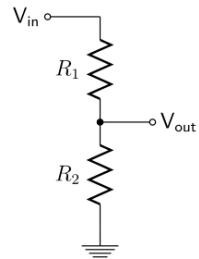

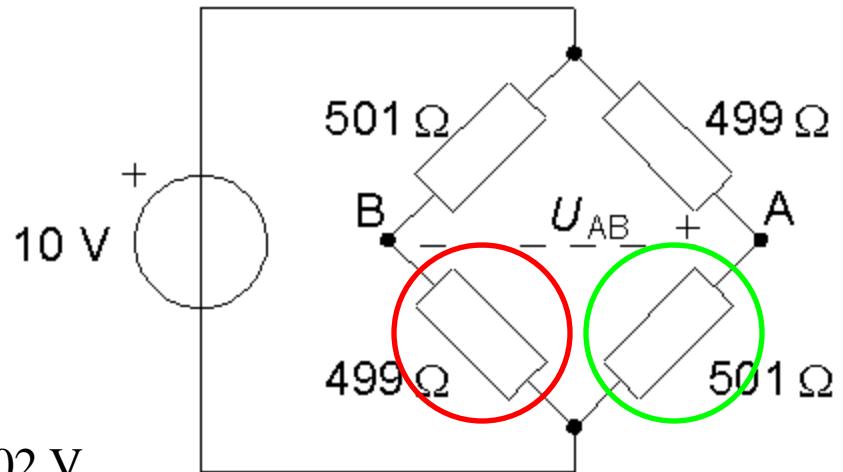
# Unbalanced Wheatstone bridge

Points A and B are approximately at half the battery voltage. A is closer to "+ pole" and B is closer to "-pole." The difference  $U_{AB}$  can be measured with a sensitive millivolt meter connected between A and B.

$$U_{AB} = 10 \frac{501}{499 + 501} - 10 \frac{499}{501 + 499} = 0,02 \text{ V}$$




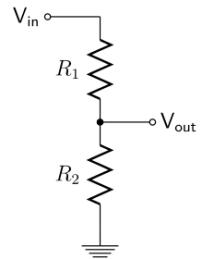
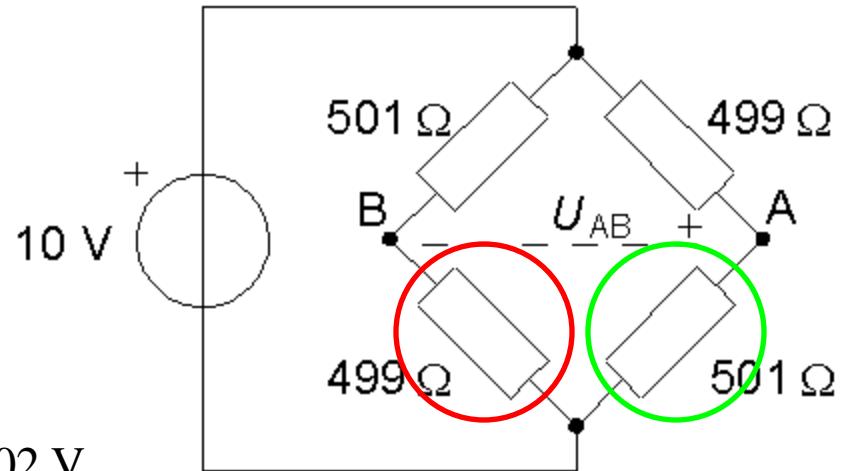
# Unbalanced Wheatstone bridge


Points A and B are approximately at half the battery voltage. A is closer to "+ pole" and B is closer to "-pole." The difference  $U_{AB}$  can be measured with a sensitive millivolt meter connected between A and B.

$$U_{AB} = 10 \frac{501}{499 + 501} - 10 \frac{499}{501 + 499} = 0,02 \text{ V}$$







*Why has the resistors values 501 and 499?*

# Loadcell

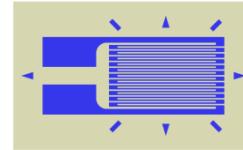


Industrial scales. Two strain gauges on the top of a beam increases from 500 to 501. Two strain gauge on the bottom of a beam decreases 500 to 499.

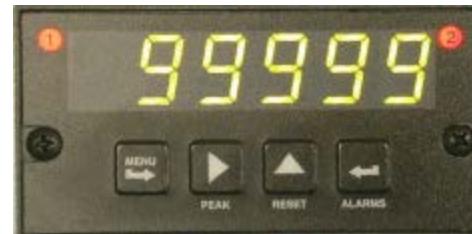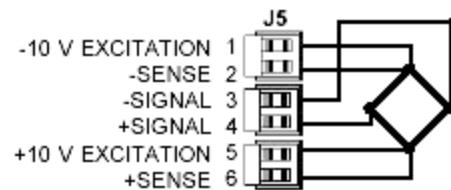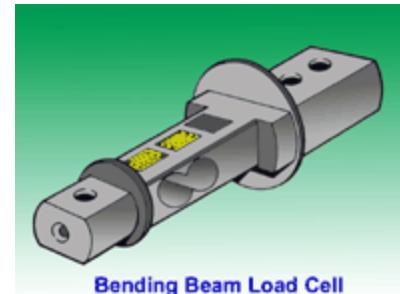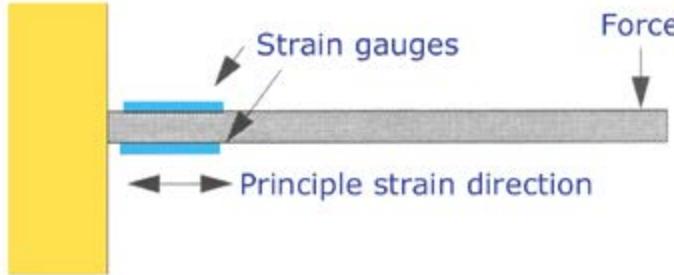The gauges are connected as a Wheatstone bridge. The unbalance voltage is a direct measure on the force  $F$  (or if it's a scale  $F = mg$ ).




William Sandqvist william@kth.se

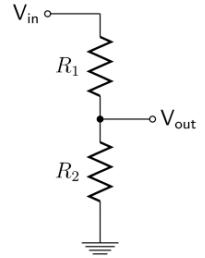

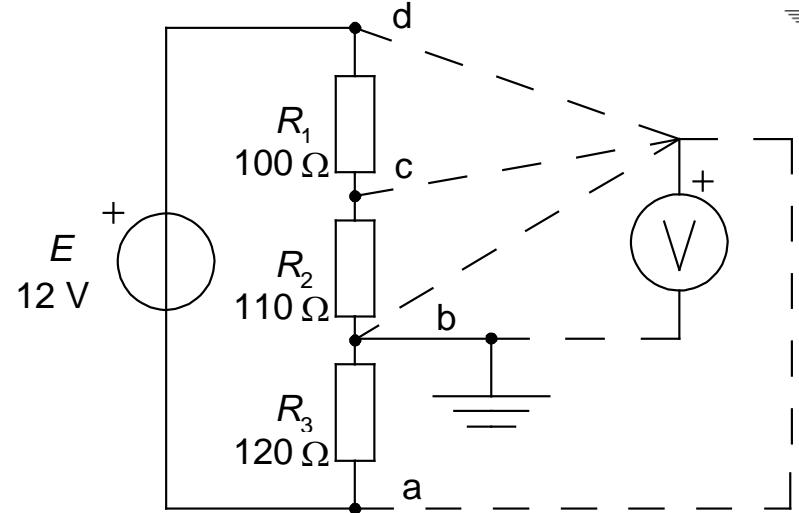
# Potential (7.1)

A voltage divider consists of three resistors  $R_1 = 100 \Omega$ ,  $R_2 = 110 \Omega$ ,  $R_3 = 120 \Omega$ , they are connected to a emf  $E = 12 \text{ V}$ .




One measures the potential (voltage relative to ground) at various sockets on the the voltage divider.

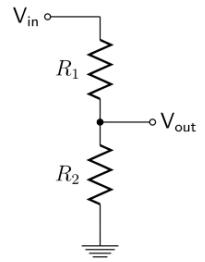
Voltmeter negative terminal is all the time connected to the socket **b**, ground, while the positive terminal of the voltmeter in turn connects to the **a**, **b**, **c**, and **d**. What does the voltmeter show?



# Potential (7.1)

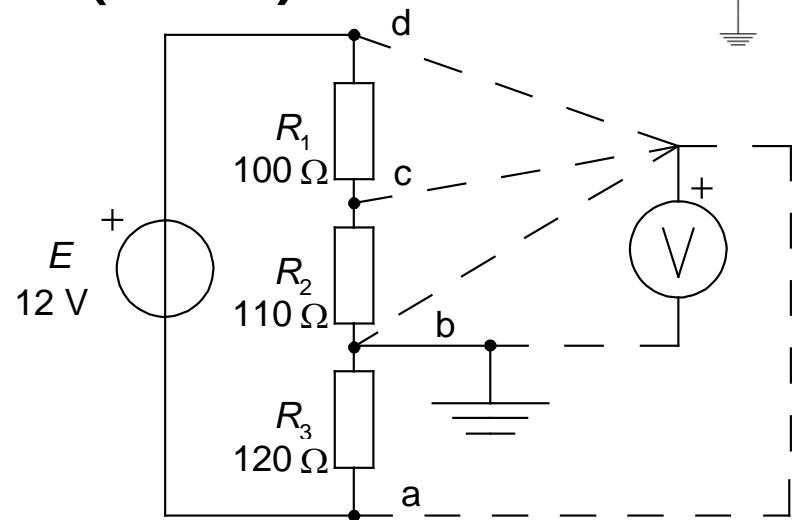


Socket	a)	b)	c)	d)
Voltmeter [V]				

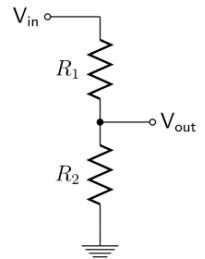

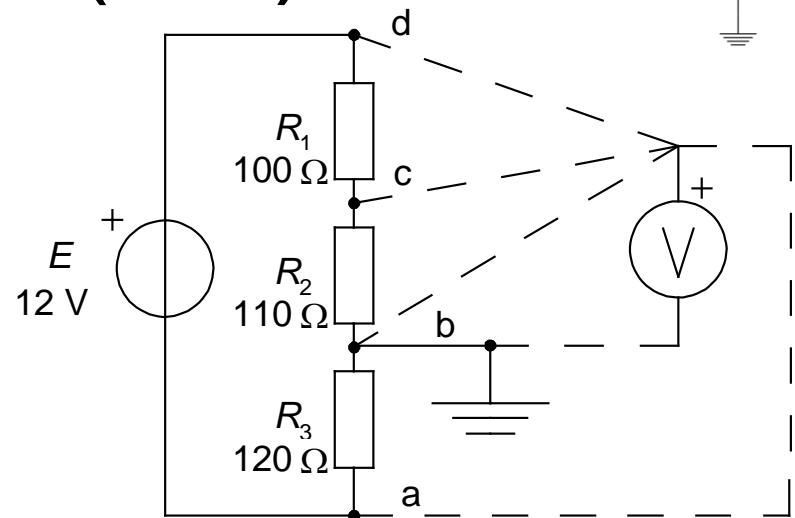
# Potential (7.1)

$$U_{ab} = -U_{ba} = -12 \frac{120}{100+110+120} = -4,37$$




Socket	a)	b)	c)	d)
Voltmeter [V]	-4,37			

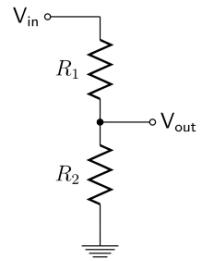

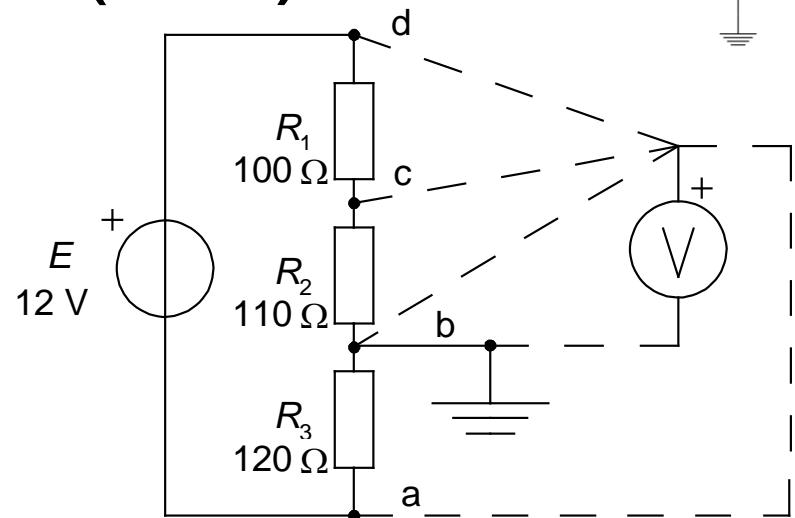
# Potential (7.1)

$$U_{ab} = -U_{ba} = -12 \frac{120}{100+110+120} = -4,37$$




Socket	a)	b)	c)	d)
Voltmeter [V]	-4,37	0		

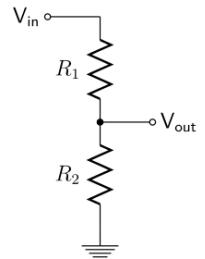

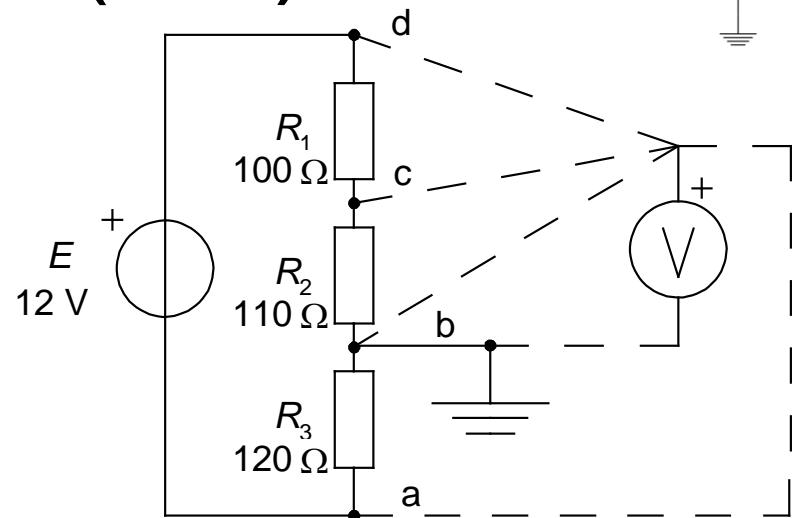
# Potential (7.1)

$$U_{ab} = -U_{ba} = -12 \frac{120}{100+110+120} = -4,37$$

$$U_{cb} = 12 \frac{110}{100+110+120} = 4$$



Socket	a)	b)	c)	d)
Voltmeter [V]	-4,37	0	4	

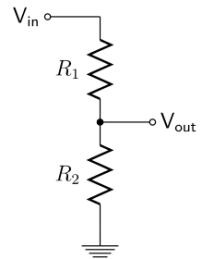


# Potential (7.1)

$$U_{ab} = -U_{ba} = -12 \frac{120}{100+110+120} = -4,37$$


$$U_{cb} = 12 \frac{110}{100+110+120} = 4$$
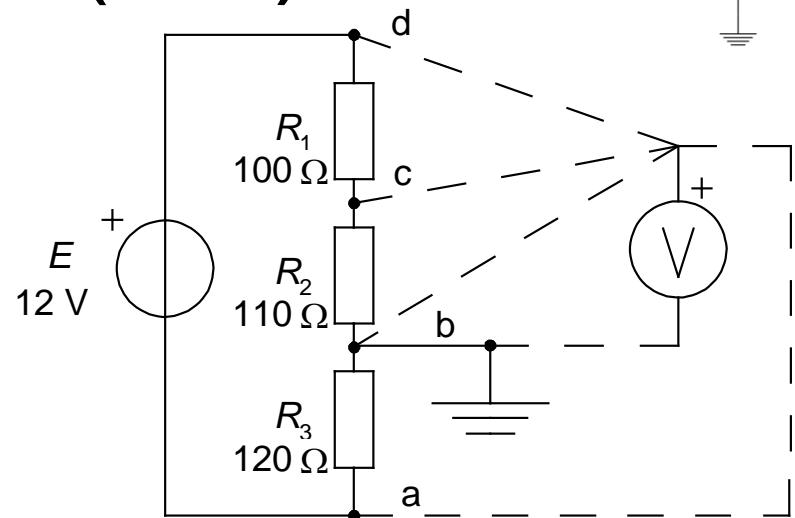
$$U_{db} = 12 \frac{100+110}{100+110+120} = 7,64$$





Socket	a)	b)	c)	d)
Voltmeter [V]	-4,37	0	4	7,64

William Sandqvist william@kth.se

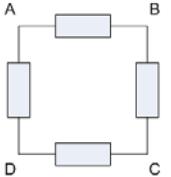


# Kirchhoff's voltage law (5.3)

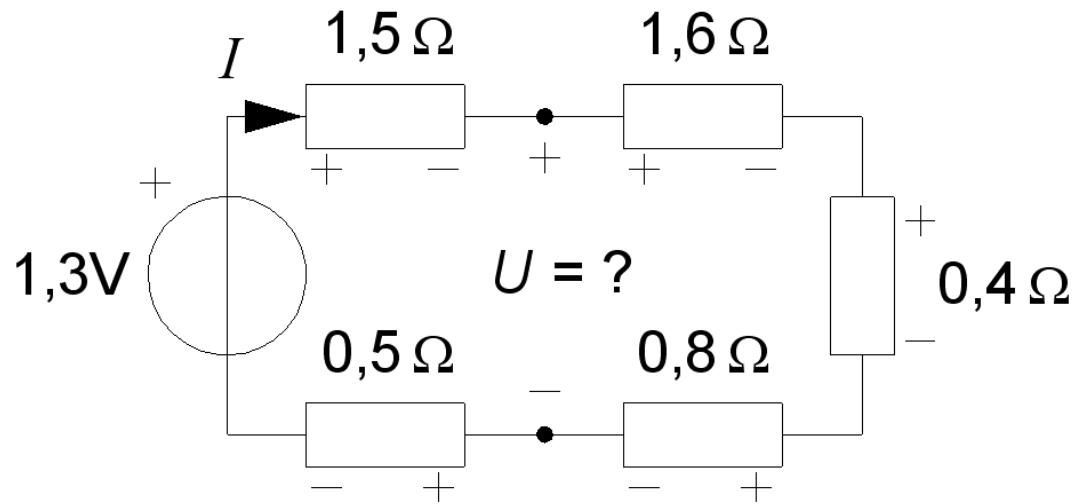


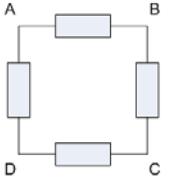


# Kirchhoff's voltage law (5.3)

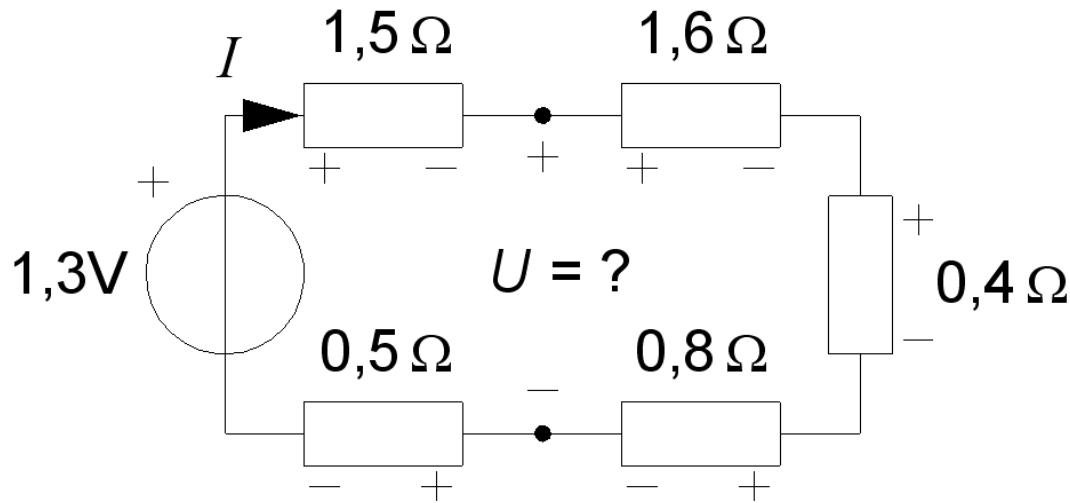
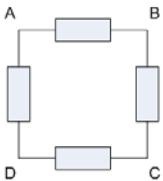
$$I = \frac{1,3}{1,5 + 1,6 + 0,4 + 0,8 + 0,5} = 0,27$$




# Kirchhoff's voltage law (5.3)

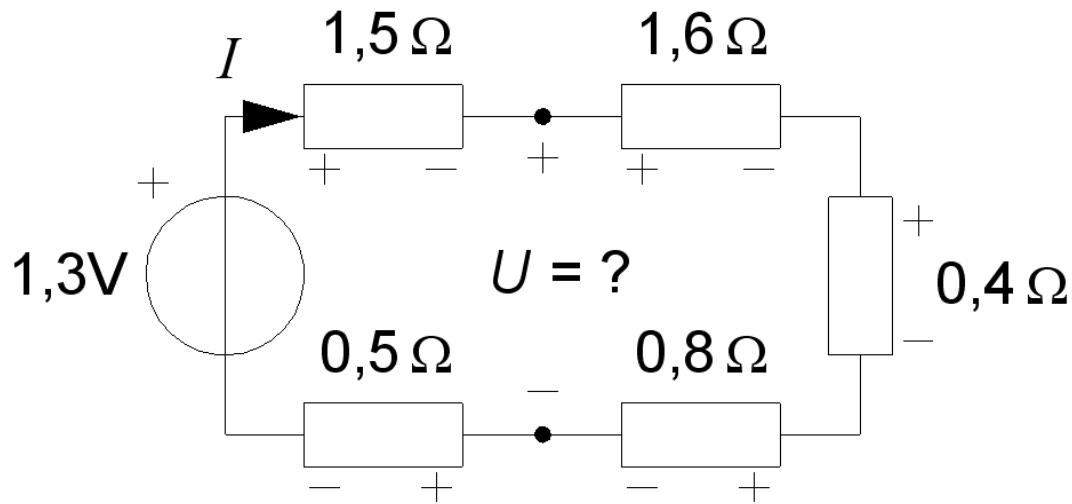


$$I = \frac{1,3}{1,5 + 1,6 + 0,4 + 0,8 + 0,5} = 0,27 \quad U_{0,5} = 0,5 \cdot 0,27 = 0,14$$

$$U_{1,5} = 1,5 \cdot 0,27 = 0,41$$

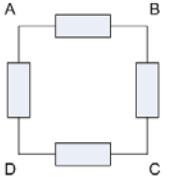

# Kirchhoff's voltage law (5.3)

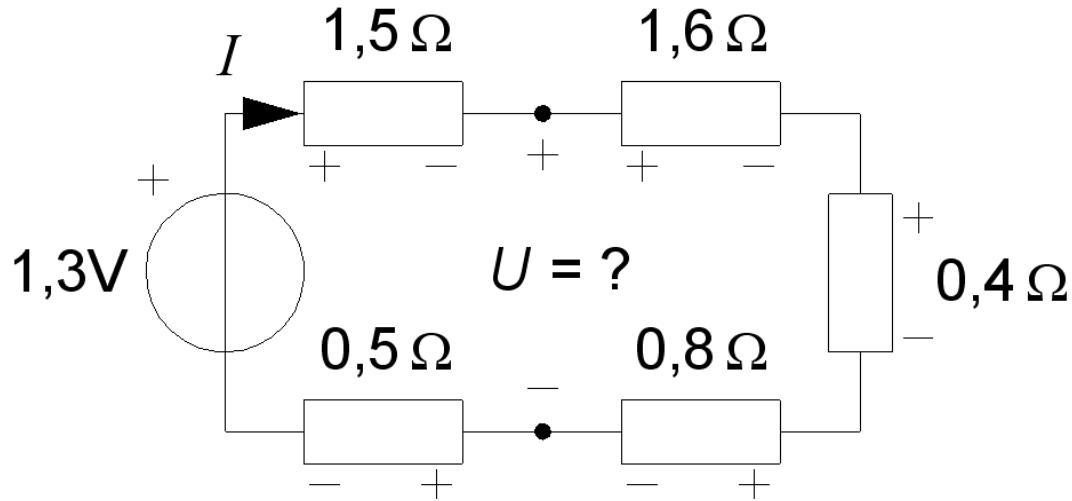


$$I = \frac{1,3}{1,5 + 1,6 + 0,4 + 0,8 + 0,5} = 0,27 \quad U_{0,5} = 0,5 \cdot 0,27 = 0,14 \\ U_{1,5} = 1,5 \cdot 0,27 = 0,41$$

$$U = -0,14 + 1,3 - 0,41 = 0,76 \text{ V}$$

$$\text{eller } U = 0,27 \cdot (0,8 + 0,4 + 1,6) = 0,76 \text{ V}$$

William Sandqvist william@kth.se

# Kirchhoffs current law (5.1)

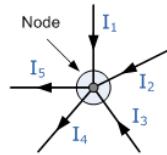


Can you guess the currents?

$$I_1 = 5 \text{ A}$$

$$I_2 = 2,5 \text{ A}$$

$$I_3 = 2,5 \text{ A}$$

$$I_4 = 5 \text{ A}$$

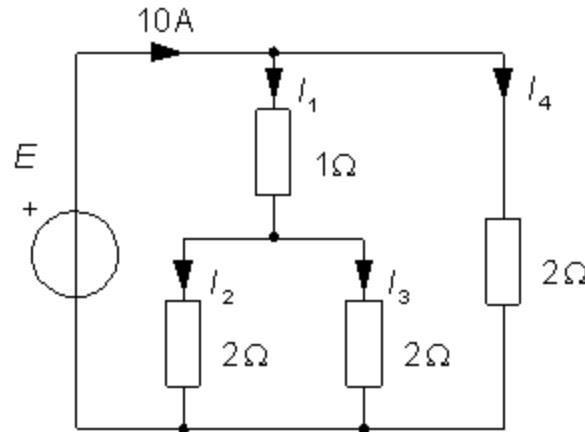

$$I_1 + I_4 = 10$$


$$I_1 = I_2 + I_3 \quad I_2 = I_3$$

Parallel circuit, OHM's law:  $I_4 \cdot 2 = I_1 \cdot (1+2//2) \Rightarrow I_4 = I_1 = 10/2 = 5$


$$I_1 = I_2 + I_3 \Rightarrow I_2 = I_3 = 5/2 = 2,5$$

William Sandqvist william@kth.se

# Kirchhoffs current law (5.2)

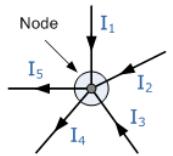

Now we must calculate

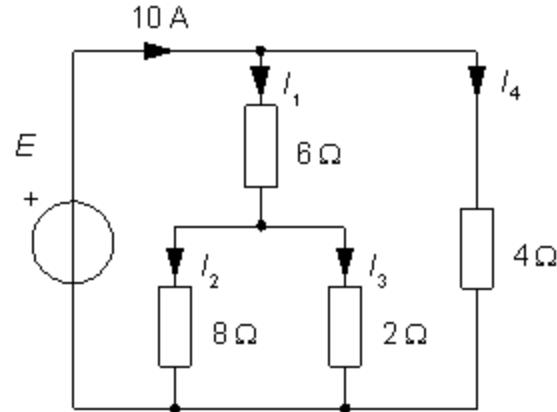


$$R_{EIS} = \frac{\left(6 + \frac{8 \cdot 2}{8+2}\right) \cdot 4}{\left(6 + \frac{8 \cdot 2}{8+2}\right) + 4} = 2,62 \Omega \quad E = R_{EIS} \cdot I = 2,62 \cdot 10 = 26,2 \text{ V}$$

$$I_4 = \frac{E}{4} = \frac{26,2}{4} = 6,55 \text{ A} \quad I_1 = I - I_4 = 10 - 6,55 = 3,45 \text{ A}$$


$$I_2 = \frac{E - 6 \cdot I_1}{8} = \frac{26,2 - 3,45 \cdot 6}{8} = \frac{5,5}{8} = 0,69 \text{ A} \quad I_3 = \frac{5,5}{2} = 2,75 \text{ A}$$

William Sandqvist william@kth.se


# Kirchhoffs laws? (6.3)

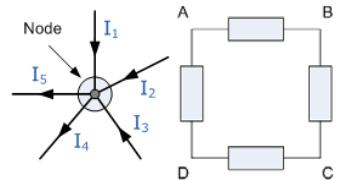

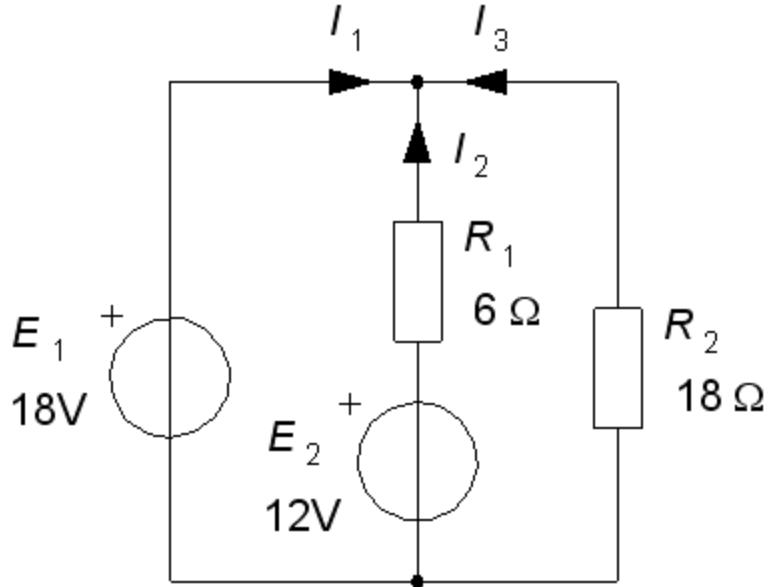- a)  $U_{R2} = ?$
- b)  $I_2 = ?$
- c)  $I_1 = ?$



# Kirchhoffs laws? (6.3)

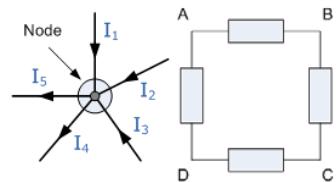


a)  $U_{R2} = ? = 18 \text{ V } (E_1)$


b)  $I_2 = ?$

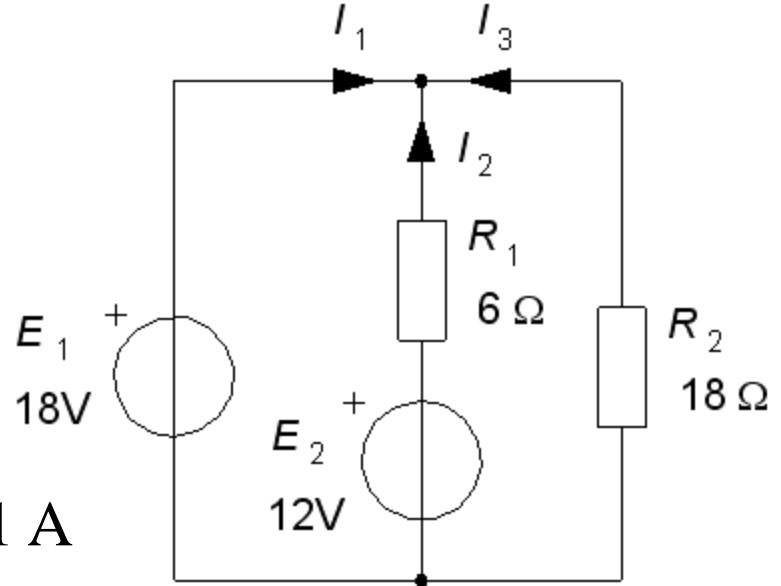c)  $I_1 = ?$

$$18 + I_3 \cdot 18 = 0 \quad I_3 = -18/18 = -1 \text{ A}$$



# Kirchhoffs laws? (6.3)

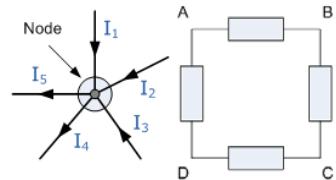


a)  $U_{R2} = ? = 18 \text{ V } (E_1)$

b)  $I_2 = ? \quad 18 + 6I_2 - 12 = 0$


$$I_2 = (12 - 18)/6 = -1 \text{ A}$$

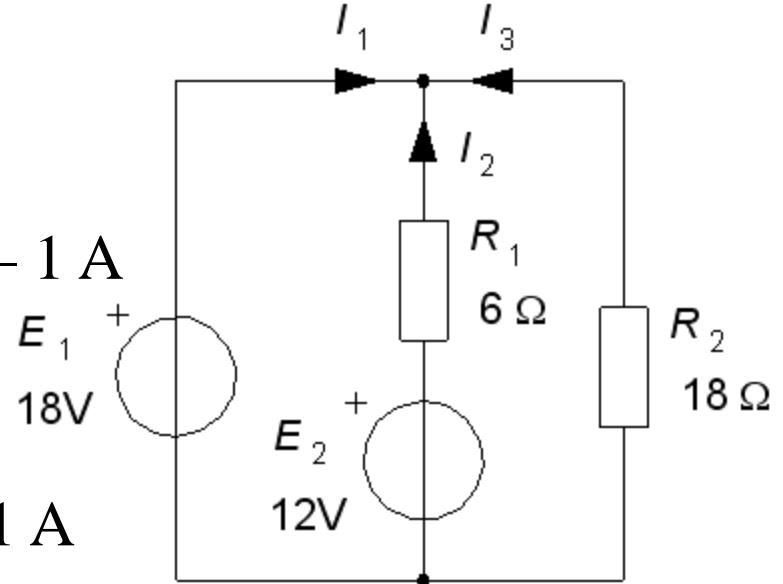c)  $I_1 = ?$

$$18 + I_3 18 = 0 \quad I_3 = -18/18 = -1 \text{ A}$$



# Kirchhoffs laws? (6.3)

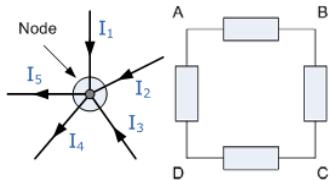

a)  $U_{R2} = ? = 18 \text{ V } (E_1)$

b)  $I_2 = ? \quad 18 + 6I_2 - 12 = 0$


$$I_2 = (12 - 18)/6 = -1 \text{ A}$$

c)  $I_1 = ?$


$$18 + I_3 18 = 0 \quad I_3 = -18/18 = -1 \text{ A}$$

$$I_1 + I_2 + I_3 = 0$$
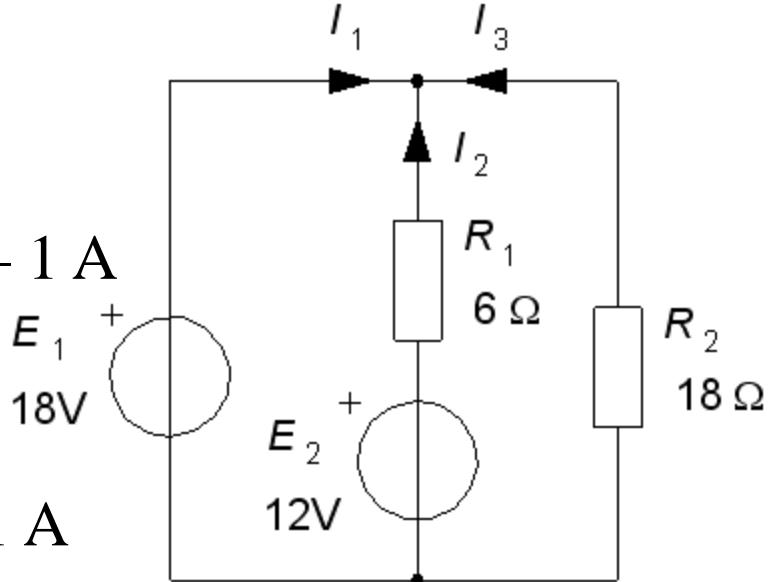
$$I_1 = -I_2 - I_3 = -(-1) - (-1) = 2 \text{ A}$$



# Kirchhoffs laws? (6.3)

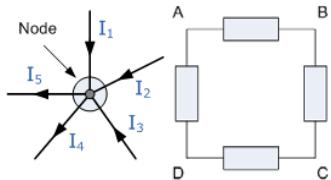

a)  $U_{R_2} = ? = 18 \text{ V } (E_1)$

b)  $I_2 = ? \quad 18 + 6I_2 - 12 = 0$


$$I_2 = (12 - 18)/6 = -1 \text{ A}$$

c)  $I_1 = ?$

$$18 + I_3 18 = 0 \quad I_3 = -18/18 = -1 \text{ A}$$

$$I_1 + I_2 + I_3 = 0$$

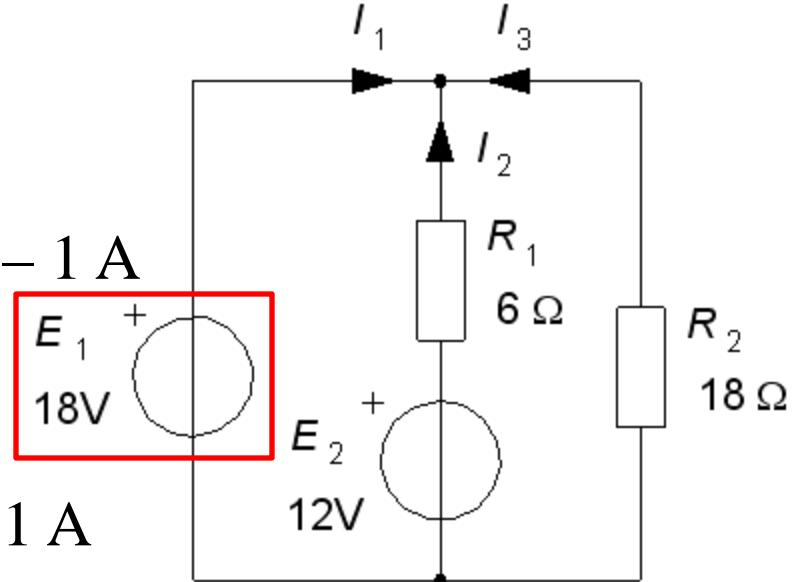
$$I_1 = -I_2 - I_3 = -(-1) - (-1) = 2 \text{ A}$$



That  $E_1$  is an ideal emf is what simplifies the calculations!

William Sandqvist william@kth.se

# Node analysis

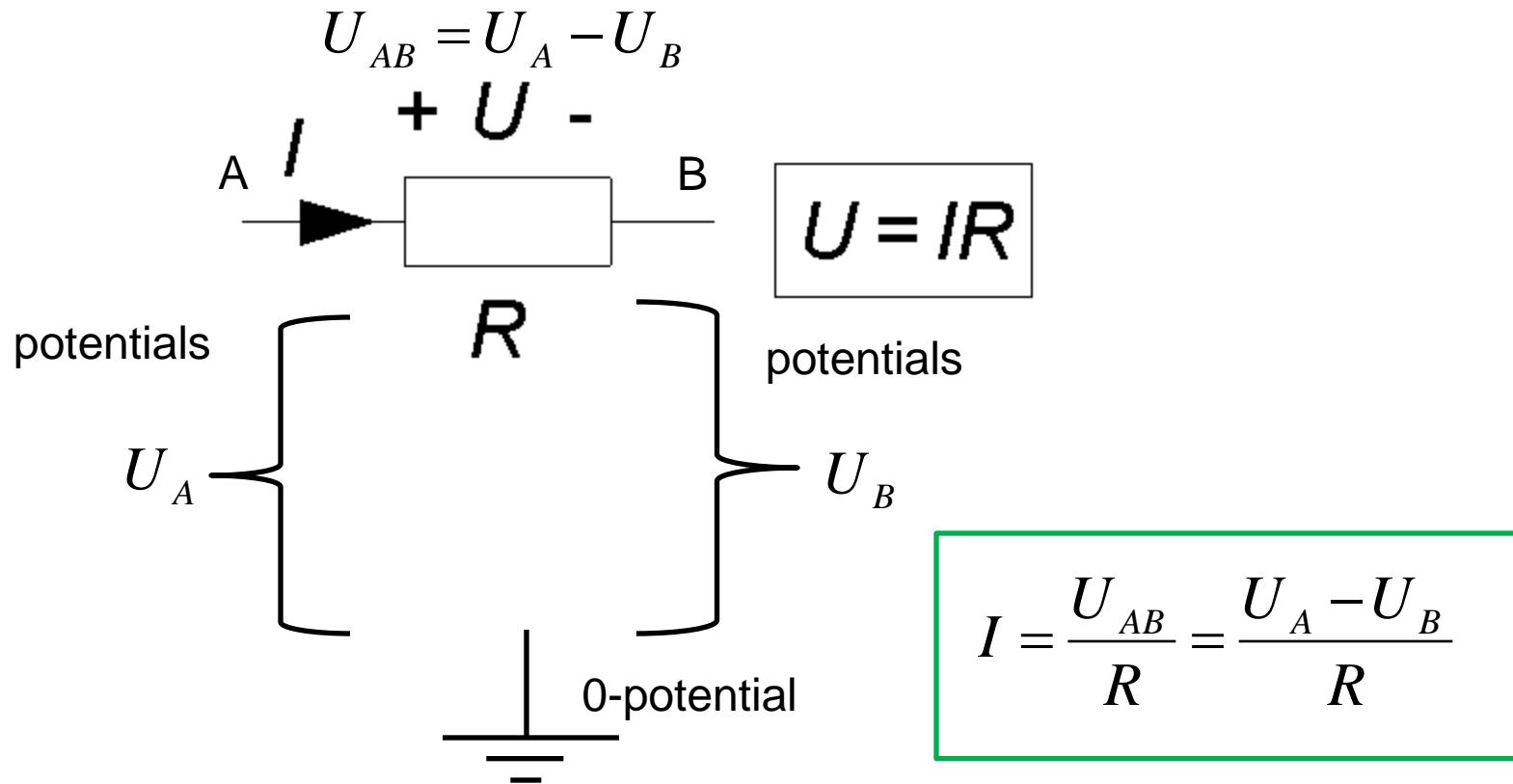

# Or with node analysis (7.3)


$$I_1 + I_2 + I_3 = 0 \quad I_1 = -I_2 - I_3$$

$$E_1 = 18 \text{ V}$$

$$\begin{aligned} I_3 &= -(E_1 - 0)/R_2 = -18/18 \\ &= -1 \text{ A} \end{aligned}$$

$$\begin{aligned} I_2 &= -(E_1 - E_2)/R_1 = -(18 - 12)/6 = \\ &= -1 \text{ A} \end{aligned}$$
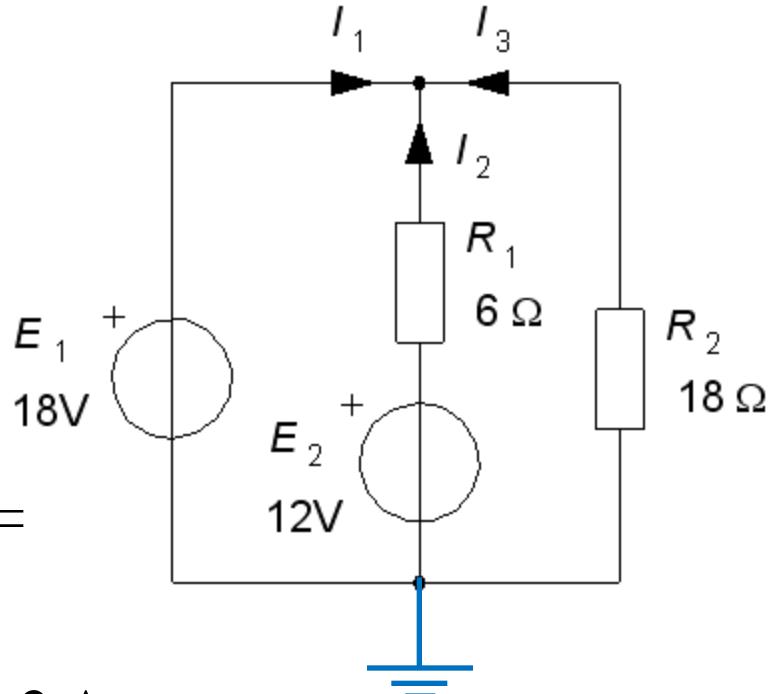
$$I_1 = -I_2 - I_3 = -(-1) - (-1) = 2 \text{ A}$$




William Sandqvist william@kth.se


# Batteries in parallel (4.4)

Three similar batteries  $E = 10 \text{ V}$  and the internal resistance  $6 \Omega$  are parallel-connected to deliver current to a resistor with resistance  $2 \Omega$ .

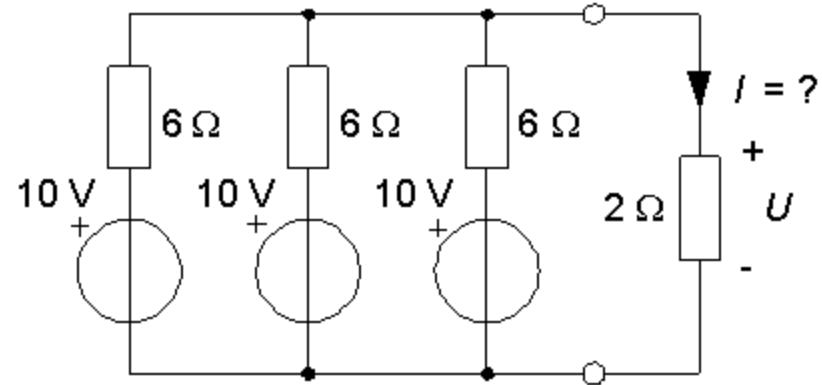
a) How much will current  $I$  and terminal voltage  $U$  be?



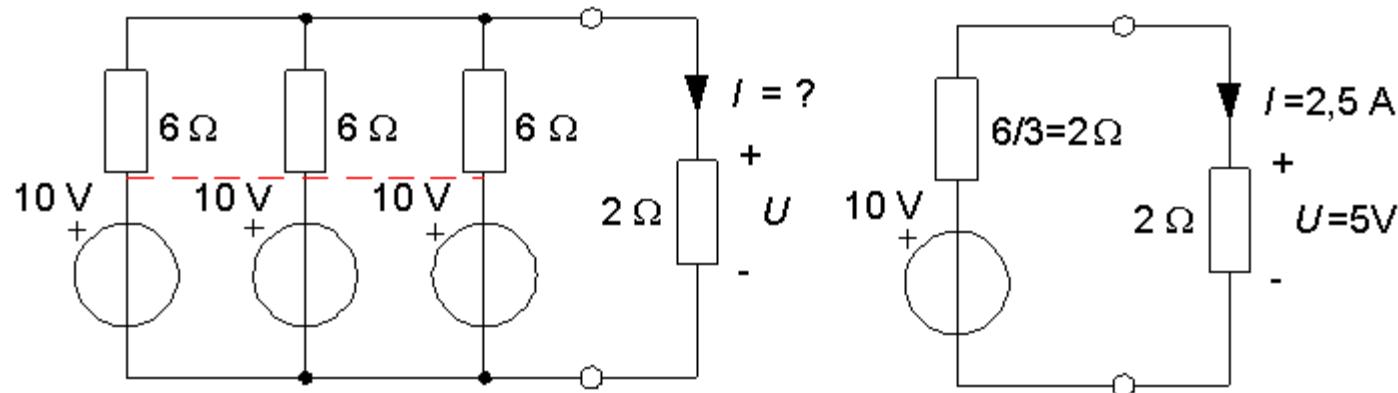
The three internal resistances  $6\Omega$  have common voltage in both ends, and is thereby effectively paralleled.  $R_I = 6/3 = 2\Omega$ .  $I = 2,5 \text{ A}$  och  $U = 5\text{V}$ .



# *One battery inserted the wrong way!*

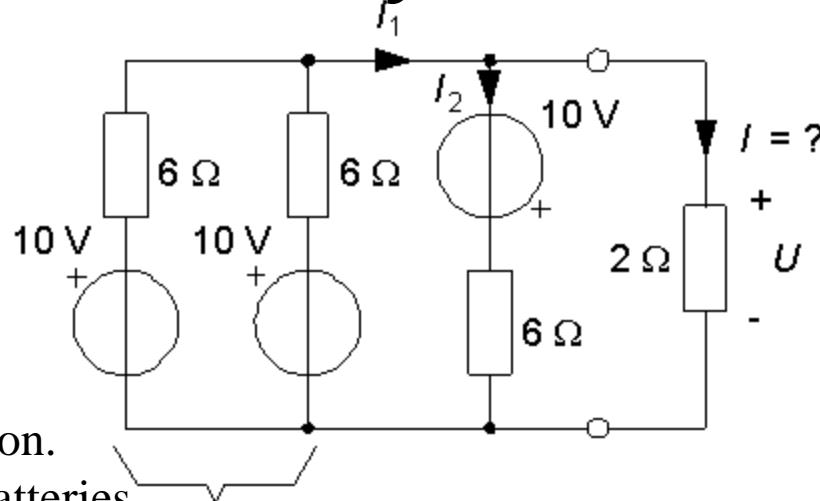


# One battery inserted the wrong way!

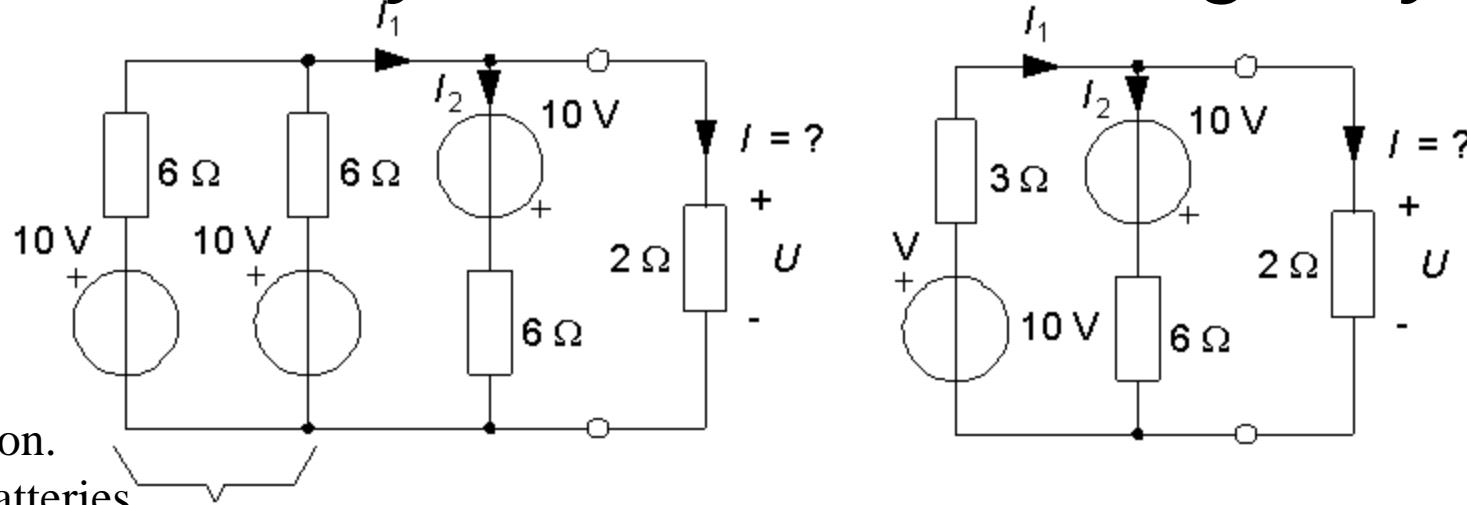

Suggestion.

Merge batteries

# *One battery inserted the wrong way!*


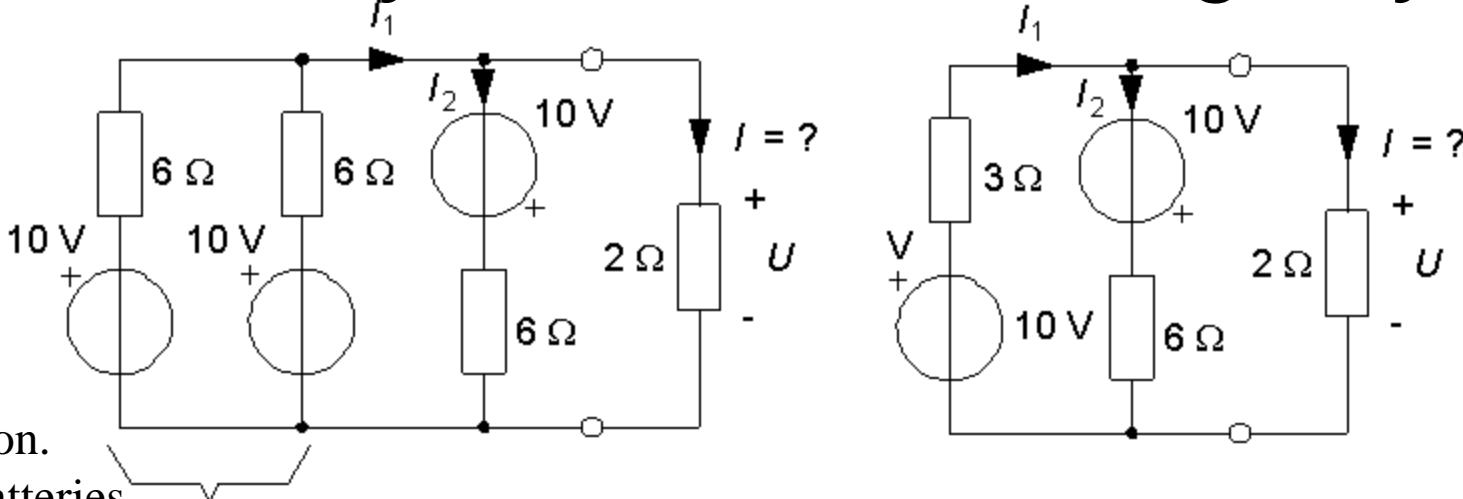


Suggestion.

Merge batteries

This is now a more complicated circuit that requires Kirchhoff's laws to be solved ...

# *One battery inserted the wrong way!*

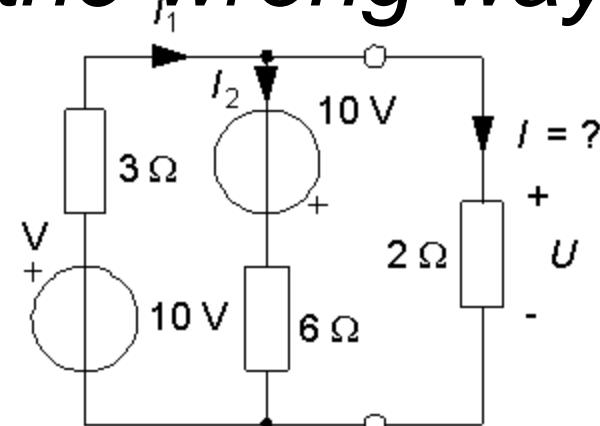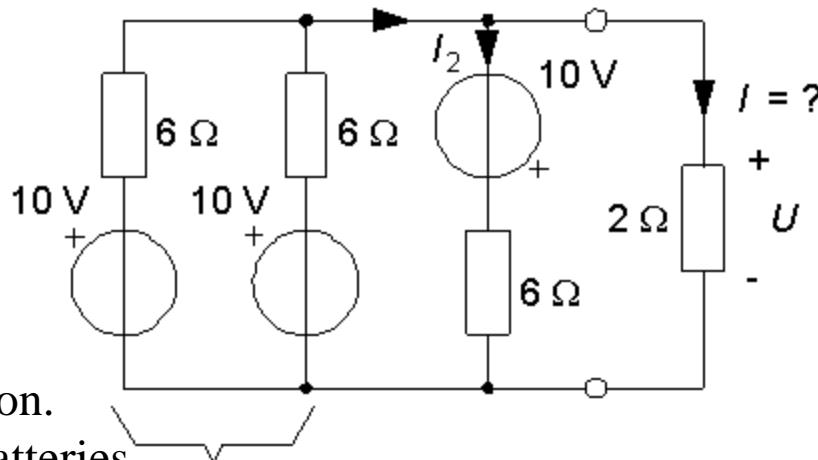



$$I_1 - I_2 - I = 0$$

$$10 - 3I_1 + 10 - 6I_2 = 0 \Leftrightarrow -3I_1 - 6I_2 + 0I = -20$$

$$6I_2 - 10 - 2I = 0 \Leftrightarrow 0I_1 + 6I_2 - 2I = 10$$

$$\begin{pmatrix} 1 & -1 & -1 \\ -3 & -6 & 0 \\ 0 & 6 & -2 \end{pmatrix} \cdot \begin{pmatrix} I_1 \\ I_2 \\ I \end{pmatrix} = \begin{pmatrix} 0 \\ -20 \\ 10 \end{pmatrix}$$

# One battery inserted the wrong way!

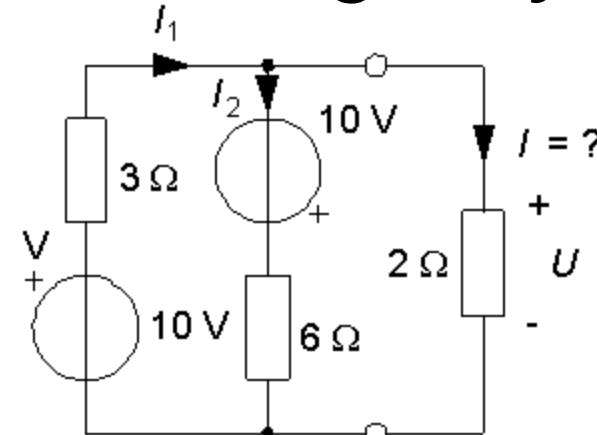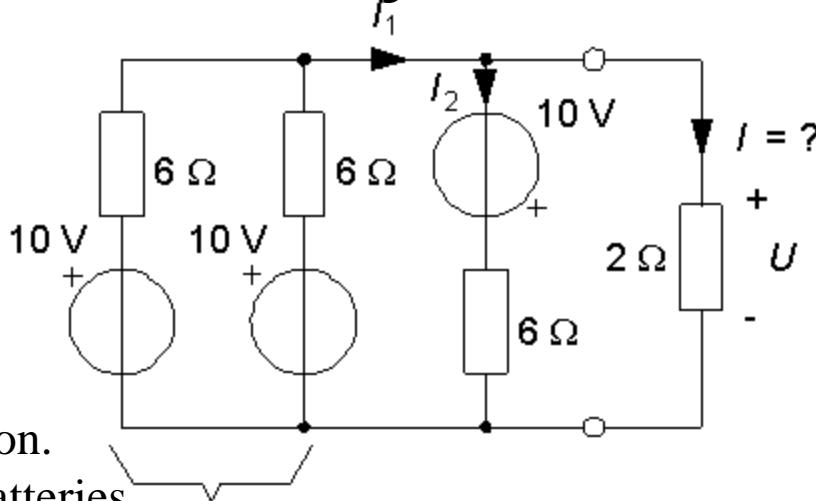

$$I_1 - I_2 - I = 0$$

$$10 - 3I_1 + 10 - 6I_2 = 0 \Leftrightarrow -3I_1 - 6I_2 + 0I = -20$$

$$6I_2 - 10 - 2I = 0 \Leftrightarrow 0I_1 + 6I_2 - 2I = 10$$

$$\begin{pmatrix} 1 & -1 & -1 \\ -3 & -6 & 0 \\ 0 & 6 & -2 \end{pmatrix} \cdot \begin{pmatrix} I_1 \\ I_2 \\ I \end{pmatrix} = \begin{pmatrix} 0 \\ -20 \\ 10 \end{pmatrix}$$

$$I_1 = 2,78 \text{ A}$$



$$I_2 = 1,94 \text{ A}$$

$$I = 0,83 \text{ A}$$

$$U = I \cdot 2 = 0,83 \cdot 2 = 1,67 \text{ V}$$



William Sandqvist william@kth.se

# Kirchhoff law's (6.5)

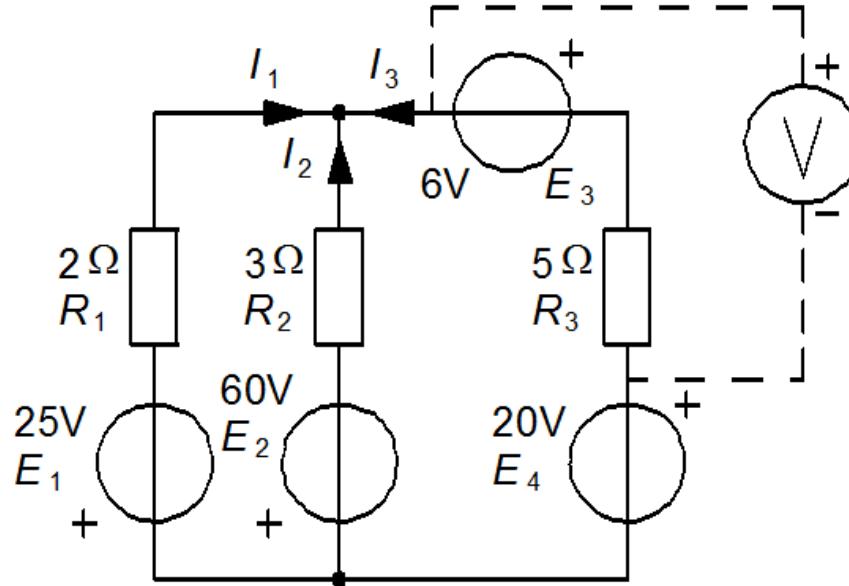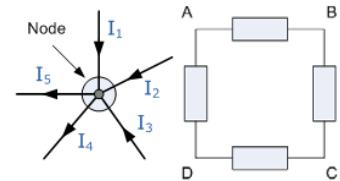


- a) Use Kirchhoff's two laws to set up an equation system by which the three currents  $I_1$ ,  $I_2$  and  $I_3$  can be calculated.  
(You need not solve the system of equations)

# Kirchhoff law's (6.5)

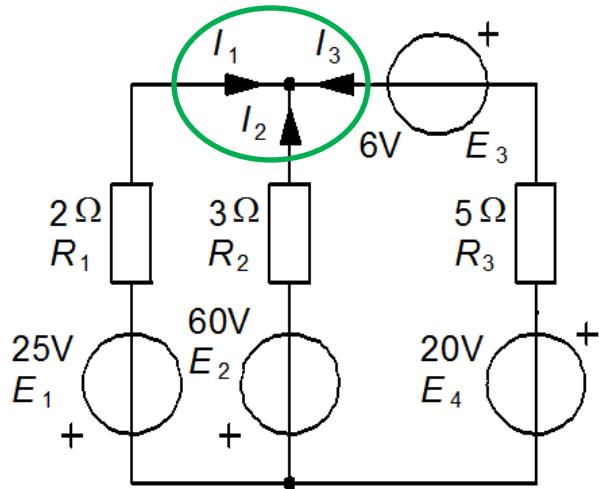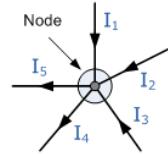


Kirchhoff current law:

$$I_1 + I_2 + I_3 = 0$$

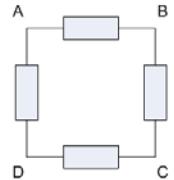

# Kirchhoff law's (6.5)

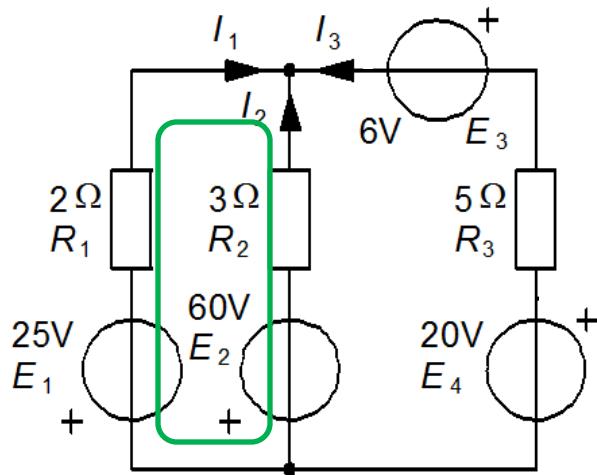



Kirchhoff current law:

$$I_1 + I_2 + I_3 = 0$$

Kirchhoff voltage law (left mesh):

$$-25 - 2 \cdot I_1 + 3 \cdot I_2 + 60 = 0$$

# Kirchhoff law's (6.5)

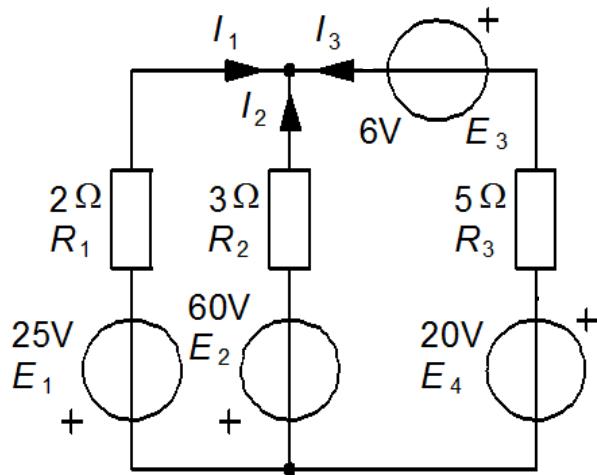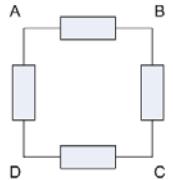

Kirchhoff current law:


$$I_1 + I_2 + I_3 = 0$$

Kirchhoff voltage law (left mesh):


$$-25 - 2 \cdot I_1 + 3 \cdot I_2 + 60 = 0$$

Trim up:
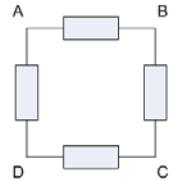
$$-2 \cdot I_1 + 3 \cdot I_2 + 0 \cdot I_3 = -35$$



# Kirchhoff law's (6.5)

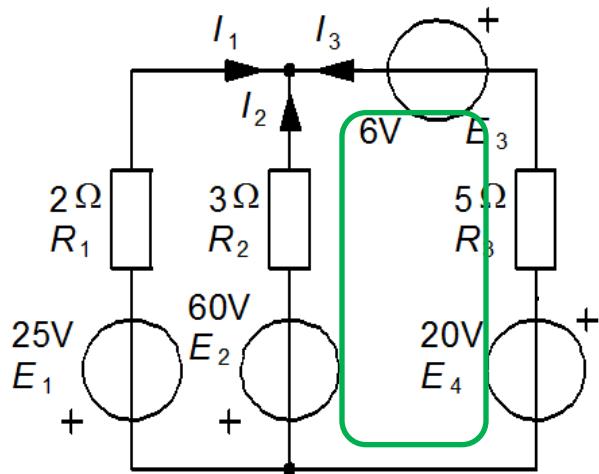

Kirchhoff current law:

$$I_1 + I_2 + I_3 = 0$$

Kirchhoff voltage law (left mesh):

$$-25 - 2 \cdot I_1 + 3 \cdot I_2 + 60 = 0$$

Trim up:

$$-2 \cdot I_1 + 3 \cdot I_2 + 0 \cdot I_3 = -35$$


Kirchhoff voltage law (right mesh):

$$-60 - 3 \cdot I_2 + 6 + 5 \cdot I_3 - 20 = 0$$

Trim up:

$$0 \cdot I_1 - 3 \cdot I_2 + 5 \cdot I_3 = 74$$

# Kirchhoff law's (6.5)

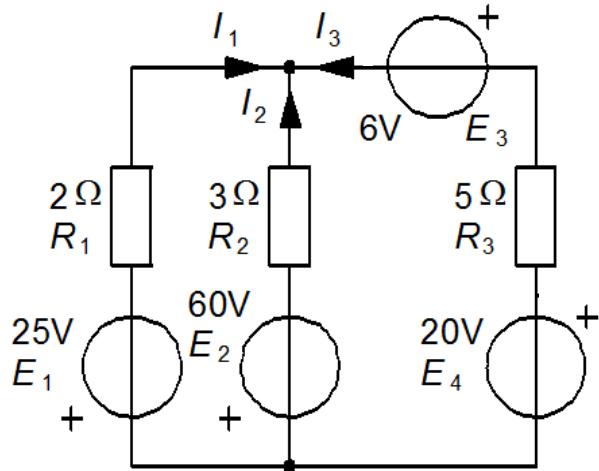

$$I_1 + I_2 + I_3 = 0$$

$$-2 \cdot I_1 + 3 \cdot I_2 + 0 \cdot I_3 = -35$$

$$0 \cdot I_1 - 3 \cdot I_2 + 5 \cdot I_3 = 74$$


$$R \cdot I = U$$

$$\begin{pmatrix} 1 & 1 & 1 \\ -2 & 3 & 0 \\ 0 & -3 & 5 \end{pmatrix} \bullet \begin{pmatrix} I_1 \\ I_2 \\ I_3 \end{pmatrix} = \begin{pmatrix} 0 \\ -35 \\ 74 \end{pmatrix}$$



$$\begin{pmatrix} I_1 \\ I_2 \\ I_3 \end{pmatrix} = \begin{pmatrix} 1,87 \\ -10,4 \\ 8,55 \end{pmatrix}$$

# Kirchhoff law's (6.5)


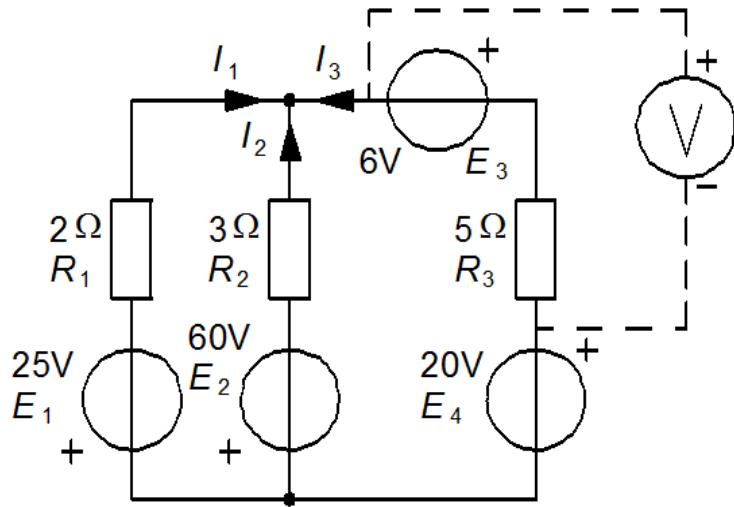



If equationsystem is solved one gets:

$$I_1 = 1,87 \quad I_2 = -10,4 \quad I_3 = 8,55 \text{ [A].}$$


- b) What does the voltmeter at the right in the figure show (give both amount and sign) [V]?

# Kirchhoff law's (6.5)

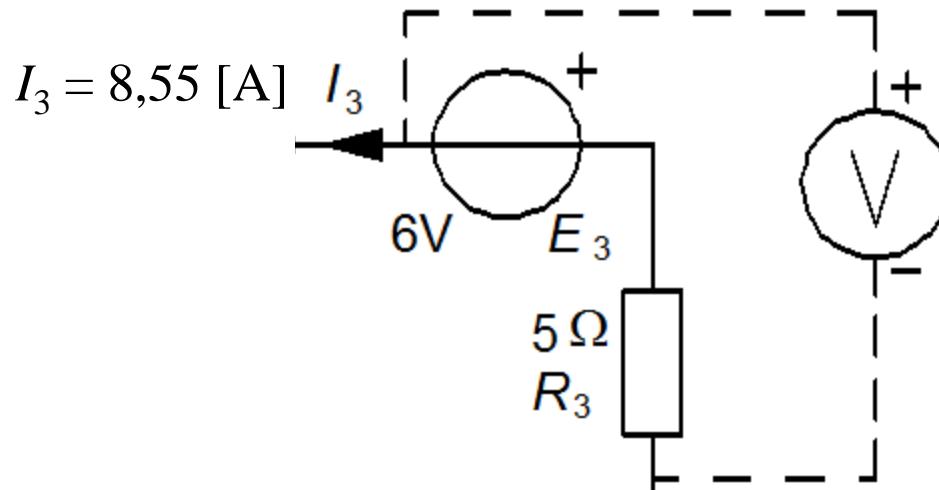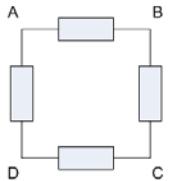

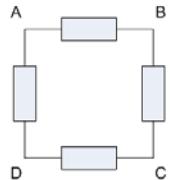

# Kirchhoff law's (6.5)

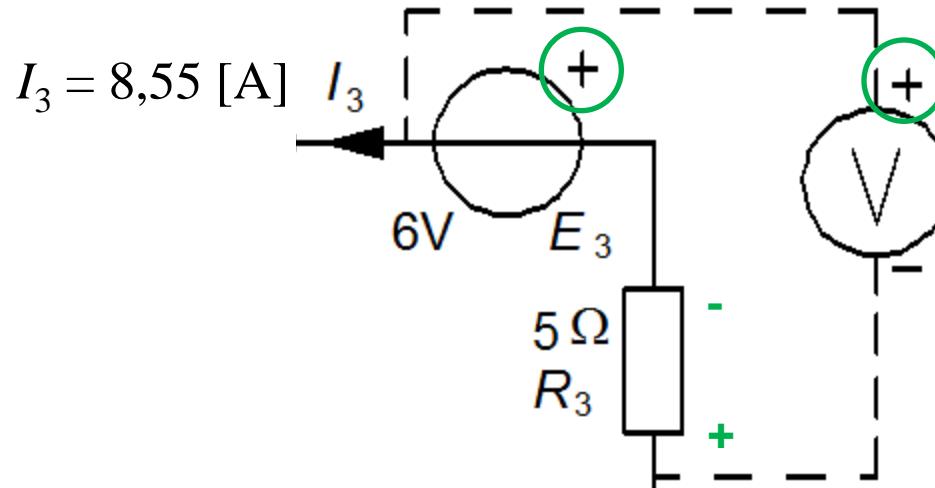

Voltmeter ( $U$ ) shows

$$U + E_3 + R_3 \cdot I_3 = 0 \Rightarrow U = -6 - 5 \cdot 8,55 = -48,75 \text{ V}$$

William Sandqvist william@kth.se