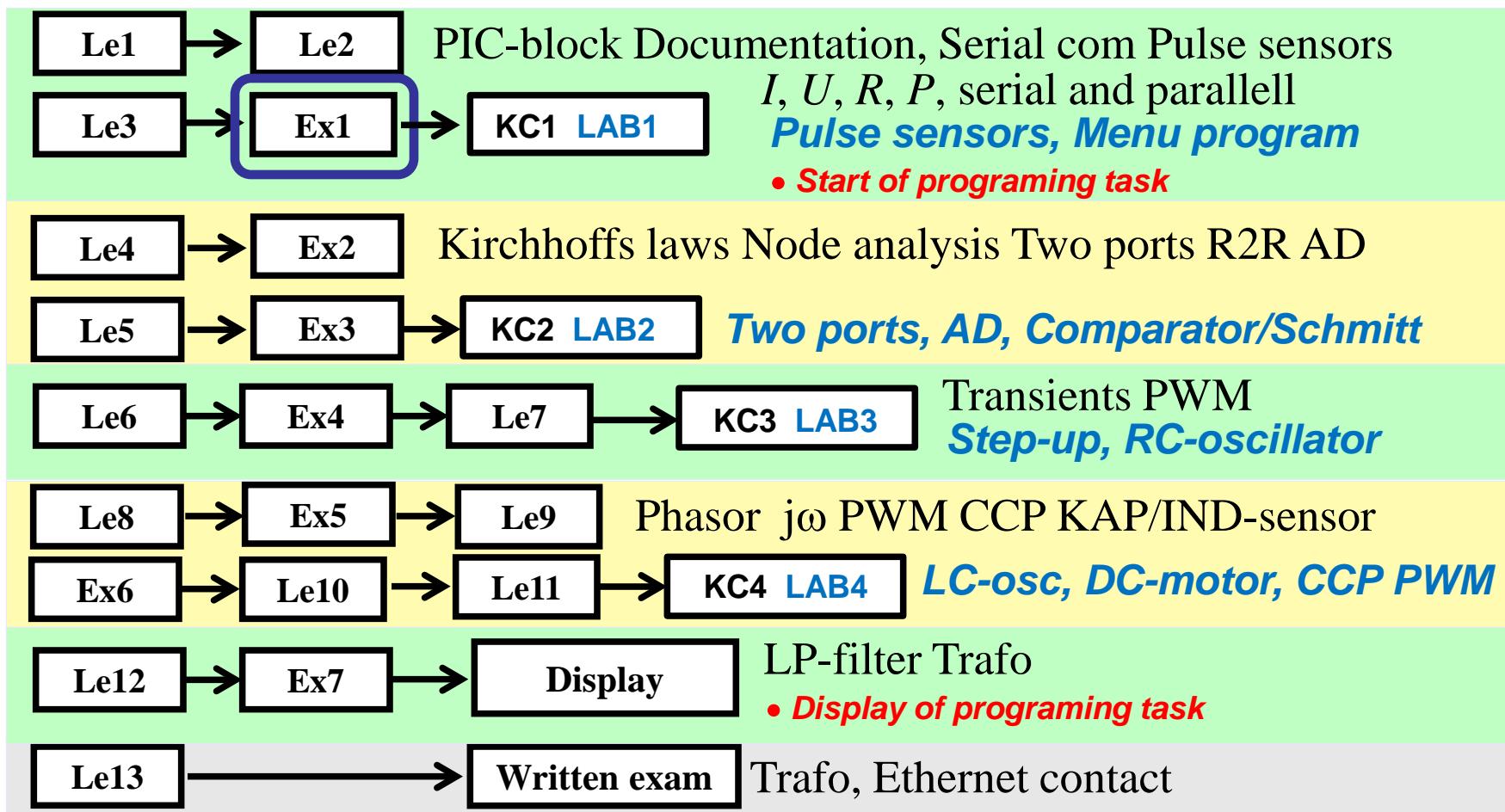


IE1206 Embedded Electronics




Closed circuit?

- *discussion.*

Current can only flow through a circuit on condition there is a closed circuit.


Describe in words the action of circuits a) ...
d) when you operate the two switches.

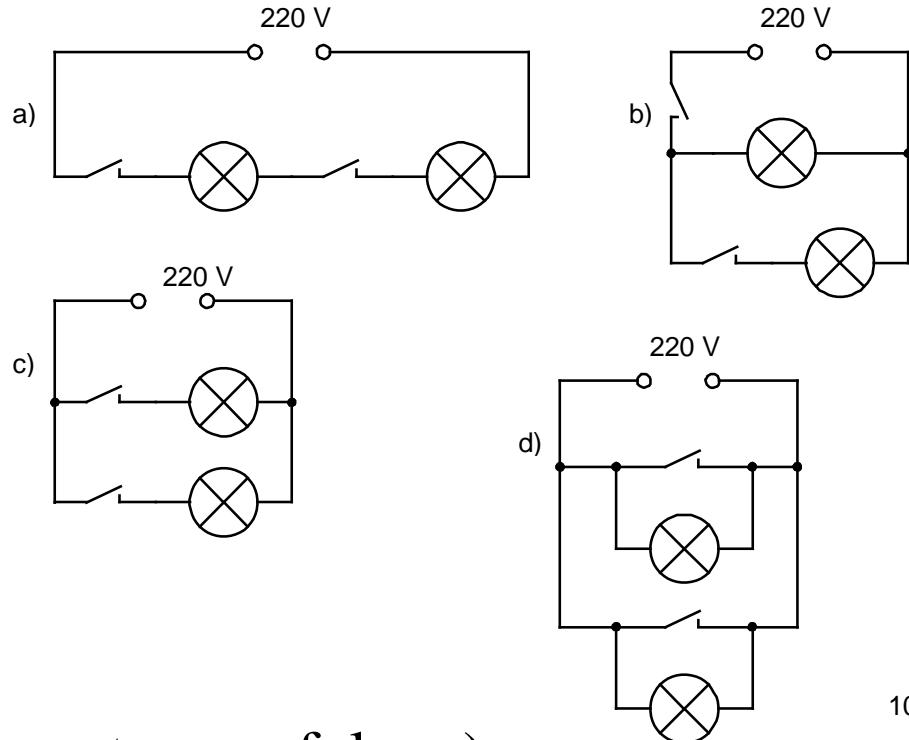(All the circuits are perhaps not as useful ...)




William Sandqvist william@kth.se

Series resistors

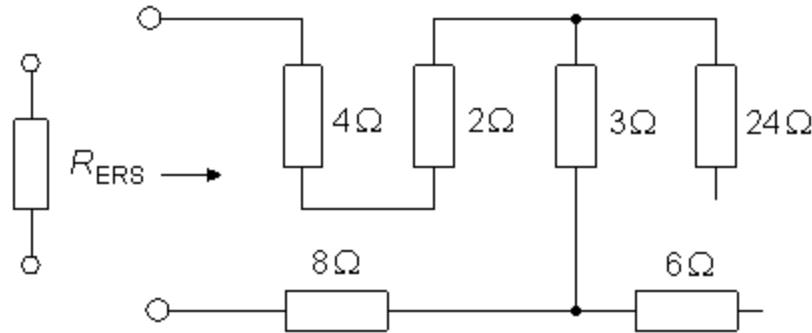


Series resistors

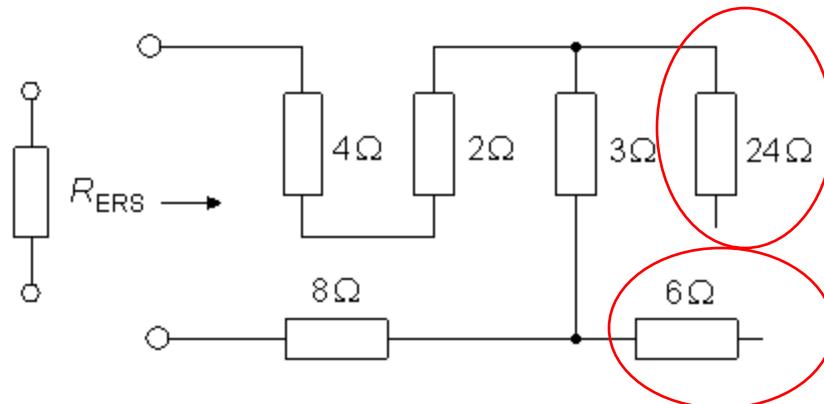

no current =
not included
in circuit!

Series resistors

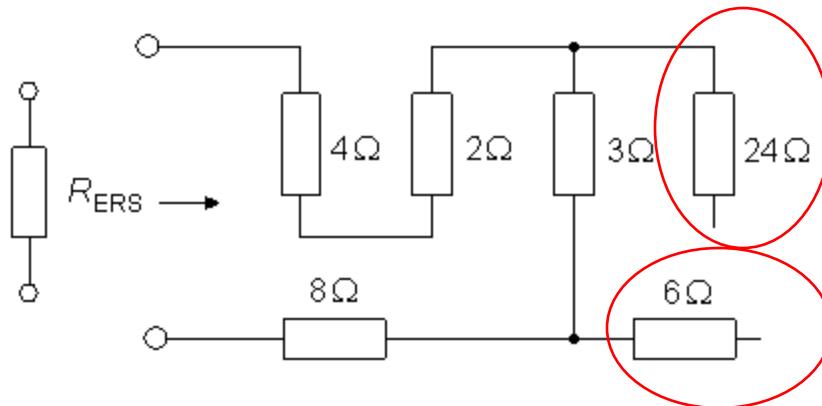


no current =
not included
in circuit!

$$R_{E\!R\!S} = 4 + 2 + 3 + 8 = 17$$

William Sandqvist william@kth.se

Two resistors in Parallel

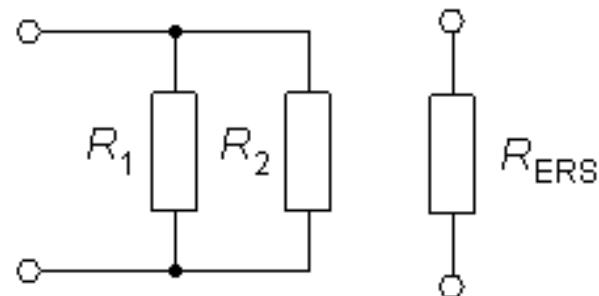

$$\frac{1}{R_{\text{ERS}}} = \frac{1}{R_1} + \frac{1}{R_2} = \frac{R_2}{R_2} \cdot \frac{1}{R_1} + \frac{R_1}{R_1} \cdot \frac{1}{R_2} = \frac{R_1 + R_2}{R_1 \cdot R_2}$$

$$R_{\text{ERS}} = \frac{R_1 \cdot R_2}{R_1 + R_2}$$


Equivalent resistance (1.2)

$$R_1 = 1 \Omega$$

$$R_2 = 21 \Omega$$

$$R_3 = 42 \Omega$$

$$R_4 = 30 \Omega$$

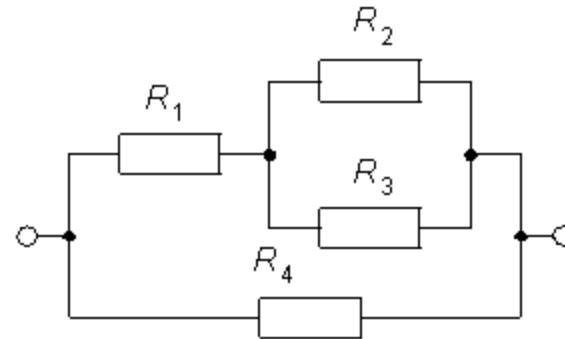


$$R_{E\!R\!S} = 30//(1+21//42)$$

$$21//42 = \frac{21 \cdot 42}{21 + 42} = 14 \Rightarrow (1 + 21//42) = 15$$

$$30//15 = \frac{30 \cdot 15}{30 + 15} = 10 \Rightarrow R_{E\!R\!S} = 10 \Omega$$

William Sandqvist william@kth.se

N same value in parallel

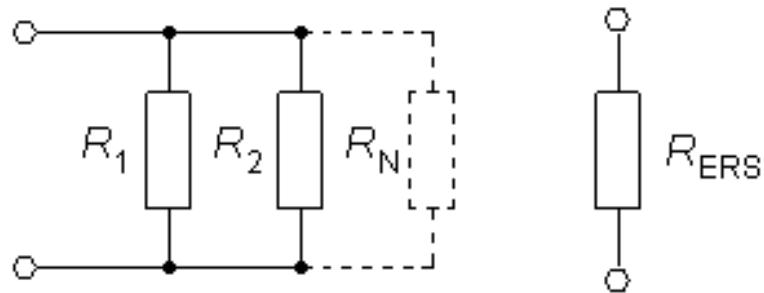


$$R_1 = R_2 = \dots = R_N = R$$


$$\frac{1}{R_{ERS}} = \frac{1}{R} + \frac{1}{R} + \dots = \frac{N}{R}$$

$$R_{ERS}(N) = \frac{R}{N}$$

OK to move ...

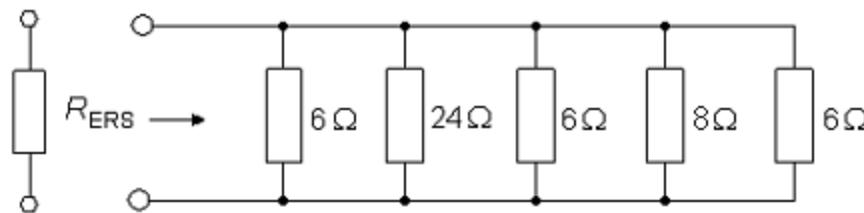

Redrawn:

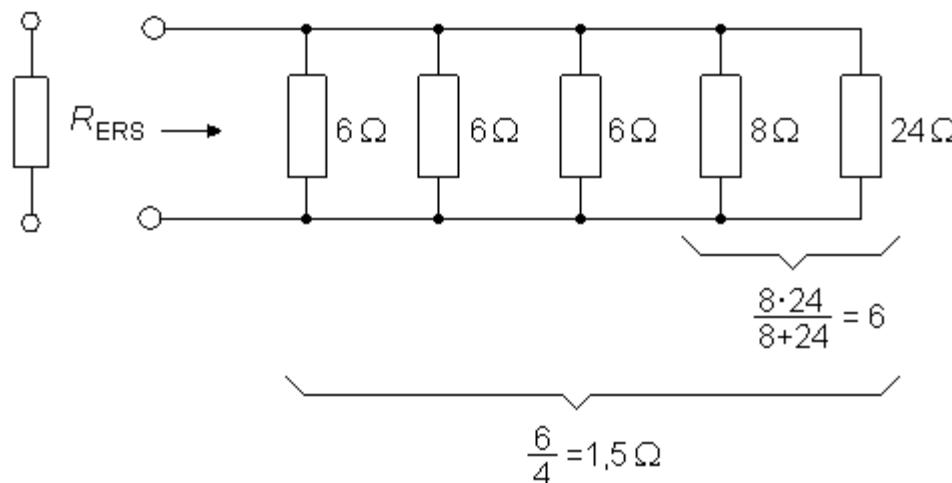

William Sandqvist william@kth.se

Equivalent resistance (1.6)


$$R_{\text{TOT}} = 2 + (12//12)/(24//24)$$

// means parallel connection


$$12//12 = 6 \quad 24//24 = 12$$

$$(12//12)/(24//24) = \frac{6 \cdot 12}{6 + 12} = 4$$

$$R_{\text{TOT}} = 2 + 4 = 6 \Omega$$

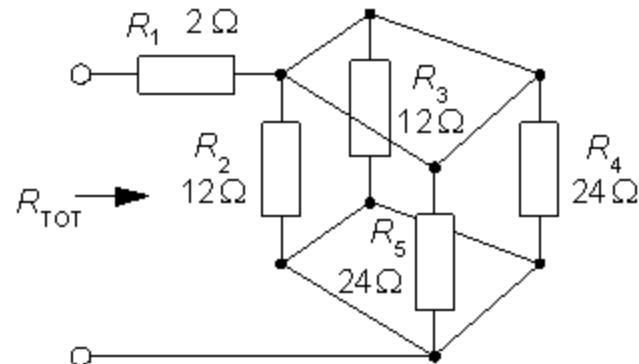


Equivalent resistance (1.1)

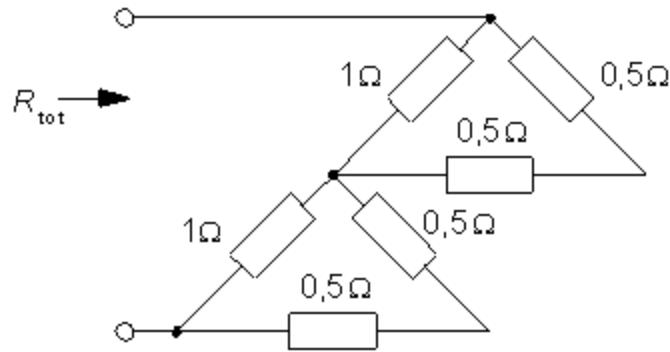

$$R_{\text{TOT}} = 1//(0,5+0,5) + 1//(0,5+0,5) = 1//1 + 1//1 = 0,5 + 0,5 = 1$$

William Sandqvist william@kth.se

Equivalent resistance (1.8)

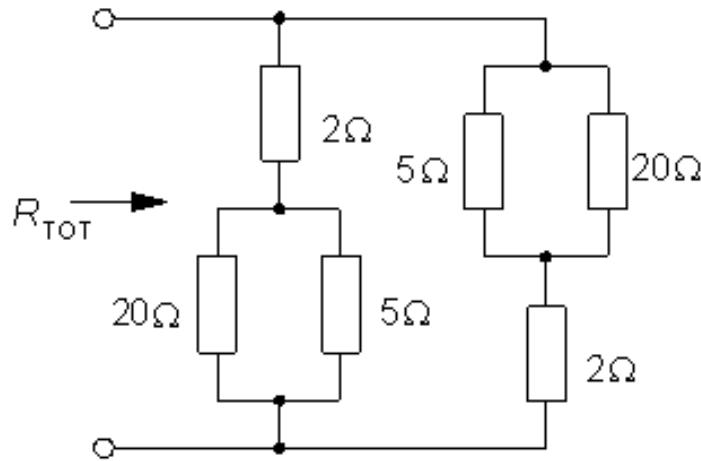



$$R_{TOT} = (2 + 20//5) // (20//5 + 2)$$

$$(2 + 20//5) = 2 + \frac{20 \cdot 5}{20 + 5} = 2 + 4 = 6 \quad 6//6 = 3$$

$$R_{TOT} = 3 \Omega$$


William Sandqvist william@kth.se

Potentiometer


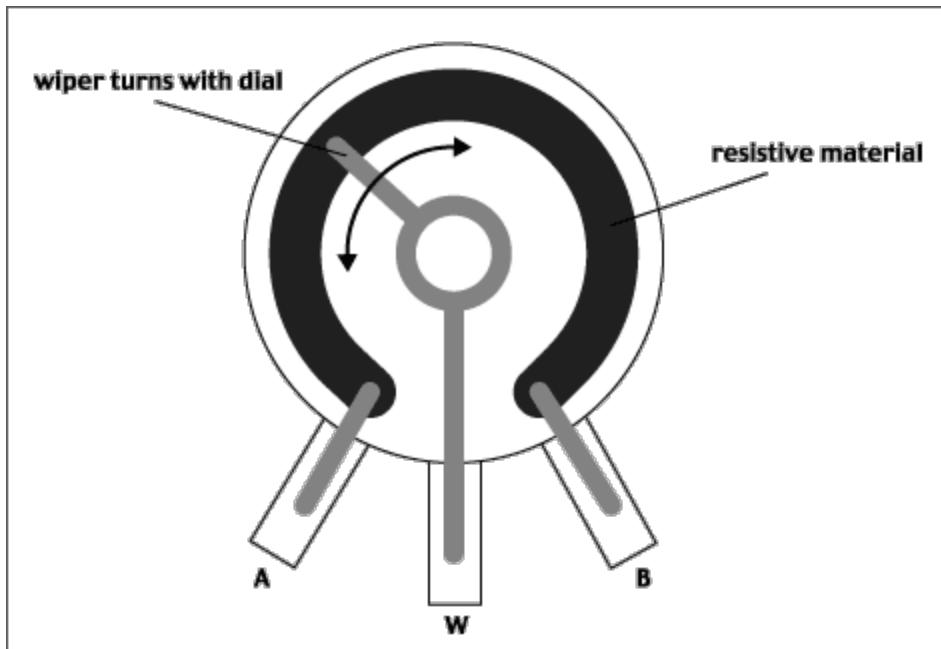
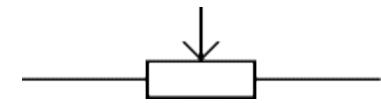


Appearance at our labs.

Equivalent resistance (1.10)

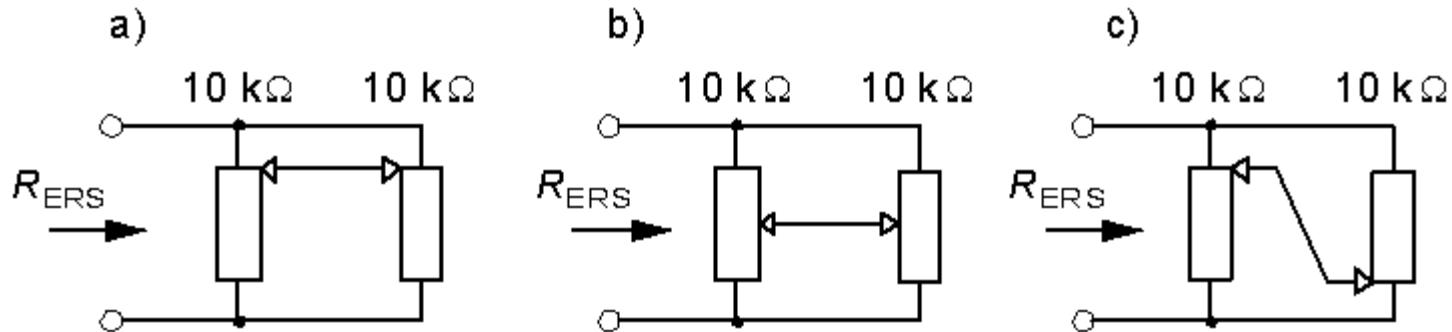




Equivalent resistance (1.10)

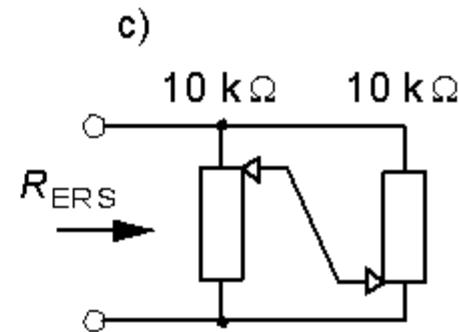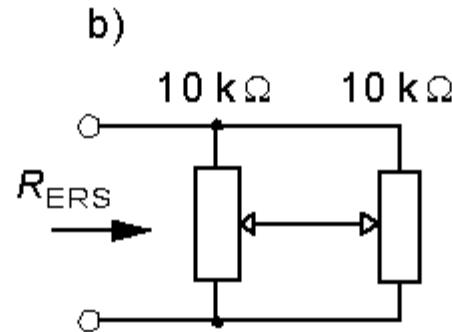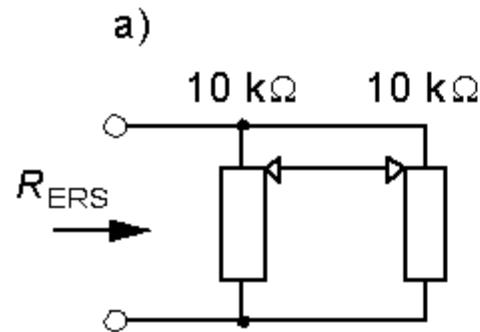

$$\text{a)} R_{\text{ERS}} = 10/2 = 5 \text{ k}\Omega$$



Equivalent resistance (1.10)

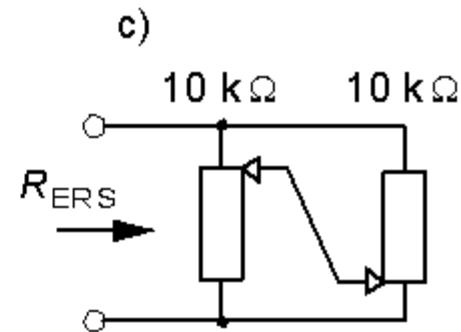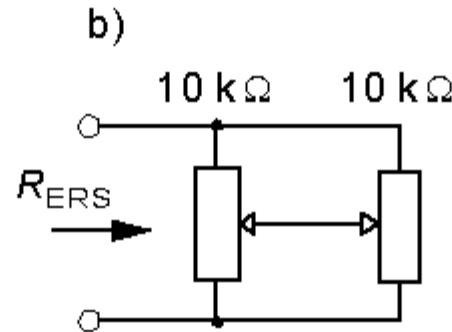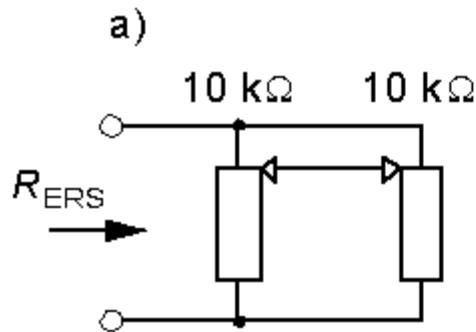


$$\mathbf{a)} R_{E\!R\!S} = 10/2 = 5\text{ k}\Omega$$




$$\mathbf{b)} R_{E\!R\!S} = 5/2 + 5/2 = 5\text{ k}\Omega$$

Equivalent resistance (1.10)


a)

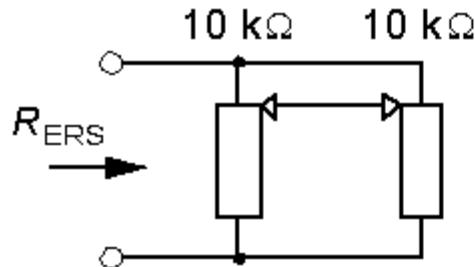

b)

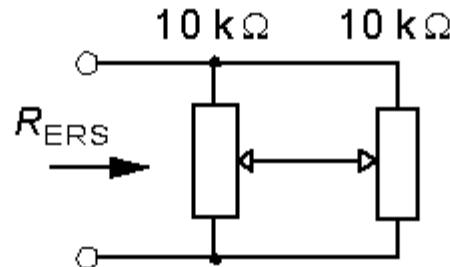

c)

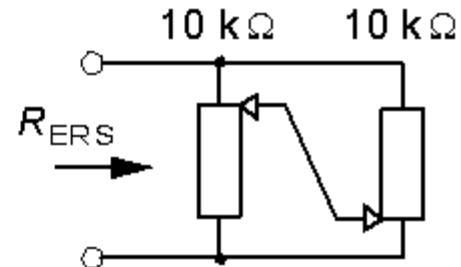

$$\mathbf{a)} R_{E\!R\!S} = 10/2 = 5\text{ k}\Omega$$


$$\mathbf{b)} R_{E\!R\!S} = 5/2 + 5/2 = 5\text{ k}\Omega$$

$$\mathbf{c)} R_{E\!R\!S} = 0\text{ }\Omega !$$





William Sandqvist william@kth.se

Voltage divider

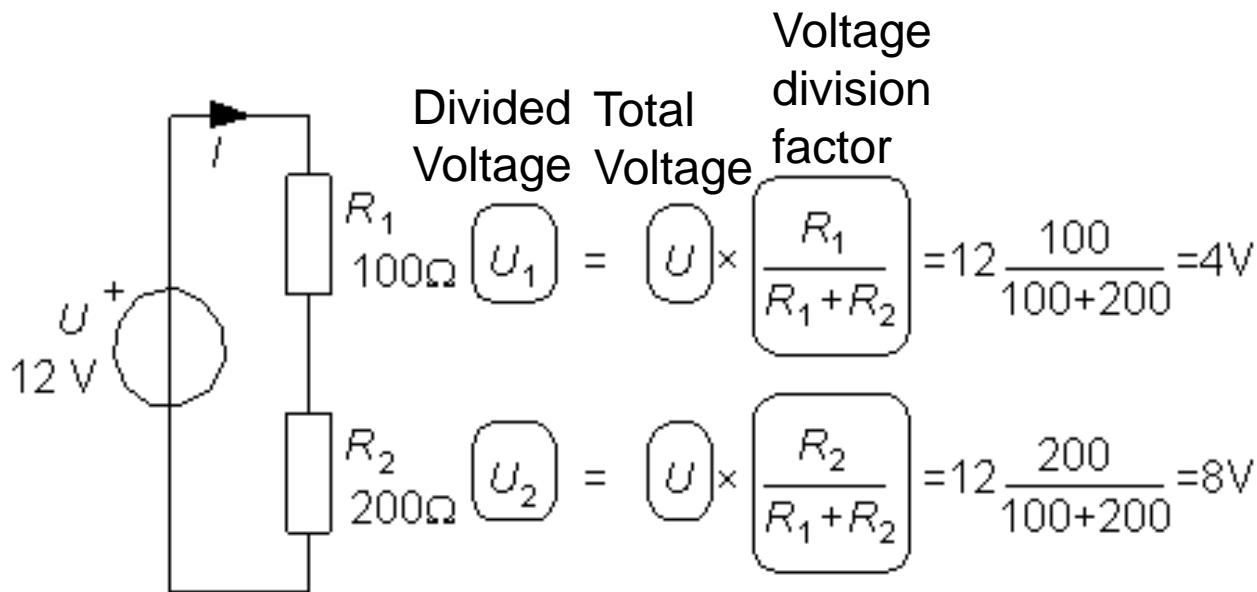

According to the voltage divider formula you get a divided voltage, for example U_1 across the resistor R_1 , by multiplying the total voltage U with a voltage division factor. This voltage division factor is the resistance R_1 divided by the sum of all the resistors that are in the series connection.

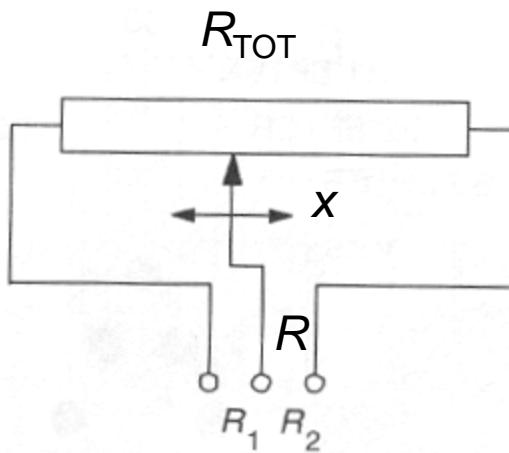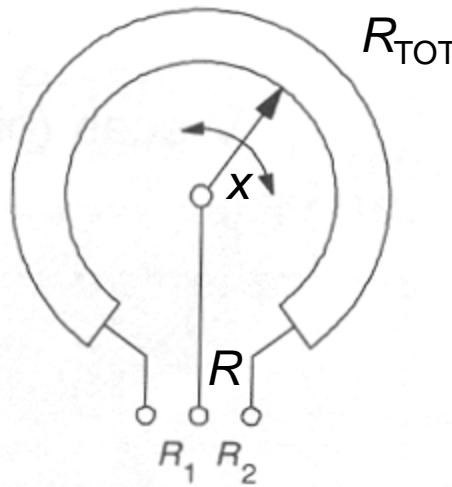Resistive sensors, rotate and slide resistances





$$R = R_{TOT} \cdot x$$

x relative movement/rotation $0 < x < 1$





Potentiometer with load (1.11)

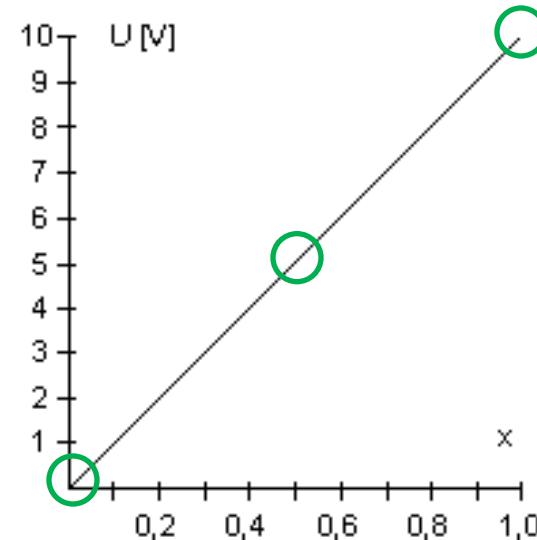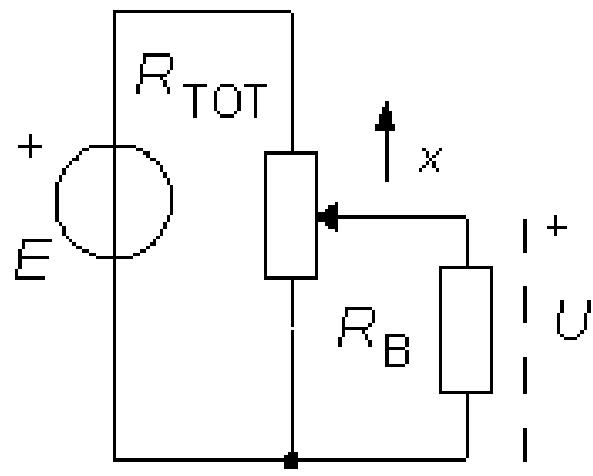

Without R_B

$$U = E \cdot x \quad \{0 \dots x \dots 1\}$$

Potentiometer with load (1.11)

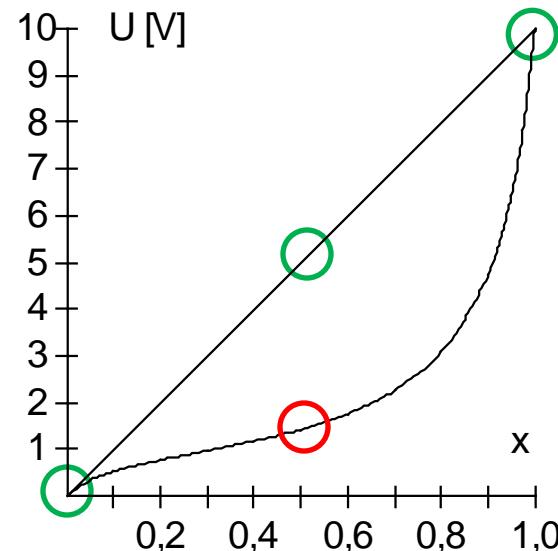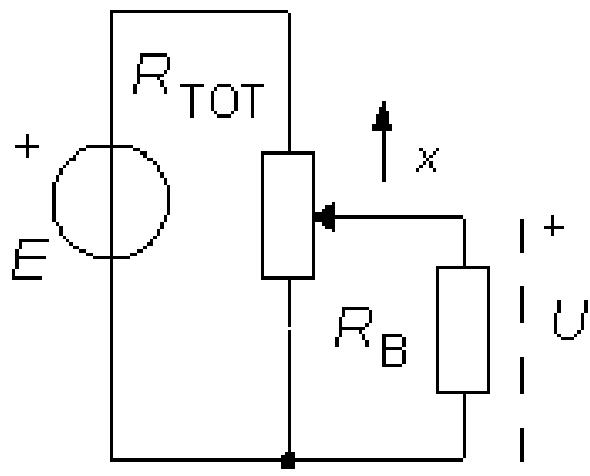


At $x = 0$ and $x = 1$ then $U = 0$ and $U = 10\text{V}$.

At $x = 0,5$ the load R_B draws current from the voltage divider and this "reduce" U .

Potentiometer with load ?

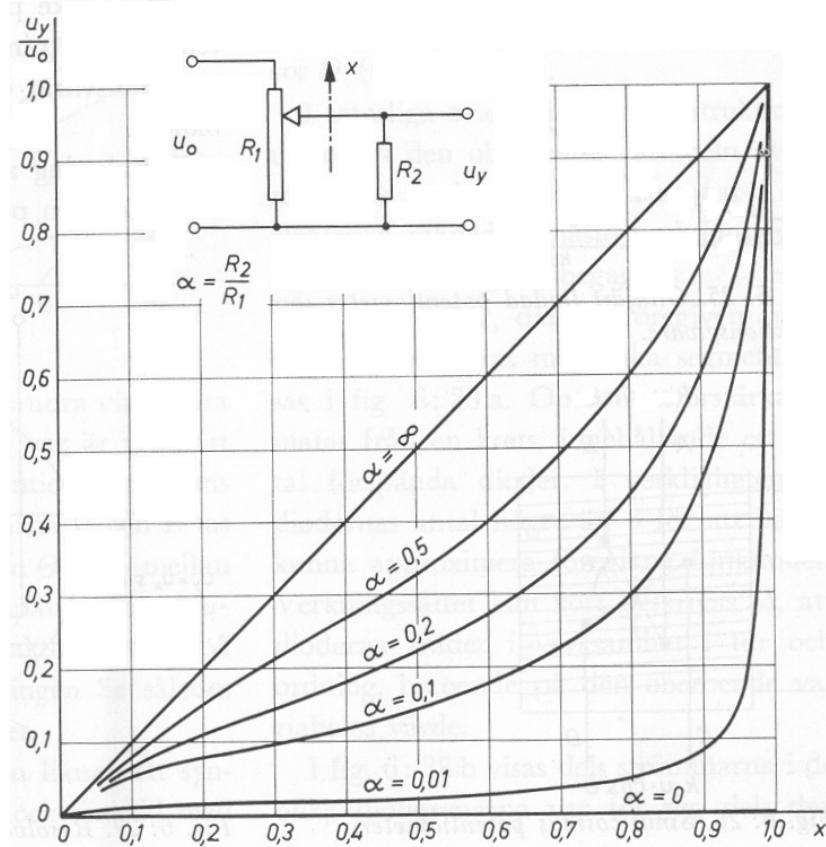
Would you happen to wish for any of the non-linear relationship that exists in the figure, it costs apparently just an extra resistor R_2 !



William Sandqvist william@kth.se


Seriell circuit (3.1)

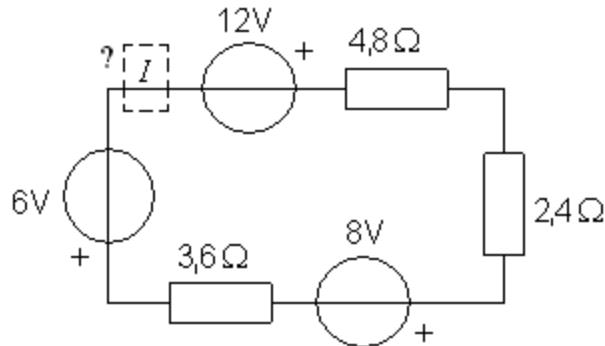Determine the current I , its magnitude and direction.



$$8 + 6 - 12 = 2 \quad 3,6 + 2,4 + 4,8 = 10,8$$

$$I = \frac{2}{10,8} = 0,19 \text{ A}$$

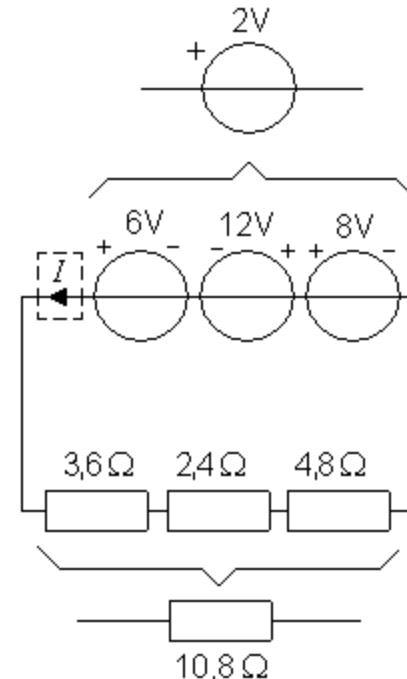

William Sandqvist william@kth.se

Serial – parallel circuits (3.4)

Calculate current $I = ?$ And voltage $U = ?$ for the serial-parallel circuit in the figure.

Calculate the equivalent resistance: 10 V


$$R_{\text{ERS}} = 2//(4//4) = 2//2 = 1\Omega$$

Calculate voltage over the equivalent resistor U_{RERS}

$$U_{\text{RERS}} = 10 \frac{1}{4+1} = 2$$

$$\text{Current } I = U_{\text{RERS}}/4 = 2/4 = 0,5 \text{ A}$$
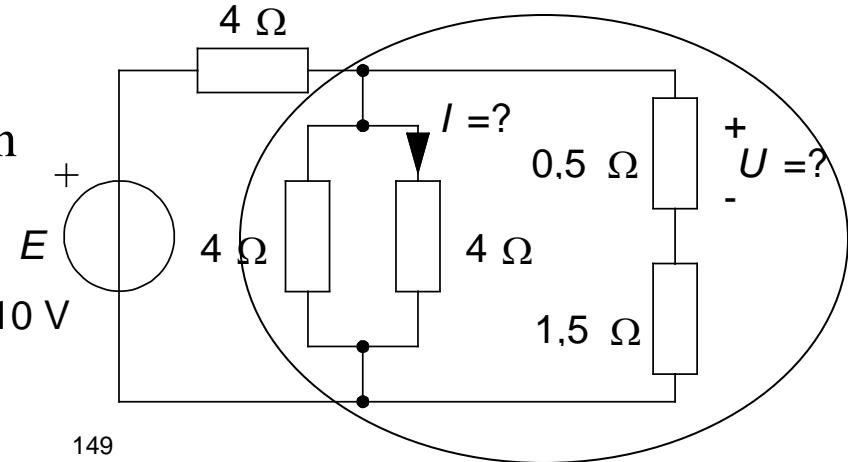
$$\text{Voltage } U = 2 \frac{0,5}{1,5 + 0,5} = 0,5 \text{ V}$$




149

William Sandqvist william@kth.se

Serial – parallel circuits (3.3)

Calculate current $I = ?$ And voltage $U = ?$ for the serial-parallel circuit in the figure.

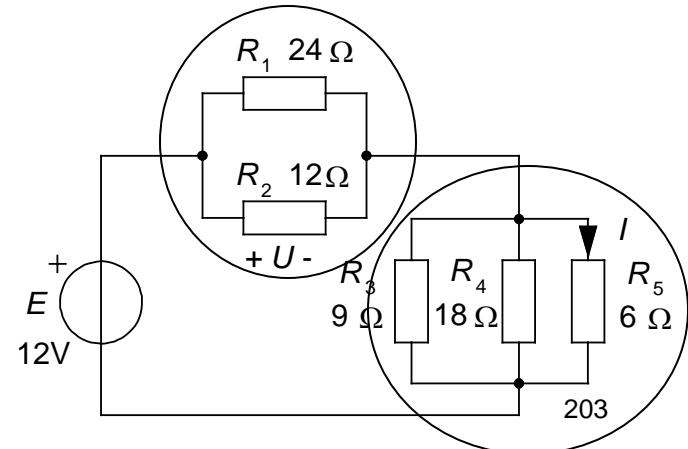We start by calculating two equivalent resistances:



$$R_{1//2} = \frac{24 \cdot 12}{24 + 12} = 8 \quad \frac{1}{R_{3//4//5}} = \frac{1}{9} + \frac{1}{18} + \frac{1}{6} = \frac{2+1+3}{18} = \frac{6}{18} \Rightarrow R_{3//4//5} = \frac{18}{6} = 3$$

Voltage divider:

$$U = 12 \frac{8}{8+3} = 8,73 \Rightarrow U_{3//4//5} = E - U \Rightarrow I = \frac{U_{3//4//5}}{R_5} = \frac{12 - 8,73}{6} = 0,55 \text{ A}$$


William Sandqvist william@kth.se

Serial – parallel circuits (3.5)

Calculate current $I = ?$ And voltage $U = ?$ for the serial-parallel circuit in the figure.

We calculates a equivalent resistance:
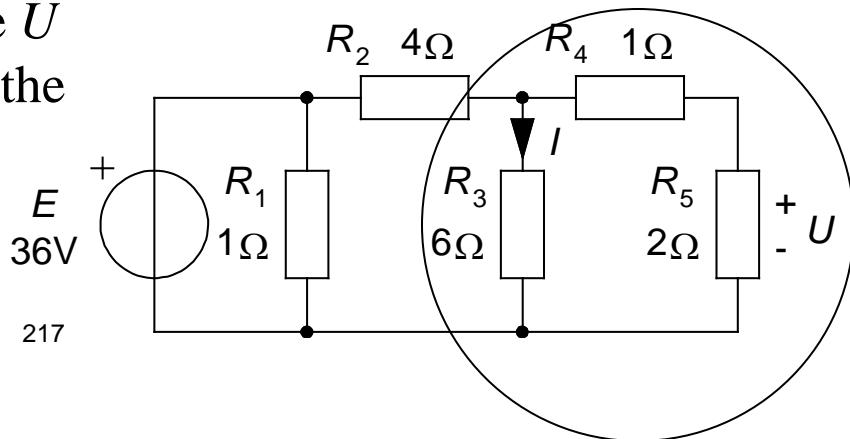
$$R_{3//4,5} = \frac{6 \cdot (1+2)}{6+1+2} = 2$$



$U_{R1} = 36 \text{ V}$. $U_{R3} = U_{R3//4,5}$ can be calculated by voltage division:

$$U_{R3} = E \frac{R_{3//4,5}}{R_{3//4,5} + R_2} = 36 \frac{2}{2+4} = 12 \quad \Rightarrow \quad I = \frac{U_{R3}}{R_3} = \frac{12}{6} = 2 \text{ A}$$

U can be calculated by voltage division:

$$U = U_{R3//4,5} \frac{R_5}{R_4 + R_5} = 12 \frac{2}{1+2} = 8 \text{ V}$$


William Sandqvist william@kth.se

(3.2) OHM's law are often enough!


a) Calculate the resultant resistance R_{ERS} for the three parallel connected branches.

b) Calculate current I and voltage U .

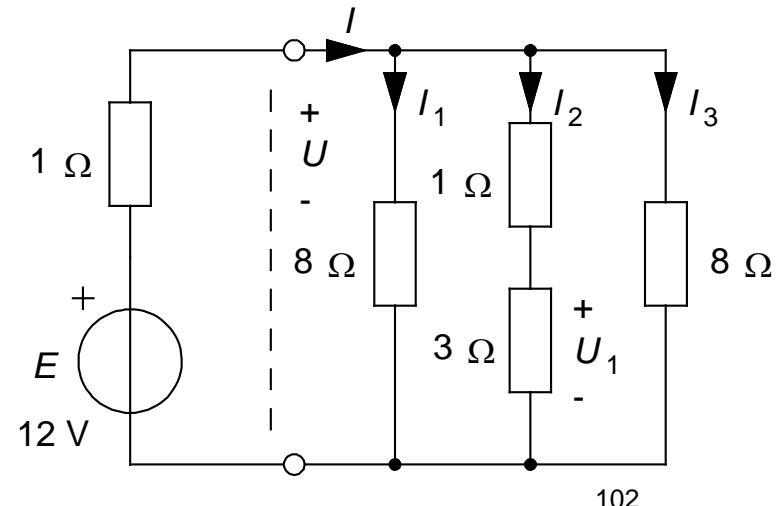c) Calculate the three currents I_1 I_2 and I_3 together with the voltage U_1 over 3Ω -resistor.




OHM's law ...

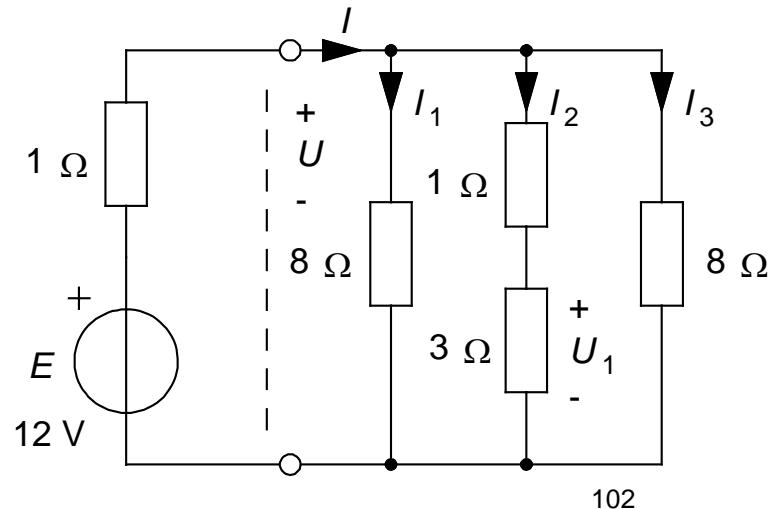

OHM's law ...

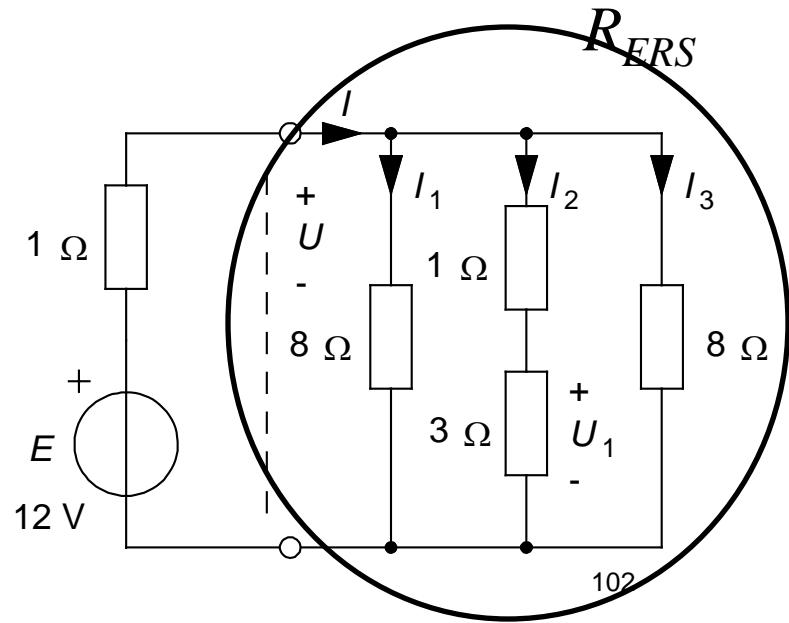
$$\frac{1}{R_{ERS}} = \frac{1}{8} + \frac{1}{1+3} + \frac{1}{8} = \frac{4}{8} \Rightarrow R_{ERS} = \frac{8}{4} = 2$$



OHM's law ...

$$\frac{1}{R_{ERS}} = \frac{1}{8} + \frac{1}{1+3} + \frac{1}{8} = \frac{4}{8} \Rightarrow R_{ERS} = \frac{8}{4} = 2$$
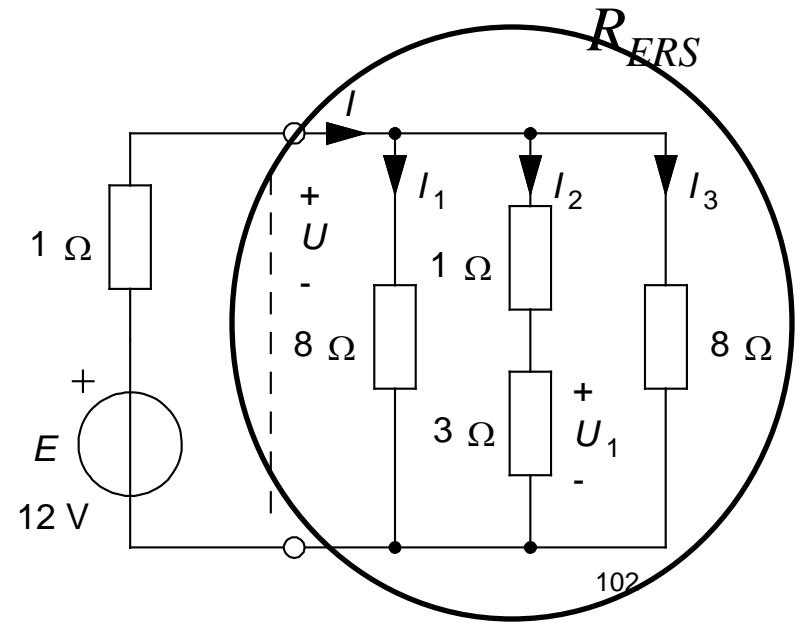
$$I = \frac{E}{1 + R_{ERS}} = \frac{12}{1 + 2} = 4$$




OHM's law ...

$$\frac{1}{R_{ERS}} = \frac{1}{8} + \frac{1}{1+3} + \frac{1}{8} = \frac{4}{8} \Rightarrow R_{ERS} = \frac{8}{4} = 2$$

$$I = \frac{E}{1 + R_{ERS}} = \frac{12}{1 + 2} = 4$$

$$U = I \cdot R_{ERS} = 4 \cdot 2 = 8$$

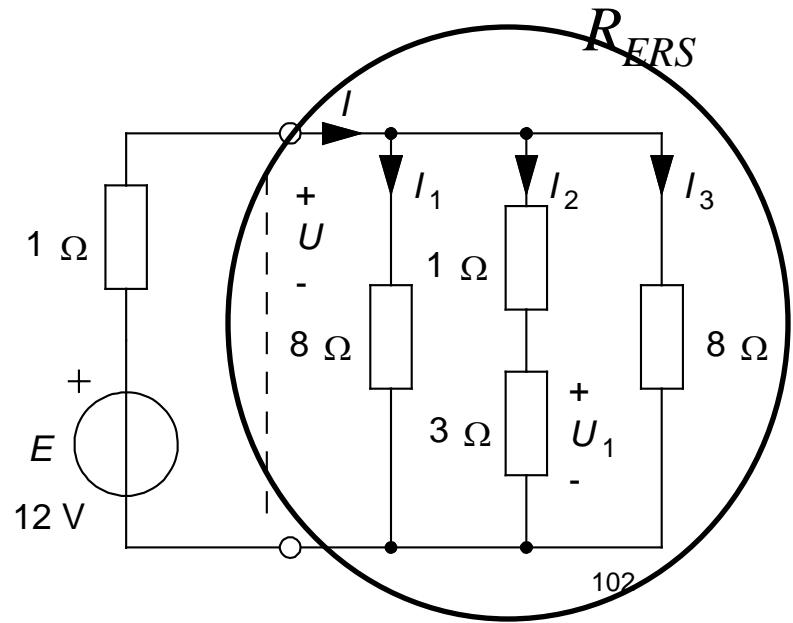


OHM's law ...

$$\frac{1}{R_{ERS}} = \frac{1}{8} + \frac{1}{1+3} + \frac{1}{8} = \frac{4}{8} \Rightarrow R_{ERS} = \frac{8}{4} = 2$$

$$I = \frac{E}{1 + R_{ERS}} = \frac{12}{1 + 2} = 4$$

$$U = I \cdot R_{ERS} = 4 \cdot 2 = 8$$

$$I_1 = \frac{U}{8} = \frac{8}{8} = 1$$

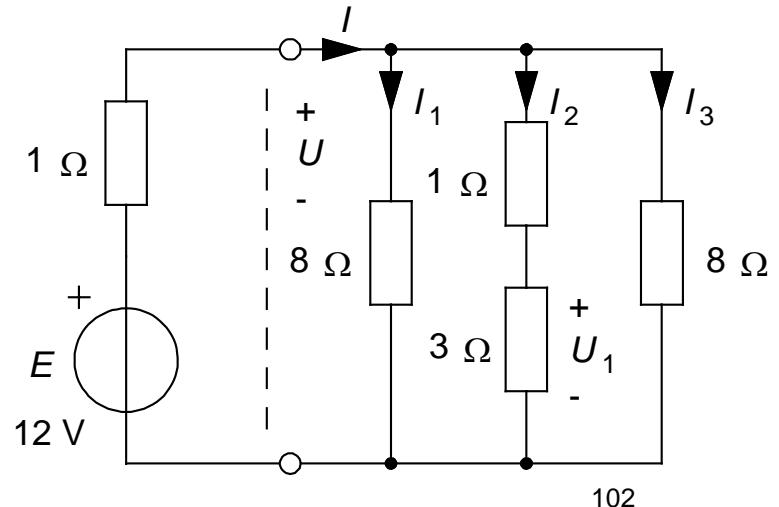

102


OHM's law ...

$$\frac{1}{R_{ERS}} = \frac{1}{8} + \frac{1}{1+3} + \frac{1}{8} = \frac{4}{8} \Rightarrow R_{ERS} = \frac{8}{4} = 2$$

$$I = \frac{E}{1+R_{ERS}} = \frac{12}{1+2} = 4$$

$$U = I \cdot R_{ERS} = 4 \cdot 2 = 8$$
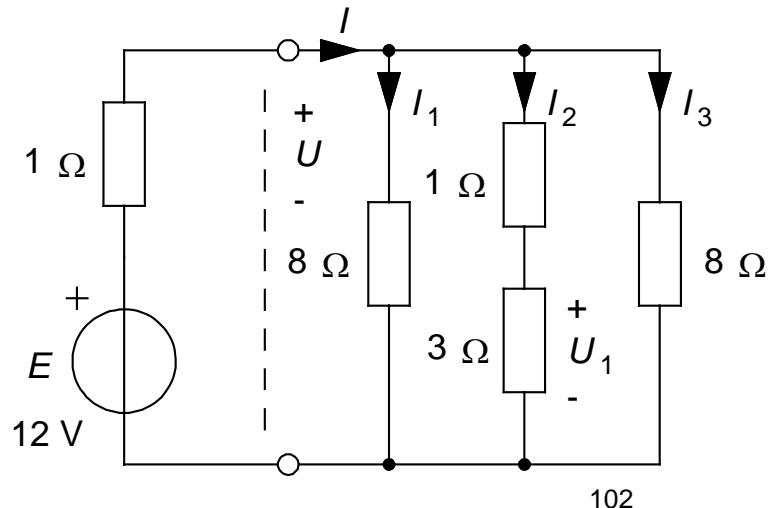
$$I_1 = \frac{U}{8} = \frac{8}{8} = 1 \quad I_2 = \frac{U}{1+3} = \frac{8}{1+3} = 2$$




OHM's law ...

$$\frac{1}{R_{ERS}} = \frac{1}{8} + \frac{1}{1+3} + \frac{1}{8} = \frac{4}{8} \Rightarrow R_{ERS} = \frac{8}{4} = 2$$

$$I = \frac{E}{1+R_{ERS}} = \frac{12}{1+2} = 4$$

$$U = I \cdot R_{ERS} = 4 \cdot 2 = 8$$
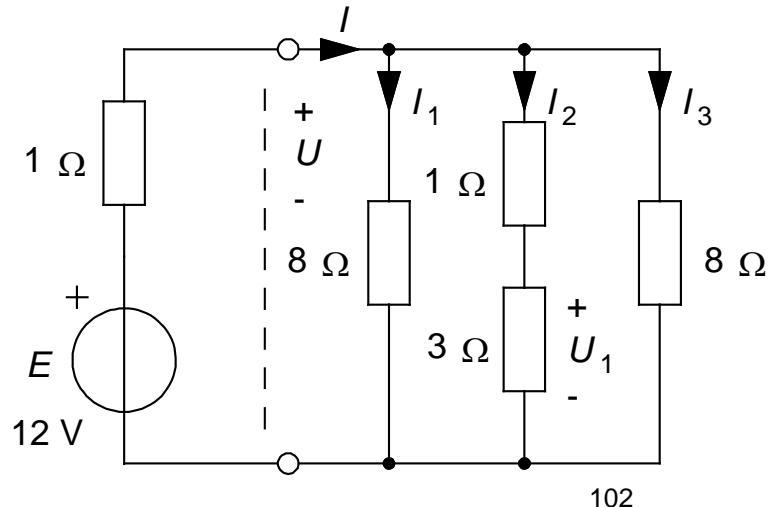
$$I_1 = \frac{U}{8} = \frac{8}{8} = 1 \quad I_2 = \frac{U}{1+3} = \frac{8}{1+3} = 2 \quad I_3 = \frac{U}{8} = \frac{8}{8} = 1$$



102

OHM's law ...


$$\frac{1}{R_{ERS}} = \frac{1}{8} + \frac{1}{1+3} + \frac{1}{8} = \frac{4}{8} \Rightarrow R_{ERS} = \frac{8}{4} = 2$$

$$I = \frac{E}{1+R_{ERS}} = \frac{12}{1+2} = 4$$

$$U = I \cdot R_{ERS} = 4 \cdot 2 = 8$$

$$I_1 = \frac{U}{8} = \frac{8}{8} = 1 \quad I_2 = \frac{U}{1+3} = \frac{8}{1+3} = 2 \quad I_3 = \frac{U}{8} = \frac{8}{8} = 1$$

$$U_1 = I_2 \cdot 3 = 2 \cdot 3 = 6$$

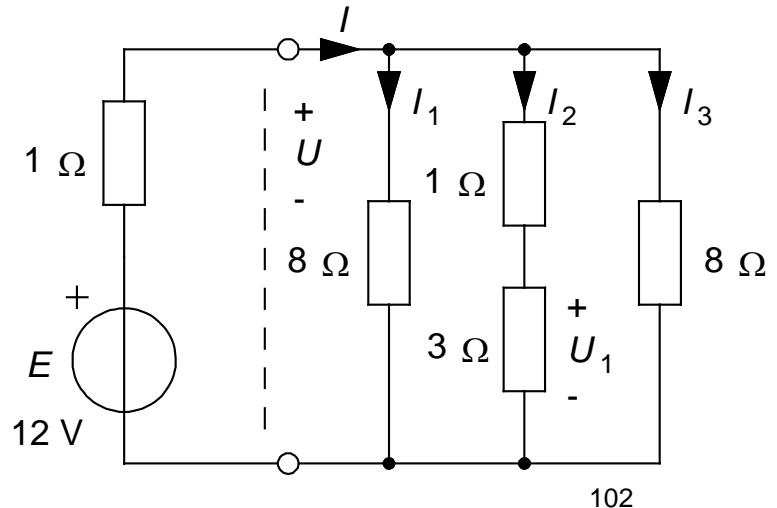

102


OHM's law ...

$$\frac{1}{R_{ERS}} = \frac{1}{8} + \frac{1}{1+3} + \frac{1}{8} = \frac{4}{8} \Rightarrow R_{ERS} = \frac{8}{4} = 2$$

$$I = \frac{E}{1+R_{ERS}} = \frac{12}{1+2} = 4$$


$$U = I \cdot R_{ERS} = 4 \cdot 2 = 8$$
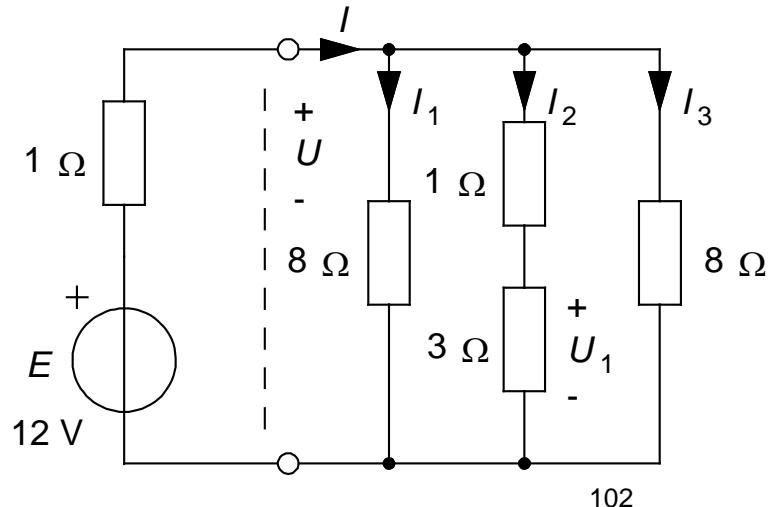
$$I_1 = \frac{U}{8} = \frac{8}{8} = 1 \quad I_2 = \frac{U}{1+3} = \frac{8}{1+3} = 2 \quad I_3 = \frac{U}{8} = \frac{8}{8} = 1$$



$$U_1 = I_2 \cdot 3 = 2 \cdot 3 = 6$$

OHM's law was enough!

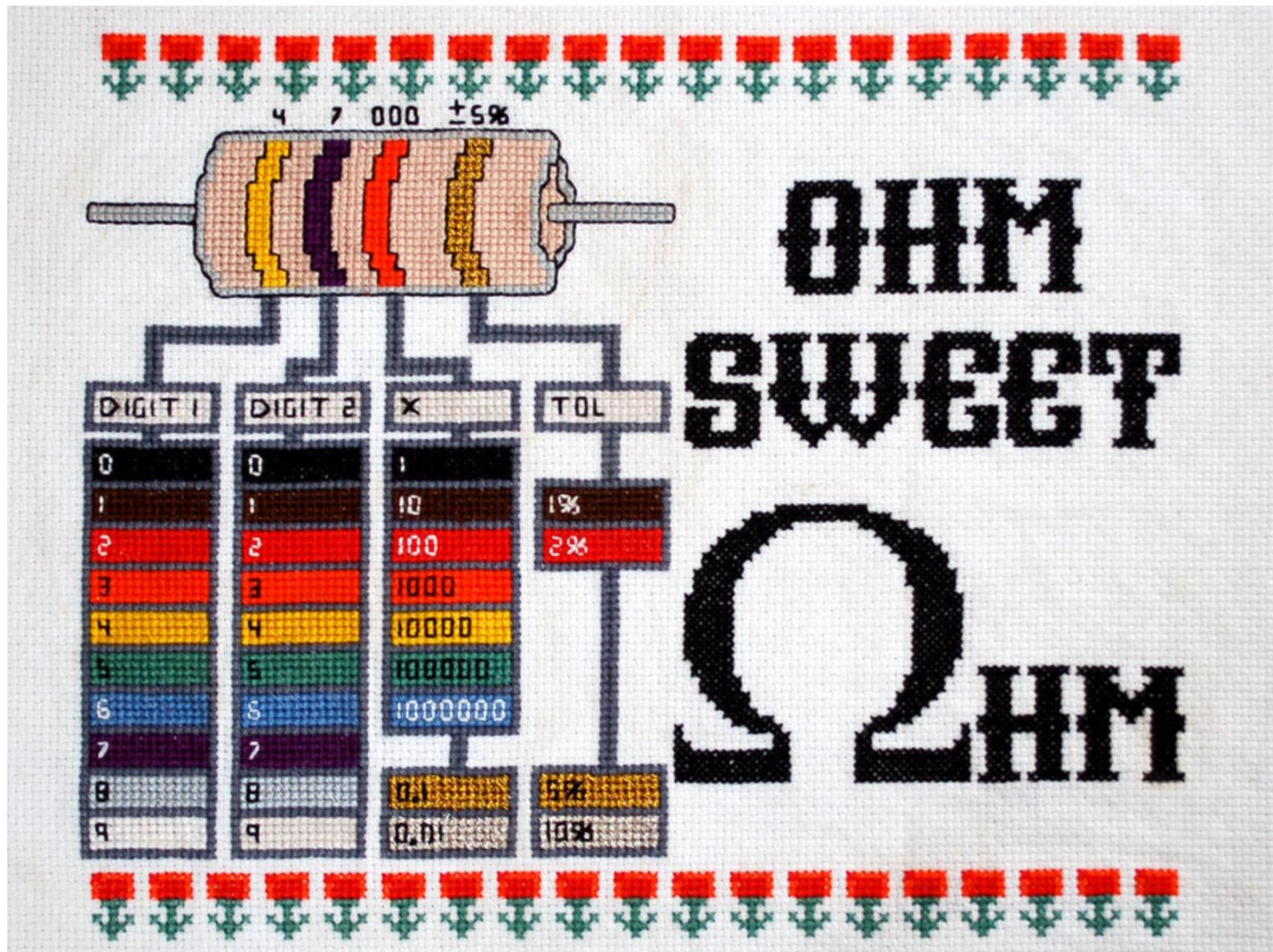

William Sandqvist william@kth.se