
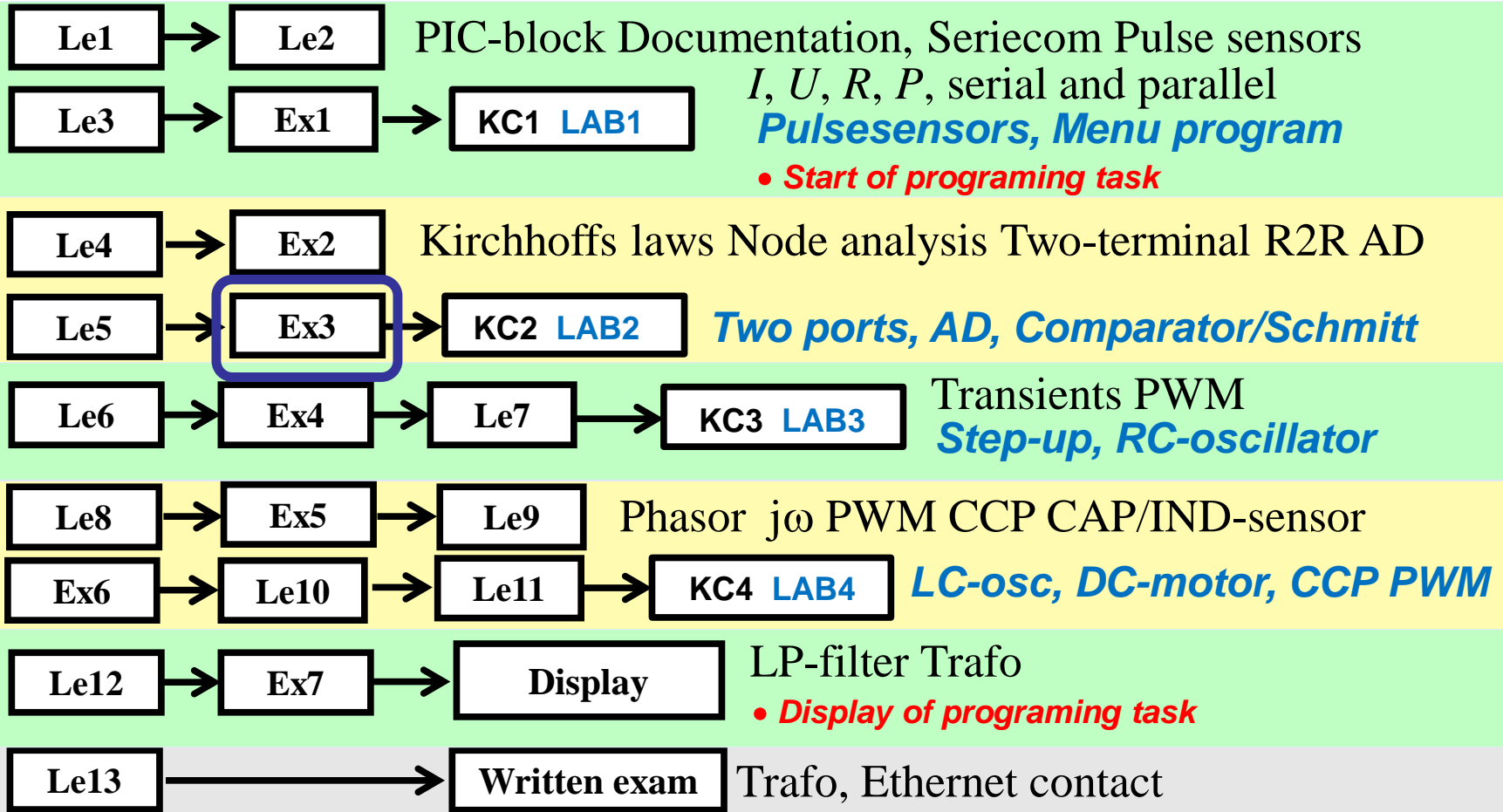


IE1206 Embedded Electronics

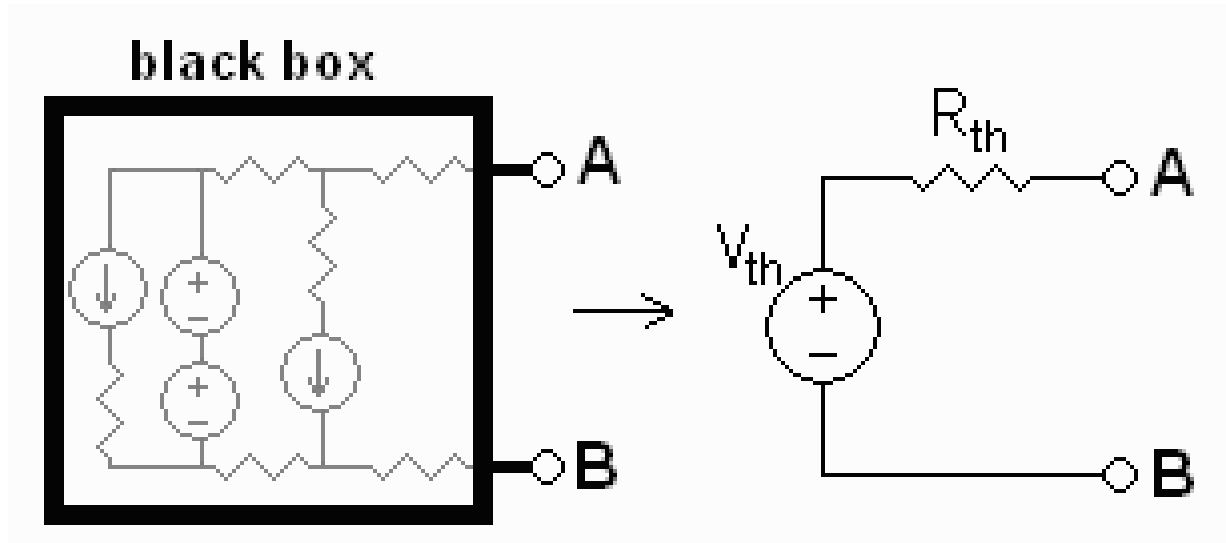

Two terminal circuits – Black box



? = !

The power supply

VOLTAGE
knob to set the
constant voltage.
Coarse and fine
adjustments.




Buttons to select
the display of
voltage or
current.

Voltage / Amps

C.V. Continuous
Voltage. Led indicating
that the unit operates as
a voltage generator.

+ and - poles

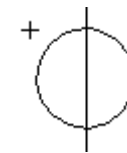
(GND is to connect the metal casing to +/- to suppress interference).



The power supply

CURRENT knob to set the current limit. Coarse and fine adjustments.

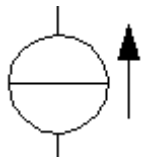C.C. Continuous Current. Led indicating that the unit operates as a current generator.





To set the current limit you show “Amps” and then short voltage poles.

The set current then becomes the maximum current that can occur.




Voltage and Current generator

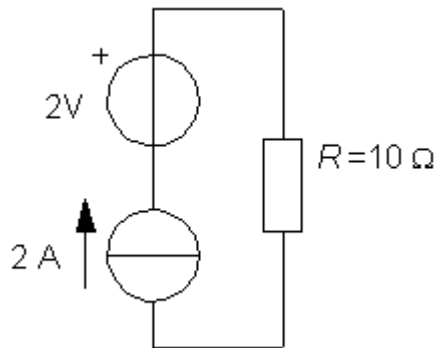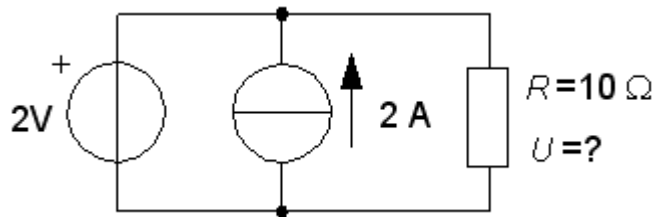(Ex. 8.1) What value will the U get in these idealized and usually unrealistic circuits?







Voltage and Current generator

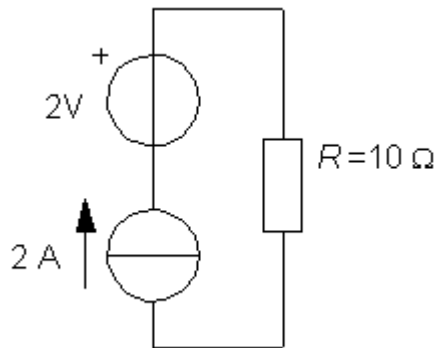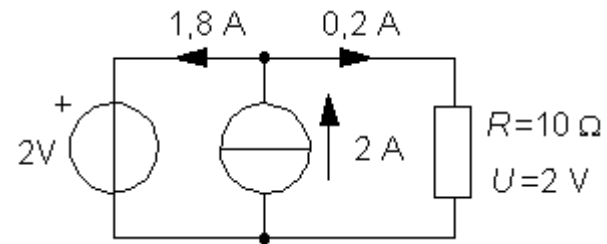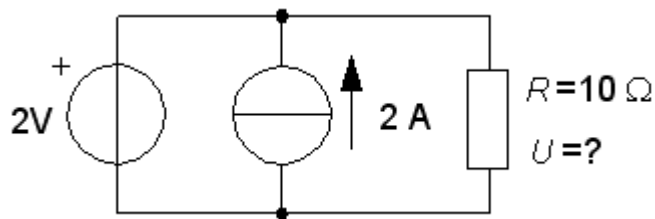(Ex. 8.1) What value will the U get in these idealized and usually unrealistic circuits?





Voltage and Current generator

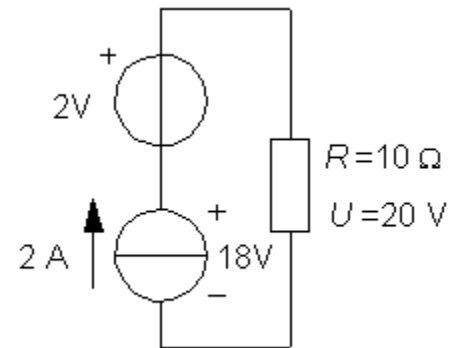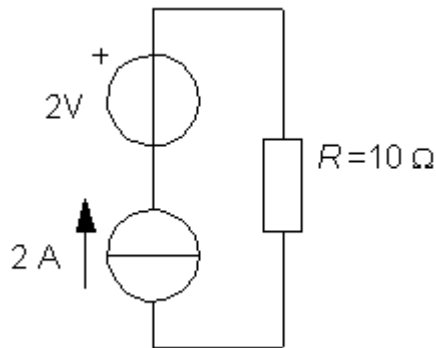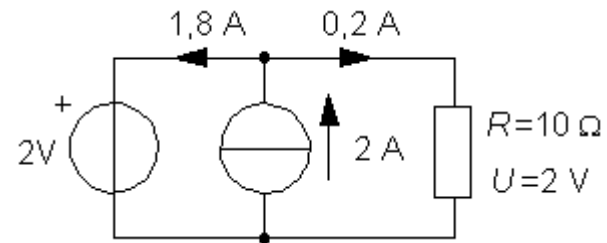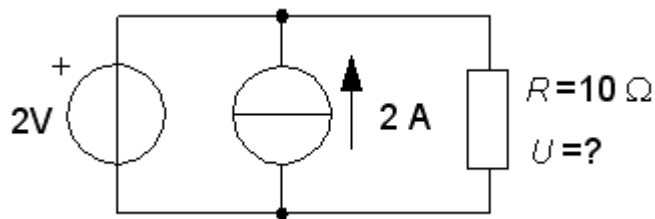(Ex. 8.1) What value will the U get in these idealized and usually unrealistic circuits?




William Sandqvist william@kth.se

Simplify ... (8.2)

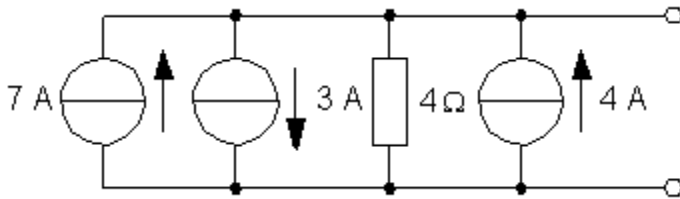
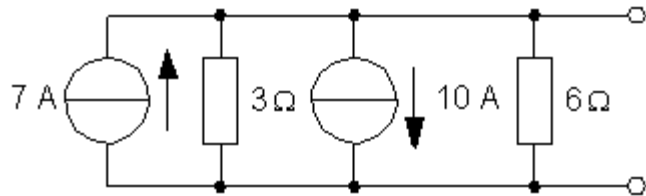


Simplify ... (8.2)

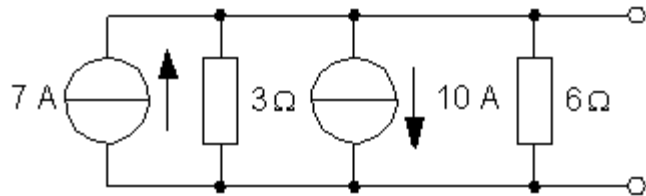


$$7 - 10 = -3$$

$$\frac{3 \cdot 6}{3 + 6} = 2$$


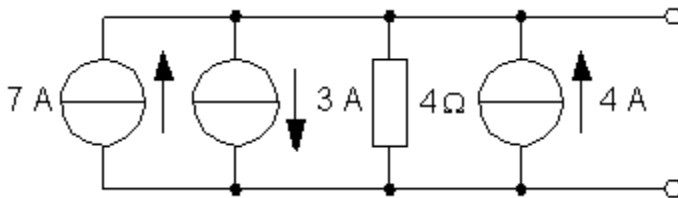
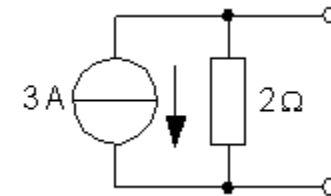


Simplify ... (8.2)

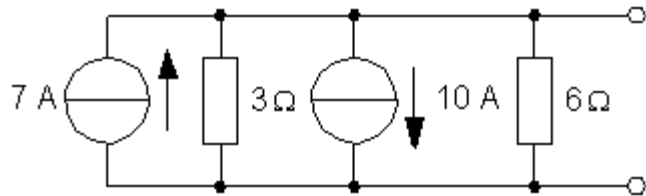

$$7 - 10 = -3$$


$$\frac{3 \cdot 6}{3 + 6} = 2$$

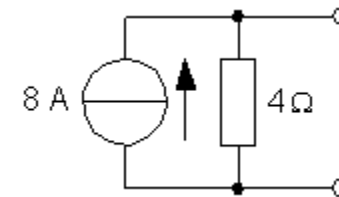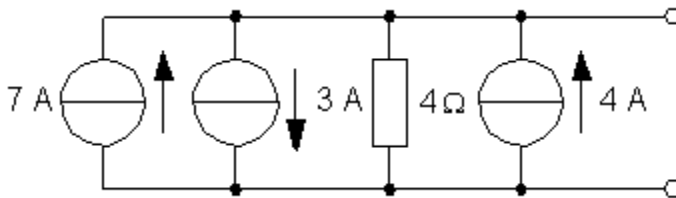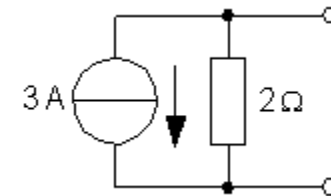

William Sandqvist william@kth.se


Equivalents step by step ...

(8.4) Electronics prefix [V] [k Ω] [mA]

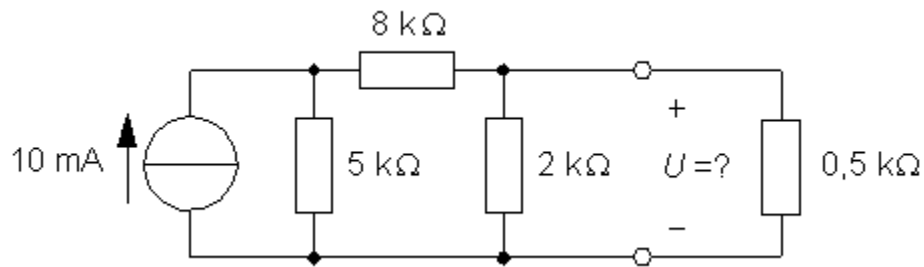


Equivalents step by step ...

(8.4) Electronics prefix [V] [kΩ] [mA]

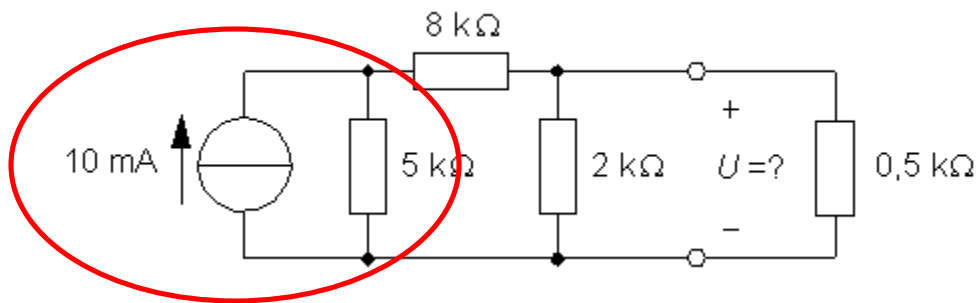


$$10 \cdot 5 = 50$$


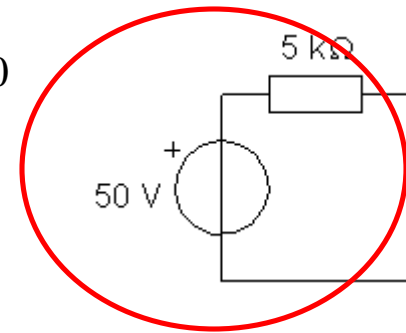


Equivalents step by step ...

(8.4) Electronics prefix [V] [kΩ] [mA]

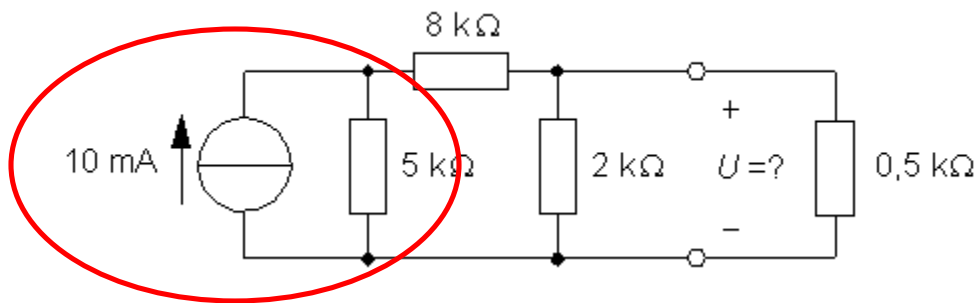


$$10 \cdot 5 = 50$$

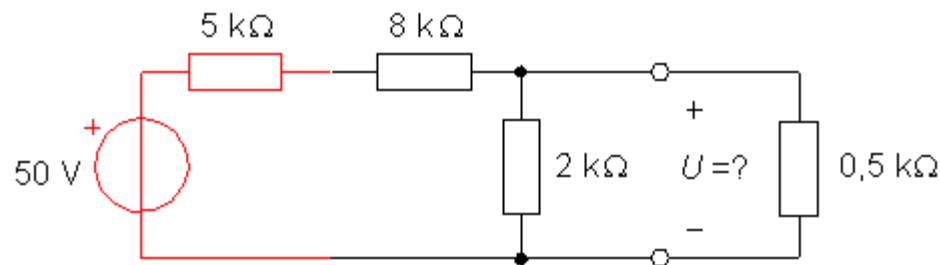
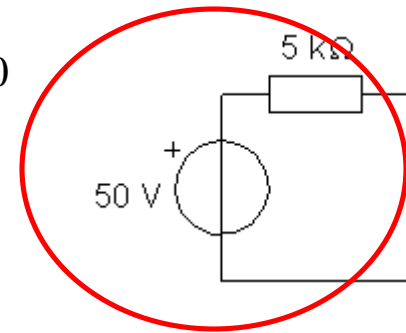


Equivalents step by step ...

(8.4) Electronics prefix [V] [kΩ] [mA]

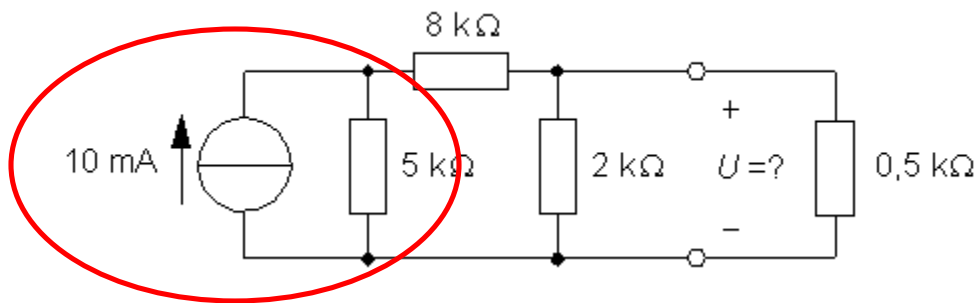


$$10 \cdot 5 = 50$$

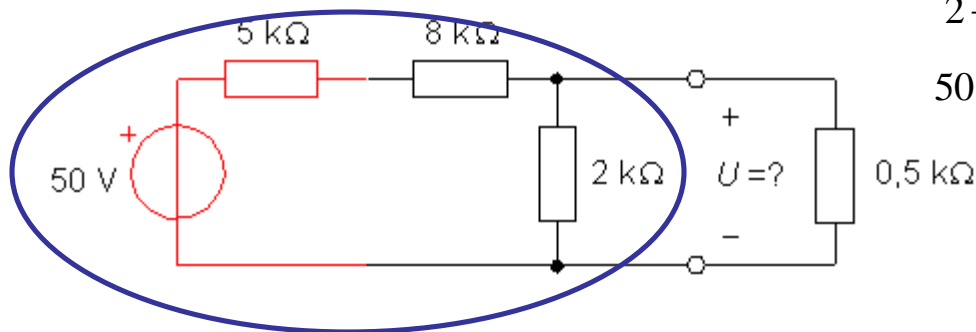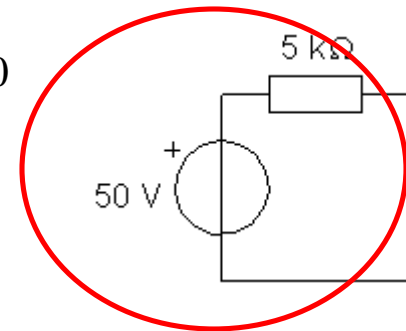


$$\frac{2 \cdot (5 + 8)}{2 + 5 + 8} = 1,73$$

$$50 \cdot \frac{2}{2 + 5 + 8} = 6,67$$

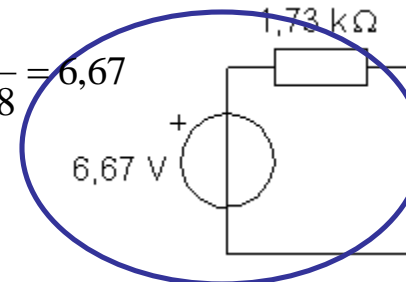

At last ...

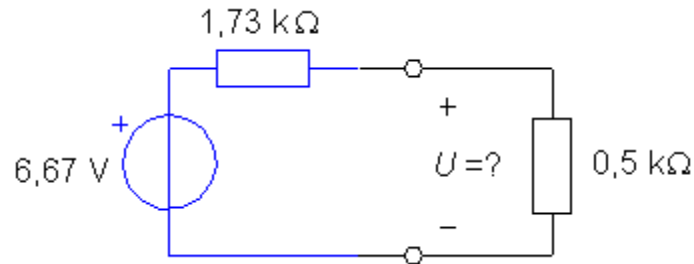

Voltage divider:


$$U = 6,67 \cdot \frac{0,5}{0,5 + 1,73} = 1,49 \text{ V}$$

- Step by step the circuit gets simpler while the numerical values becomes more complicated!

You will need a calculator. Even with adapted numbers in the exercises you can come to select a computation path that generates unwieldy decimal numbers towards the intended simple answer.

William Sandqvist william@kth.se


(Wheatstone bridge equivalent)

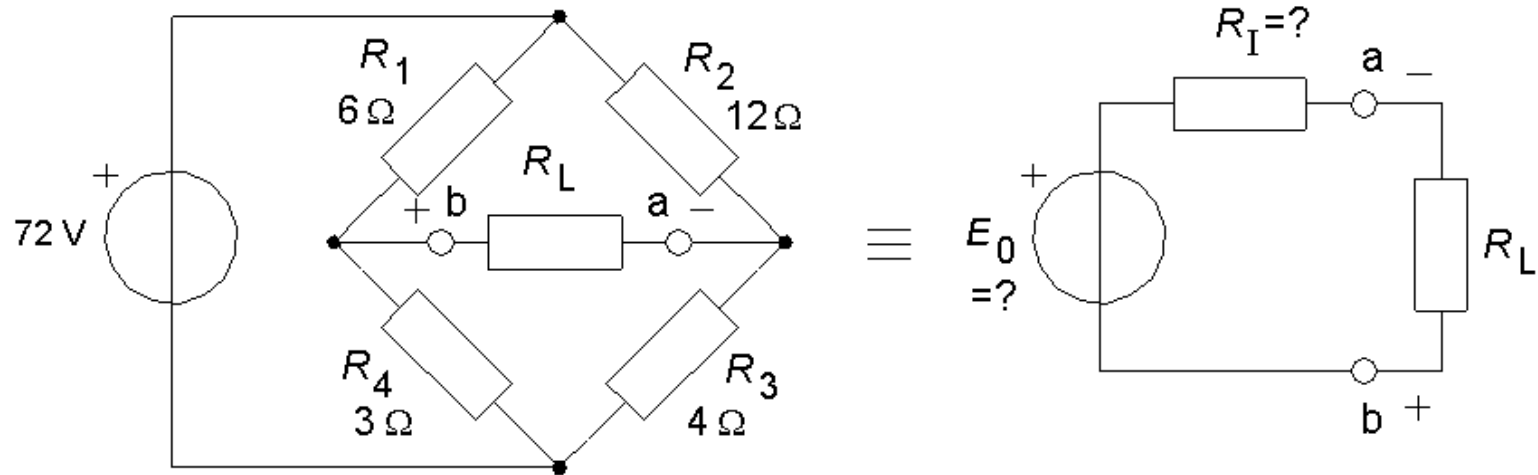

Determine the Wheatstone bridge Thevenin equivalent.


(Determine R_I)

Voltage turned
down to zero

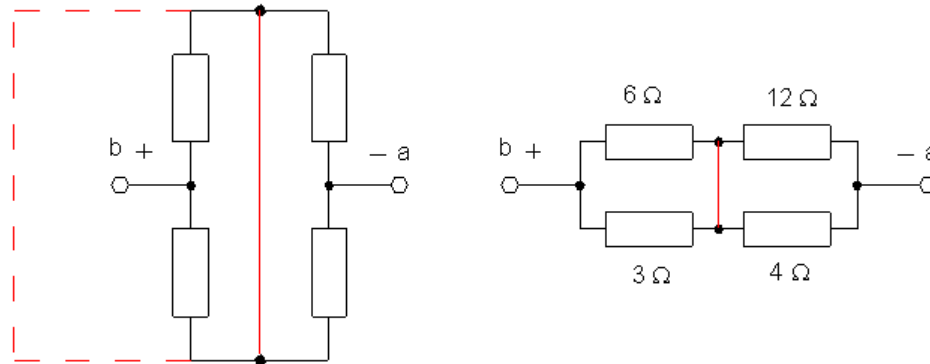

$$R_I = \frac{6 \cdot 3}{6 + 3} + \frac{12 \cdot 4}{12 + 4} = 5 \Omega$$

(Determine E_0)

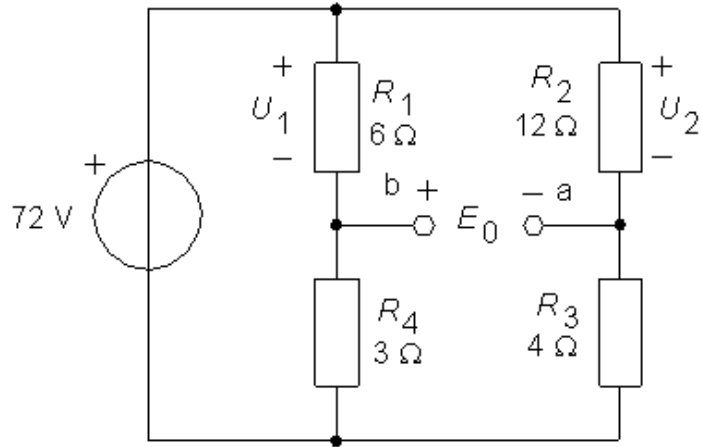


$$U_1 = 72 \cdot \frac{6}{6+3} = 48$$

$$U_2 = 72 \cdot \frac{12}{12+4} = 54$$

$$E_0 = 54 - 48 = 6\text{ V}$$

(Determine $R_1 E_0$)

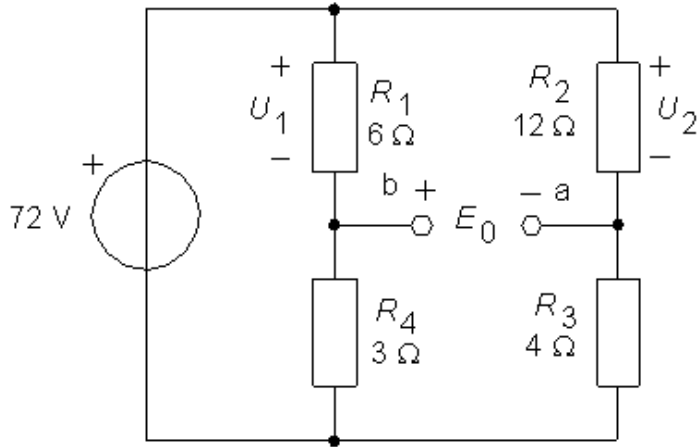


$$U_1 = 72 \cdot \frac{6}{6+3} = 48$$


$$U_2 = 72 \cdot \frac{12}{12+4} = 54$$

$$E_0 = 54 - 48 = 6\text{ V}$$

Done!

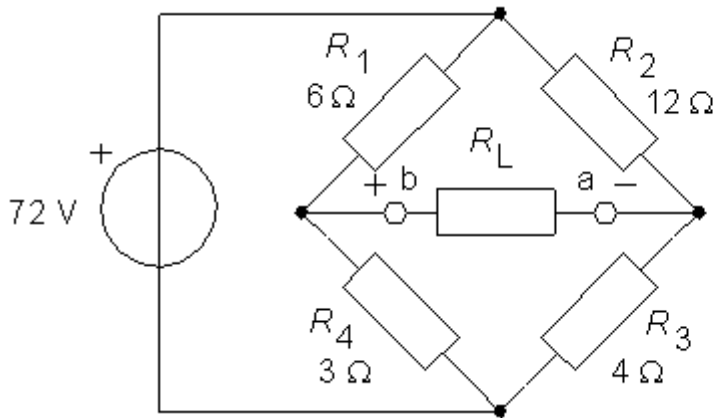


\equiv

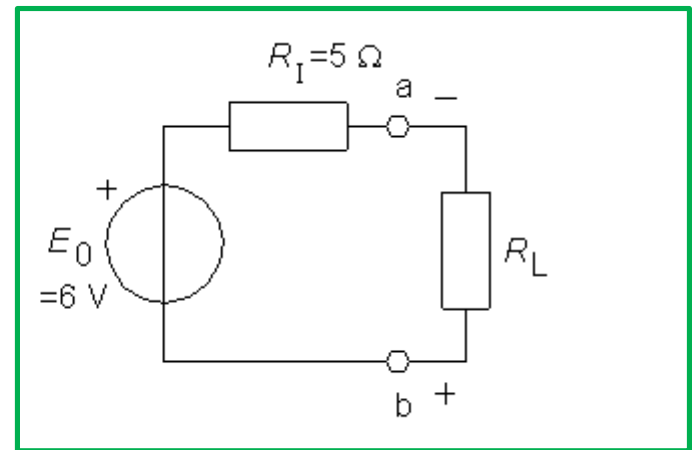


William Sandqvist william@kth.se


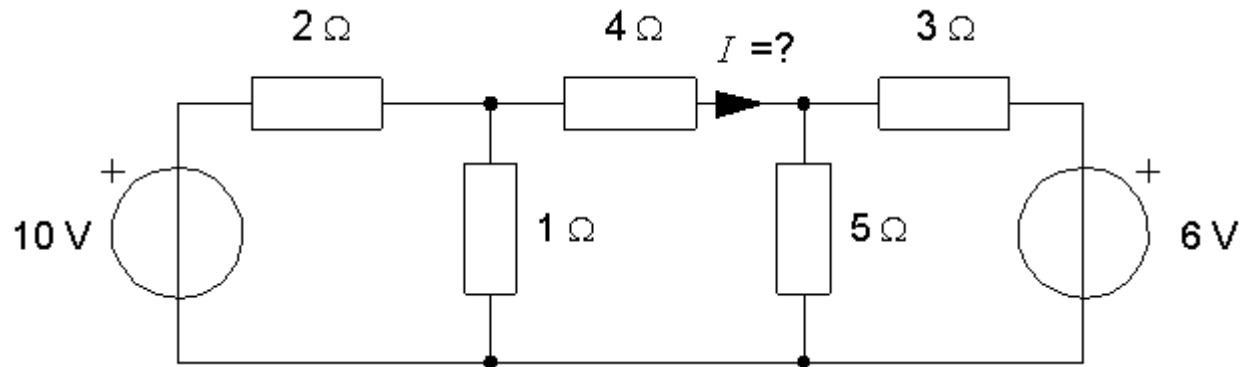
Equivalent circuits (instead of mesh analysis)!




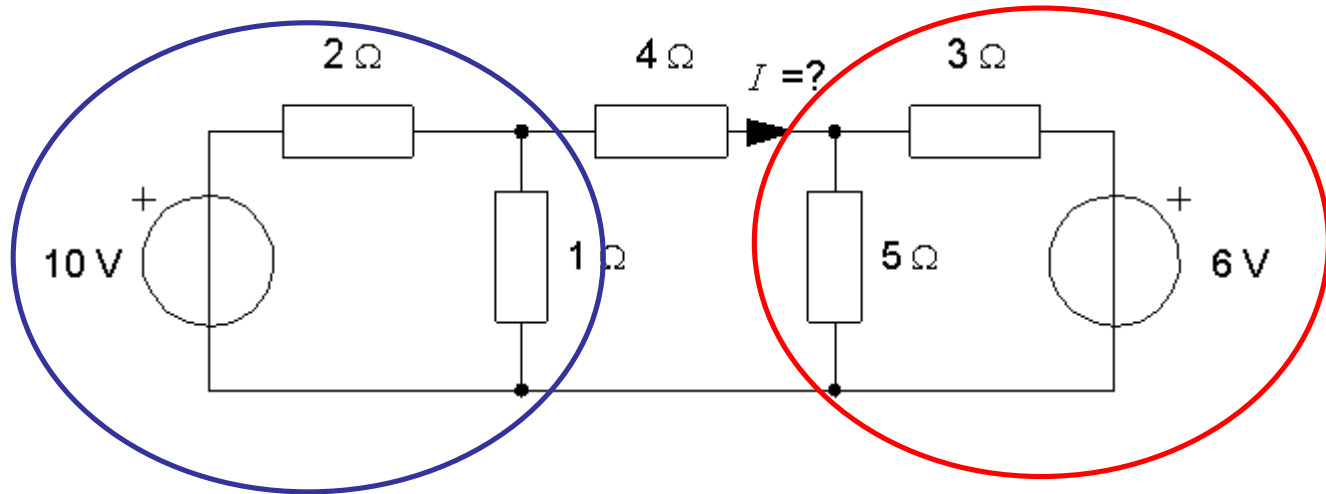
Equivalent circuits (instead of mesh analysis)!



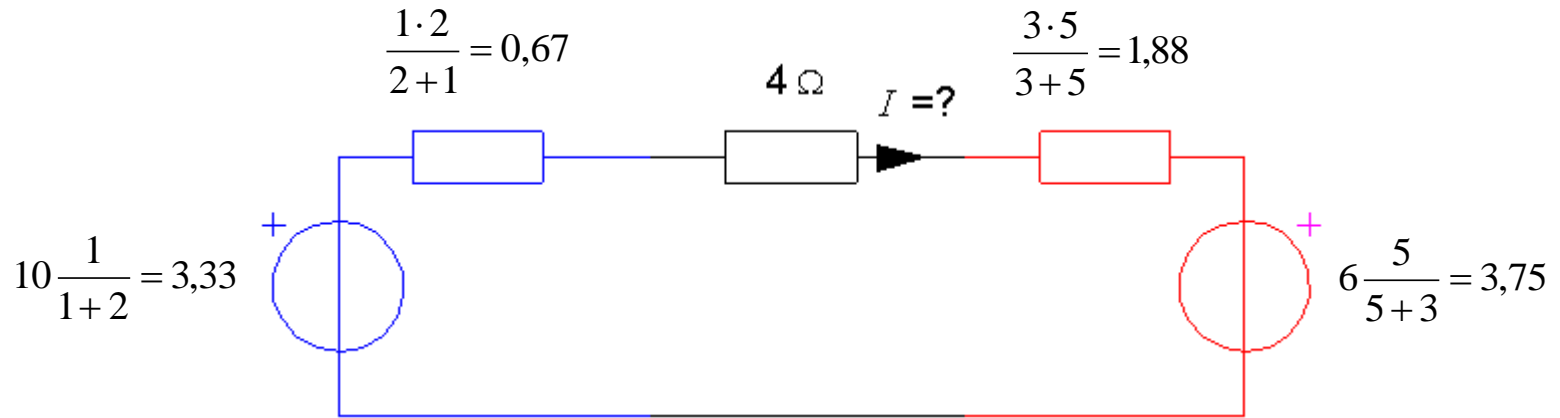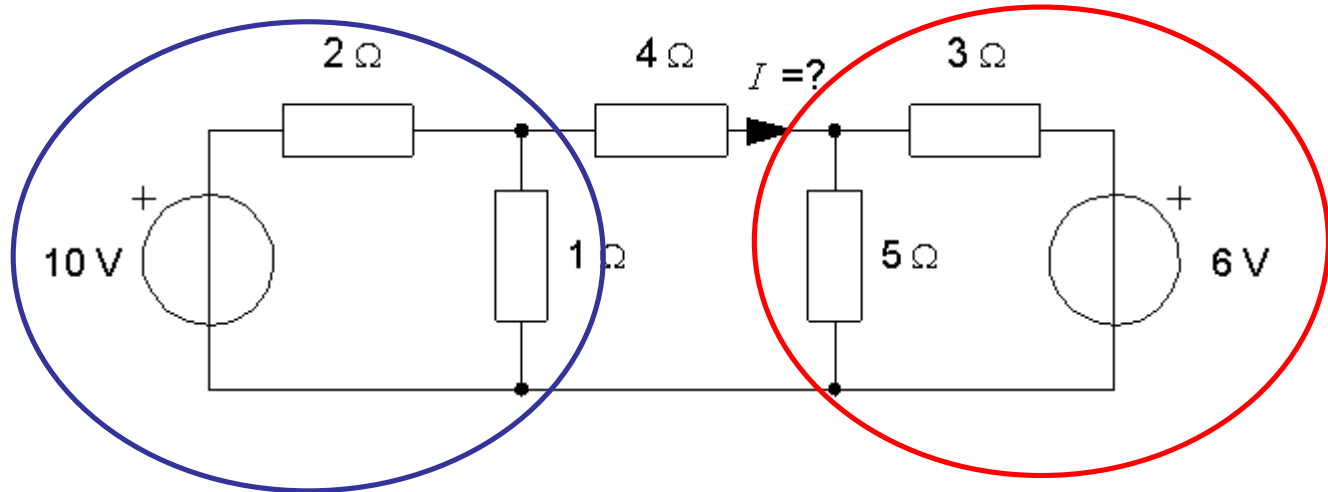Equivalent circuits (instead of mesh analysis)!




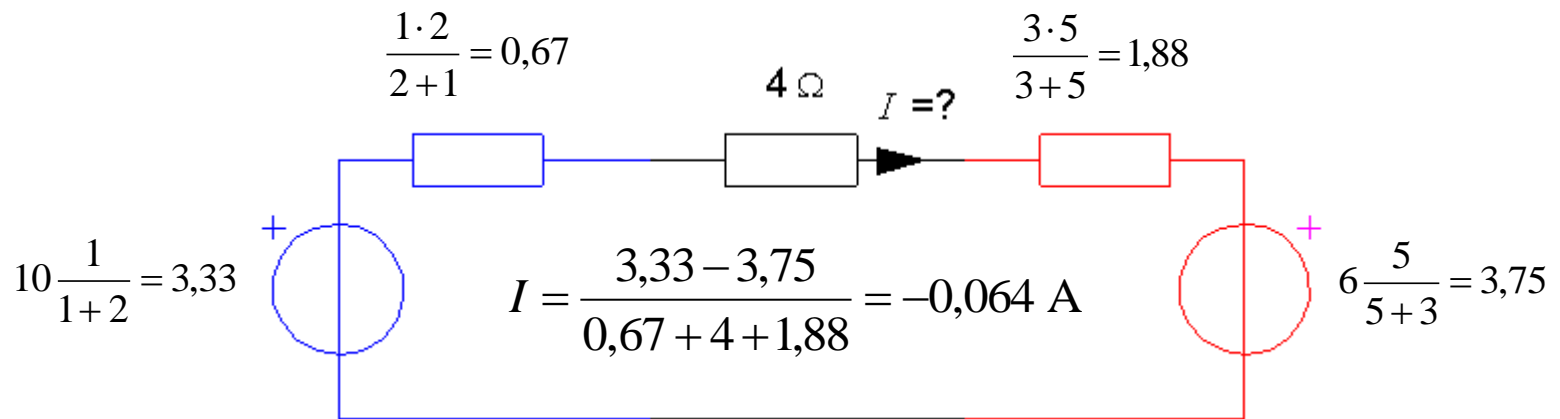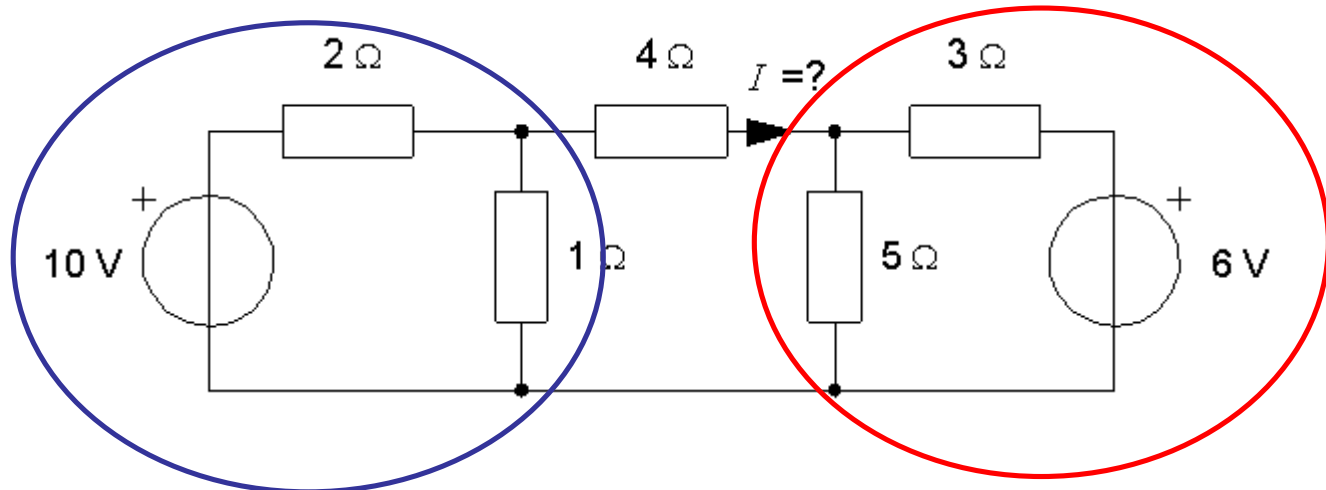Equivalent circuits (instead of mesh analysis)!



William Sandqvist william@kth.se


Example (8.10)

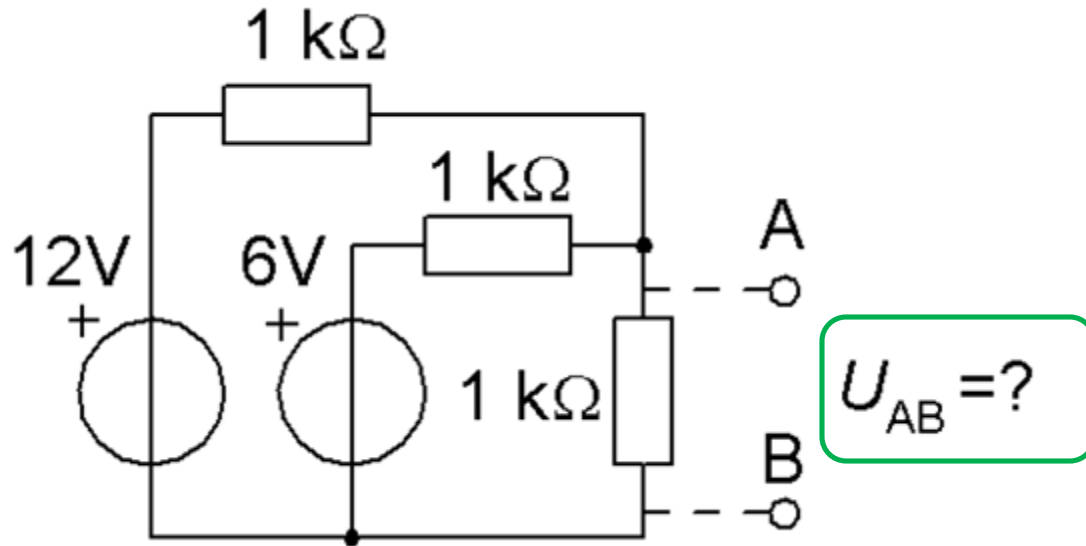

What value has the voltage U_{AB} ?

- Use Thevenine equivalent to at "same time" get value of U_{AB} !


Example (8.10)

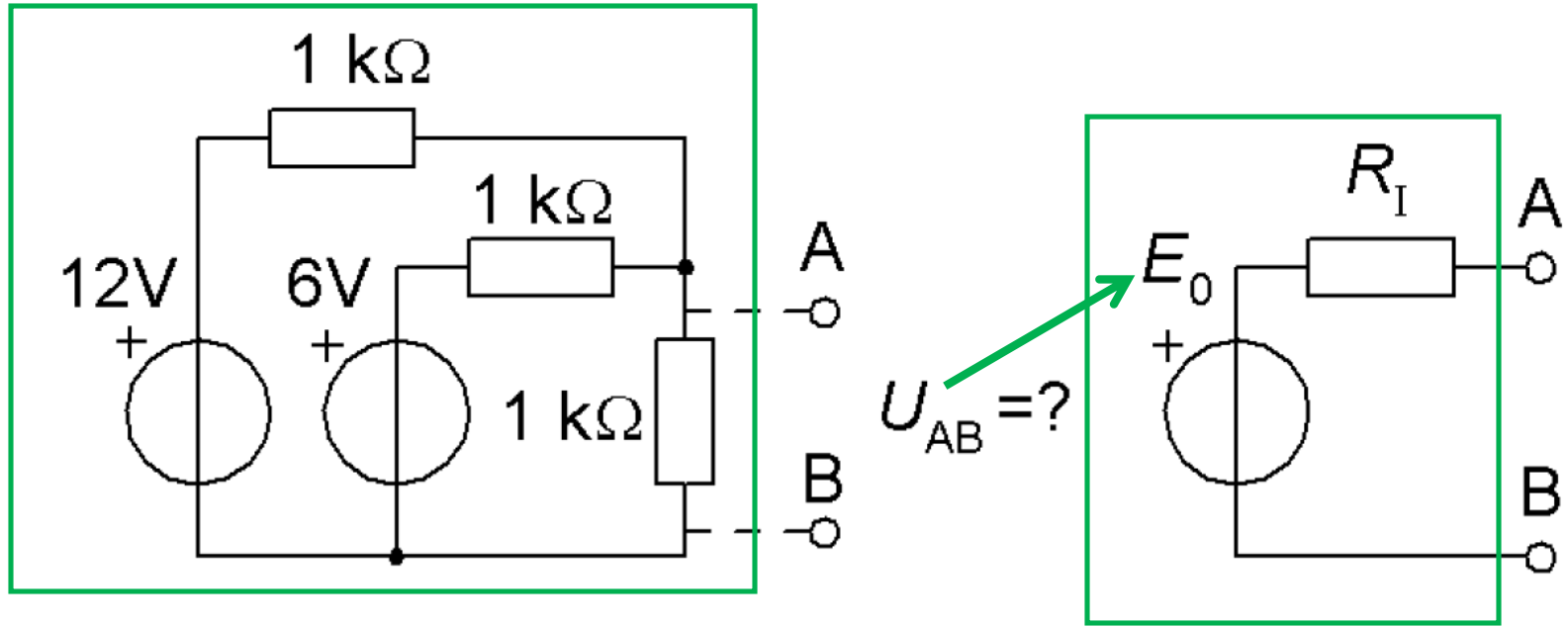

- Derive a Thevenin's equivalent, E_0 R_I , to the circuit with the two voltage sources and the three resistors.
- How big is the voltage drop U_{AB} over 1 kΩ resistor in the original circuit?

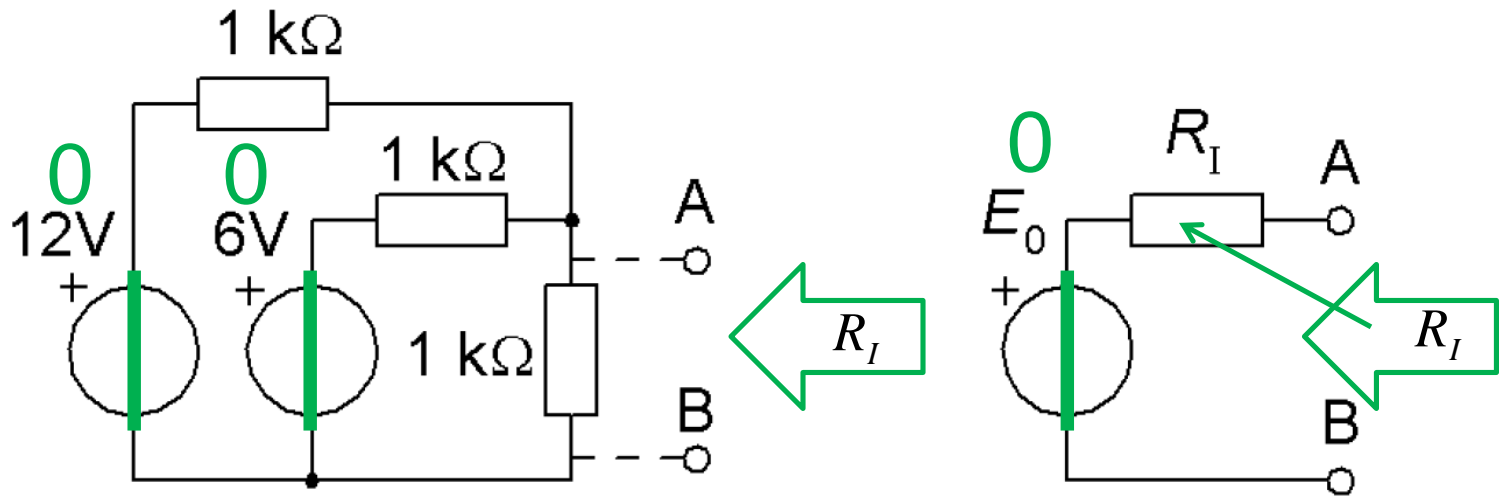Example (8.10)

Let's calculate the voltage drop U_{AB} over the $1\text{ k}\Omega$ resistor in the circuit, from the Thevenin's equivalent, as then U_{AB} will be the same as the E_0 !




- R_I is the equivalent resistance when the both voltage sources are turned down to zero:

$$R_I = \frac{1}{\frac{1}{1\text{k}\Omega} + \frac{1}{1\text{k}\Omega} + \frac{1}{1\text{k}\Omega}} = \frac{1}{3} \text{k}\Omega$$

Example (8.10)


- I_K short circuit current.

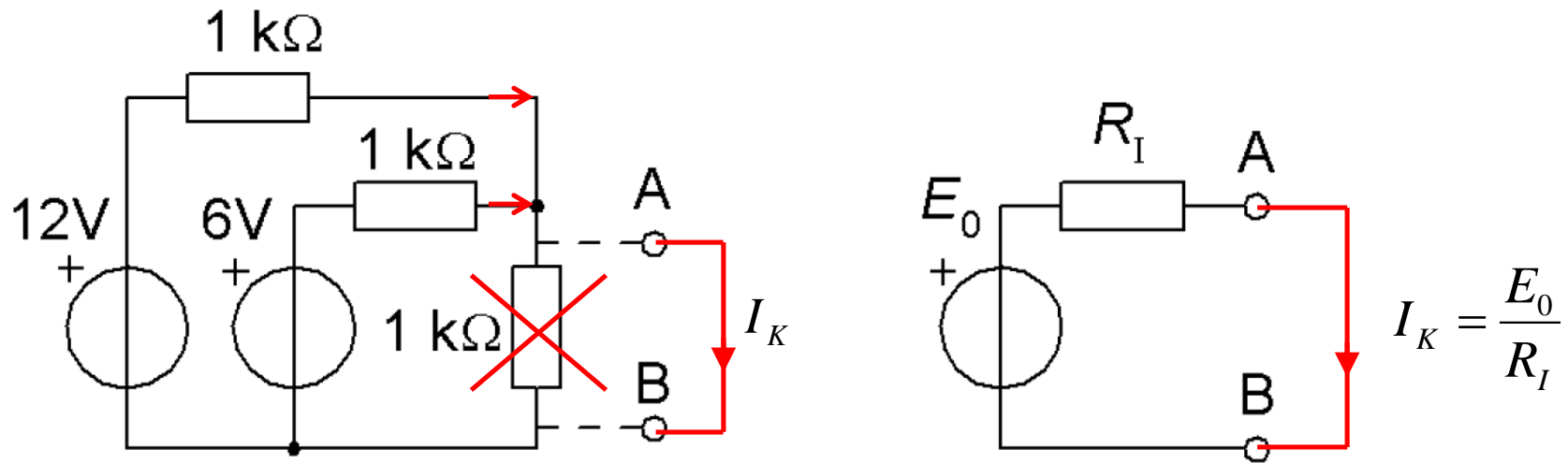

Suppose A and B are directly connected to each other. The third 1 kΩ resistor will be short circuit and get no current and can therefore be ignored. The short circuit current will come from the two voltage sources through their 1k Ω resistors:

$$I_K = \frac{12\text{V}}{1\text{k}\Omega} + \frac{6\text{V}}{1\text{k}\Omega} = 18 \text{ mA}$$

Example (8.10)

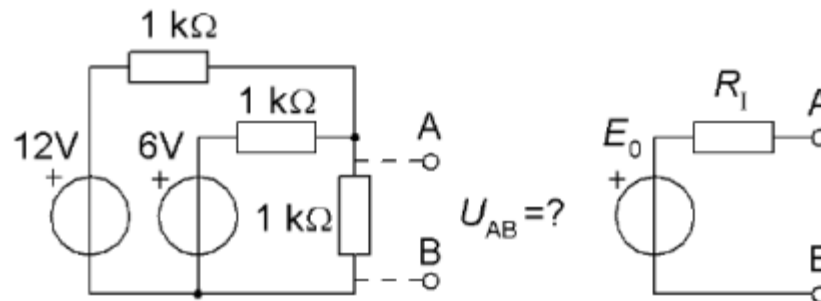


The Thevenin equivalent will have the same short circuit current $I_K = 18$ mA. This makes it easy to calculate E_0 :

$$I_K = \frac{E_0}{R_I} \Rightarrow E_0 = I_K \cdot R_I = 18 \cdot \frac{1}{3} = 6 \text{ V}$$

And the voltage drop U_{AB} is the same E_0 .


$$U_{AB} = 6 \text{ V.}$$

Example (8.10)

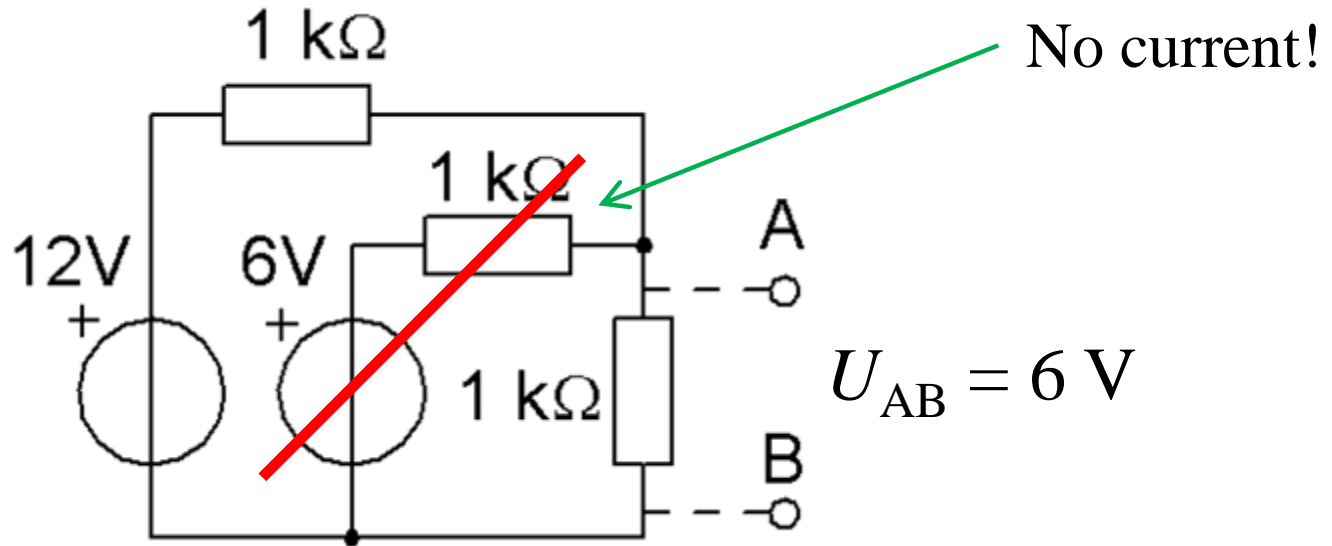

- What would happen if one removed the 6V battery?

Example (8.10)

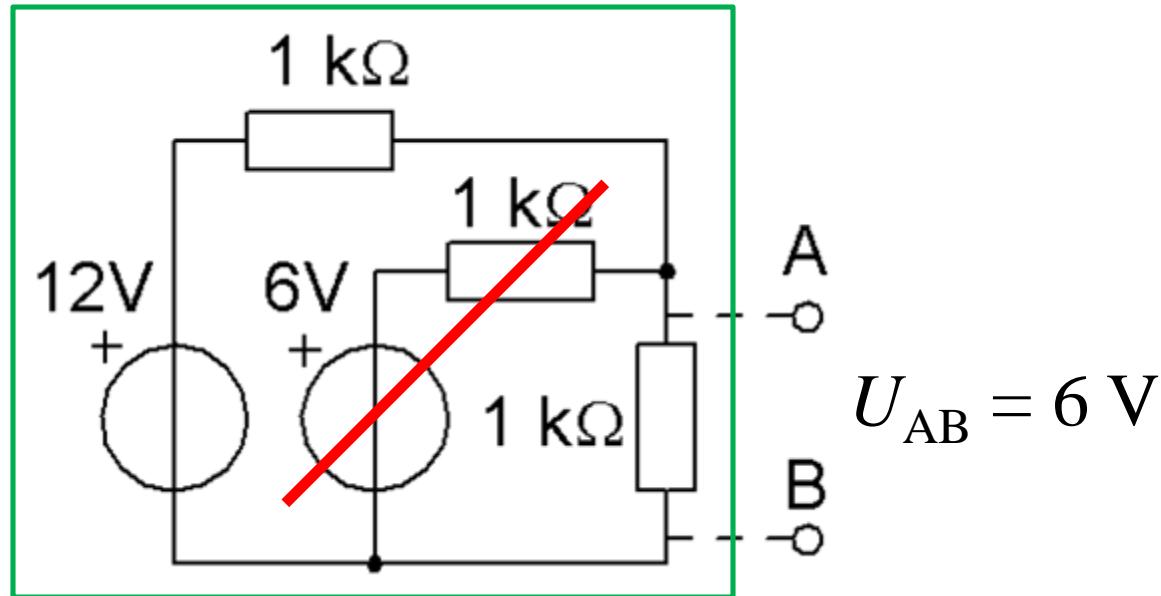


- What would happen if one removed the 6V battery?

This is now another two terminal circuit.



U_{AB} is unchanged $U_{AB} = \mathbf{6V}$, but R_I increases to $R_I = \mathbf{0,5\ k\Omega}$.
($I_K = 6/0,5 = \mathbf{12\ mA}$).

William Sandqvist william@kth.se

Tips & Tricks

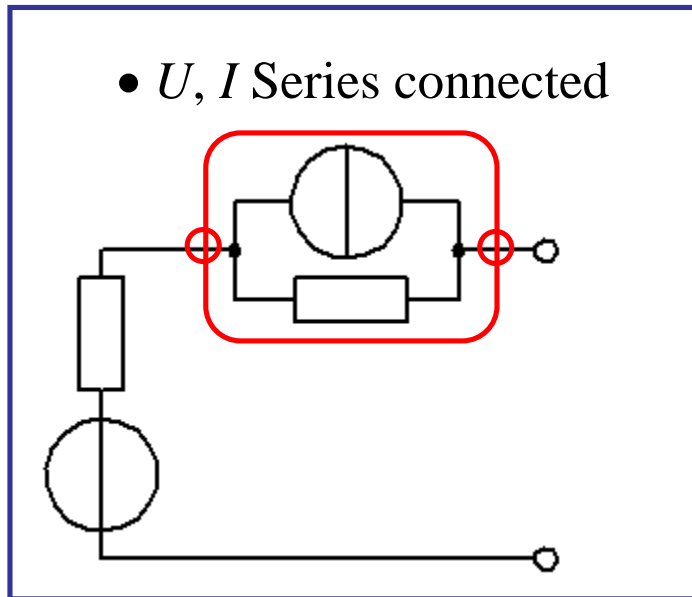


Transform to voltage source!

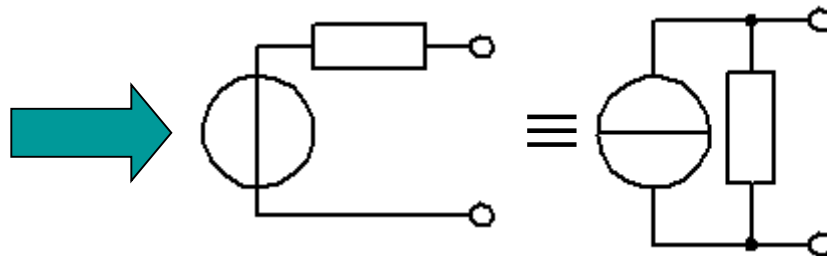
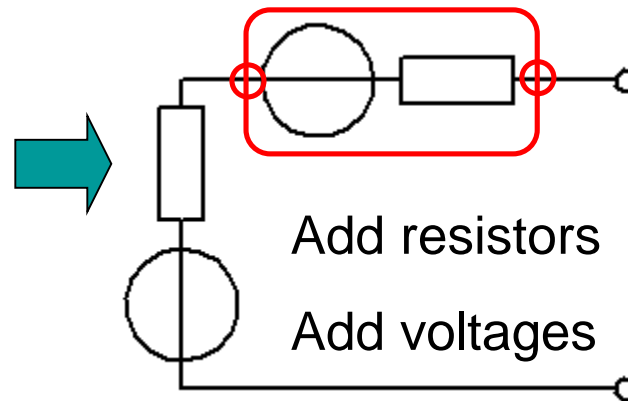


Tips & Tricks

- U, I Parallel connected



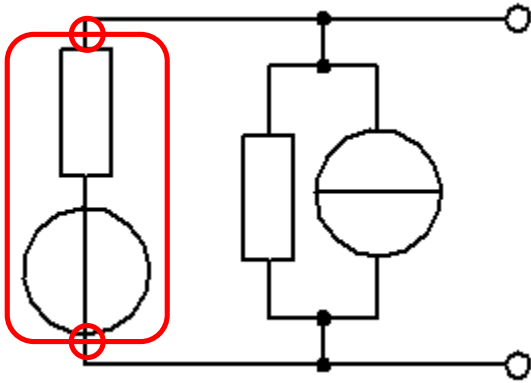


Transform to current source!

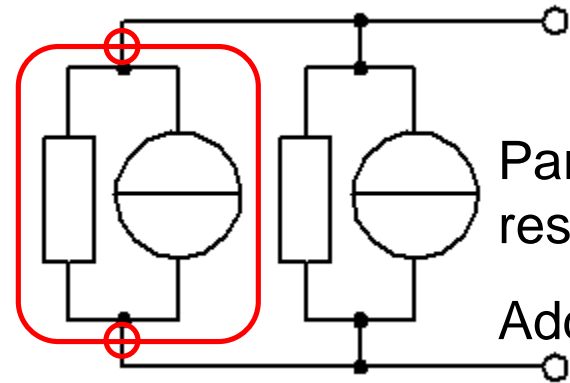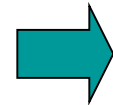


Parallel resistors

Add currents

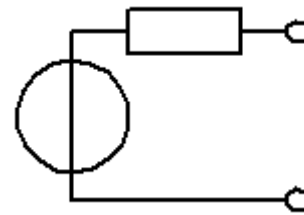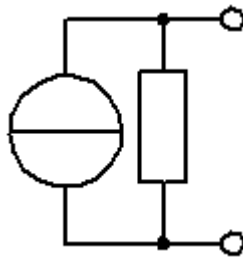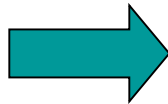


William Sandqvist william@kth.se

Example (8.9)

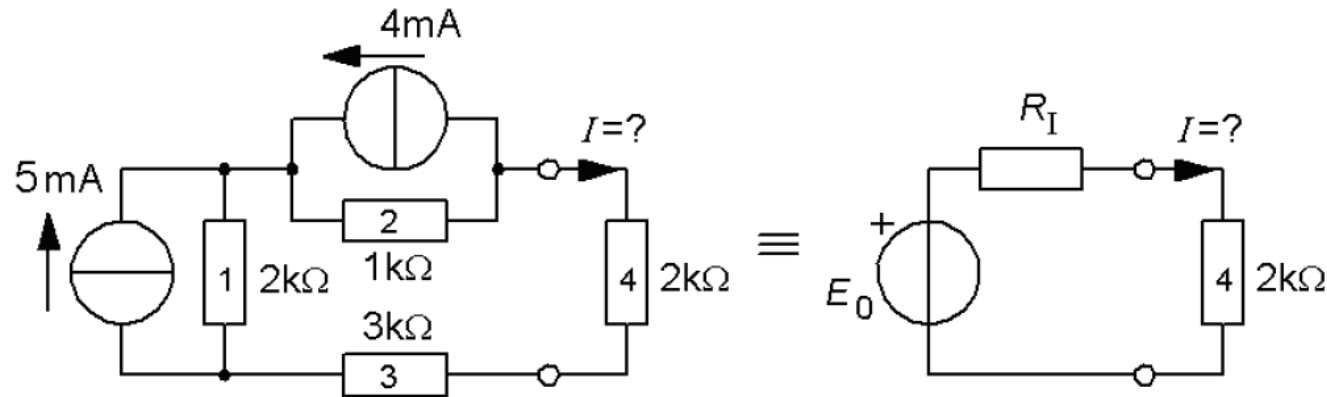

- Derive a Thevenin's equivalent, $E_0 R_I$, to the circuit with the two current sources.
- Calculate how big the current I would be if you connected a resistor $R_4 = 2 \text{ k}\Omega$ to the circuit (or its equivalent).

Example (8.9)

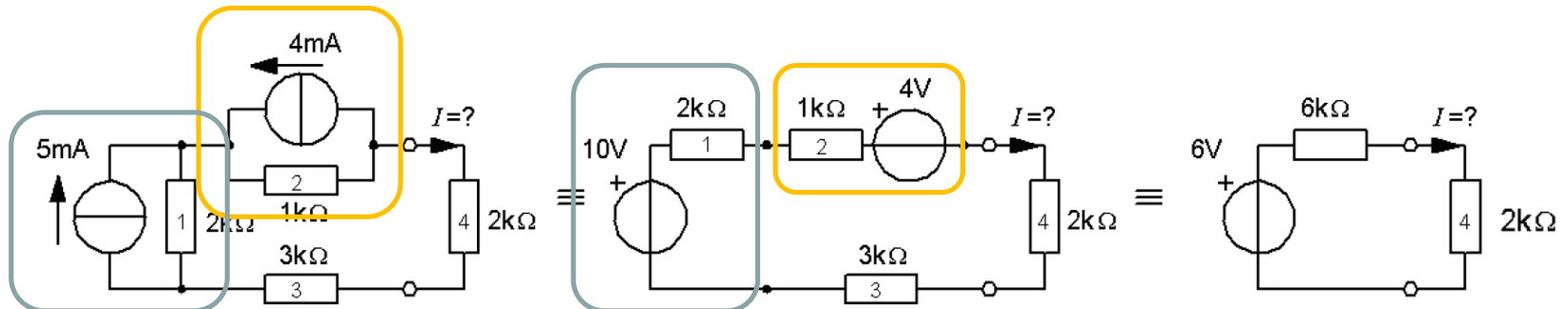


$$5\text{mA} \parallel 2\text{k}\Omega \Leftrightarrow 10\text{V} + 2\text{k}\Omega, \quad 4\text{mA} \parallel 1\text{k}\Omega \Leftrightarrow 4\text{V} + 1\text{k}\Omega \Rightarrow 6\text{V} + 6\text{k}\Omega$$

$$I = \frac{E_0}{R_I + R_L} = \frac{6}{6 + 2} = 0,75 \text{ mA}$$


William Sandqvist william@kth.se

Example (8.11)

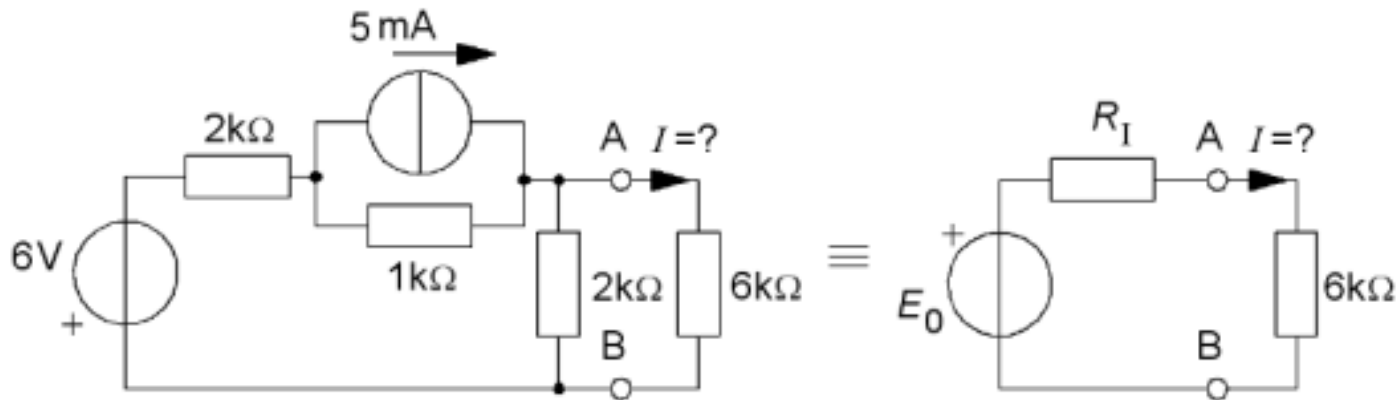

- Derive a Thevenin's equivalent, E_0 R_T , to the circuit with the voltage source and the current source and the three resistors. (The 6 kΩ resistor is not included in the circuit).
- Calculate how big current I would flow in a resistor $R = 6$ kΩ connected to A-B? What direction will the current have?

Example (8.11)

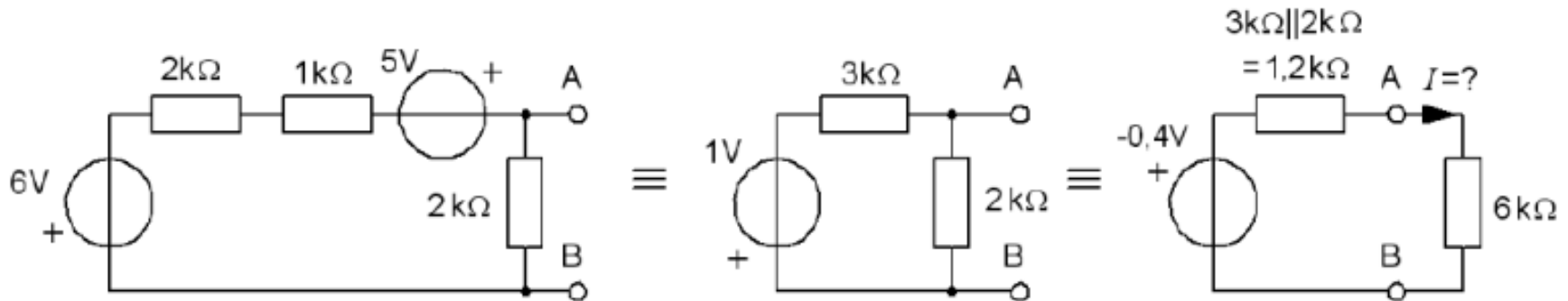

The current source with the $1\text{ k}\Omega$ resistor can be transformed to a voltage source. The circuit then becomes a 1 V voltage source with a voltage divider.

$$E_0 = 1 \frac{2}{3+2} = 0,4\text{ V} \quad R_I = \frac{3 \cdot 2}{3+2} = 1,2\text{ k}\Omega$$




The open circuit voltage is $0,4\text{ V}$, and the internal resistance $3\text{ k}\Omega \parallel 2\text{ k}\Omega = 1,2\text{ k}\Omega$. Note. The voltage source $0,4\text{ V}$ is opposite to the definition of the figure ($-0,4\text{ V}$).

William Sandqvist william@kth.se

(Dependent sources)

Electronics semiconductor components must be described by dependent sources. Such source has an entity E or I that is decided by some other current or voltage in the circuit.

(Eg. Transistor).

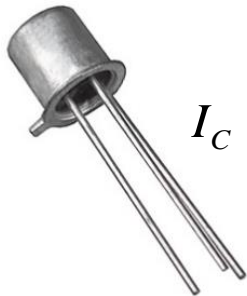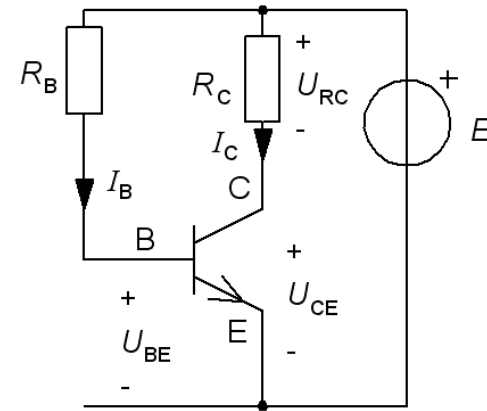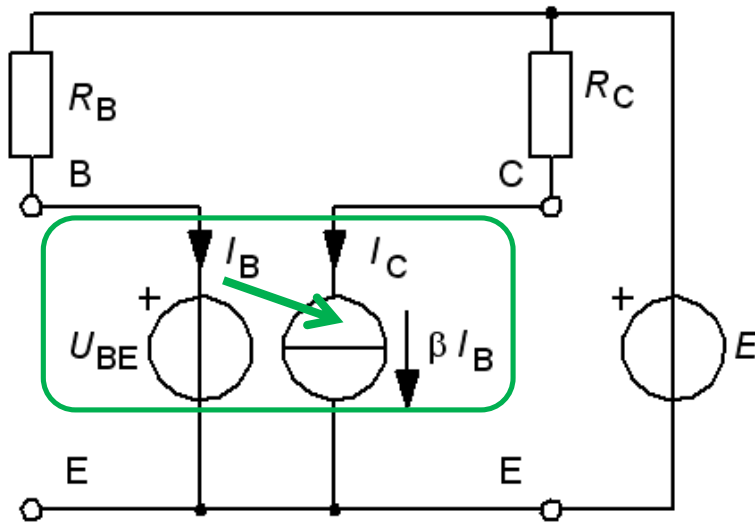


$$I_C = \beta \cdot I_B$$

*This example could be an transistor,
and the calculation of its operating
point ...*

(Eg. Transistor).

- Derive the value of resistor R_B so the voltage drop over resistor R_C will be the **half** of E ?

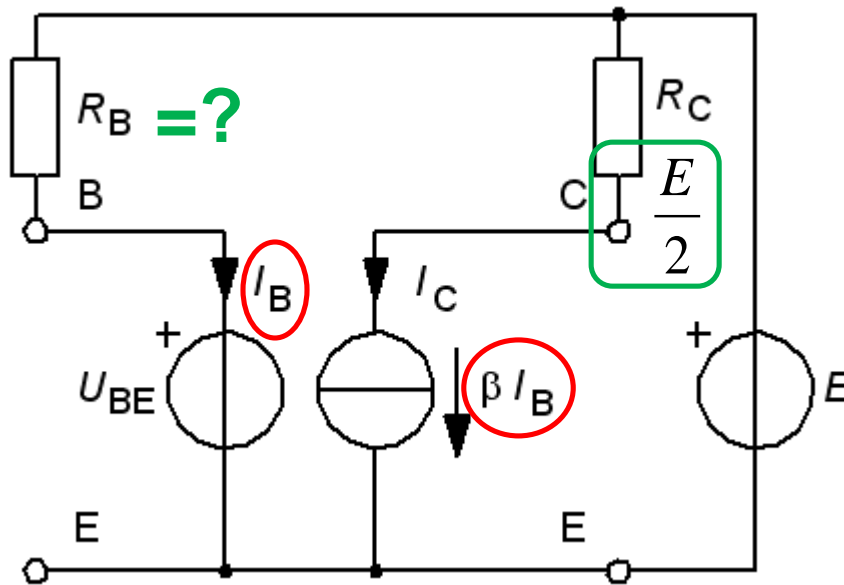The current source I_C is depending on current I_B by the equation: $I_C = \beta \cdot I_B$.



We do not introduce any new special symbols dependent sources.

(Eg. Transistor).

Derive the value of R_B so the voltage drop over R_C will be the **half** of E ?


$$E = 10 \text{ V} \quad U_{BE} = 0,5 \text{ V} \quad \beta = 40 \quad R_C = 10 \text{ k}\Omega$$

$$U_{RC} = R_C \cdot I_{RC} = \frac{E}{2} \Rightarrow I_{RC} = \frac{5}{10 \cdot 10^3} = 0,5 \cdot 10^{-3}$$

$$I_{RC} = \beta \cdot I_B + \frac{E}{2R_O} \Rightarrow I_B = \frac{0,5 \cdot 10^{-3} - 0,1 \cdot 10^{-3}}{40} = 10 \cdot 10^{-6}$$

$$I_B = \frac{E - U_{BE}}{R_B} \Rightarrow R_B = \frac{10 - 0,5}{10 \cdot 10^{-6}} = 950 \text{ k}\Omega$$

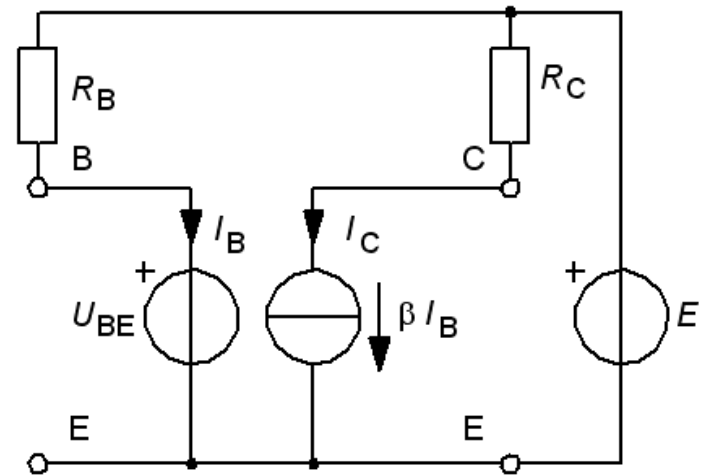Calculations with depending sources can thus take place in a similar way as with independent sources, *but beware ...*




Avoid ...

Do not use the superposition principle with dependent generators. To *reset* a source can break the dependence with the the rest of the circuit.

Do not reset dependent sources to find the internal resistance of a two terminal circuit. To *reset* a source can break the dependence with the the rest of the circuit.

However, it will always work to use calculations on *open* and *shorted* two terminal circuits.


Eg. current depending voltage source ...

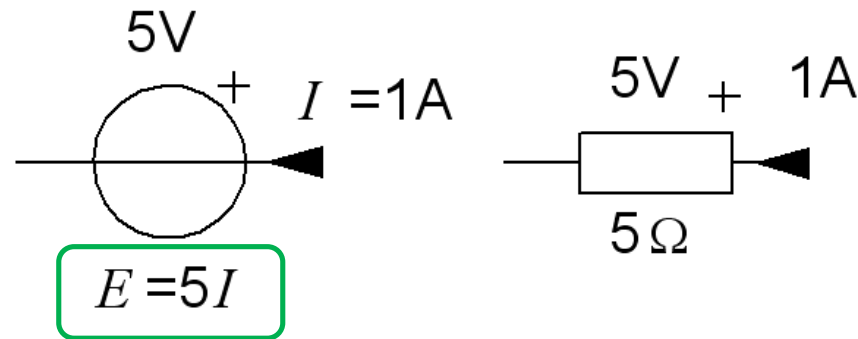

Suppose we got an emf E that in some way is dependent of its own current I , eg. $E = 5 \cdot I$. It will then act as an resistor with the value 5Ω !

If you reset all sources in such a circuit, you will no longer see all resistors that exist in the circuit.


A Spice-simulation

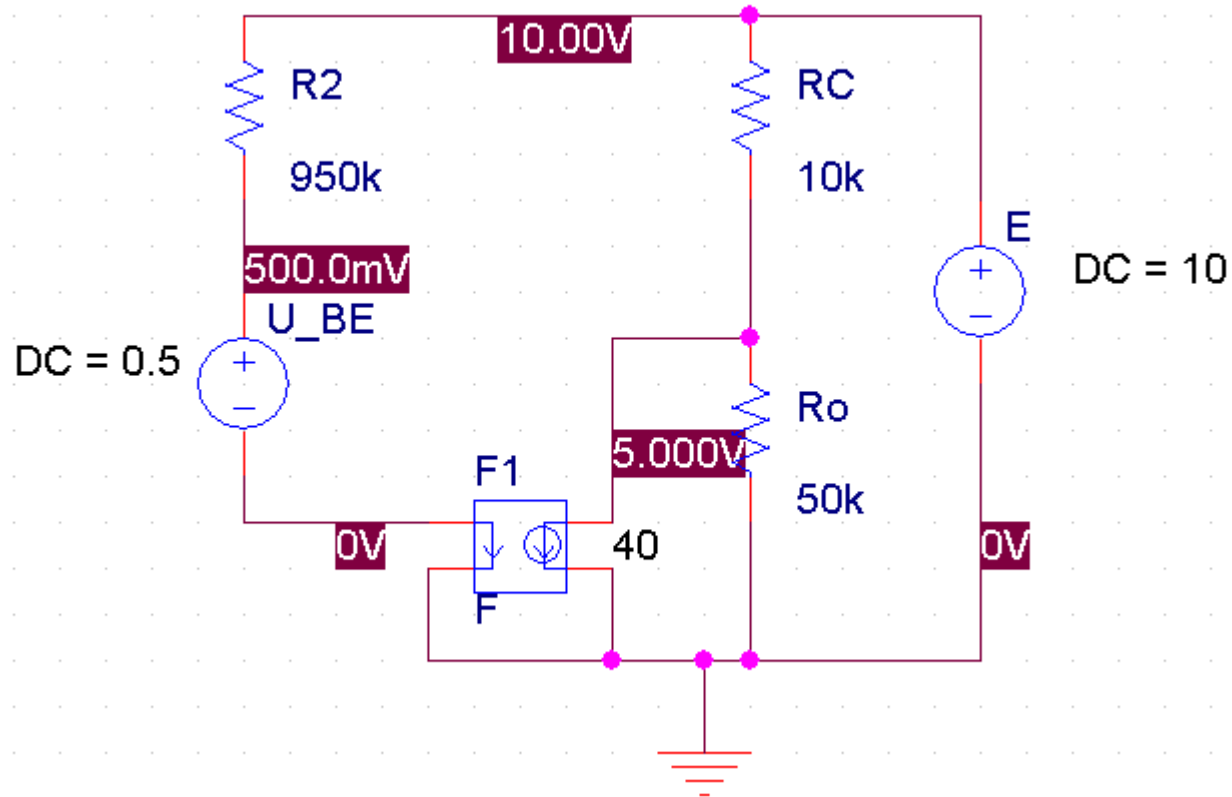


It is possible to simulate circuits with dependent generators.

William Sandqvist william@kth.se

7.4 Depending source

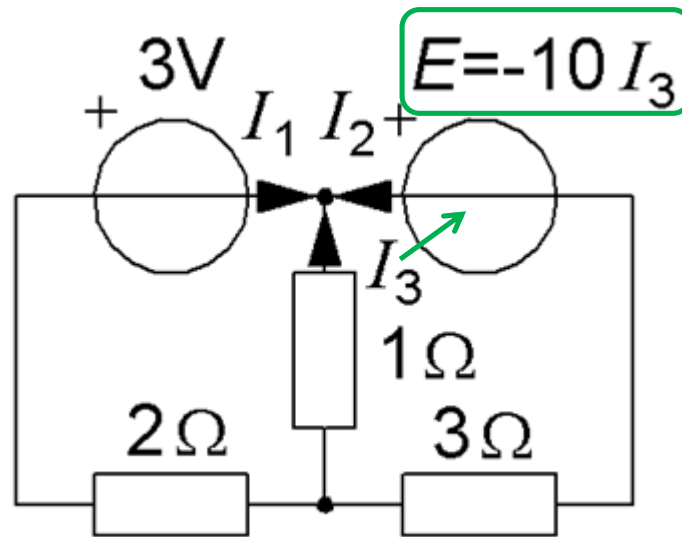

7.4 Depending source

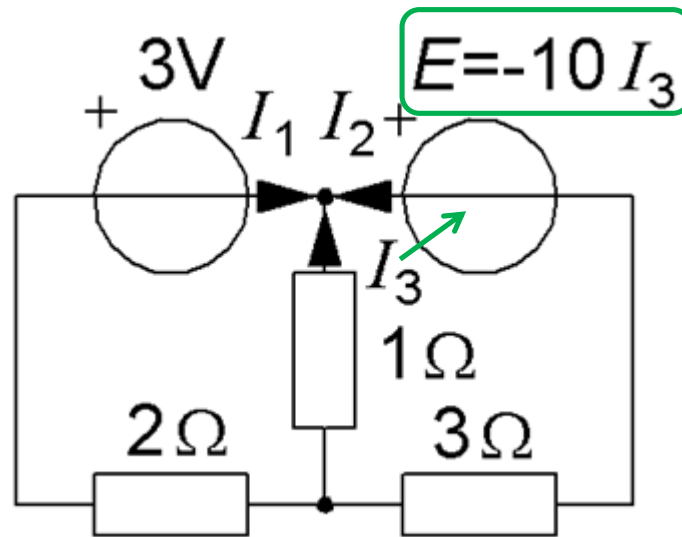

Kirchhoff current law: $I_1 + I_2 + I_3 = 0$

Kirchhoff's voltage law (the mesh with the *not depending emf*):


$$-2I_1 - 3 + 1I_1 = 0 \Leftrightarrow -2I_1 + 0I_2 + 1I_3 = 3$$

Kirchhoff's voltage law (the mesh with the *depending emf*):

$$-1I_3 - (-10I_3) + 3I_2 = 0 \Leftrightarrow 0I_1 + 3I_2 + 9I_3 = 0$$

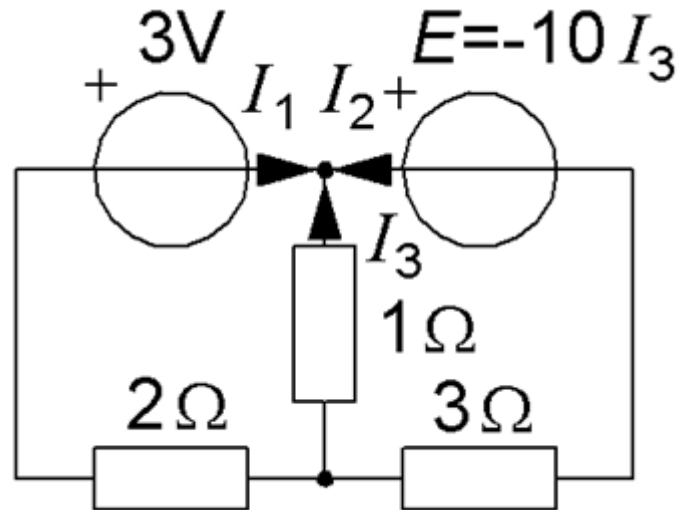7.4 Depending source

$$\begin{aligned} I_1 + I_2 + I_3 &= 0 \\ -2I_1 + 0I_2 + 1I_3 &= 3 \\ 0I_1 + 3I_2 + 9I_3 &= 0 \end{aligned}$$




The values are the same as used throughout the course example.

$$\begin{pmatrix} 1 & 1 & 1 \\ -2 & 0 & 1 \\ 0 & 3 & 9 \end{pmatrix} \cdot \begin{pmatrix} I_1 \\ I_2 \\ I_3 \end{pmatrix} = \begin{pmatrix} 0 \\ 3 \\ 0 \end{pmatrix} \quad I_1 = -2 \quad I_2 = 3 \quad I_3 = -1$$


It is possible to calculate circuits with dependent generators.

William Sandqvist william@kth.se

Node analysis

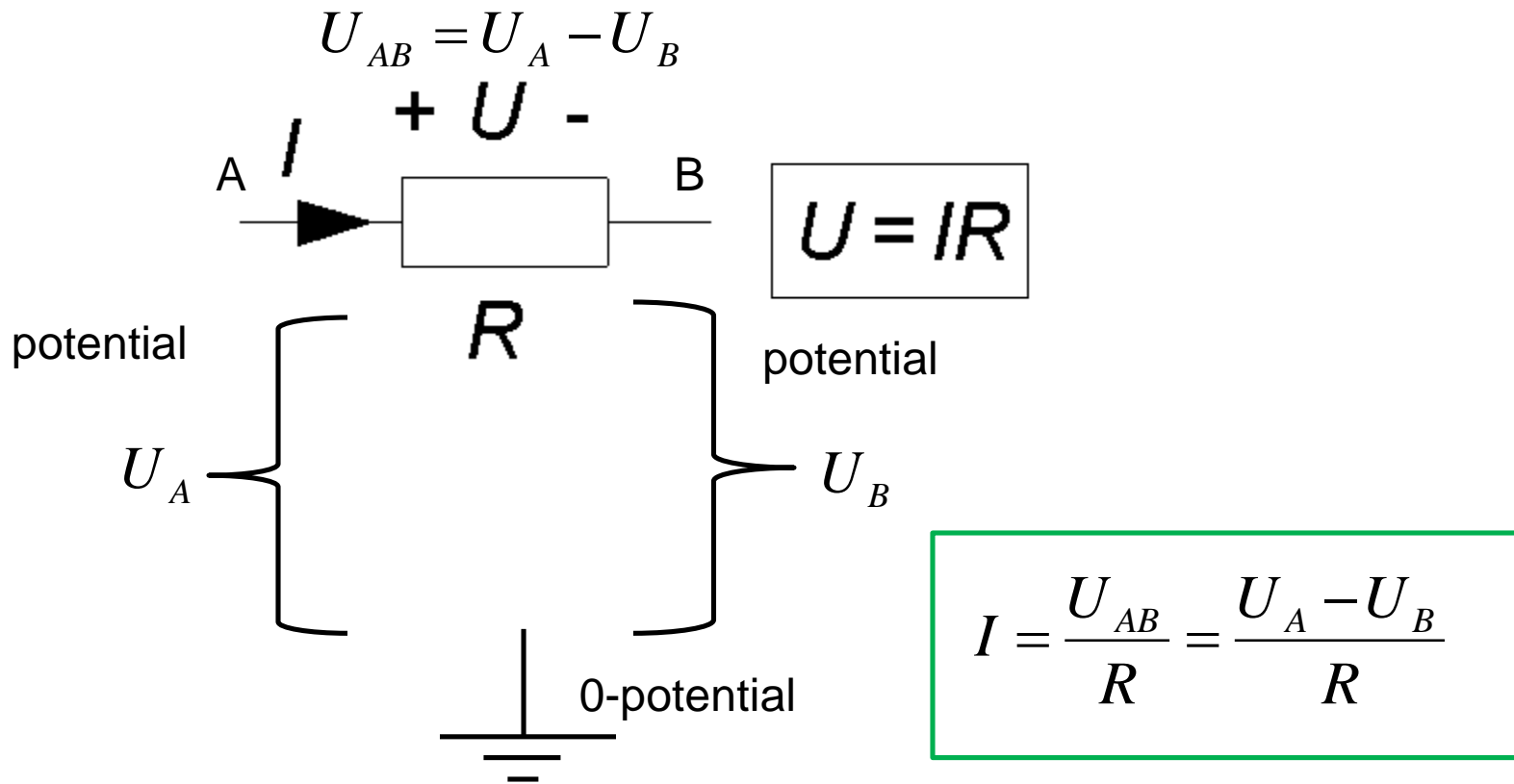


Node analysis

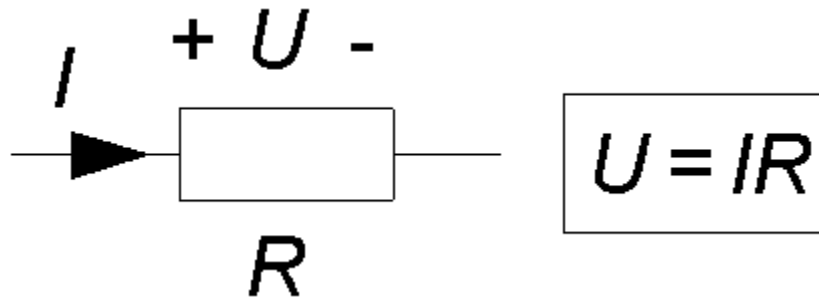


OHM's law

(Current source at node analysis)

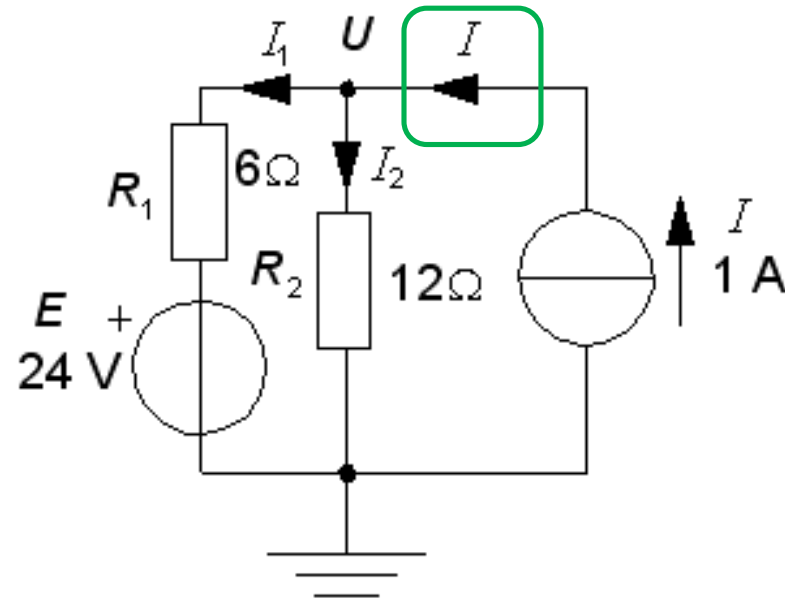

$$I = ?$$


(Current source at node analysis)

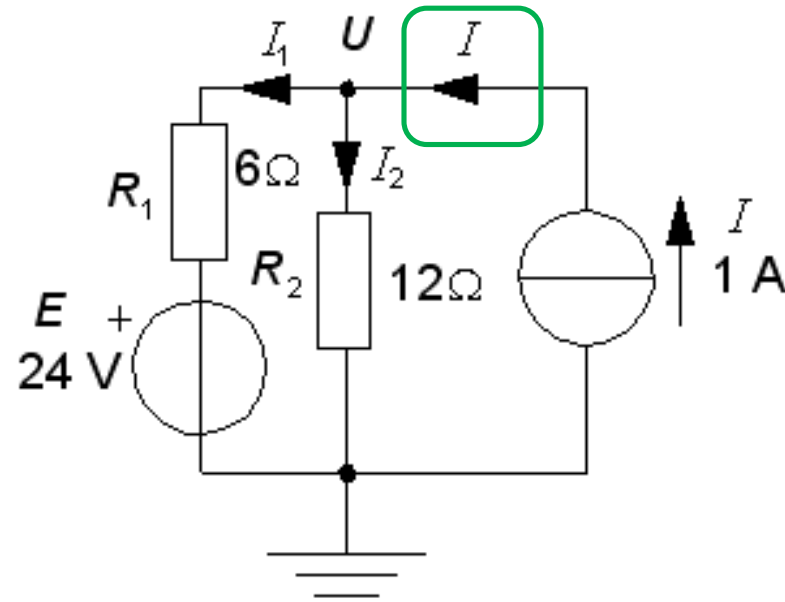

$$I = ? \quad I = 1 \text{ A}$$


(Current source at node analysis)
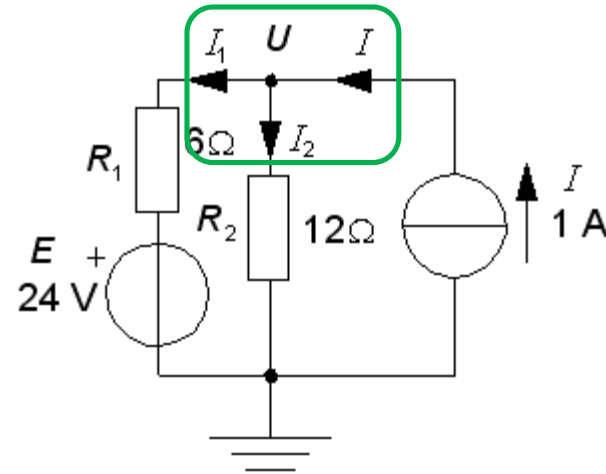
$$-I_1 - I_2 + 1 = 0 \quad I_1 + I_2 = 1$$



(Current source at node analysis)
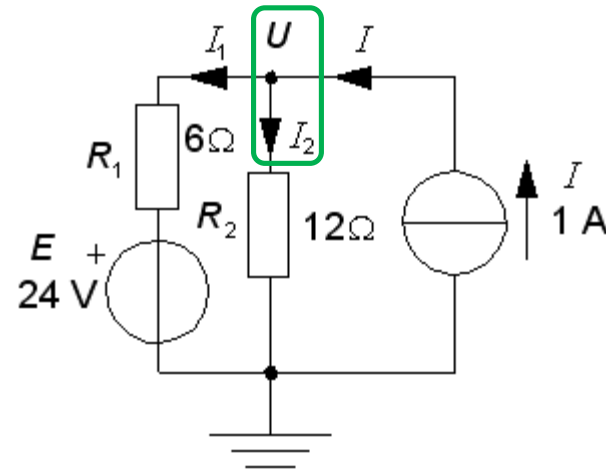
$$-I_1 - I_2 + 1 = 0 \quad I_1 + I_2 = 1$$
$$I_2 = \frac{U - 0}{R_2} = \frac{U}{12}$$




(Current source at node analysis)

$$-I_1 - I_2 + 1 = 0 \quad I_1 + I_2 = 1$$

$$I_2 = \frac{U - 0}{R_2} = \frac{U}{12}$$
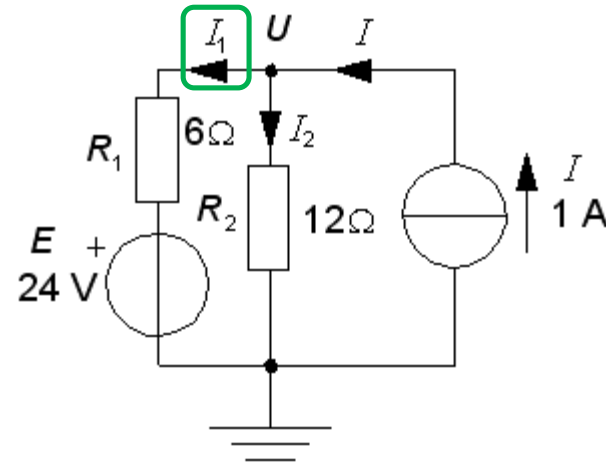
$$I_1 = \frac{U - E}{R_1} = \frac{U - 24}{6}$$



(Current source at node analysis)


$$-I_1 - I_2 + 1 = 0 \quad I_1 + I_2 = 1$$

$$I_2 = \frac{U - 0}{R_2} = \frac{U}{12}$$

$$I_1 = \frac{U - E}{R_1} = \frac{U - 24}{6}$$

$$1 = \frac{U}{12} + \frac{U - 24}{6} = \frac{2 \cdot U - 48 + U}{12}$$

$$U = 20 \text{ V}$$

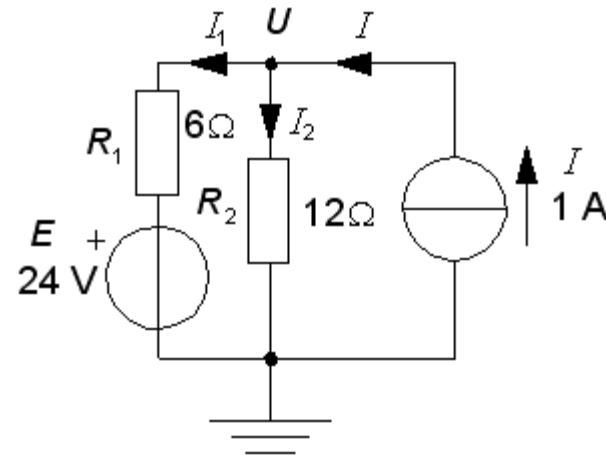


$$\Leftrightarrow 12 = 3 \cdot U - 48$$

(Node analyses – currents)

$$I_2 = \frac{20}{12} = 1,67$$

$$I_1 = \frac{20 - 24}{6} = -0,67$$
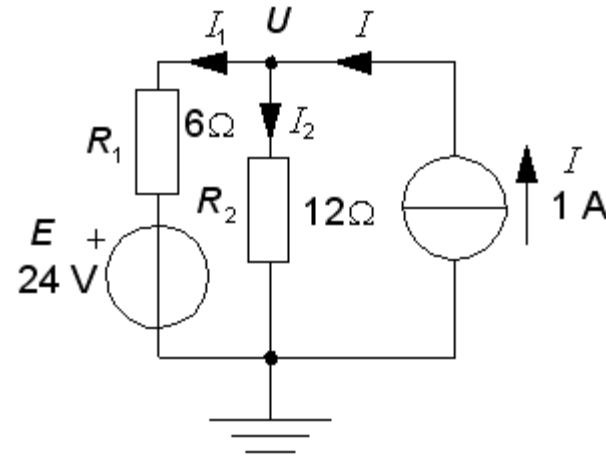
$$\text{Check: } I_1 + I_2 = 1 \Rightarrow -0,67 + 1,67 = 1$$



William Sandqvist william@kth.se