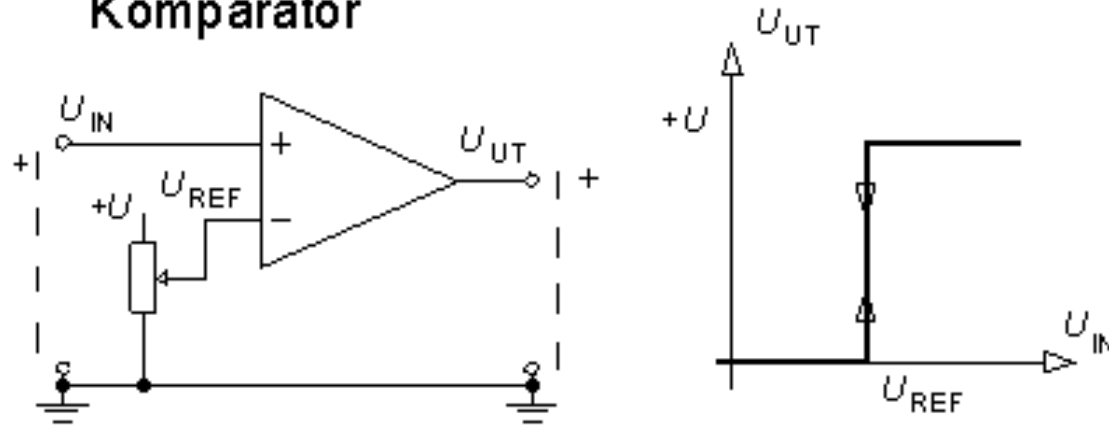


Comparator an 1 bit AD-converter


Komparator



A comparator is a sensitive amplifier for the *difference* between input voltages. The slightest positive difference means that the output get (1) or negative difference get (0).



The comparator can be used to accurately determine when a voltage U_{IN} pass a certain reference voltage U_{REF} .

PIC-processor comparators

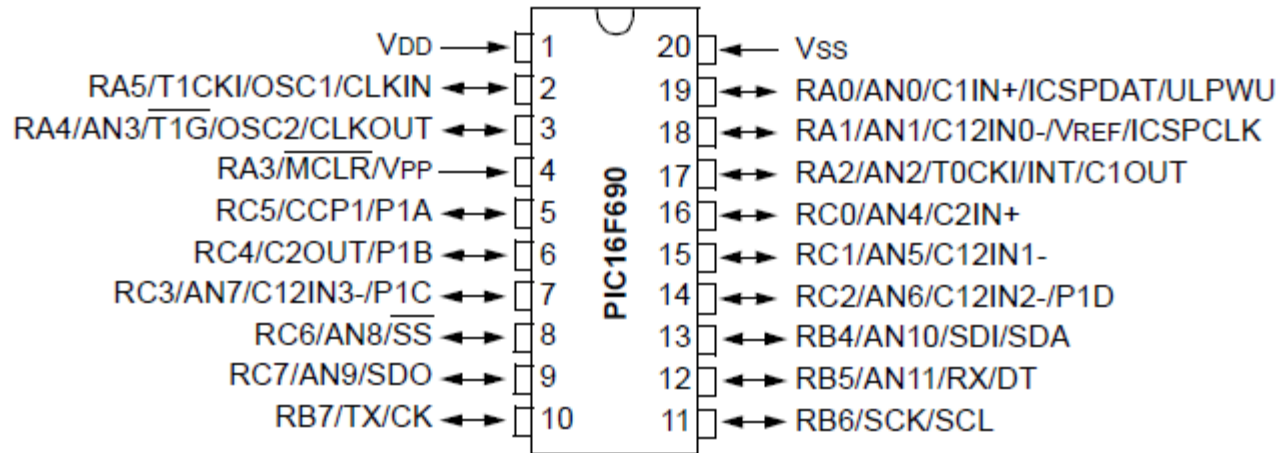

PIC16F690 has *two* internal analog comparators. They can be connected to different pins or to internal units. The comparator is a very versatile component..

Many configuration options!

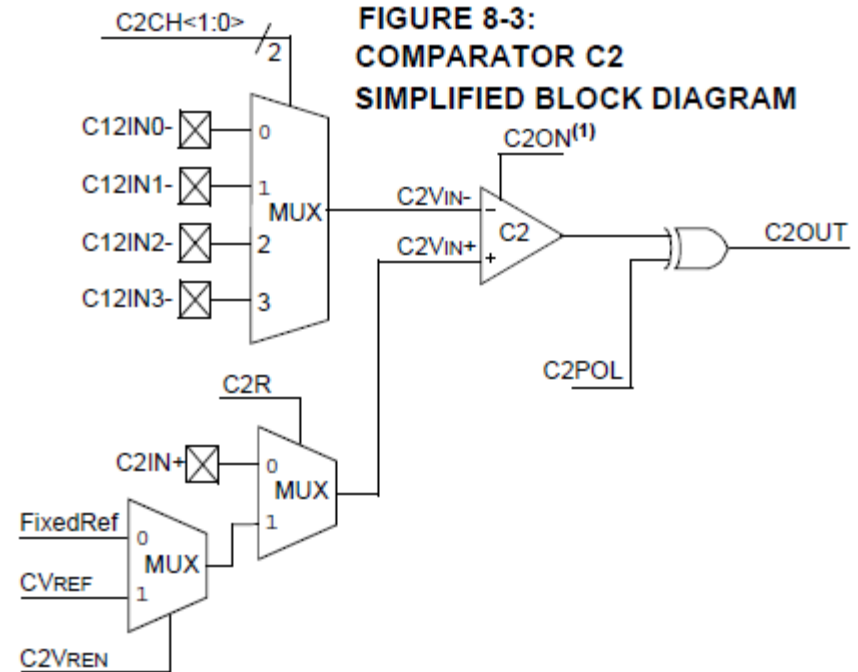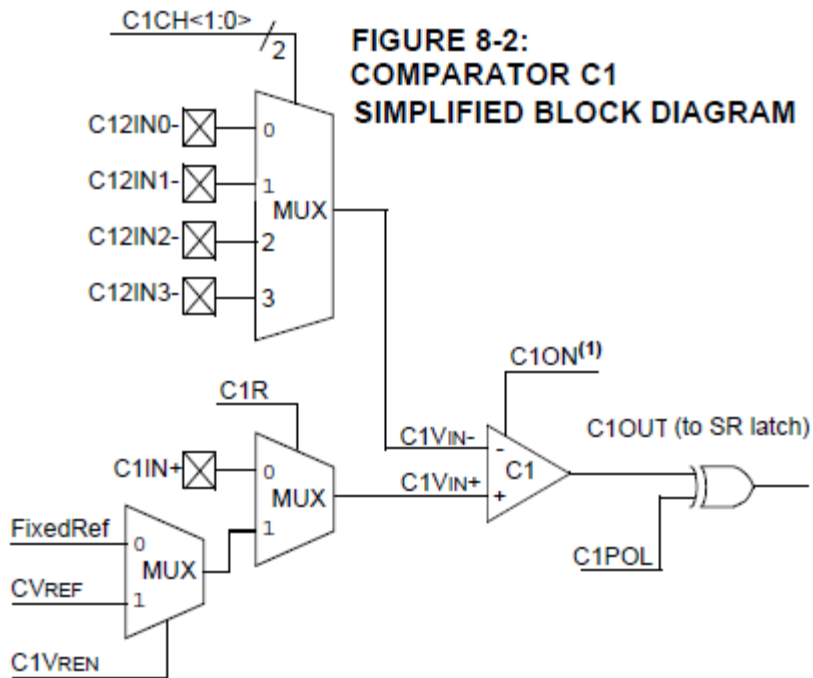

C1:s and C2:s outputs are accessible internally, but can also be connected to external pins (eg. C2OUT → **RC4**).

Analog function?

One choose to use the "analog" function on pins with the ANSEL registers. **PIC16F690:**

REGISTER 4-3: ANSEL: ANALOG SELECT REGISTER

R/W-1	R/W-1	R/W-1	R/W-1	R/W-1	R/W-1	R/W-1	R/W-1
ANS7	ANS6	ANS5	ANS4	ANS3	ANS2	ANS1	ANS0
bit 7							bit 0
RC3	RC2	RC1	RC0	RA4	RA2	RA1	RA0

REGISTER 4-4: ANSELH: ANALOG SELECT HIGH REGISTER

U-0	U-0	U-0	U-0	R/W-1	R/W-1	R/W-1	R/W-1
—	—	—	—	ANS11	ANS10	ANS9	ANS8
bit 7							bit 0
				RB5	RB4	RC7	RC6

Default-setting is the analog function – so in practice choose to remove analogous function when you need digital.

Control registers

REGISTER 8-1: CM1CON0: COMPARATOR C1 CONTROL REGISTER 0

R/W-0	R-0	R/W-0	R/W-0	U-0	R/W-0	R/W-0	R/W-0
C1ON	C1OUT	C1OE	C1POL	—	C1R	C1CH1	C1CH0
bit 7							bit 0


REGISTER 8-2: CM2CON0: COMPARATOR C2 CONTROL REGISTER 0

R/W-0	R-0	R/W-0	R/W-0	U-0	R/W-0	R/W-0	R/W-0
C2ON	C2OUT	C2OE	C2POL	—	C2R	C2CH1	C2CH0
bit 7							bit 0

REGISTER 8-3: CM2CON1: COMPARATOR C2 CONTROL REGISTER 1

R-0	R-0	U-0	U-0	U-0	U-0	R/W-1	R/W-0
MC1OUT	MC2OUT	—	—	—	—	T1GSS	C2SYNC
bit 7							bit 0

CMP2 at lab

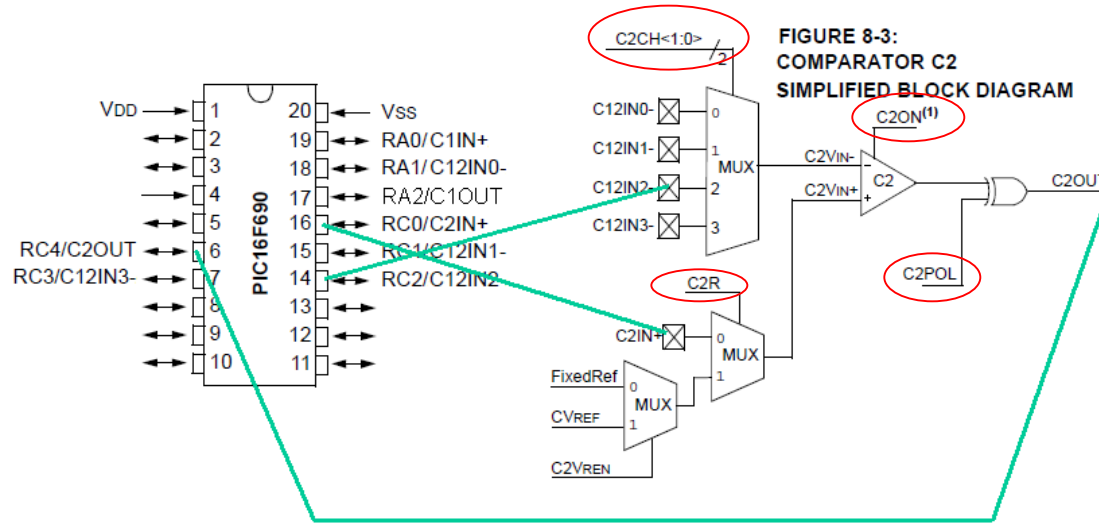


REGISTER 8-2: CM2CON0: COMPARATOR C2 CONTROL REGISTER 0

R/W-0	R-0	R/W-0	R/W-0	U-0	R/W-0	R/W-0	R/W-0
C2ON	C2OUT	C2OE	C2POL	—	C2R	C2CH1	C2CH0
bit 7							bit 0

1 - 1 0 - 0 1 0

**C2CH.0=0 ; C2CH.1=1 ; C2R=0 ; C2POL=0 ; C2OE=1 ;
C2ON=1 ;**

CMP2 at lab


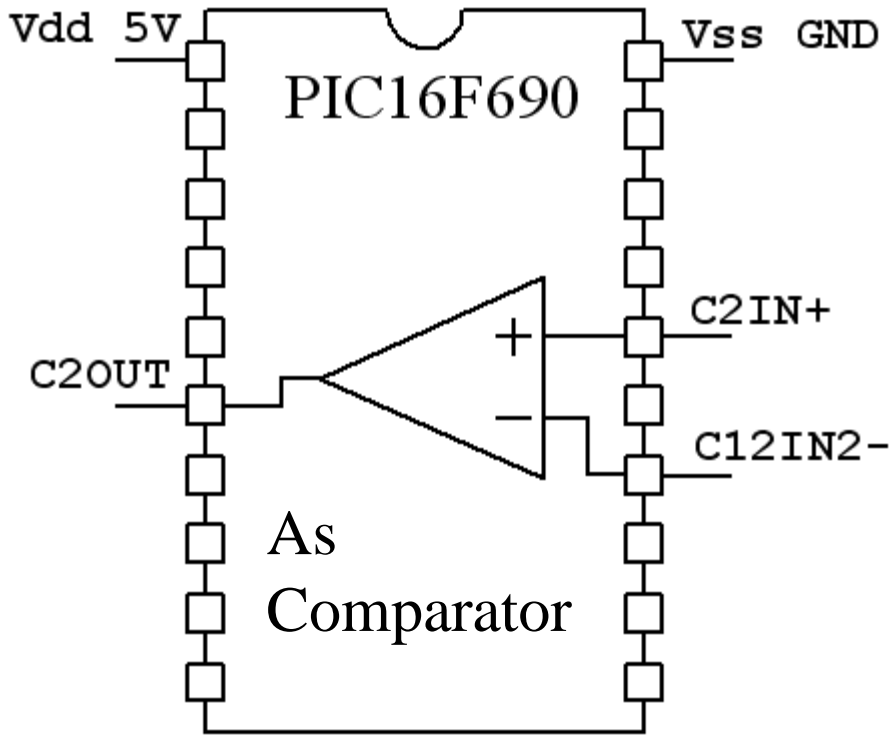


```
C2CH.0=0; // C12IN2-
C2CH.1=1; // C12IN2-
C2R=0; // C2IN+
C2POL=0; // not invert
SR1=0; // no SR-latch
C2OE=1; // out to pin
C2ON=1; // C2 on
ANSEL.4=1; // analog
ANSEL.6=1; // analog
TRISC.0=1; // RC0 input
TRISC.2=1; // RC2 input
TRISC.4=0; // RC4 output
```

With these settings we use Comparator 2 as independent stand alone component!




In gray
– default setting

Lab: try a Comparator

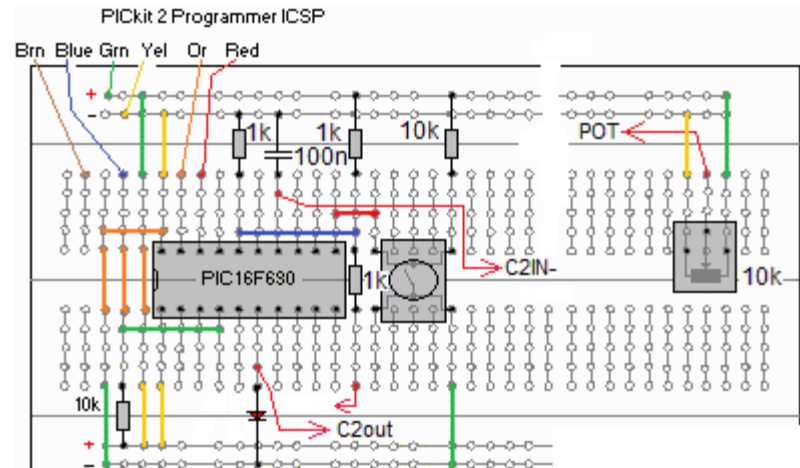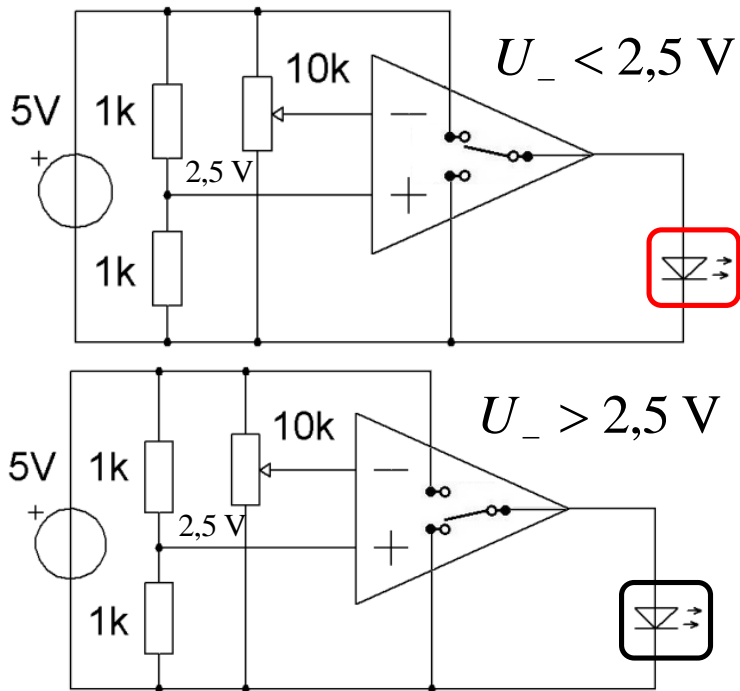


When the voltage at the terminal on the 10k potentiometer is passing reference voltage 2.5V (5V divided by two) the comparator output turns on. The trip point is very distinct.

Lab: try a Schmitt-trigger

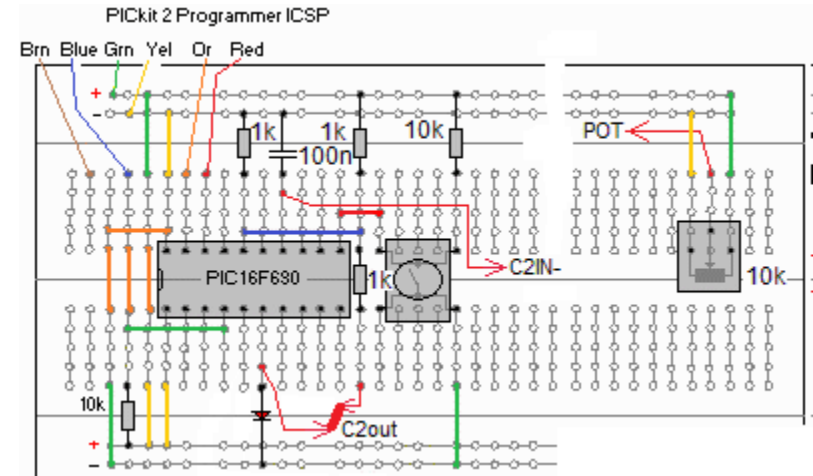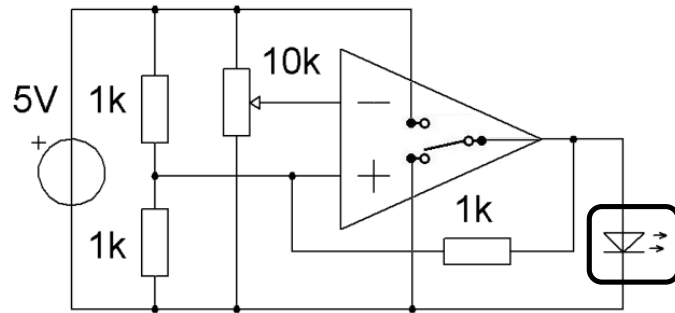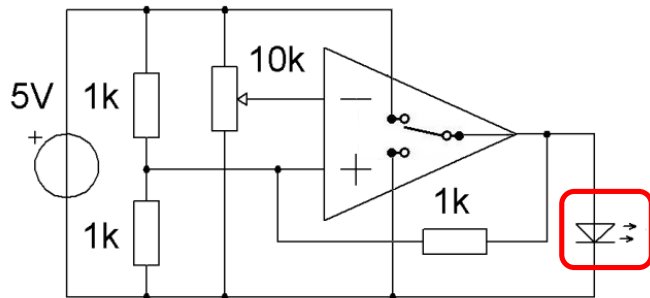


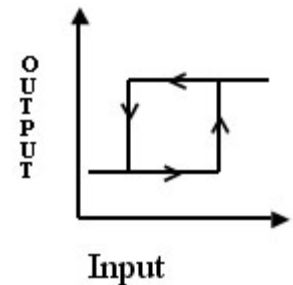
A third 1k resistor from the output to the "+" input shifts the reference level so that we must now turn more to change the output. There are dual threshold for on and off. The function will be more secure. The connection is called the Schmitt trigger and the phenomenon of dual thresholds is called hysteresis.



Hysteresis.




Otto Schmitt

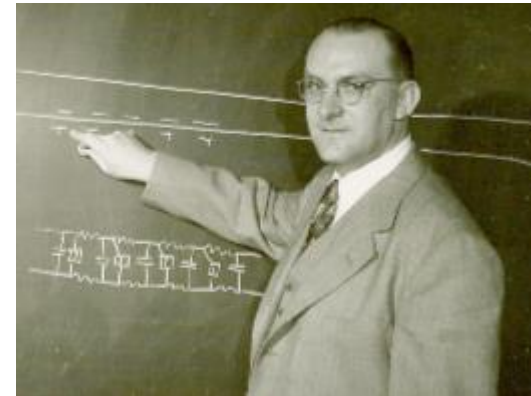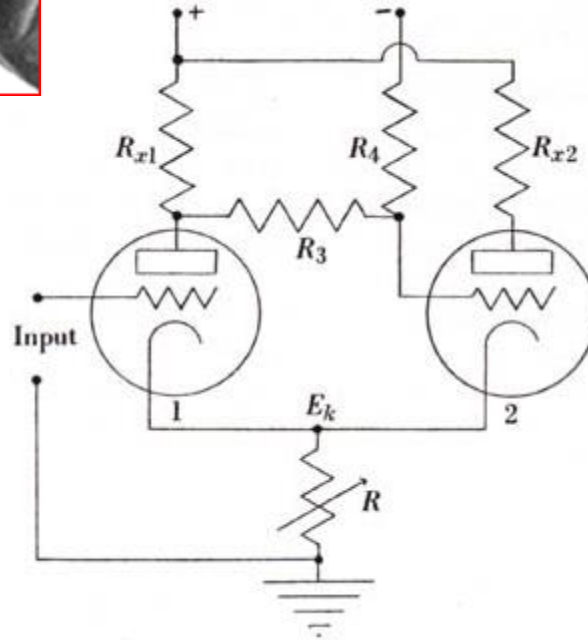


A schmitt-trigger has "snap action". When you have passed the trip-point the process is no longer possible to prevent ...

Threshold voltages? (10.10)

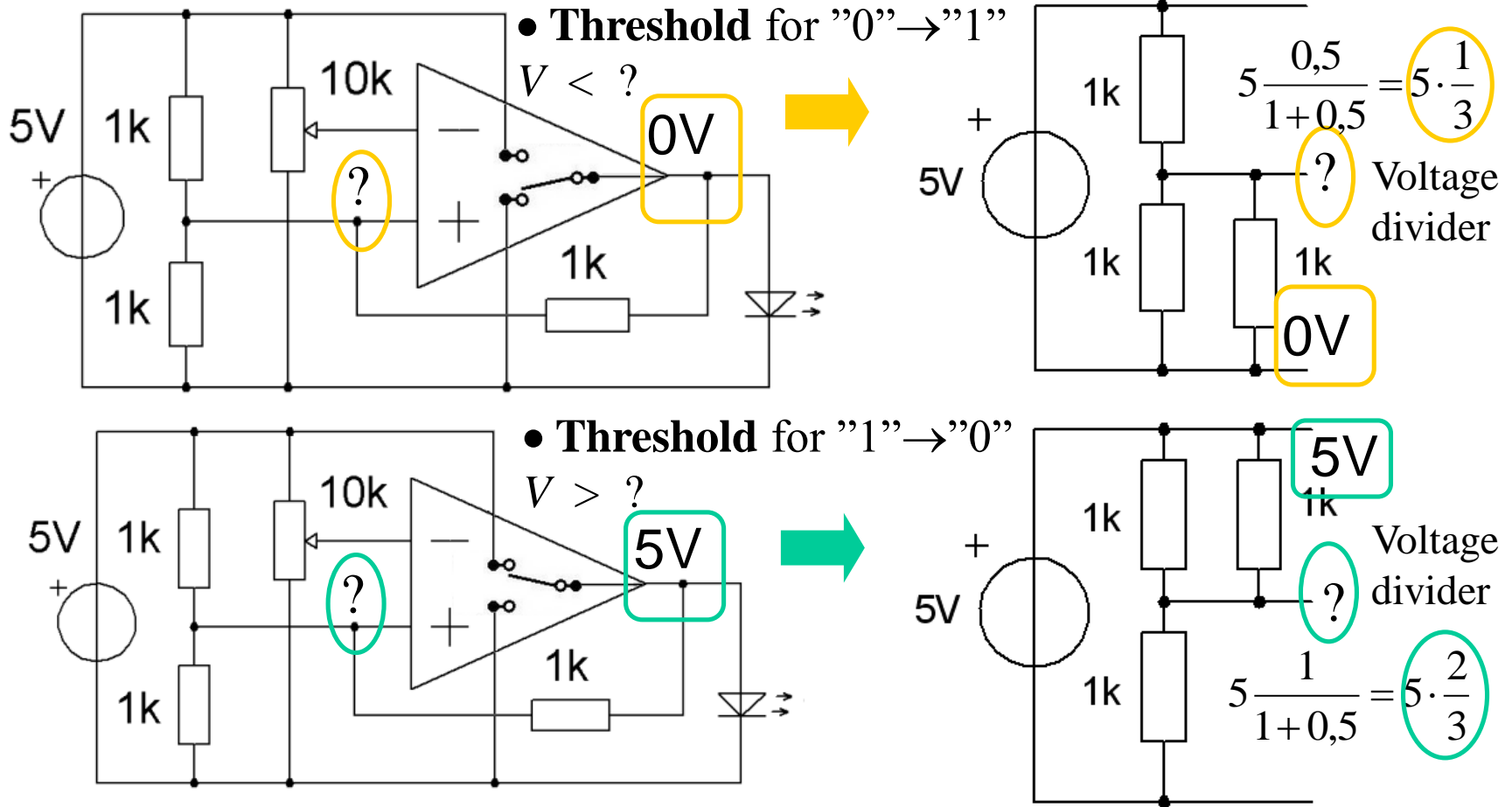


RC-oscillator

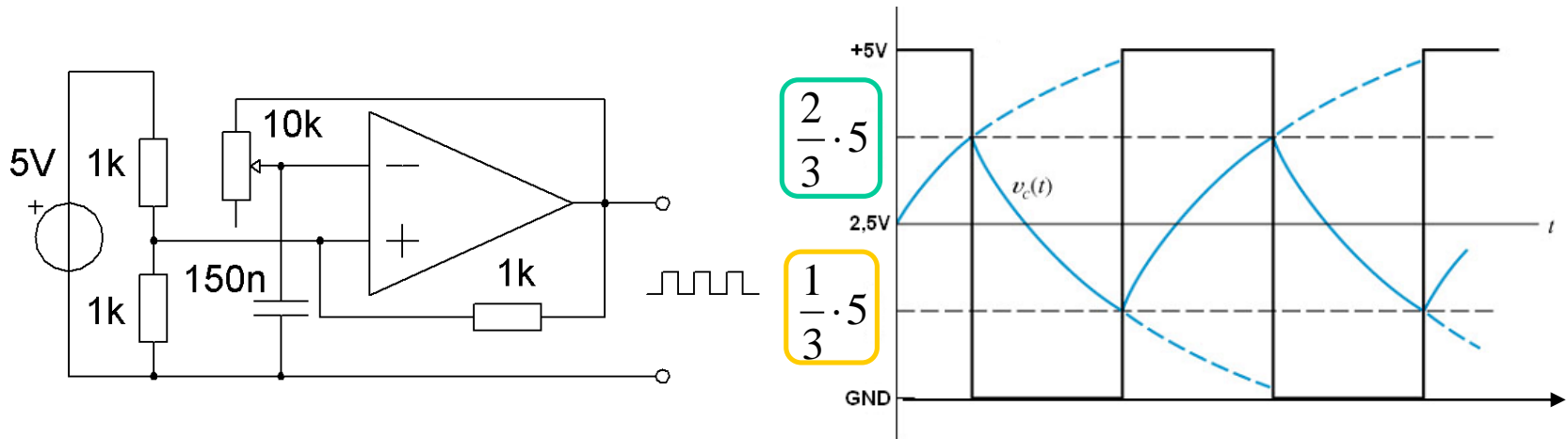


The comparator charges the capacitor to the upper trigger level, then turn the output on and discharges the capacitor to the lower trigger level. The frequency of the output of the comparator depends on the product $R \cdot C$. As C is constant **R will determine the frequency.**

Lab: try RC-oscillator

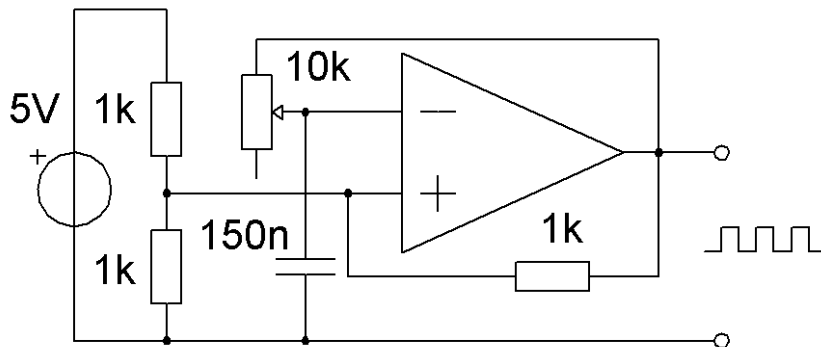

Schmitt trigger is continuously charging and discharging the capacitor voltage between the two threshold levels.

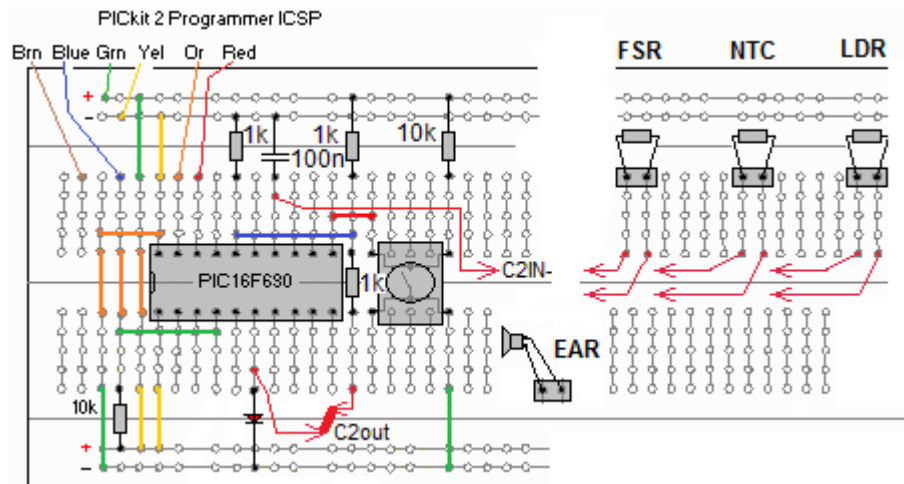Along with the earphone, we now have a buzzer!





Sensors

Try some resistive sensors ...



NTC-Thermistor

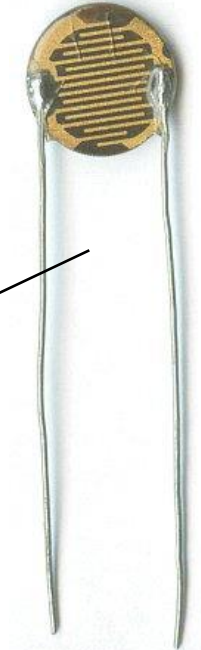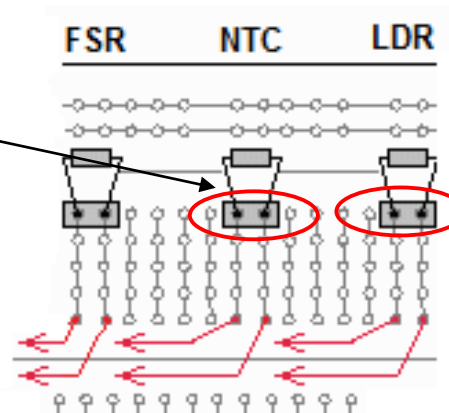


LDR-Photo resistor

We will measure frequency with the PIC-processor's CCP-unit later in the course ...


Sensors

Try some resistive sensors ...

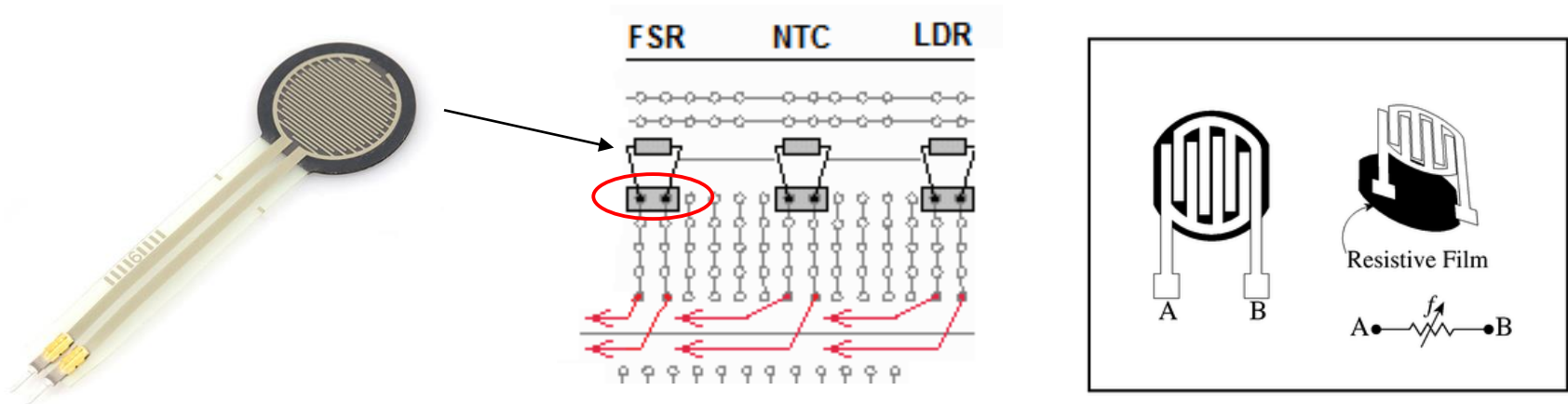


FSR-Force Sensitive Resistor, press between your fingers.

Simulate the RC-oscillator

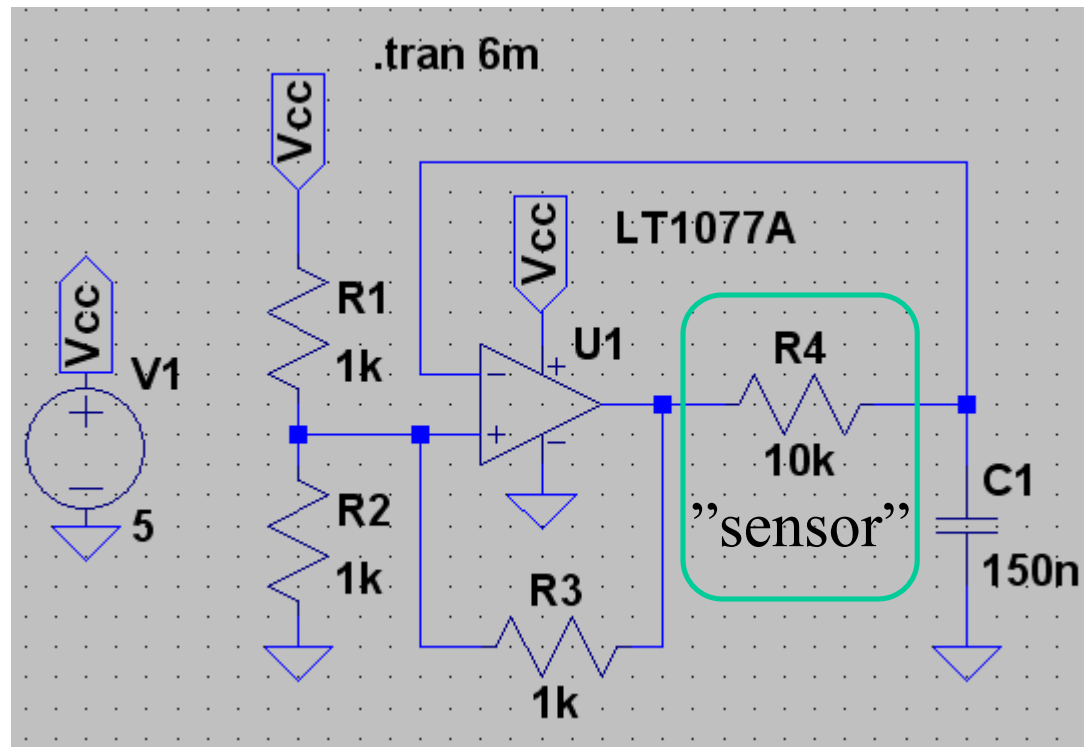


Simulate RC-oscillator

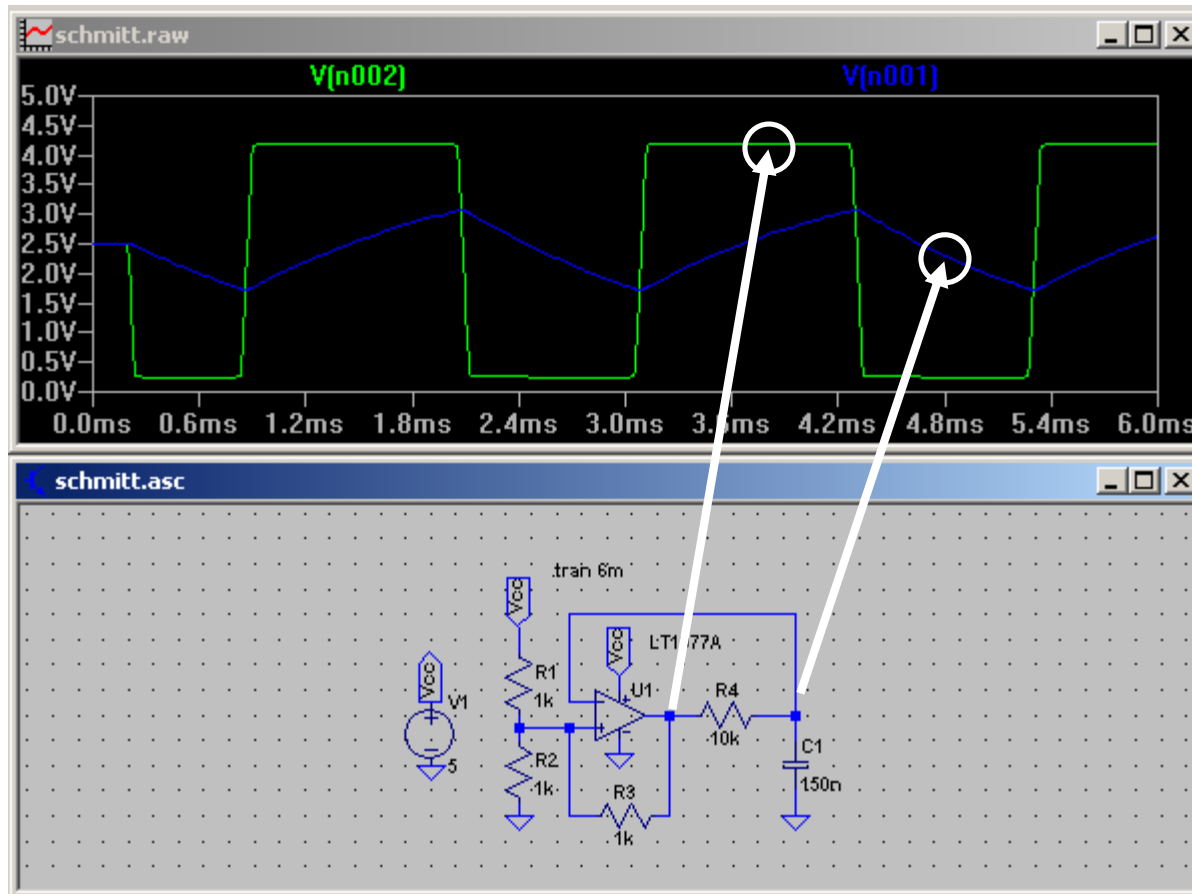

William Sandqvist william@kth.se

A more stable RC-oscillator

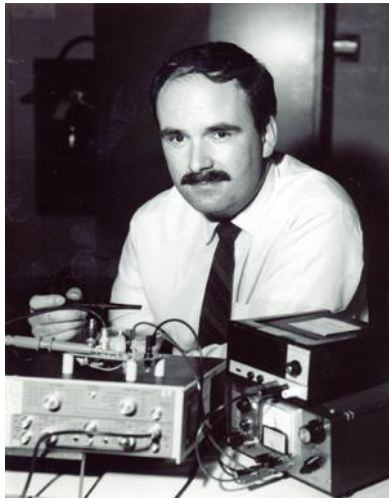

Hans Camenzind
designer of the
555 timer
(1934-2002)

Signetics 1970





Google

555 timer





About **2 130 000** results
(0,30 sekonds)



555 as RC-oscillator

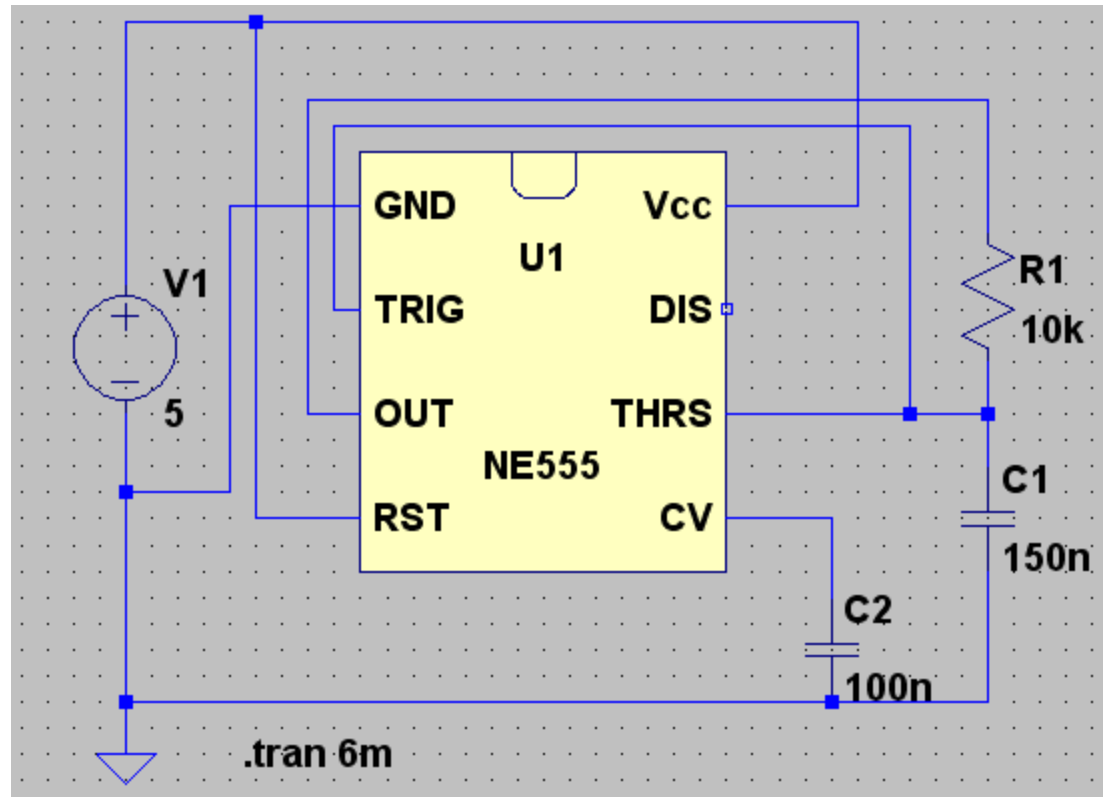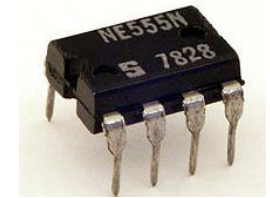

555 RC-oscillator

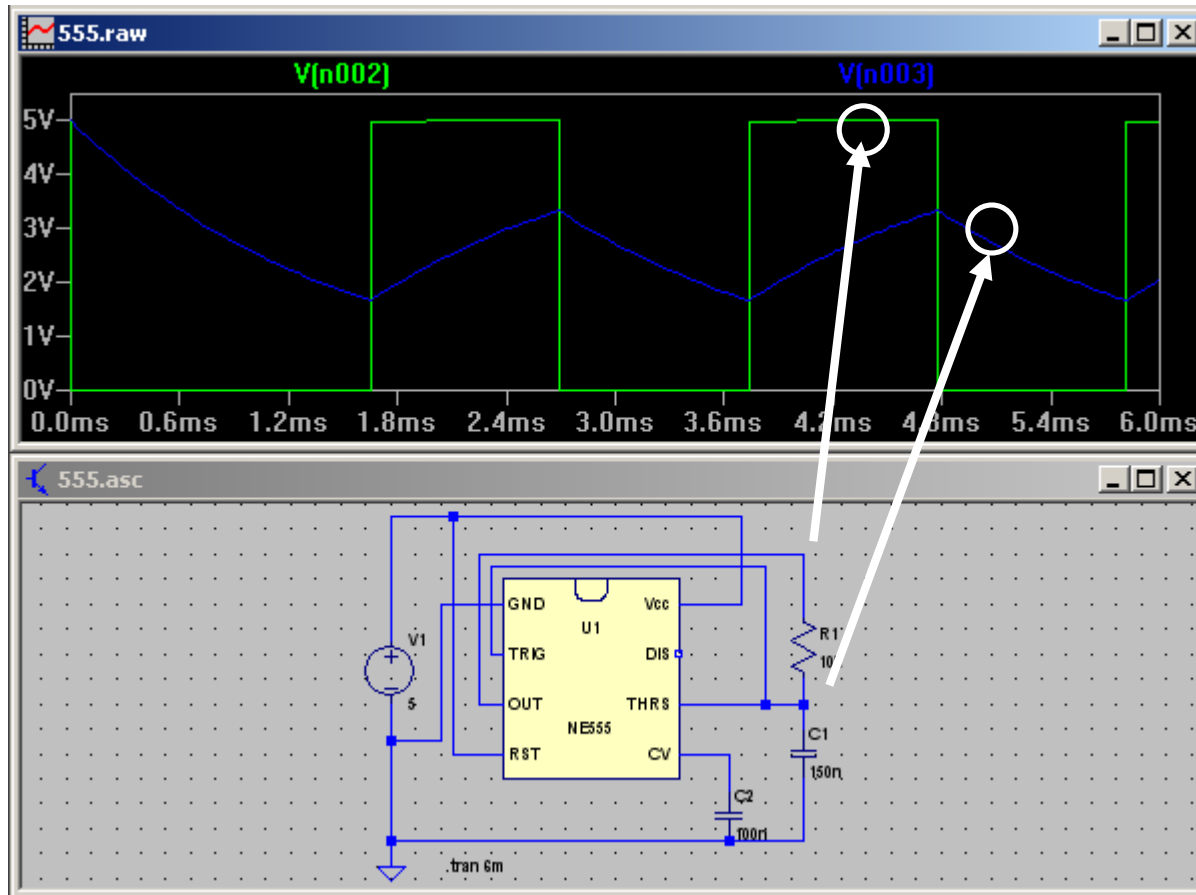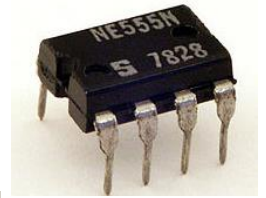


The 555 inside story

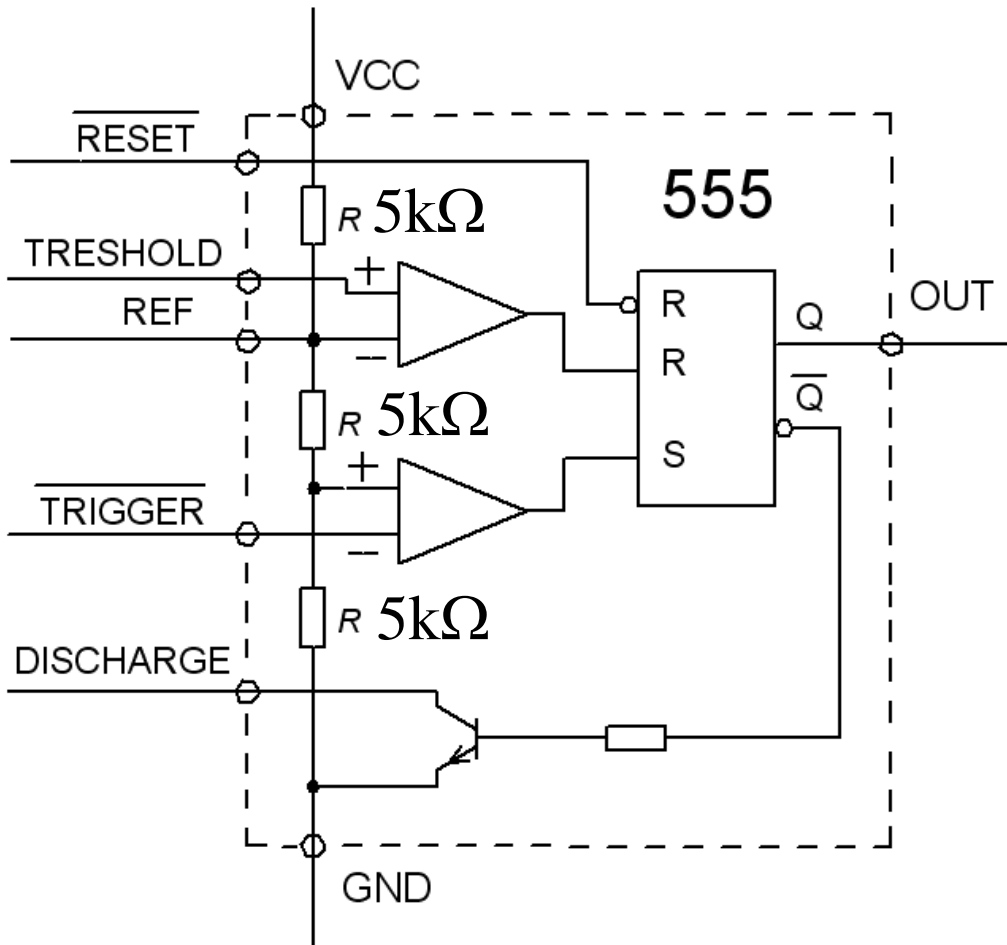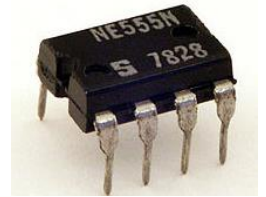


**Two
comparators
and one
SR-latch.**

555 as Schmitt-trigger

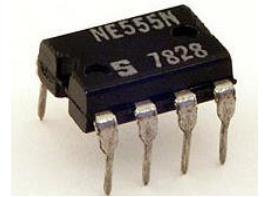

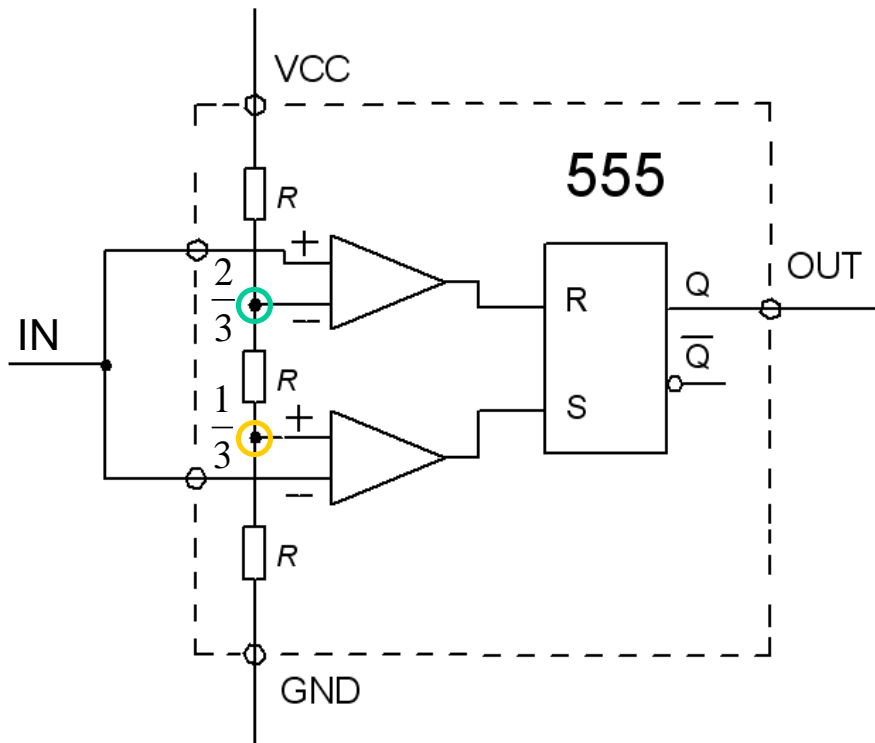With these connections the 555 becomes a Schmitt-trigger with the threshold levels $1/3$ and $2/3$ of the supply voltage.




This circuit has better "performance" than the single comparator connected as Schmitt trigger we have shown previously.

William Sandqvist william@kth.se

PIC-processor SR-latch

SR-latch **output** can be read by the program (C1OUT, C2OUT), or connected directly to the chip pins (C1OUT/RA2, C2OUT/RC4).

**FIGURE 8-7:
SR LATCH SIMPLIFIED BLOCK DIAGRAM**

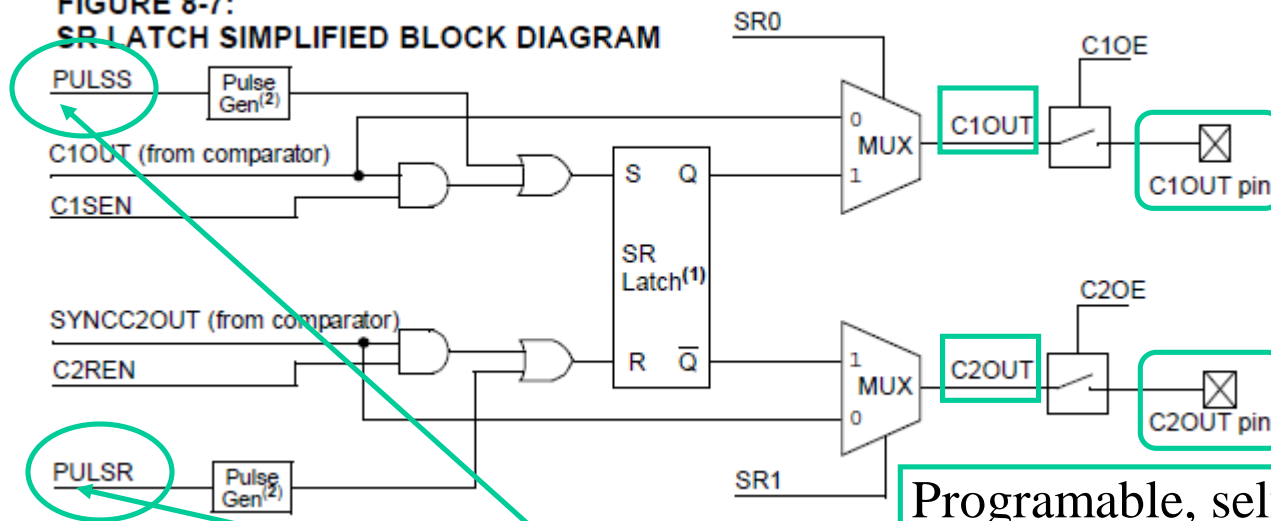


Programmable, self resetting, bits to generate pulses on S and R.

REGISTER 8-4: SRCON: SR LATCH CONTROL REGISTER

R/W-0	R/W-0	R/W-0	R/W-0	R/S-0	R/S-0	U-0	U-0
SR1 ⁽²⁾	SR0 ⁽²⁾	C1SEN	C2REN	PULSS	PULSR	—	—
bit 7							bit 0

PIC-processorns SR-latch

SR-latches **inputs** can be configured to connect to the comparators.

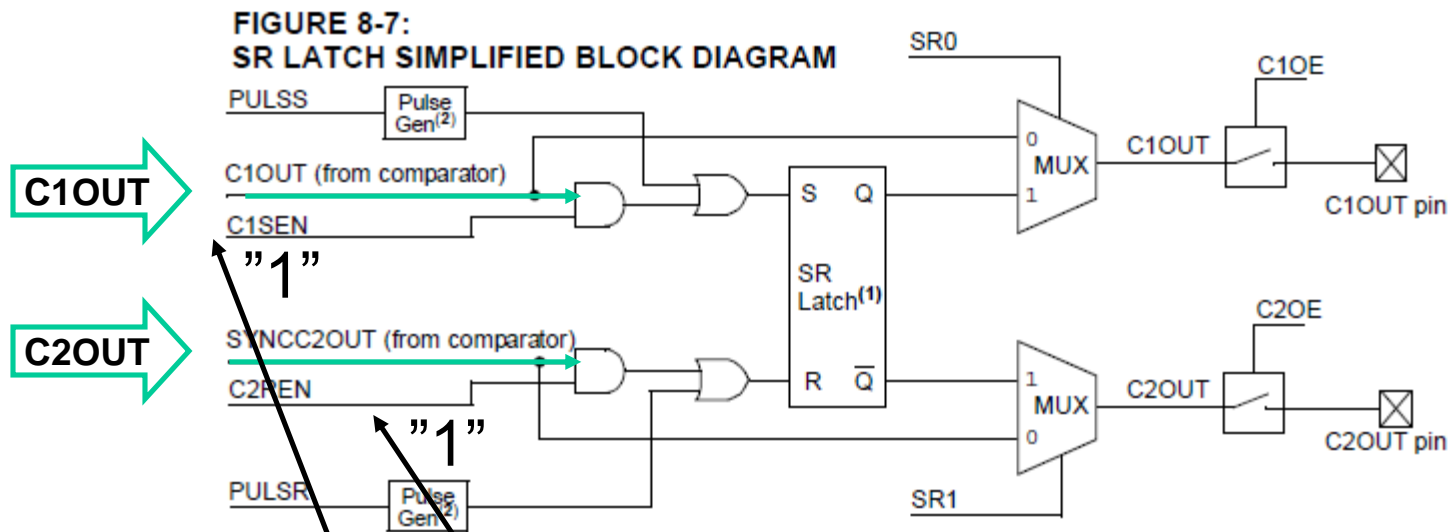


REGISTER 8-4: SRCON: SR LATCH CONTROL REGISTER

R/W-0	R/W-0	R/W-0	R/W-0	R/S-0	R/S-0	U-0	U-0	
SR1 ⁽²⁾	SR0 ⁽²⁾	C1SEN	C2REN	PULSS	PULSR	—	—	
bit 7							bit 0	

William Sandqvist william@kth.se


PIC-processor as oscillator

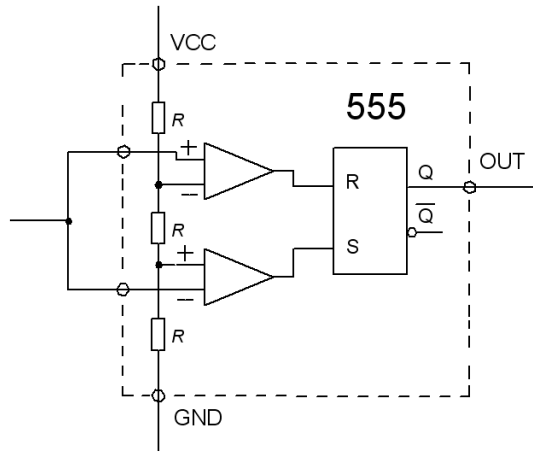PIC-processor two comparators and SR-latch can be configured as a RC-oscillator, "555 style"



A stable oscillator is needed when it is C that the sensor is – as the capacitive sensing.

Oscillator Circuit




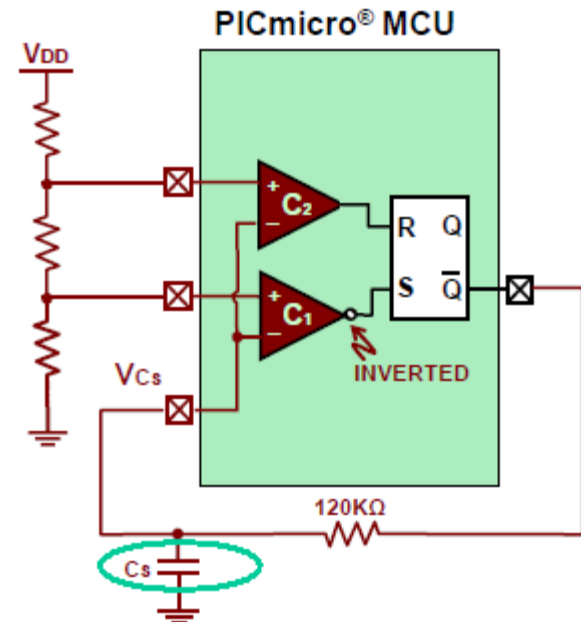






Touch-control

Vandal proof button at the pedestrian crossing!

Oscillator Circuit

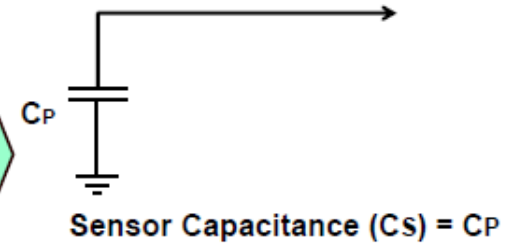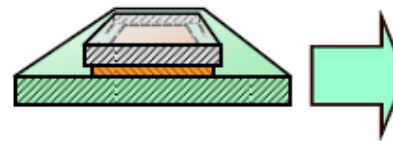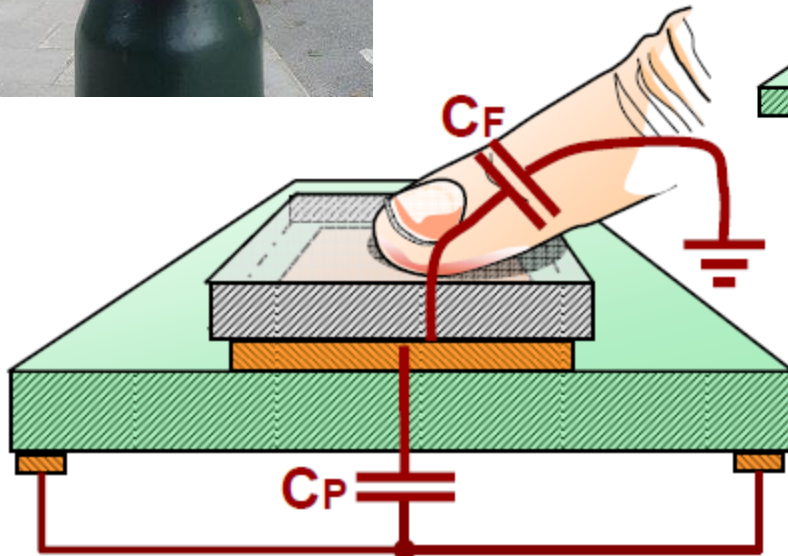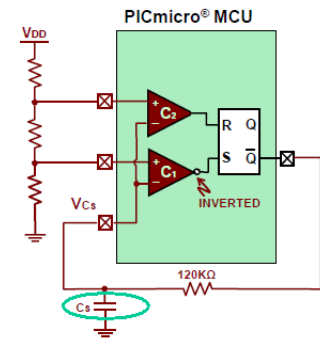



Sensor Capacitance (C_s) = C_P

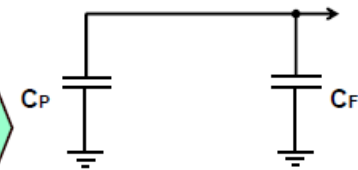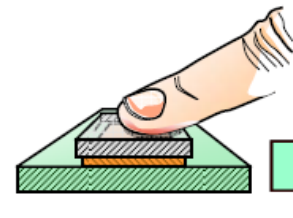


Sensor Capacitance (C_s) = $C_P + C_F$

Touch-control

Moore contacts – Keyboard.

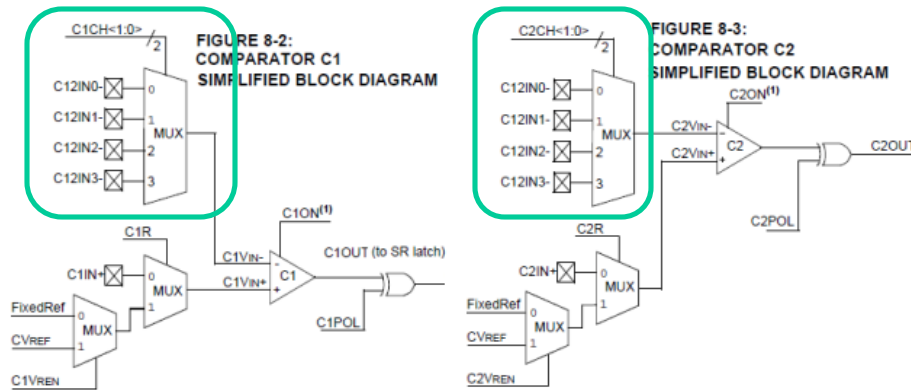
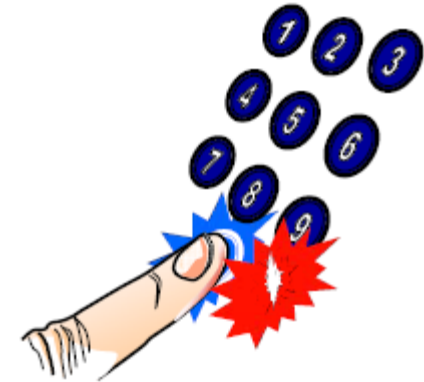


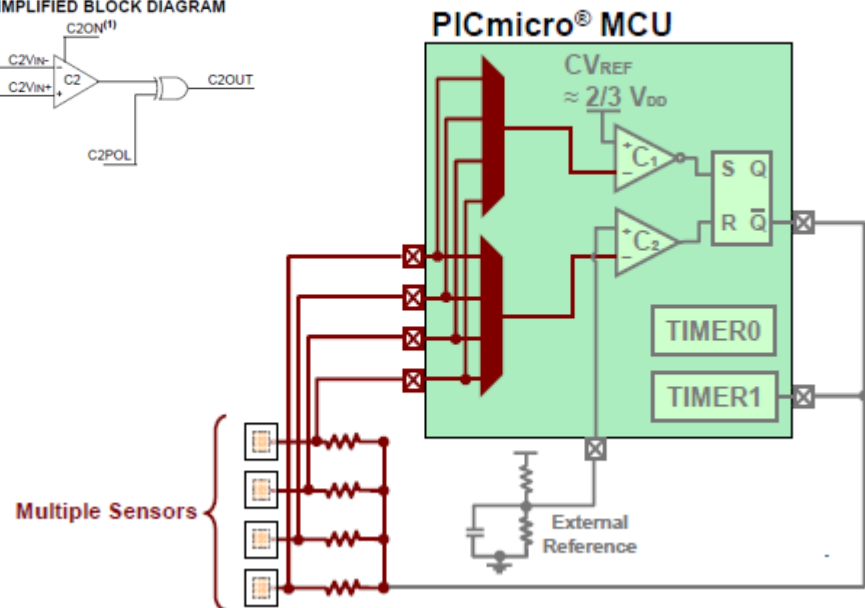Comparators inputs are multiplexed to the same pins – useful when you want to sense several keys ...



Touch-control

Moore contacts – Keyboard.

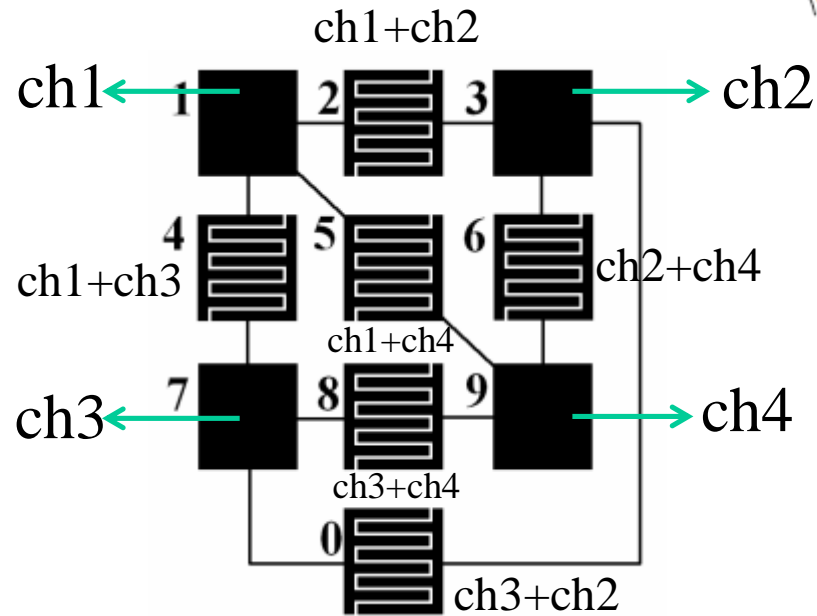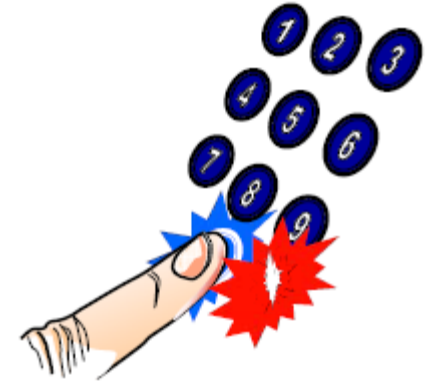



For More Information

- **AN1101: Introduction to Capacitive Sensing**
- **AN1102: Layout and Physical Design Guidelines for Capacitive Sensing**
- **AN1103: Software Handling for Capacitive Sensing**
- **AN1104: Capacitive Multi-Button Configurations**
- **mTouch™ Design Center at www.microchip.com/mTouch**