



# Written exam

## IE1206 Embedded Electronics

## IF1330 Electrical principles

### Monday 3/6 2019 14.00-18.00

---

### General Information

Examiner: Carl-Mikael Zetterling

Responsible teacher at exam: Per-Erik Hellström 08-790 43 25

**All sheets** that are handed in need **your name and personal number** written on them.

**Mark every sheet** with the **problem it deals with**.

**You cannot have more than one problem per sheet.**

### Aids: Calculator

The exam consists of 8 problems (5 points each) distributed over the 4 modules in the course:

Module 1: problem 1 and 2

Module 2: problem 3 and 4

Module 3: problem 5 and 6


Module 4: problem 7 and 8

To **pass the exam** requires at least **2 points** from each module and preliminary **20 points** in total.


**Grades** are given as follows:

Points	<20	20-23	24-27	28-31	32-35	36-40
Grades	F	E	D	C	B	A

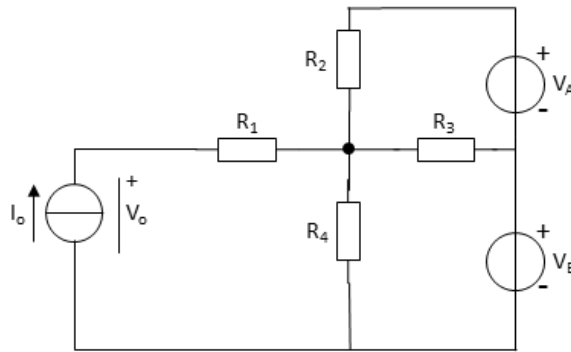
1. Determine the voltage  $V_o$  over the current source.  
 $R_1=1\text{ k}\Omega$ ,  $R_2=3\text{ k}\Omega$ ,  $R_3=2\text{ k}\Omega$ ,  $R_4=6\text{ k}\Omega$ ,  $I_o=1\text{ mA}$ ,  $V_A=1\text{ V}$ ,  $V_B=5\text{ V}$ .



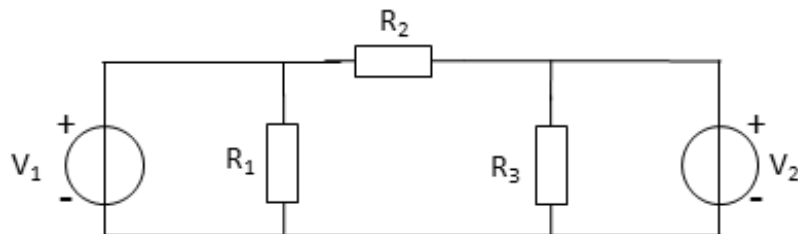2.  $V_1=2\text{ V}$ ,  $V_2=4\text{ V}$ ,  $R_1=2\text{ k}\Omega$ ,  $R_2=8\text{ k}\Omega$ ,  $R_3=4\text{ k}\Omega$ .  
 (A) Determine the power consumed in  $R_2$ .  
 (B) What is the total power delivered by the voltage sources to the resistors?



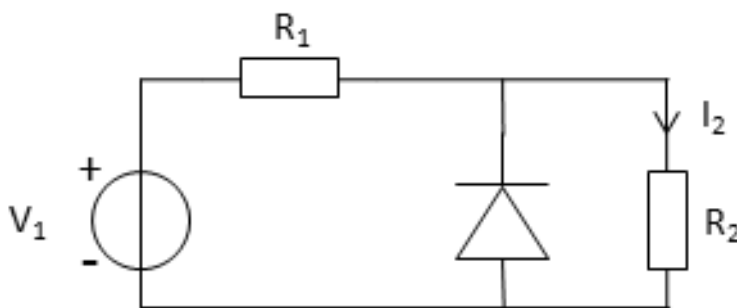
3. Determine the current  $I_2$ .  $V_1=4\text{ V}$ ,  $R_1=10\text{ k}\Omega$  and  $R_2=30\text{ k}\Omega$ .




4. Assume that the operational amplifier is ideal.

(A) Express  $V_{out}$  as function of  $V_{in}$ ,  $R_1$  and  $R_2$  when the operational amplifier works in the linear region.

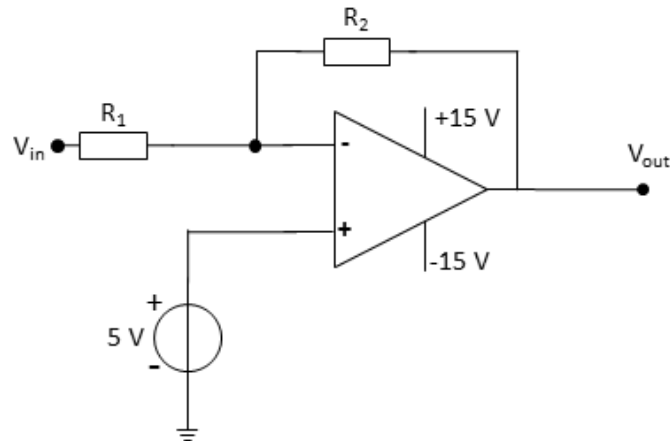
(B) Plot  $V_{out}$  versus  $V_{in}$  for  $-15\text{ V} < V_{in} < +15\text{ V}$  when  $\frac{R_2}{R_1} = 2$ .



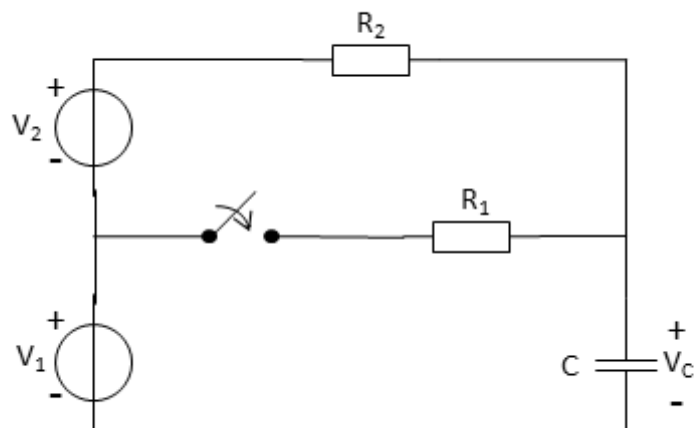
5. The switch has been open for a long time. At  $t=0\text{ s}$  the switch closes. Determine the voltage  $V_c$  over the capacitor at  $t=6\text{ }\mu\text{s}$ .  $V_1=1\text{ V}$ ,  $V_2=6\text{ V}$ ,  $R_1=10\text{ k}\Omega$ ,  $R_2=15\text{ k}\Omega$  and  $C=1\text{ nF}$ .



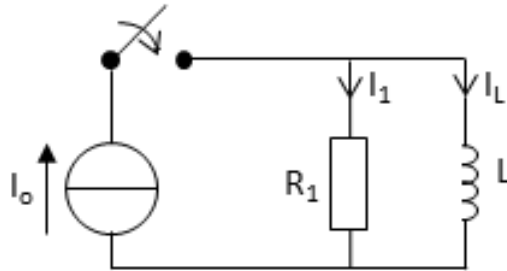
6. The switch has been open for a long time. At  $t=0$  s the switch closes.  
 (A) Derive an expression for the current  $I_1$  as a function  $I_o$ ,  $R_1$ ,  $L$  and  $t$ .  
 (B) Plot  $I_1(t)$  for  $-3 \mu\text{s} < t < 3 \mu\text{s}$  when  $R_1=1 \text{ k}\Omega$ ,  $L=1 \text{ mH}$ ,  $I_o=1 \text{ mA}$ .



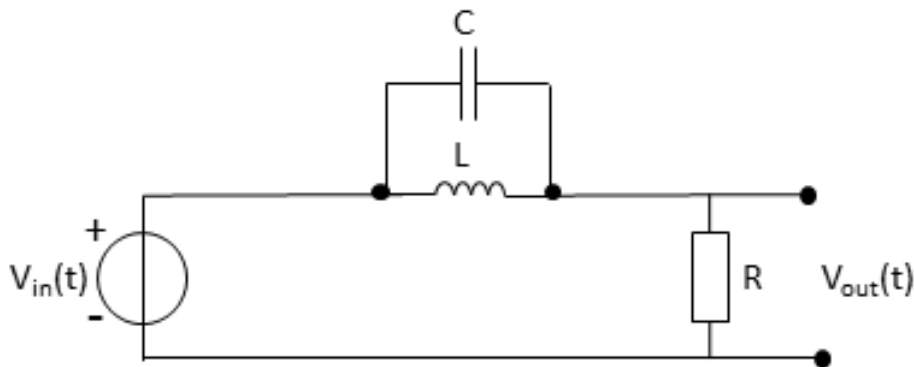
7.  $v_{in}(t)$  is a steady-state cosine voltage source with amplitude  $A$ , angular frequency  $\omega$  and phase angle  $\phi$ .  
 (A) Determine  $v_{out}$  when the angular frequency  $\omega = \frac{1}{\sqrt{LC}}$ .  
 (B) What type of filter function does the circuit perform? Motivate your answer.



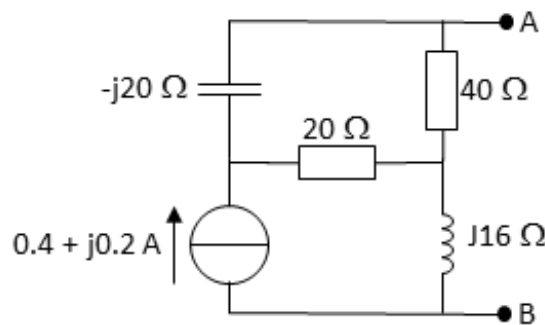8. Determine the Thévenin equivalent circuit seen at A-B.  
 Draw a schematic of the Thévenin equivalent circuit and express all parameters in the time domain when  $\omega=1000 \text{ rad/s}$ .



①

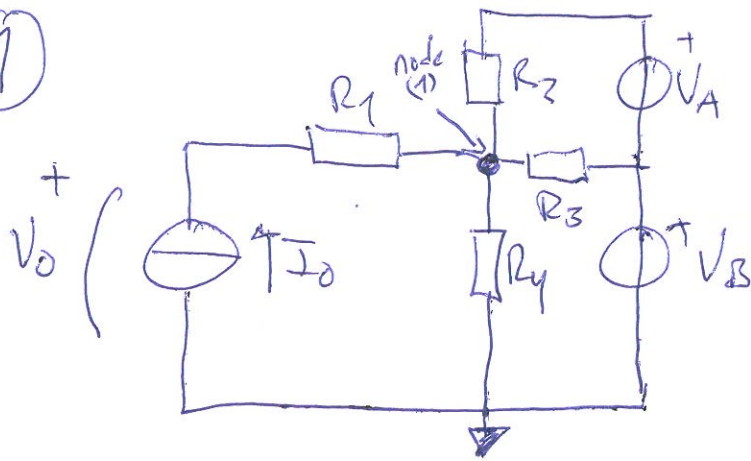

$$\begin{aligned} R_1 &= 1 \text{ k}\Omega & V_A &= 1 \text{ V} \\ R_2 &= 3 \text{ k}\Omega & V_B &= 5 \text{ V} \\ R_3 &= 2 \text{ k}\Omega & I_0 &= 1 \text{ mA} \\ R_4 &= 6 \text{ k}\Omega \end{aligned}$$

$$\text{KCL in node 1: } I_0 + \frac{V_A + V_B - V_1}{R_2} + \frac{V_B - V_1}{R_3} + \frac{0 - V_1}{R_4} = 0$$

$$\Rightarrow V_1 \left[ \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4} \right] = I_0 + \frac{V_A + V_B}{R_2} + \frac{V_B}{R_3}$$

$$\Rightarrow V_1 \left[ \frac{1}{3} + \frac{1}{2} + \frac{1}{6} \right] = 1 + \frac{6}{3} + \frac{5}{2} \Rightarrow V_1 [2 + 3 + 1] = 6 + 2 + 2.5$$

$$\Rightarrow V_1 = \frac{33}{6} = 5.5 \text{ V}$$

$$V_1 + I_0 R_1 = V_0 \Rightarrow V_0 = 5.5 + 1 \cdot 1 = 6.5 \text{ V}$$

$$\text{Answer: } V_0 = 6.5 \text{ V}$$

$I_2$  is the current through  $R_2$

②

①

$$P_2 = I_2 \cdot V_2 = R_2 I_2^2 = \left\{ I_2 = \frac{V_2 - V_1}{R_2} \right\} = \frac{(V_2 - V_1)^2}{R_2} =$$
$$= \left\{ \begin{array}{l} V_2 = 4V \\ V_1 = 2V \quad R_2 = 8k\Omega \end{array} \right\} = \frac{2^2}{8 \cdot 10^3} = 0,5 \text{ mW}$$

③

Power in resistors = Power in sources.

$$\text{Power in } R_1 : P_1 = \frac{V_1^2}{R_1} = \frac{2^2}{2} = 2 \text{ mW}$$

$$\text{Power in } R_3 : P_3 = \frac{V_2^2}{R_3} = \frac{4^2}{4} = 4 \text{ mW}$$

$$\text{Total power in sources is } P_1 + P_2 + P_3 = \del{6,5} 0,5 + 2 + 4 =$$
$$= 6,5 \text{ mW}$$


4 (A)

$$\frac{V_{in} - 5}{R_1} + \frac{V_{out} - 5}{R_2} = 0 \Rightarrow \frac{V_{out}}{R_2} = \frac{5}{R_2} + \frac{5}{R_1} - \frac{V_{in}}{R_1}$$

$$\Rightarrow V_{out} = 5 + \frac{R_2}{R_1} \cdot 5 - \frac{R_2}{R_1} V_{in}$$

(B)
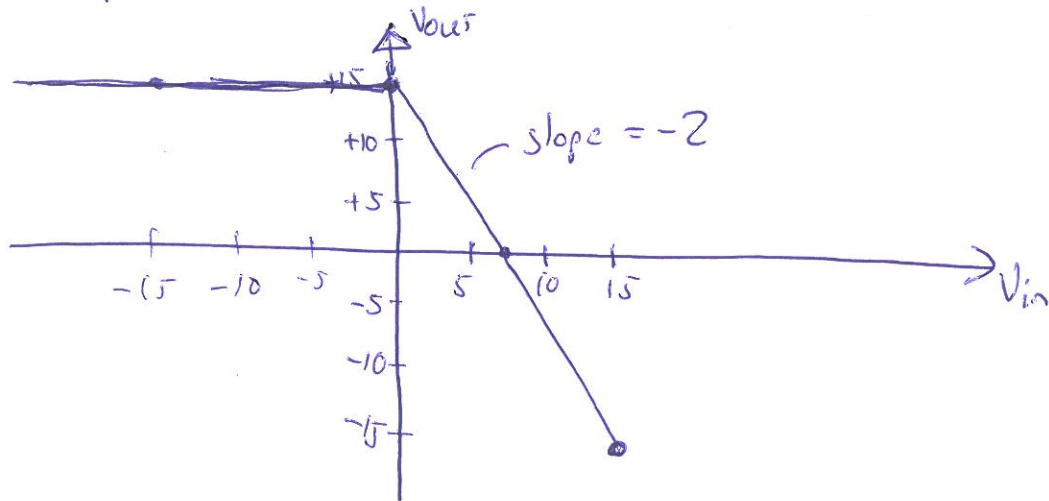
$$\frac{R_2}{R_1} = 2 \Rightarrow V_{out} = 15 - 2V_{in}$$




$$5.) \quad V_c(t) = V_c(\infty) + [V_c(0) - V_c(\infty)] e^{-\frac{t-t_0}{\tau}}$$

$t_0 = 0 \text{ s}$

at  $t < 0 \text{ s}$ : The capacitor is charged to  $V_c = V_1 + V_2$

$$\Rightarrow V_c(0) = V_1 + V_2 = 1 + 6 = 7 \text{ V}$$

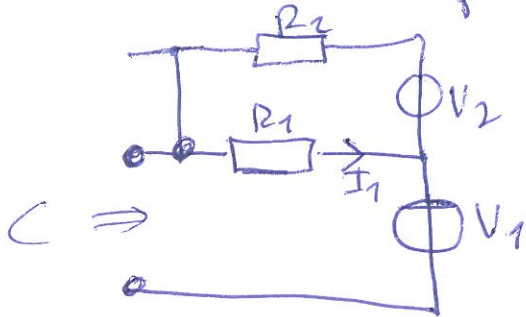at  $t > 0 \text{ s}$ : The capacitor sees the circuit:



$$V_{TH} = V_1 + I_1 \cdot R_1 = V_1 + \frac{V_2}{R_1 + R_2} \cdot R_1 =$$

$$= 1 + 6 \cdot \frac{10}{25} = 3,4 \text{ V}$$

$$R_{TH} = R_1 // R_2 = \frac{10 \cdot 15}{10 + 15} = 6 \text{ k}\Omega$$

$$V_c(\infty) = V_{TH} = 3,4 \text{ V}$$

$$\tau = R_{TH} \cdot C = 6 \cdot 10^3 \cdot 1 \cdot 10^{-9} = 6 \mu\text{s}$$


$$\Rightarrow V_c(t) = 3,4 + [7 - 3,4] e^{-\frac{t}{6 \mu\text{s}}} = 3,4 + 3,6 e^{-\frac{t}{6 \mu\text{s}}}$$

$$V_c(6 \mu\text{s}) = 3,4 + 3,6 e^{-1} = 4,7 \text{ V}$$

Answer:  $V_c(t = 6 \mu\text{s}) = 4,7 \text{ V}$



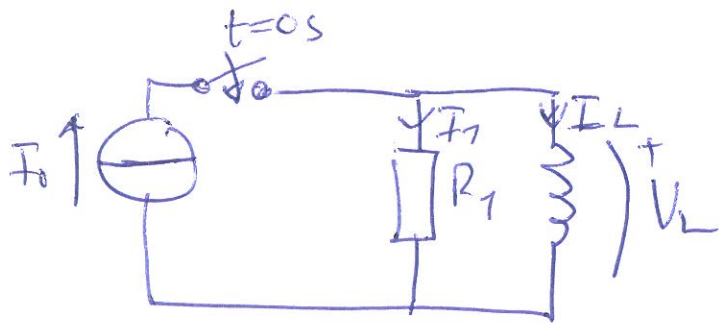6. (A)  $I_1 = \frac{V_L}{R_1}$   $V_L = L \frac{dI_L}{dt}$



$$I_L = I_L(\infty) + [I_L(0) - I_L(\infty)] e^{-\frac{t-t_0}{\tau}}$$

$$\left( \begin{array}{l} t_0 = 0s \\ \tau = \frac{L}{R_1} = \frac{10^{-3}}{10^3} = 1\mu s \end{array} \right)$$

$$I_L(0) = 0 A$$


$$I_L(\infty) = I_0 \Rightarrow I_L = I_0 (1 - e^{-\frac{t}{\tau}}) \quad \tau = \frac{L}{R_1}$$

$$\Rightarrow V_L = L \cdot \frac{dI_L}{dt} = L \left( -I_0 e^{-\frac{t}{\tau}} \cdot \left(-\frac{1}{\tau}\right) \right) = \frac{L I_0}{\tau} e^{-\frac{t}{\tau}} = \left\{ \tau = \frac{L}{R_1} \right\}$$

$$= R_1 I_0 e^{-\frac{t}{\tau}}$$

$$\Rightarrow \boxed{I_1(t) = \frac{V_L}{R_1} = I_0 e^{-\frac{t}{\tau}}}$$

(B)  $\tau = 1\mu s$   $I_0 = 1mA$

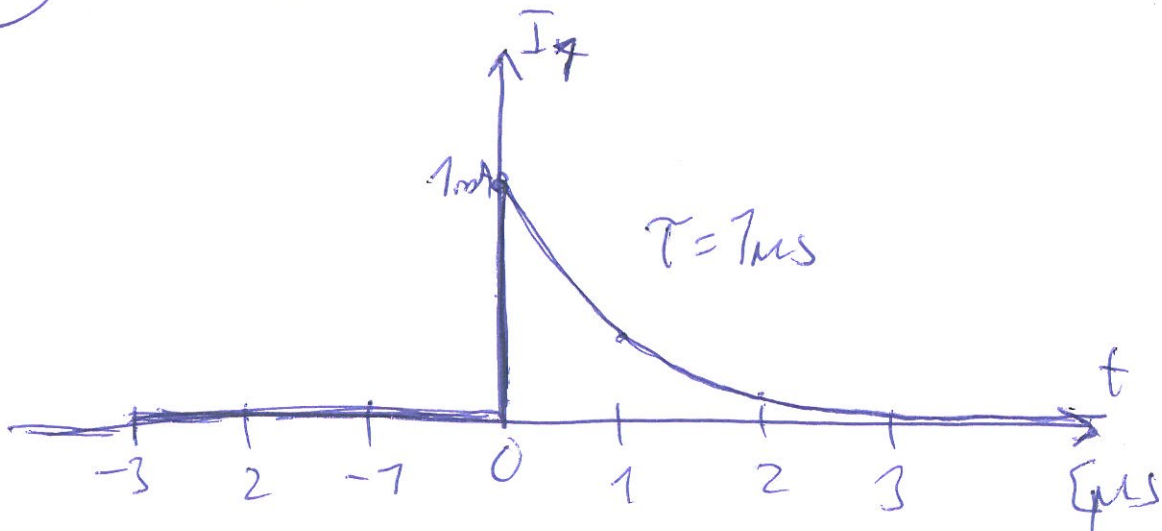


7. (A)  $\hat{V}_{out} = \hat{V}_{in} \frac{R}{Z_1 + R}$  where  $Z_1 = j\omega L // \frac{1}{j\omega C}$

$$Z_1 = \frac{j\omega L \cdot \frac{1}{j\omega C}}{\frac{1}{j\omega C} + j\omega L} = \frac{j\omega L}{1 - \omega^2 LC} \quad Z_1 \rightarrow \infty \text{ when } \omega \rightarrow \frac{1}{\sqrt{LC}}$$

$\Rightarrow \hat{V}_{out} \rightarrow 0$  Answer:  $V_{out}(t) = 0$  at  $\omega = \frac{1}{\sqrt{LC}}$

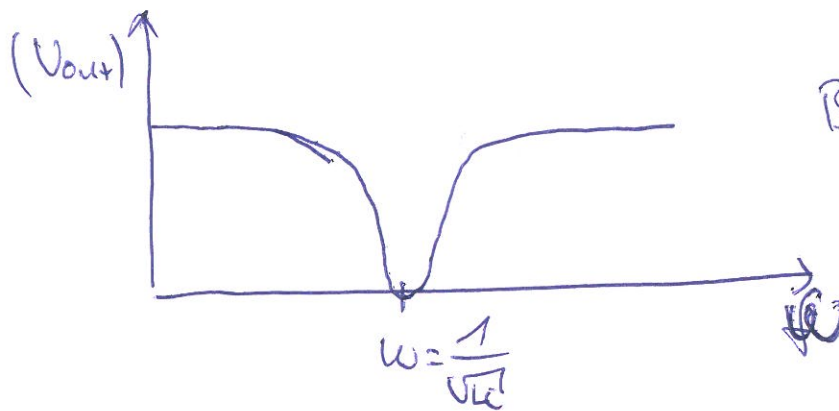(B)  $\omega \rightarrow 0 \Rightarrow j\omega L \rightarrow 0 \Rightarrow V_{out} = V_{in}$

$\omega \rightarrow \infty \Rightarrow \frac{1}{j\omega C} \rightarrow 0 \Rightarrow V_{out} = V_{in}$



Band-reject filter.


8. Determine  $Z_{TH}$ : Zero current source and find  $Z_{AB} = Z_{TH}$

$$Z_{TH} = Z_1 + j16 \text{ when}$$

$$\begin{aligned} Z_1 &= 40 // (20 - j20) = \\ &= \frac{40 \cdot 20 (1 - j)}{60 - j20} = 40 \frac{1 - j}{3 - j} = \\ &= 40 \frac{(1 - j)(3 + j)}{9 + 1} = 4(3 + j - 3j + 1) = 16 - 8j \Omega \end{aligned}$$

$$Z_{TH} = 16 - 8j + j16 = 16 + 8j$$

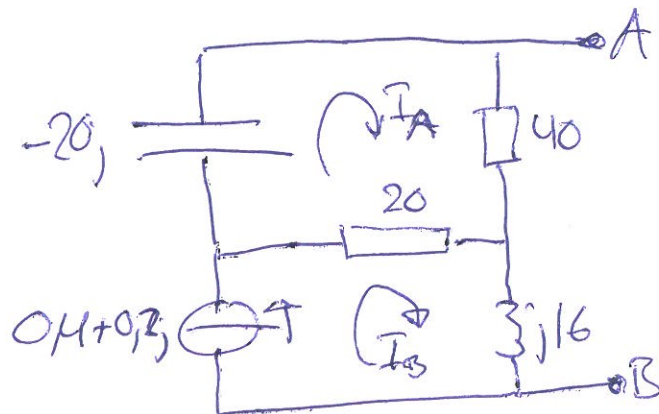Find  $V_{TH}$   
 $V_{TH} = V_{AB}$  when open between A-B



$$I_B = 0.4 + 0.2j \text{ A}$$

$$I_A: -(-j20)I_A - 40I_A - 20(I_A - I_B) = 0$$

$$j20I_A - 40I_A - 20I_A + 20(0.4 + 0.2j) = 0$$

$$-I_A(60 - 20j) + (8 + 4j) = 0 \Rightarrow I_A = \frac{8 + 4j}{60 - 20j} =$$

$$= \frac{2 + j}{15 - 5j} = \frac{(2 + j)(15 + 5j)}{15^2 + 5^2} = \frac{1}{250} (30 + 10j + 15j - 5) = \frac{25 + 25j}{250} =$$

$$= 0.1 + 0.1j \text{ A}$$

cont.  $\rightarrow$

$$V_{TH} = 40 I_A + j16 I_B = 40 (0,1 + 0,1j) + 16j (0,4 + 0,2j) =$$

$$= 4 + 4j + 6,4j - 3,2 = 0,8 + 10,4j$$

$$\Rightarrow V_{TH} = 10,4 \angle 85,6^\circ \Rightarrow V_{TH} = 10,4 \cos(\omega t + 85,6^\circ)$$

