

IE1204 Exam 20191021 Answers version 2

Part 1

1

$$A = 93_{10} = 01011101_2 = 5D_{16}$$

$$B = -42_{10} = 11010110_2 = D6_{16}$$

$$A + B = 00110011_2 = 51_{10}$$

2

$$C = 01011010_2 = 90_{10} = 5A_{16}$$

$$D = 00110011_2 = 51_{10} = 33_{16}$$

$$-D = 11001101_2 = -51_{10} = CD_{16}$$

$$C - D = 00100111_2 = 39_{10}$$

3

A	B	C	D	Y
0	0	0	0	1
0	0	0	1	1
0	0	1	0	0
0	0	1	1	1
0	1	0	0	1
0	1	0	1	1
0	1	1	0	0
0	1	1	1	1
1	0	0	0	0
1	0	0	1	0
1	0	1	0	0
1	0	1	1	1
1	1	0	0	0
1	1	0	1	0
1	1	1	0	1
1	1	1	1	1

		C, D			
		00	01	11	10
A, B	00	1	1	1	0
	01	1	1	1	0
	11	0	0	1	1
	10	0	0	1	0


$\bar{A}\bar{C} + CD + ABC$

Can't be further simplified!

4

$$Z = \bar{A} \cdot \bar{B} \cdot \bar{C} = \overline{A + B + C} \quad \text{Three input NOR} \rightarrow$$

$$Z = \bar{A} \cdot \bar{B} \cdot \bar{C} = \overline{\overline{\bar{A} \cdot \bar{B} \cdot \bar{C}}} \quad \text{(three input NAND also ok)}$$

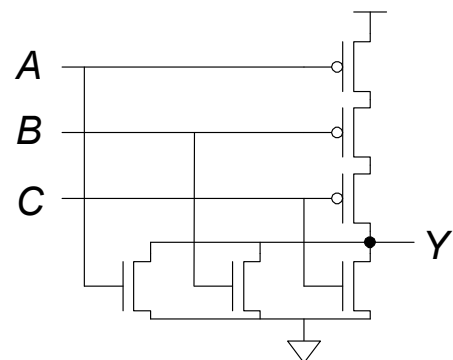

Part 2

5

$$Y = \bar{A} \cdot \bar{B} \cdot C + \bar{A} \cdot \bar{B} \cdot \bar{D} + A \cdot \bar{B} \cdot C + A \cdot \bar{B} \cdot \bar{D}$$

Format: Sum of products



		C, D			
		00	01	11	10
A, B	00	1	0	1	1
	01	0	0	0	0
	11	0	0	0	0
	10	1	0	1	1

$\bar{B}\bar{D} + \bar{B}C$

Format: Product of sums

		C, D			
		00	01	11	10
A, B	00	1	0	1	1
	01	0	0	0	0
	11	0	0	0	0
	10	1	0	1	1

$(C + \bar{D})\bar{B}$

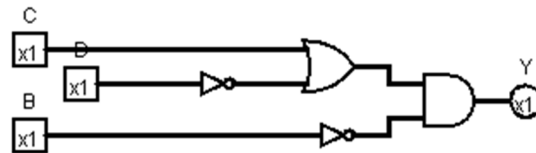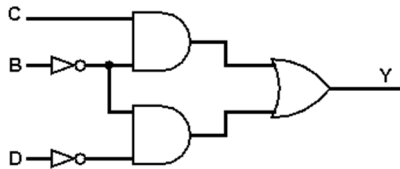

6

Format: Sum of products

		C, D			
		00	01	11	10
A, B	00	1	1	0	x
	01	x	0	1	1
	11	0	1	1	0
	10	1	1	0	x

$\bar{B}\bar{C} + \bar{A}BC + ABD$



Format: Product of sums

		C, D			
		00	01	11	10
A, B	00	1	1	0	x
	01	x	0	1	1
	11	0	1	1	0
	10	1	1	0	x

$(B + \bar{C})(A + \bar{B} + C)(\bar{A} + \bar{B} + D)$





$$Y = \bar{B} \cdot \bar{C} + \bar{A} \cdot B \cdot C + A \cdot B \cdot D = \bar{B} \cdot \bar{C} + \bar{A} \cdot B \cdot C + A \cdot B \cdot D = \bar{B} \cdot \bar{C} \cdot \bar{A} \cdot B \cdot C \cdot A \cdot B \cdot D$$
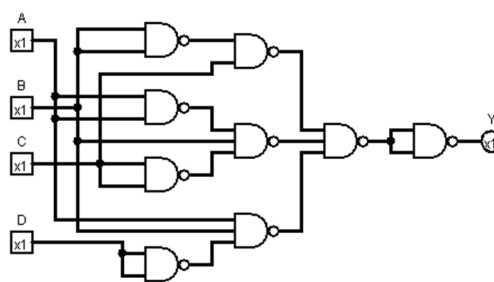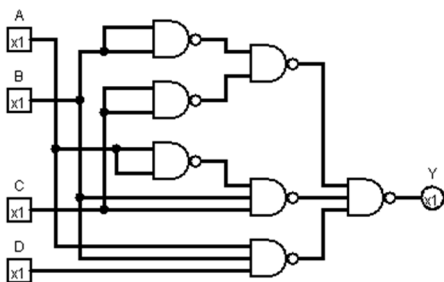
$$Y = (B + \bar{C})(A + \bar{B} + C)(\bar{A} + \bar{B} + D) = \bar{B} \cdot \bar{C} \cdot \bar{A} \cdot B \cdot \bar{C} \cdot A \cdot B \cdot \bar{C}$$





One point was deducted if the expression was not simplest possible. $\bar{A} \cdot \bar{D}$ should not be included.

7

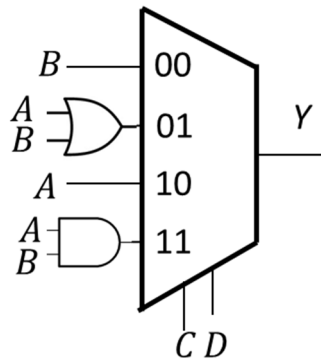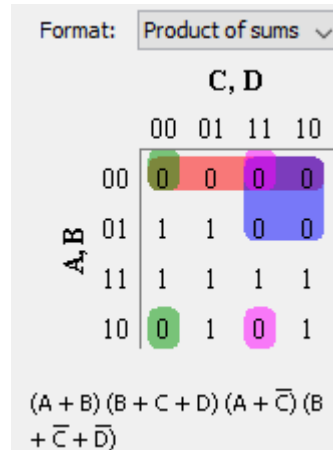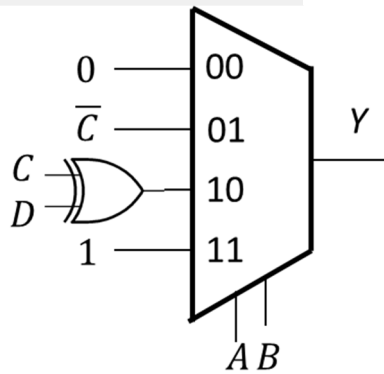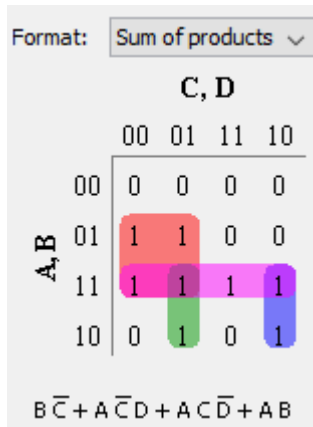

8

q3	q2	q1	q0	B4	B3	B2	B1	B0
0	0	0	0	0	0	0	0	0
0	0	0	1	0	0	0	0	1
0	0	1	0	0	0	0	1	0
0	0	1	1	0	0	0	1	1
0	1	0	0	0	0	1	0	0
0	1	0	1	0	0	1	0	1
0	1	1	0	0	0	1	1	0
0	1	1	1	0	0	1	1	1
1	0	0	0	0	1	0	0	0
1	0	0	1	0	1	0	0	1
1	0	1	0	1	0	0	0	0
1	0	1	1	1	0	0	0	1
1	1	0	0	1	0	0	1	0
1	1	0	1	1	0	0	1	1
1	1	1	0	1	0	1	0	0
1	1	1	1	1	0	1	0	1

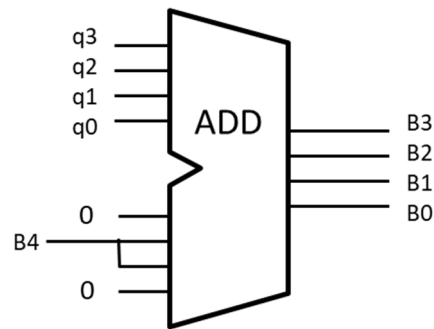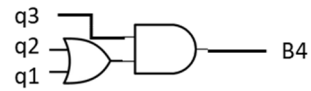

$$B4 = q3 \cdot q2 + q3 \cdot q1 = q3(q2 + q1)$$

$$B3 = q3 \cdot \bar{B4} \text{ or } B3 = q3 \cdot q2 \cdot q1$$

$$B2 = q2 \cdot \bar{B4} + q3 \cdot q2 \cdot q1 \text{ or } B2 = \bar{q3} \cdot q2 + q2 \cdot q1$$

$$B1 = q1 \oplus B4 \text{ or } B1 = \bar{q3} \cdot q1 + q3 \cdot q2 \cdot q1$$

$$B0 = q0$$

The expressions can be derived from examination, or K-maps (next page).

Variations with MUX (5 x 16:1 or 3 x 2:1 and others are also possible)

Or use the first expression (B4) plus an ADDER: add 6 if the value is 10 or higher.

(has the same effect as subtracting 10 when the carry is not used, see above)

Output:

Format:

Q1, Q0

	00	01	11	10
00	0	0	0	0
01	0	0	0	0
11	1	1	1	1
10	0	0	1	1

$Q3 Q1 + Q3 Q2$

Output:

Format:

Q1, Q0

	00	01	11	10
00	0	0	0	0
01	0	0	0	0
11	0	0	0	0
10	1	1	0	0

$Q3 \overline{Q2} \overline{Q1}$

Output:

Format:

Q1, Q0

	00	01	11	10
00	0	0	0	0
01	1	1	1	1
11	0	0	1	1
10	0	0	0	0

$\overline{Q3} Q2 + Q2 Q1$

Output:

Format:

Q1, Q0

	00	01	11	10
00	0	0	1	1
01	0	0	1	1
11	1	1	0	0
10	0	0	0	0

$\overline{Q3} Q1 + Q3 Q2 \overline{Q1}$

Output:

Format:


Q1, Q0

	00	01	11	10
00	0	1	1	0
01	0	1	1	0
11	0	1	1	0
10	0	1	1	0

$Q0$

Part 3

9

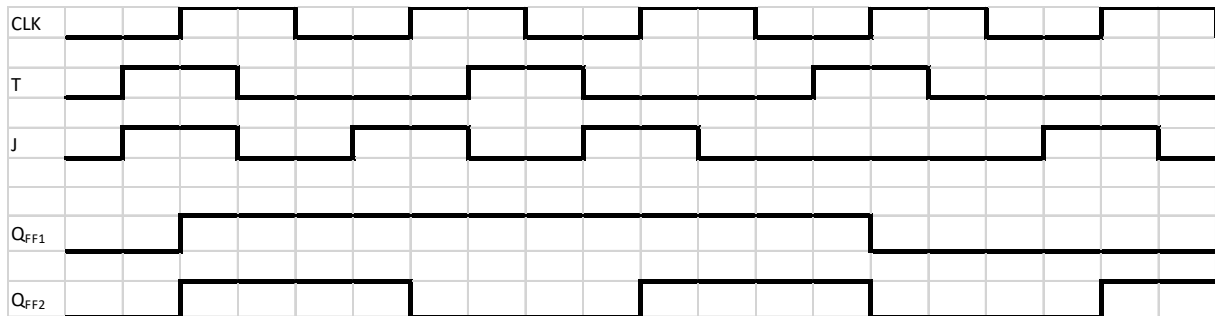

10


$$q_1^+ = D \cdot q_0 + \overline{D} \cdot q_1$$

$$q_0^+ = D \cdot \overline{q_1} + \overline{D} \cdot q_0$$


$$B = \overline{q_1 + q_0} = \overline{q_1} \cdot \overline{q_0}$$

$$H = q_1 \cdot q_0$$

Present state		Next state				Out	
q1	q0	D=0		D=1		B	H
0	0	0	0	0	1	1	0
0	1	0	1	1	1	0	0
1	1	1	1	1	0	0	1
1	0	1	0	0	0	0	0

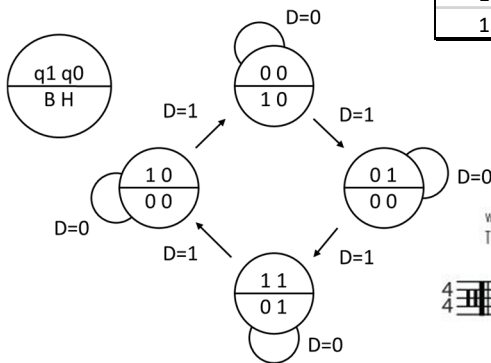

Billie Jean
by Michael Jackson

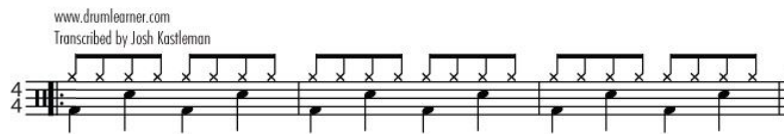

The FSM can be used as a drum machine: B = Base, H = Hi-hat, clk = Snare, D=1 drum, D=0 pause

11

Present state			Next state		
c	b	a	c+	b+	a+
0	0	0			
0	0	1			
0	1	0	0	1	1
0	1	1	1	0	1
1	0	0			
1	0	1	1	1	1
1	1	0			
1	1	1	0	1	0

c+	ba =			
	00	01	11	10
c = 0	x	x	1	0
1	x	1	0	x

b+	ba =			
	00	01	11	10
c = 0	x	x	0	1
1	x	1	1	x



a+	ba =			
	00	01	11	10
c = 0	x	x	1	1
1	x	1	0	x

$$c^+ = \overline{b} + \overline{c} \cdot a$$

$$b^+ = c + \overline{a}$$

$$a^+ = \overline{c} + \overline{b}$$

Present state			Next state		
c	b	a	c+	b+	a+
0	0	0	1	1	1
0	0	1	1	0	1
0	1	0	0	1	1
0	1	1	1	0	1
1	0	0	1	1	1
1	0	1	1	1	1
1	1	0	0	1	0
1	1	1	0	1	0

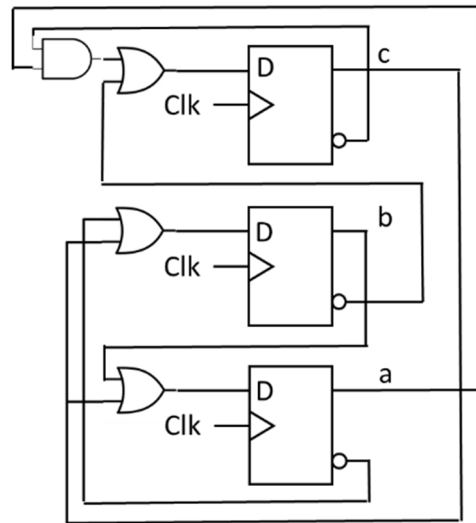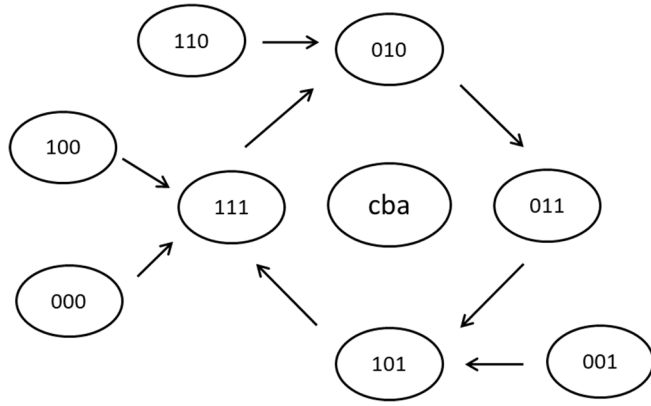

12

Present state		Next state							
q2	q1	a b = 00		a b = 01		a b = 11		a b = 10	
q2	q1	q2+	q1+	q2+	q1+	q2+	q1+	q2+	q1+
0	0	0	0	1	0	<u> </u>		0	1
0	1	0	0	0	1	1	1	0	1
1	1	<u> </u>		0	1	1	1	0	1
1	0	0	0	1	0	1	1	<u> </u>	

q2+	ab =	00	01	11	10
q2q1 = 00	0	0	1	X	0
01	0	0	0	1	0
11	X	0	0	1	0
10	0	0	1	1	X

$$q_2^+ = a \cdot b + \overline{q_1} \cdot b$$

q1+	ab =	00	01	11	10
q2q1 = 00	0	0	0	X	1
01	0	0	1	1	1
11	X	0	1	1	1
10	0	0	0	1	X

$$q_1^+ = q_1 \cdot b + a$$

Part 4

13

Ripple carry critical path is $2 \times 4 = 8$ gates. $t_{pd} = 8 \times 40 = 320$ ps

74hc283 critical path is 6 gates. $t_{pd} = 6 \times 40 = 240$ ps (even though the carry-chain has 5)

$$T_c \geq t_{pcq} + t_{pd} + t_{setup} = 40 + 320 + 50 = 410 \text{ ps. } f_{clock} = 1 / T_c = 2,5 \text{ GHz}$$

$$T_c \geq t_{pcq} + t_{pd} + t_{setup} = 40 + 240 + 50 = 330 \text{ ps. } f_{clock} = 1 / T_c = 3,0 \text{ GHz}$$

Hold time does not affect max clock speed.

14

$$E = 01010101_2 = 85_{10}$$

$$F = 00101010_2 = 42_{10}$$

$$G = 00010001_2 = 17_{10}$$

$$P = E \times F = 0000 \ 1101 \ 1111 \ 0010_2 = 3570_{10} = 85 \times 42$$

$$K = E / G = 00000101_2 = 5_{10} = 85 / 17$$

15

The opcodes for the ALU is as below (did not need to be shown).

First case $A = 1010$, $B = 0011$, $S2 = 0$, $S1 = 1$, $S0 = 1$: $Y = A \text{ NOR } B = 0100$

Second case if $S2 = 1$: $Y = A - B = 0111$ ($10 - 3 = 7$, calculate decimal or binary with 2 complement)

S2	S1	S0	Operation
0	0	0	A AND B
0	0	1	A NAND B
0	1	0	A OR B
0	1	1	A NOR B
1	0	0	A + A = 2A
1	0	1	A - A = 0
1	1	0	A + B
1	1	1	A - B

16

$$A_4A_3A_2A_1A_0 = 01001$$

$$D_3D_2D_1D_0 = 0101 \text{ (diodes are zero, no inverters on this ROM)}$$

