

IE1204 Digital Design Answer Form 2021-04-07



Full Name		Personal Number						Program		
Exam Answers 2021-04-07		YYYYMMDD-XXXX						NN		
#	Answer with	Answer						Points		
1	Decimal number	-57						1		
2	8 bit two's complement binary number	0	1	1	1	0	1	0	1	1
3	8 bit two's complement binary number	1	0	1	0	1	0	1	1	1
4	Boolean expression, Y =	$A \cdot B \cdot C \cdot D$						1		
5	Boolean expression, Y =	$(A + B + \bar{C})(\bar{A} + B + C)(\bar{A} + \bar{B} + \bar{C})$						1		
6	Boolean expression, Y = OR $(B + \bar{D})(A + \bar{B})(\bar{B} + D)$	$\bar{B} \cdot \bar{D} + A \cdot B \cdot D$						1		
7	MUX connections	$\overline{A + B}$						1		
	Row CD = 00	$\overline{A \oplus B}$								
	Row CD = 01	$A \cdot B$								
	Row CD = 10	B								
	Row CD = 11									
8	Timing diagram							1		
9	Timing diagram							1		
10	Setup condition	<input checked="" type="checkbox"/> Yes		<input type="checkbox"/> No				1		
	Hold condition	<input type="checkbox"/> Yes		<input checked="" type="checkbox"/> No						
11	Boolean expression (Hazard fix only)	$\bar{B} \cdot C$						1		
12	16 bit two's complement binary number, MSB	1	1	1	1	1	1	1	0	1
	LSB	1	1	0	1	1	0	1	0	
13	8 bit two's complement binary number	1	1	1	0	1	0	0	1	1
14	Number interval	-8 to 7.9375						1		
15	5 result bits (S4 S3 S2 S1 S0)				1	0	0	0	1	1
16	4 flag bits (V C N Z)				0	0	1	0	1	
TOTAL POINTS		Examiner sign CMZ						16		

IE1204 Digital Design Exam 2021-04-07 K-maps

4 CMOS

Swedish: Bestäm den logiska funktionen $Y = f(A, B, C)$ för CMOS-grindnätet. Förenkla så långt som möjligt.

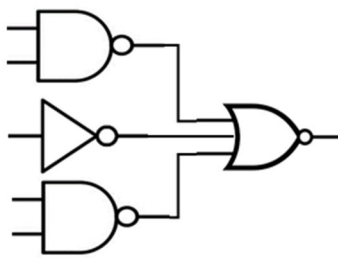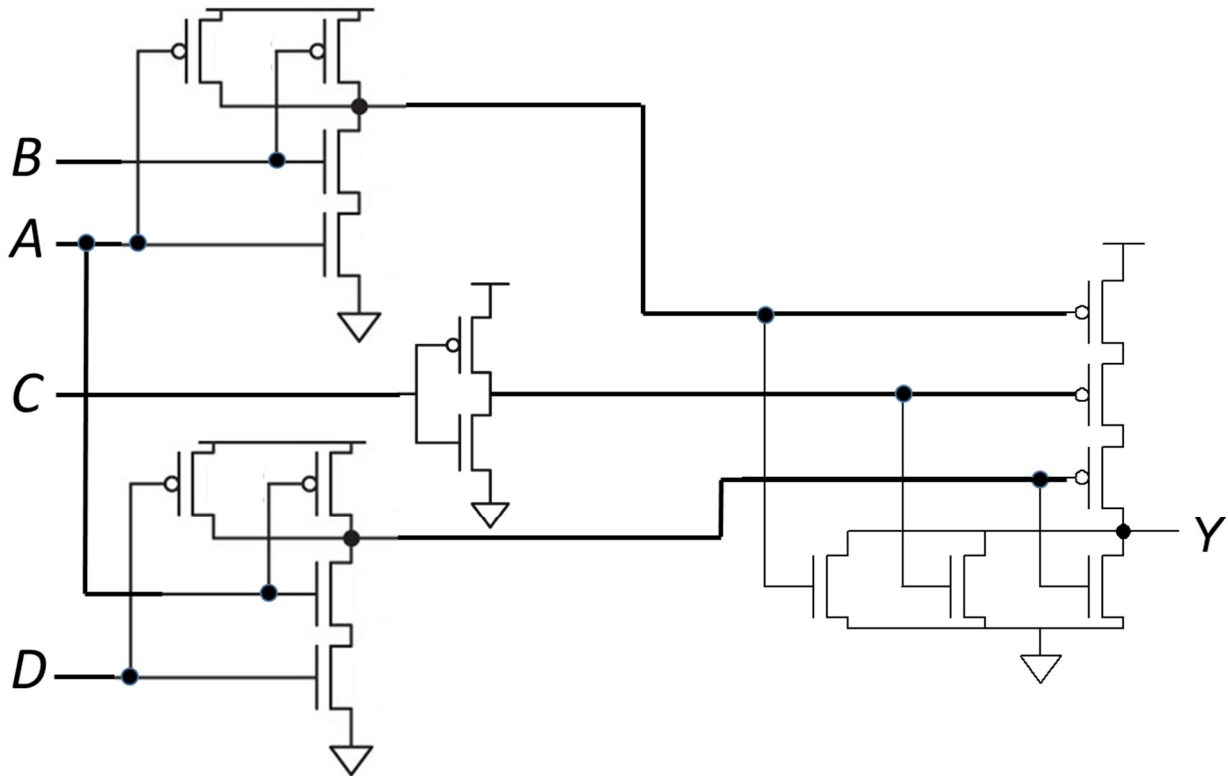English: Determine the logic function $Y = f(A, B, C)$ for the CMOS-circuit. Simplify as much as possible.



$$Y = \overline{\overline{(A \cdot B) + C + (A \cdot D)}} = AB \cdot C \cdot AD = A \cdot B \cdot C \cdot D$$

5 SoP / PoS

Swedish: Ta fram booleskt uttryck på PoS form för sanningstabellen nedan.

English: Derive the Boolean expression in PoS form for the truth table below.

A	B	C	Y
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	0

		AB			
		00	01	11	10
C	0	1	1	1	0
	1	0	1	0	1

$$Y = (A + B + \bar{C})(\bar{A} + B + C)(\bar{A} + \bar{B} + \bar{C})$$

6 K-map

Swedish: Uttnyttja x = don't care.

Ta fram enklast möjliga booleska uttryck från K-map.

English: Use x = don't care.

Derive simplest possible Boolean expression from the K-map.

Y	CD 00	CD 01	CD 11	CD 10
AB 00	1	X	X	1
AB 01	0	X	0	0
AB 11	0	1	1	0
AB 10	1	0	0	1

Output: Y

Format: Sum of products

C, D

	00	01	11	10
00	1	x	x	1
01	0	x	0	0
11	0	1	1	0
10	1	0	0	1

$\bar{B}\bar{D} + ABD$

Output: Y

Format: Product of sums

C, D

	00	01	11	10
00	1	x	x	1
01	0	x	0	0
11	0	1	1	0
10	1	0	0	1

$(B + \bar{D})(A + \bar{B})(\bar{B} + D)$

IE1204 Digital Design Exam 2021-04-07 Solutions


17 Analysis of Combinational Circuit

Swedish:

1. Ta fram booleskt uttryck för kretsen nedan.
2. Rita K-map för kretsen med variabelordning som i figuren.
3. Förenkla uttrycket med hjälp av K-map.
4. Rita ny krets med enbart 2- och 3-ingångars NOR-grindar.

English:

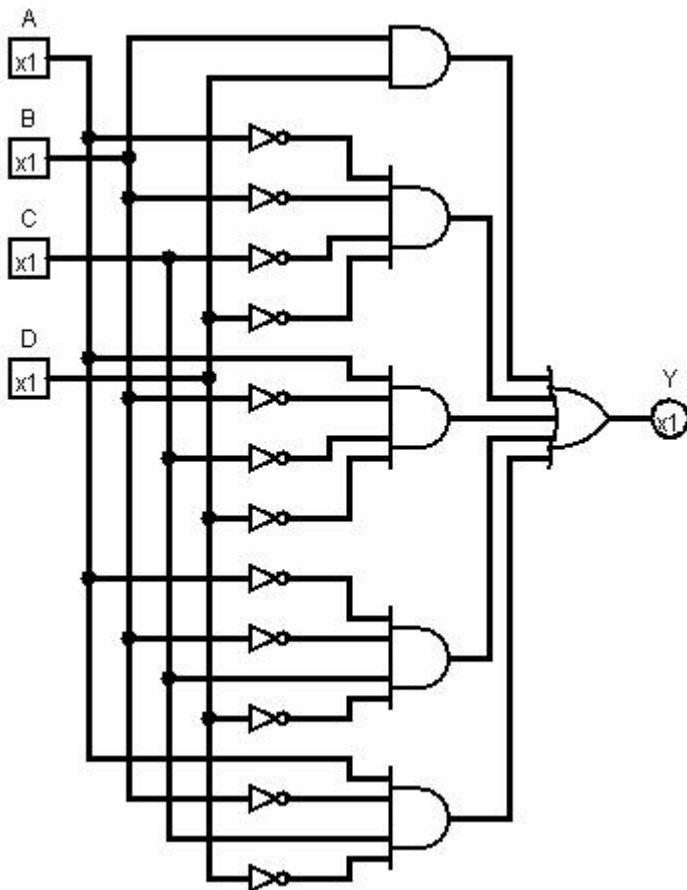1. Derive the Boolean expression for the circuit below.
2. Draw a K-map for the circuit with variables as in the figure.
3. Simplify the expression using the K-map.
4. Draw a new circuit using only 2 and 3 input NOR gates.



(Answer on next page)

Use POS for NOR only (inverters are ok if you note that they can be made with a NOR)
 No deductions if not simplest possible.

$$BD + \overline{A}\overline{B}\overline{C}\overline{D} + A\overline{B}\overline{C}\overline{D} + \overline{A}B\overline{C}\overline{D} + A\overline{B}C\overline{D}$$

	CD = 00	01	11	10
AB = 00	1	0	0	1
01	0	1	1	0
11	0	1	1	0
10	1	0	0	1

Format: Sum of products

		C, D			
		00	01	11	10
A, B	00	1	0	0	1
	01	0	1	1	0
	11	0	1	1	0
	10	1	0	0	1


$\overline{B}\overline{D} + BD$

Format: Product of sums

		C, D			
		00	01	11	10
A, B	00	1	0	0	1
	01	0	1	1	0
	11	0	1	1	0
	10	1	0	0	1


$(B + \overline{D})(\overline{B} + D)$

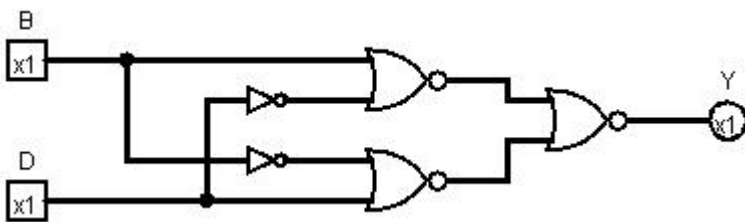For POS, draw $Y = \overline{\overline{(B + \overline{D})} \cdot \overline{(\overline{B} + D)}}$



For SOP, draw $Y = \overline{\overline{\overline{\overline{B \cdot \overline{D}} + \overline{B \cdot D}}}}$

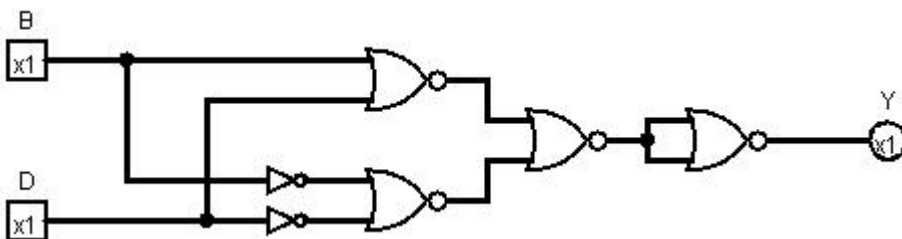(Note the double inversion bars, an extra inverter/NOR is needed)



18 Design of Combinational Circuit

Swedish:

Designa en kombinatorisk krets för $Y=f(Q_3, Q_2, Q_1, Q_0)$, $Q_3 = \text{MSB}$ där

$Y = 1$ för 0, 5, 10, 15

$Y = x$ (don't care) för 2, 7, 8, 13

$Y = 0$ för alla övriga tal

1. Rita sanningstabellen.
2. Rita K-map för sanningstabellen med variabelordning som i figuren.
3. Utnyttja $x = \text{don't care}$. Ta fram enklast möjliga booleska uttryck från K-map.
4. Rita en krets för uttrycket med enbart NAND-grindar.

English:

Design a combinational circuit for $Y=f(Q_3, Q_2, Q_1, Q_0)$, $Q_3 = \text{MSB}$ where

$Y = 1$ for 0, 5, 10, and 15

$Y = x$ (don't care) for 2, 7, 8, and 13

$Y = 0$ for all other numbers

1. Draw the truth table.
2. Draw a K-map for the truth table with variables as in the figure..
3. Use $x = \text{don't care}$. Derive simplest possible Boolean expression from the K-map.
4. Draw a circuit for the expression using only NAND-gates.

	$Q_1Q_0 =$			
	00	01	11	10
$Q_3Q_2 =$				
00				
01				
11				
10				

Rita om K-map i dina inlämnade svar.

Redraw the K-map in your answer sheets.

(Answer on next page)

18 Design of Combinational Circuit

Q3	Q2	Q1	Q0	Y
0	0	0	0	1
0	0	0	1	0
0	0	1	0	x
0	0	1	1	0
0	1	0	0	0
0	1	0	1	1
0	1	1	0	0
0	1	1	1	x
1	0	0	0	x
1	0	0	1	0
1	0	1	0	1
1	0	1	1	0
1	1	0	0	0
1	1	0	1	x
1	1	1	0	0
1	1	1	1	1

Format:

		Q1, Q0			
		00	01	11	10
Q3, Q2	00	1	0	0	x
	01	0	1	x	0
	11	0	x	1	0
	10	x	0	0	1

$\overline{Q2} \overline{Q0} + Q2 Q0$


Format:

		Q1, Q0			
		00	01	11	10
Q3, Q2	00	1	0	0	x
	01	0	1	x	0
	11	0	x	1	0
	10	x	0	0	1


$(Q2 + \overline{Q0})(\overline{Q2} + Q0)$

**Use SOP for NAND only (inverters are ok if you note that they can be made with a NAND)
No deductions if not simplest possible.**

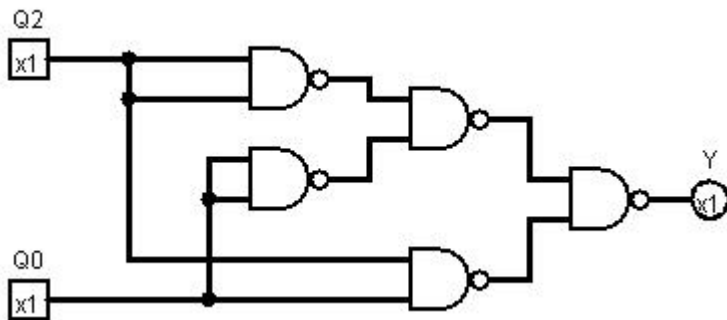For SOP draw $Y = \overline{\overline{Q2} \cdot \overline{Q0}} + \overline{\overline{Q2} \cdot Q0} = \overline{\overline{Q2} \cdot \overline{Q0} \cdot \overline{Q2} \cdot Q0}$



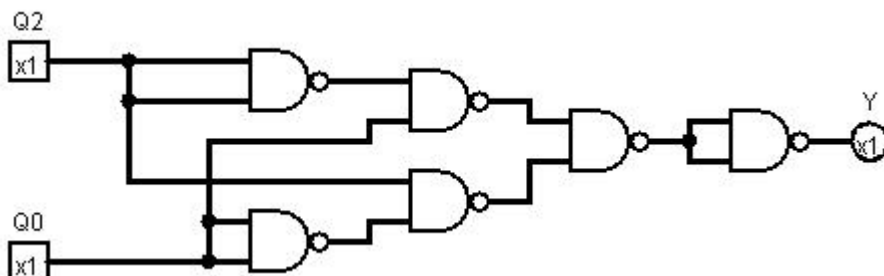For POS draw $Y = \overline{\overline{(Q2 + \overline{Q0}) \cdot (\overline{Q2} + Q0)}} = \overline{\overline{Q2} \cdot \overline{Q0} \cdot \overline{Q2} \cdot Q0}$



(Note the double inversion bars, an extra inverter/NAND is needed)


19 Analysis of FSM

Swedish: Analysera vad nedanstående tillståndsmaskin (FSM) utför.

1. Ta fram Boolska uttryck för nästa tillstånd.
2. Rita tillståndstabell.
3. Rita tillståndsdigram.
Använd ordningen Q2:0

English: Analyze the state machine (FSM) below.

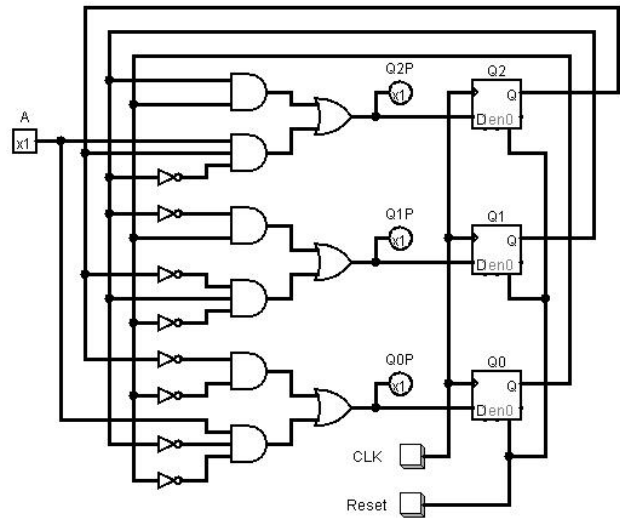1. Derive Boolean expressions for next state.
2. Draw a state table.
3. Draw a state diagram.
Use the order Q2:0




$$Q2+ = Q1 \cdot Q0 + A \cdot Q2 \cdot \overline{Q1}$$

$$Q1+ = \overline{Q1} \cdot Q0 + \overline{Q2} \cdot Q1 \cdot \overline{Q0}$$

$$Q0+ = \overline{Q2} \cdot \overline{Q0} + A \cdot \overline{Q1} \cdot \overline{Q0}$$

Present state			Next state A = 0			Next state A = 1		
Q2	Q1	Q0	Q2+	Q1+	Q0+	Q2+	Q1+	Q0+
0	0	0	0	0	1	0	0	1
0	0	1	0	1	0	0	1	0
0	1	0	0	1	1	0	1	1
0	1	1	1	0	0	1	0	0
1	0	0	0	0	0	1	0	1
1	0	1	0	1	0	1	1	0
1	1	0	0	0	0	0	0	0
1	1	1	1	0	0	1	0	0

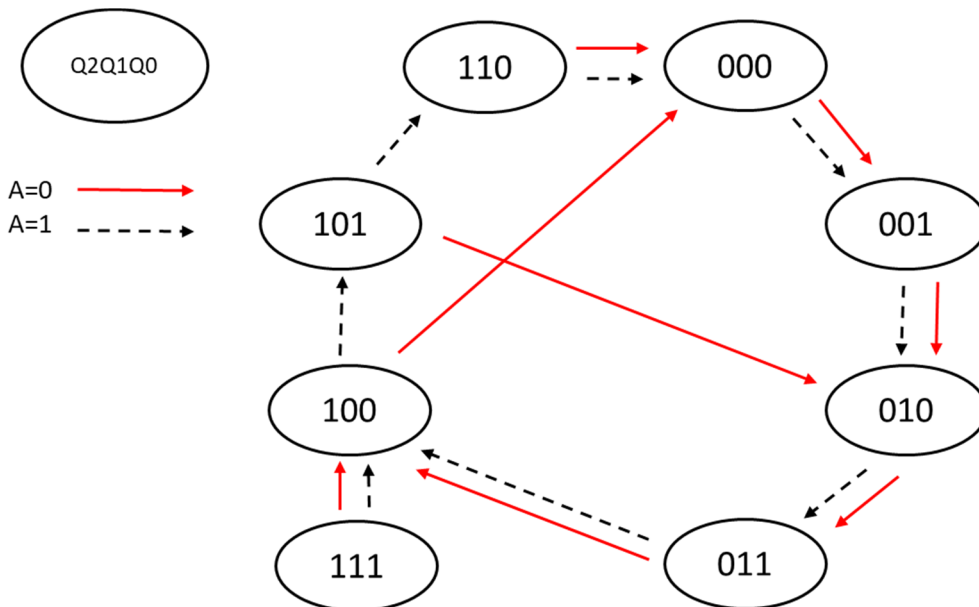

If A=0: divide by 5
If A=1: divide by 7


20 Design of FSM

Swedish: Konstruera en tillståndsmaskin (FSM) enligt tillståndsdigrammet nedan.

1. Rita tillståndstabell.
2. Ta fram K-map för nästa tillstånd.
3. Ta fram minimerade uttryck för nästa tillstånd och utsignal.
4. Rita kretsschema för en FSM med DFFs och vilka grindar som helst.

English: Design a state machine (FSM) according to the state diagram below.

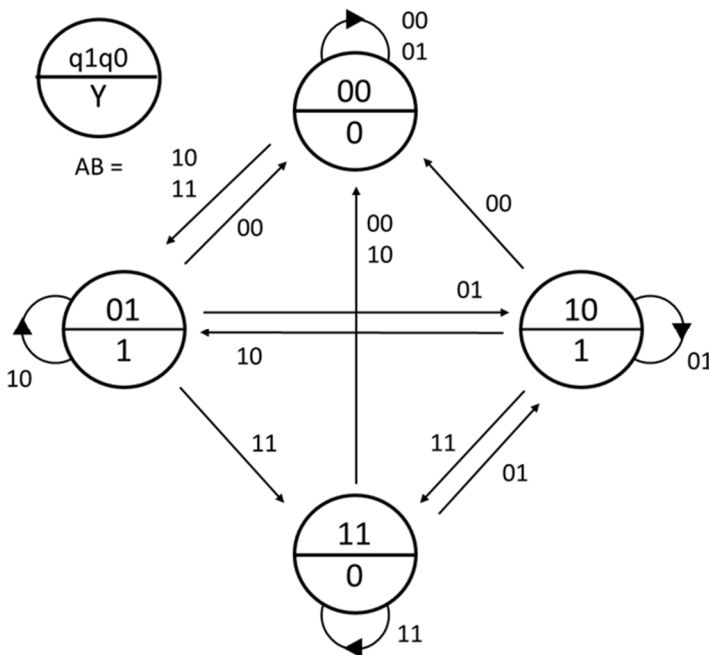1. Draw a state table.
2. Derive K-maps for next states.
3. Derive minimized expressions for next state and output.
4. Draw the FSM circuit diagram with DFFs and any gates.



q1q0	A B =			
	00	01	11	10
00				
01				
11				
10				

Rita om K-map i dina inlämnade svar.

Redraw the K-map in your answer sheets.

Present state		Next state								Out
		AB = 00		AB = 01		AB = 11		AB = 10		
q1	q0	q1+	q0+	q1+	q0+	q1+	q0+	q1+	q0+	Y
0	0	0	0	0	0	0	1	0	1	0
0	1	0	0	1	0	1	1	0	1	1
1	1	0	0	1	0	1	1	0	0	0
1	0	0	0	1	0	1	1	0	1	1

q1+	AB=				
q1q0	00	01	11	10	
00	0	0	0	0	
01	0	1	1	0	
11	0	1	1	0	
10	0	1	1	0	

q0+	AB=				
q1q0	00	01	11	10	
00	0	0	1	1	
01	0	0	1	1	
11	0	0	1	0	
10	0	0	1	1	

K-map not needed for Y, $Y = q1 \oplus q0$

Continues on next page

Output: q1p

Format: Sum of products

A, B

	00	01	11	10
00	0	0	0	0
01	0	1	1	0
11	0	1	1	0
10	0	1	1	0

q0 B + q1 B

Output: q1p

Format: Product of sums

A, B

	00	01	11	10
00	0	0	0	0
01	0	1	1	0
11	0	1	1	0
10	0	1	1	0

(q1 + q0) B

Output: q0p

Format: Sum of products

A, B

	00	01	11	10
00	0	0	1	1
01	0	0	1	1
11	0	0	1	0
10	0	0	1	1

q1 A + q0 A + A B

Output: q0p

Format: Product of sums

A, B

	00	01	11	10
00	0	0	1	1
01	0	0	1	1
11	0	0	1	0
10	0	0	1	1

A (q1 + q0 + B)

