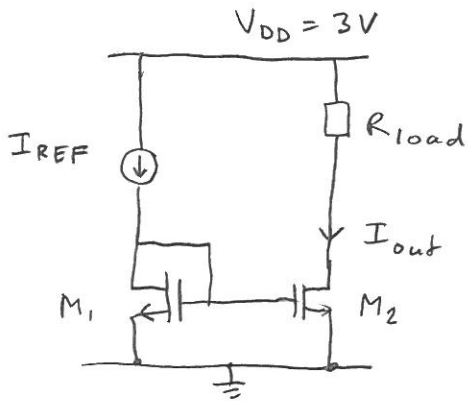


# Example current mirror

2010-01-24/Bengt M.

# 1.




Suppose  $I_{REF} = 50 \mu A$   
and  $I_{out} = 200 \mu A$   
is wanted.

Design # 1

$$\left(\frac{W}{L}\right)_2 = 4 \cdot \left(\frac{W}{L}\right)_1$$

# 2.

Cascode current mirror

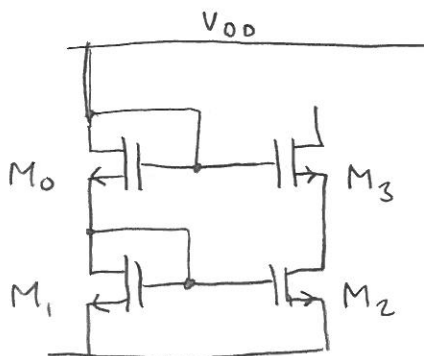


Design # 2

$$\frac{\left(\frac{W}{L}\right)_3}{\left(\frac{W}{L}\right)_0} = \frac{\left(\frac{W}{L}\right)_2}{\left(\frac{W}{L}\right)_1}$$

# Design of a current mirror 2010-01-24 Bengt Molin

## Design #1 Basic mirror

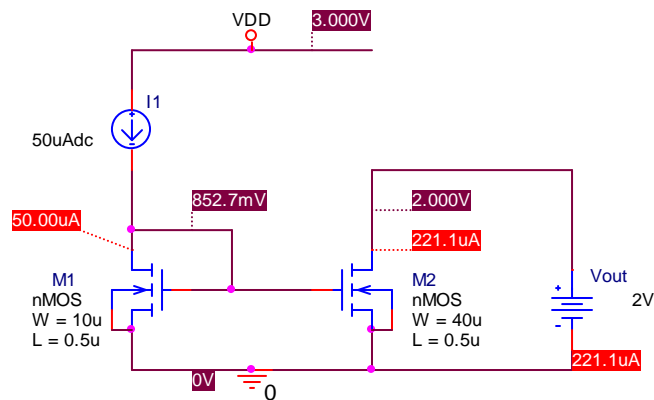


From output file Vout= 2V DC

NAME	M_M2	M_M1
MODEL	nMOS	nMOS
ID	2.21E-04	5.00E-05
VGS	8.53E-01	8.53E-01
VDS	2.00E+00	8.53E-01
VBS	0.00E+00	0.00E+00
VTH	7.00E-01	7.00E-01
VDSAT	1.53E-01	1.53E-01
GM	2.90E-03	6.55E-04
GDS	1.84E-05	4.61E-06

$$r_o = \frac{1}{GDS} = \frac{1}{1.84 \cdot 10^{-5}} = 54.3 \text{ k}\Omega$$


DC-sweep Vout from 0V to 3V

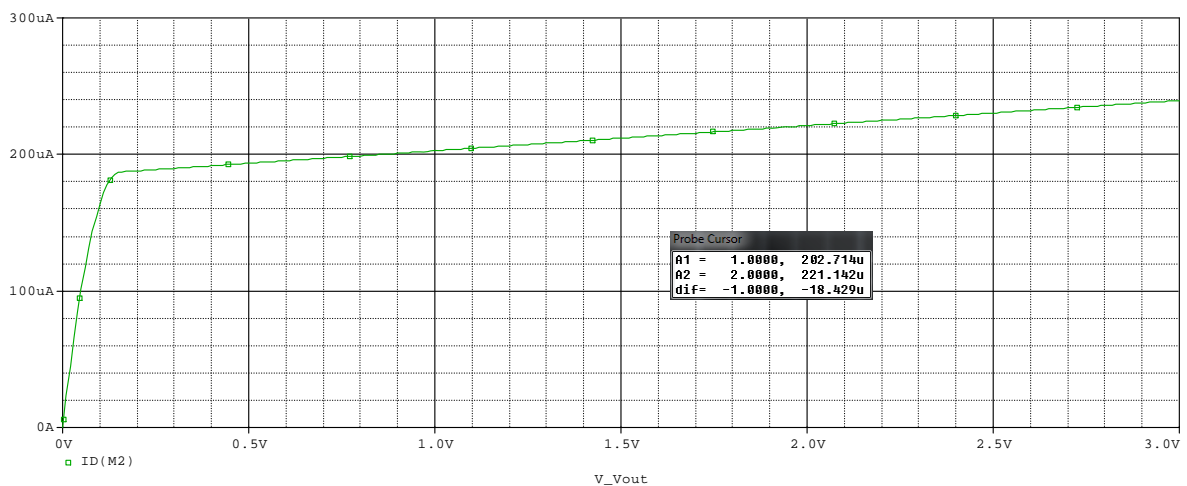

From the slope:  $r_o = \frac{1}{18.429\mu} = 54.3 \text{ k}\Omega$


$\lambda=0.1$  means an increase of current 10% for a 1 V increase of  $V_{DS}$ .

Design #2 Cascode mirror

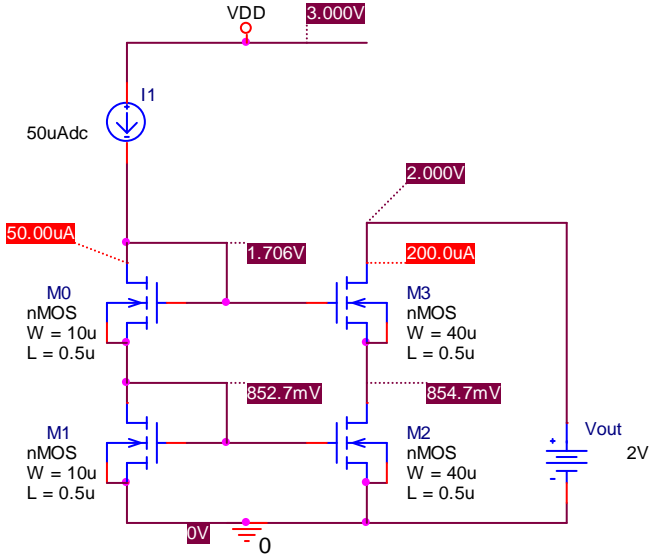

Woow, it works!

DC-sweep  $V_{out}$  from 0V to 3V

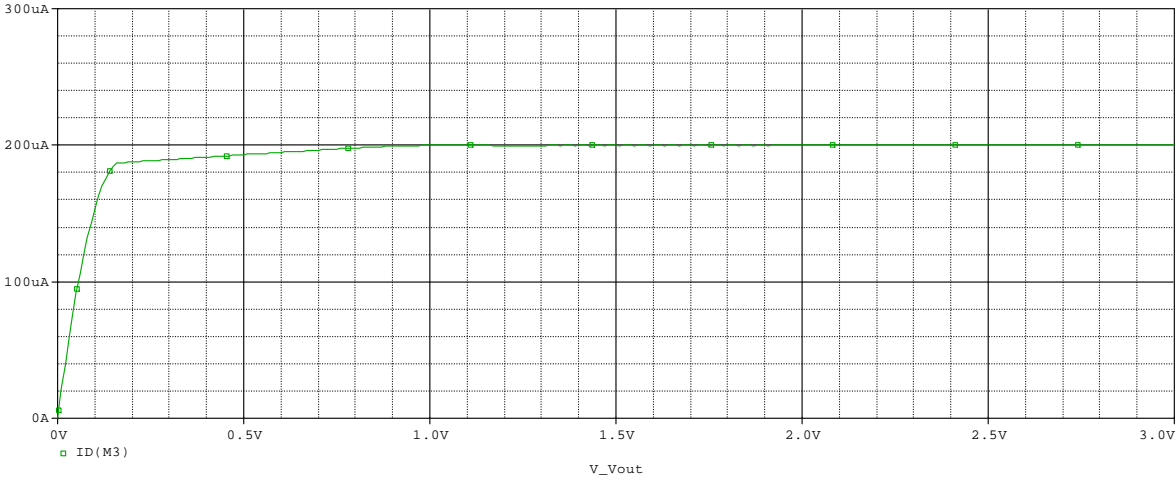

Good current source 200 uA for  $V_{out} > 1V$ .