

Lecture 9

IL2218 Analog electronics, advanced course

- Ch 9 Operational amplifiers
 - One stage OP amps
 - Cascode OP amps, telescopic
 - Design example 9.5
 - Folded Cascode OP amps
 - Design example 9.6
 - Two stage OP amps

Important Parameters

Gain

Input resistance

Output resistance

Small-Signal Bandwidth

Large-Signal Bandwidth

Output Swing


Linearity

Noise and Offset


Supply Rejection

One-stage Operational Amplifier

Single ended output

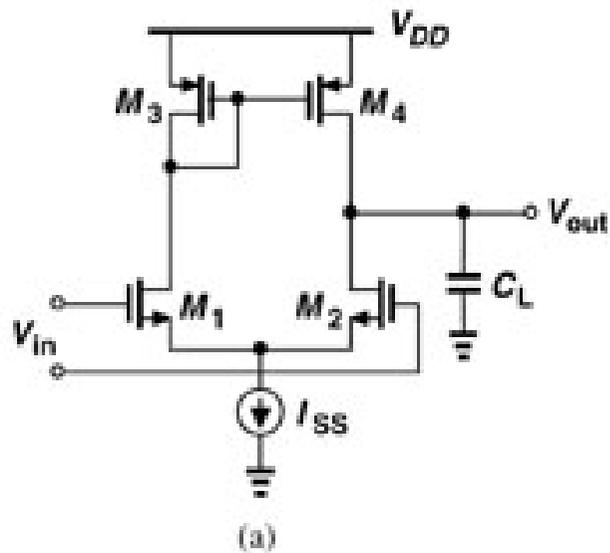


Differential output

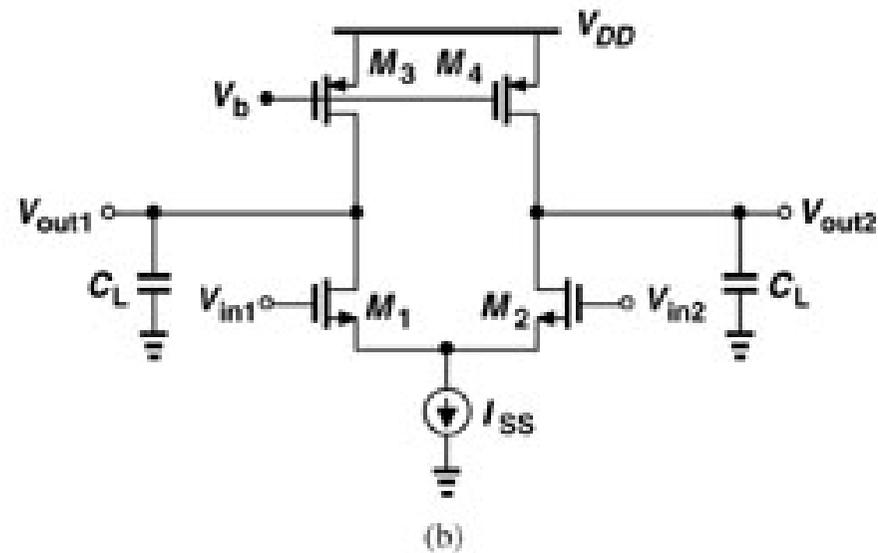


$$A_v \approx g_{mN} (r_{oN} // r_{oP})$$

Max gain ≈ 20

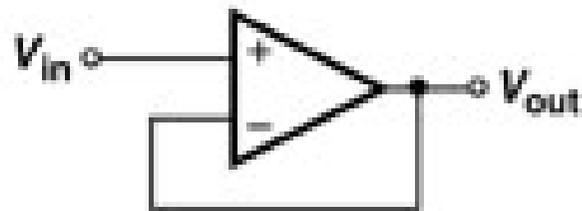One-Stage Op Amp in Unity Gain Configuration




?

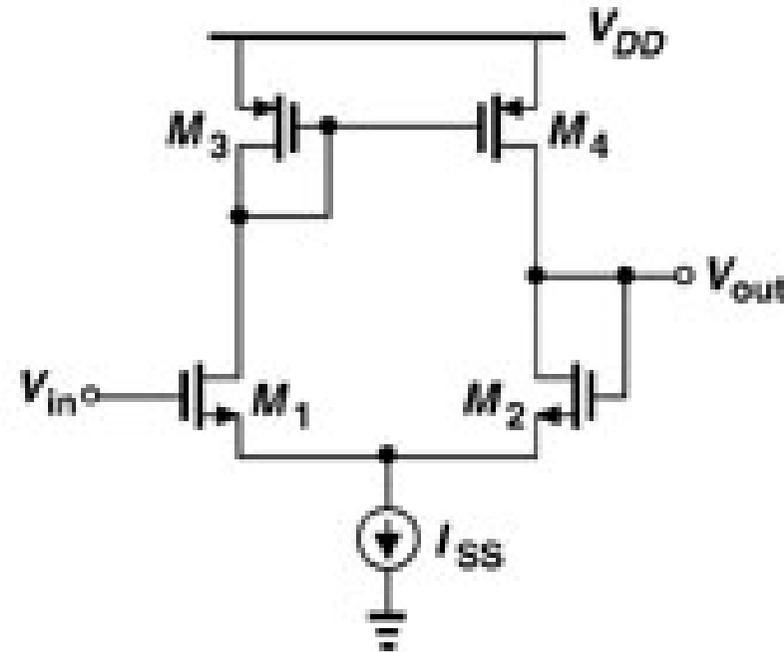


Cascode Op Amps, telescopic

Single ended output

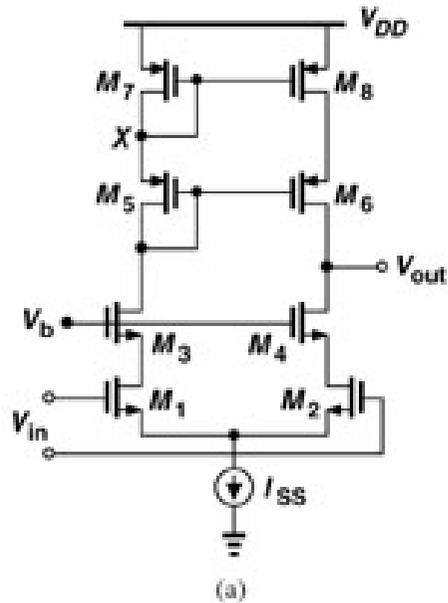

Differential output

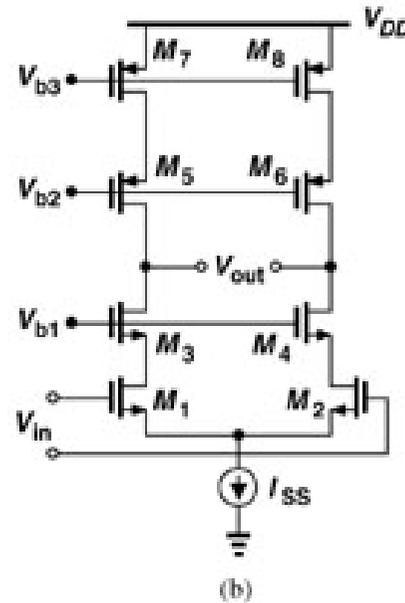


Higher gain

Lower swing


Additional poles

$$A_v \approx g_{mN} \left(g_{mN} r_{oN}^2 \parallel g_{mP} r_{oP}^2 \right)$$

Unity Gain One Stage Cascode

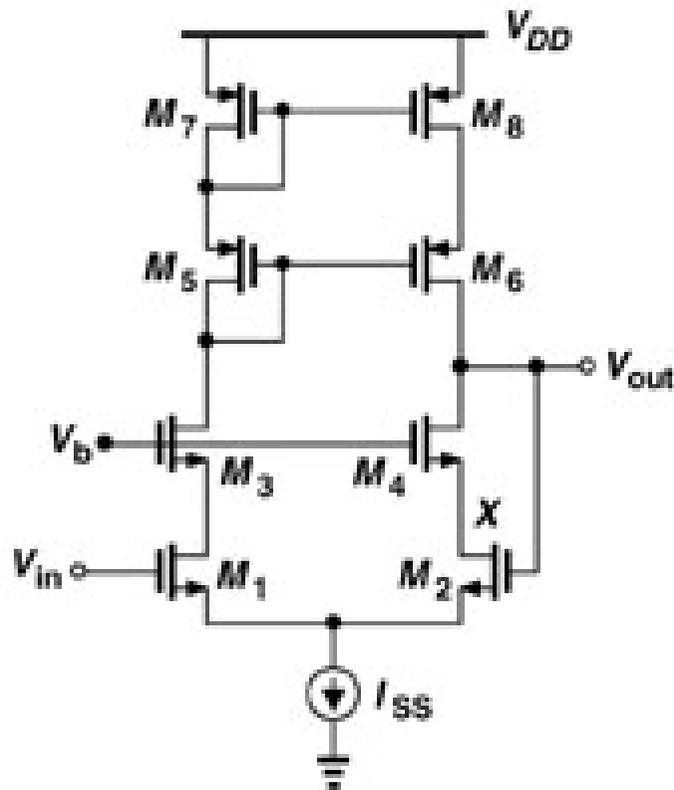

Limited output swing
In unity gain feedback

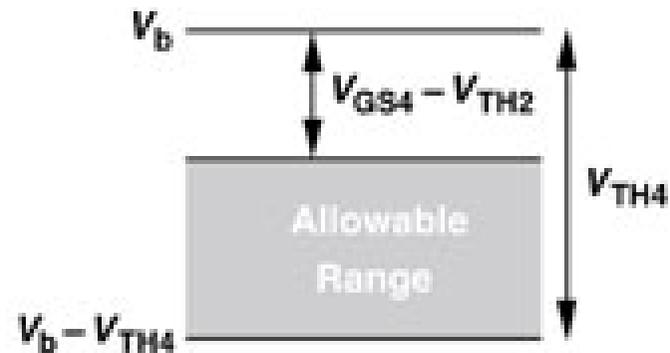

Example 9.5

Example 9.5

Design a fully differential telescopic op amp with the following specifications: $V_{DD} = 3\text{ V}$, differential output swing = 3 V, power dissipation = 10 mW, voltage gain = 2000. Assume $\mu_n C_{ox} = 60\ \mu\text{A}/\text{V}^2$, $\mu_p C_{ox} = 30\ \mu\text{A}/\text{V}^2$, $\lambda_n = 0.1\ \text{V}^{-1}$, $\lambda_p = 0.2\ \text{V}^{-1}$ (for an effective channel length of $0.5\ \mu\text{m}$), $\gamma = 0$, $V_{THN} = |V_{THP}| = 0.7\ \text{V}$.



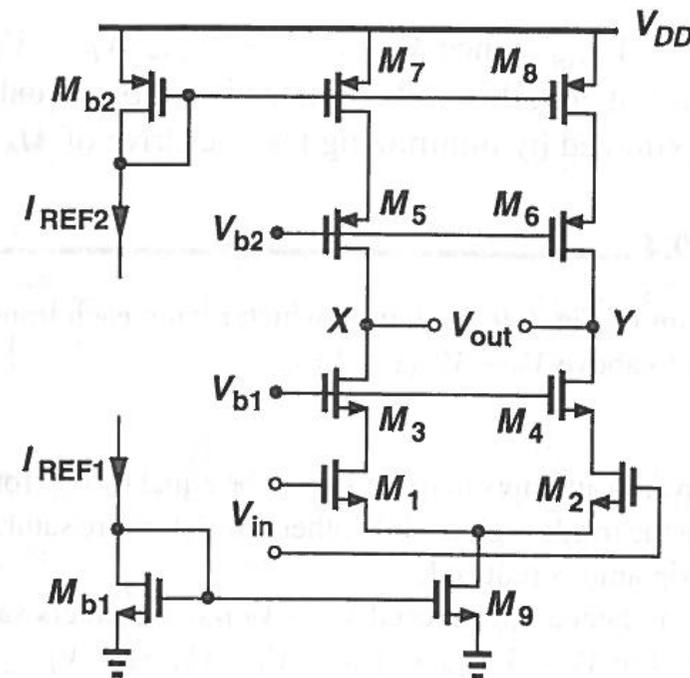


Figure 9.10

Telescopic Cascode Op Amps

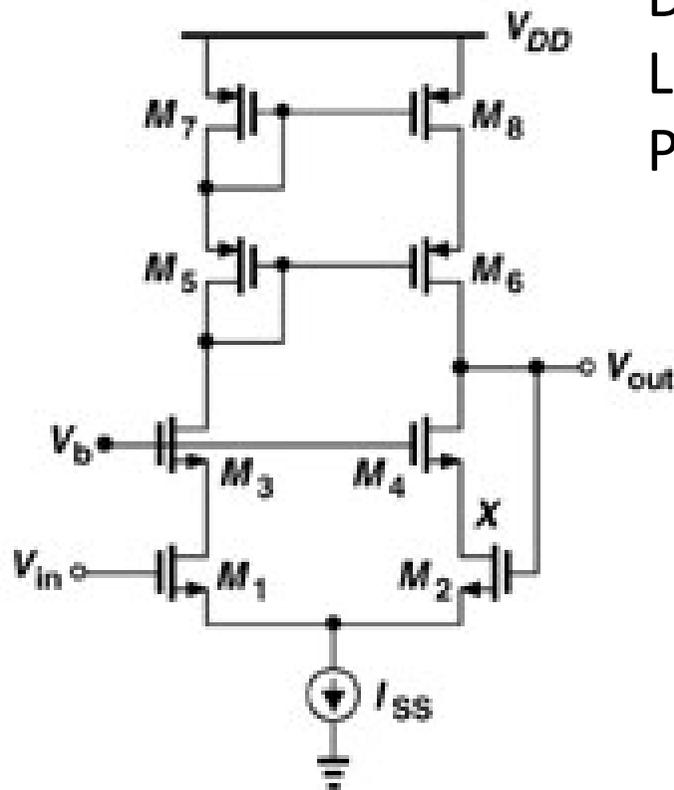

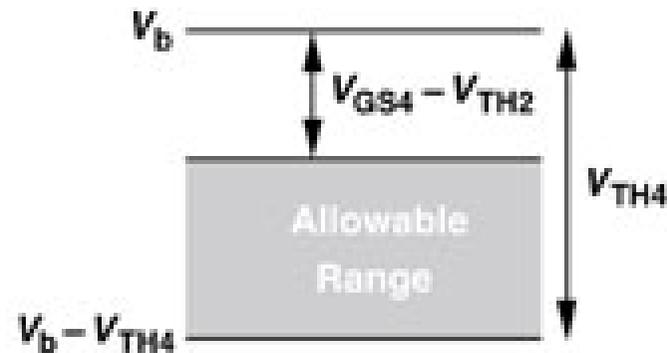
Drawbacks:
 Limited output swing
 Problem to short input and output




$$V_{\max} - V_{\min} = V_{TH4} - (V_{GS4} - V_{TH2})$$

Maximized by minimizing the overdrive of M_4 , but always less than V_{TH2}

Folded Cascode Amplifier

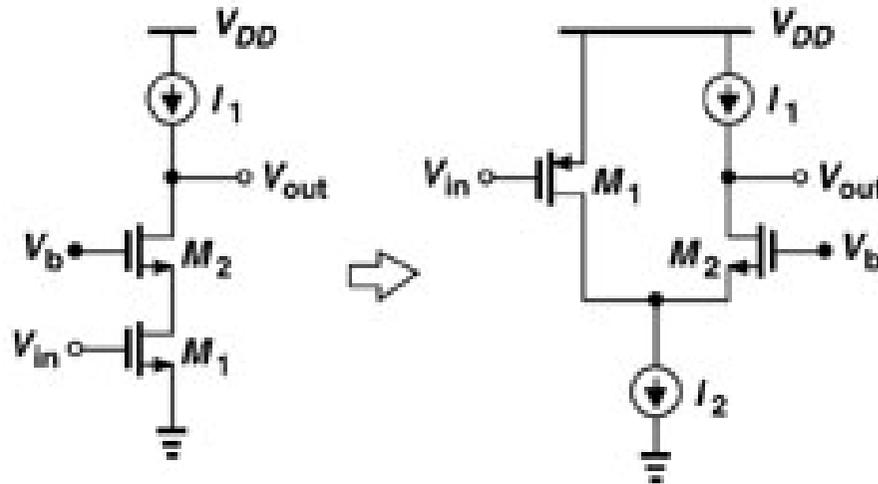


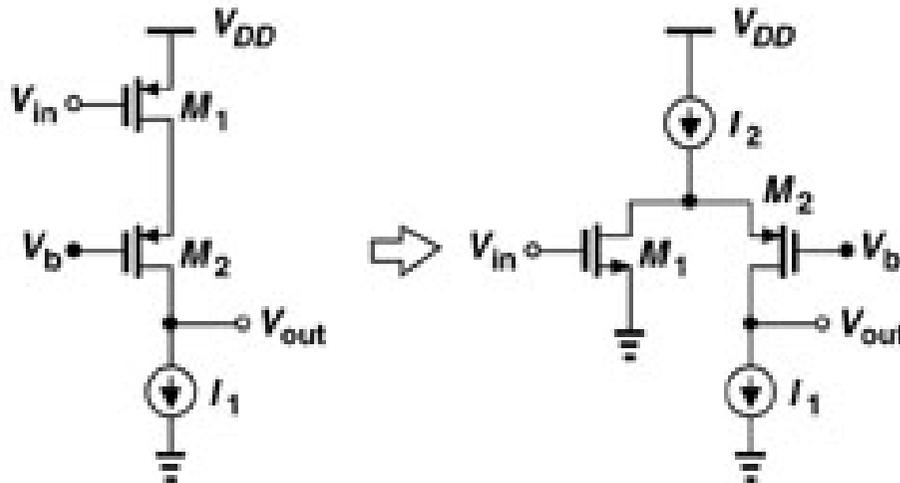The small signal current generated by M_1 flows through M_2 and the load




$$A_v \approx g_{m1} R_{out}$$

Folded Cascode Op Amps

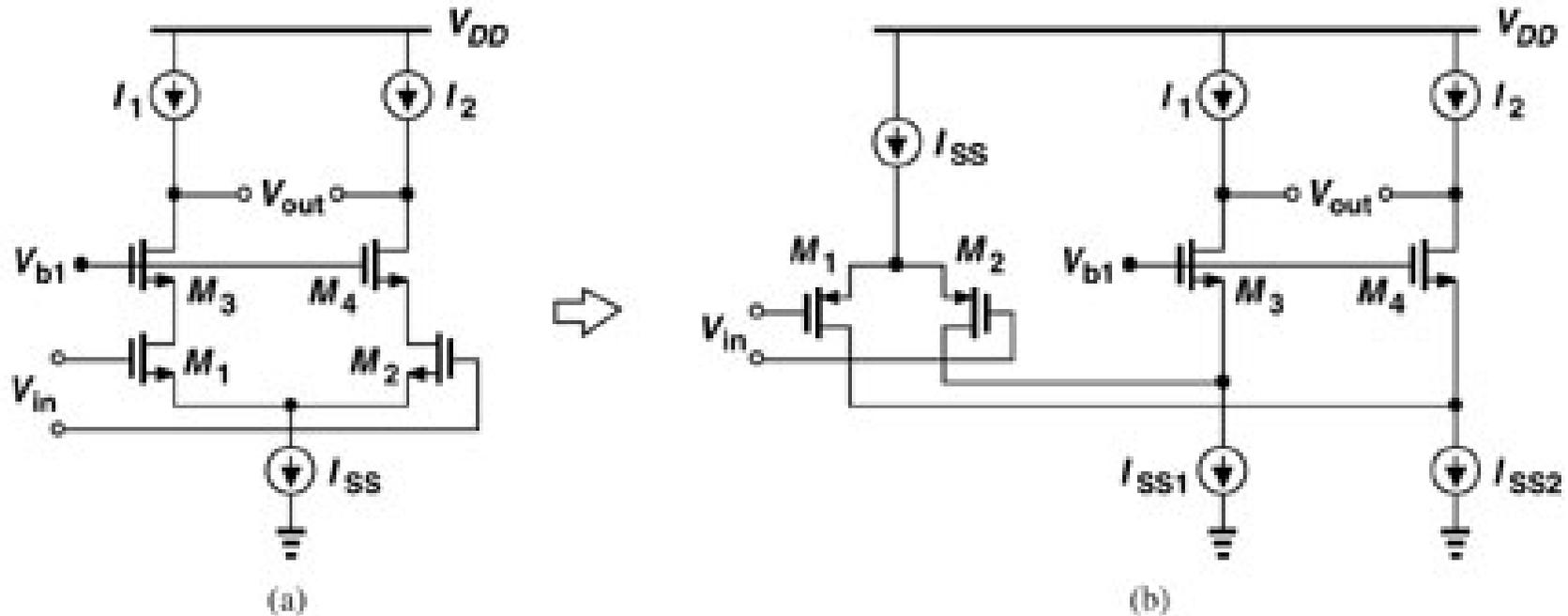

Folded Cascode Op Amps

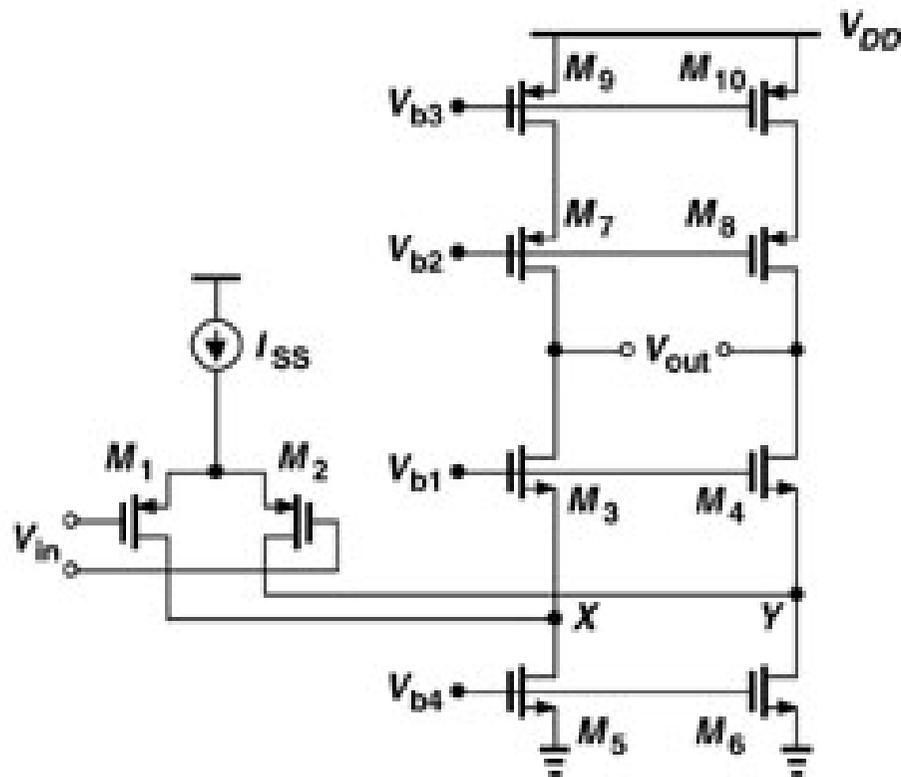

Why, so many transistors?


Swing

Lower end $V_{OD3} + V_{OD5}$

Upper end $V_{DD} - (|V_{OD7}| + |V_{OD9}|)$



$$|A_v| \approx g_{m1} \{ [(g_{m3} + g_{mb3})r_{o3}(r_{o1} \parallel r_{o5})] // [(g_{m7} + g_{mb7})r_{o7}r_{o9}] \}$$

Design example 9.6

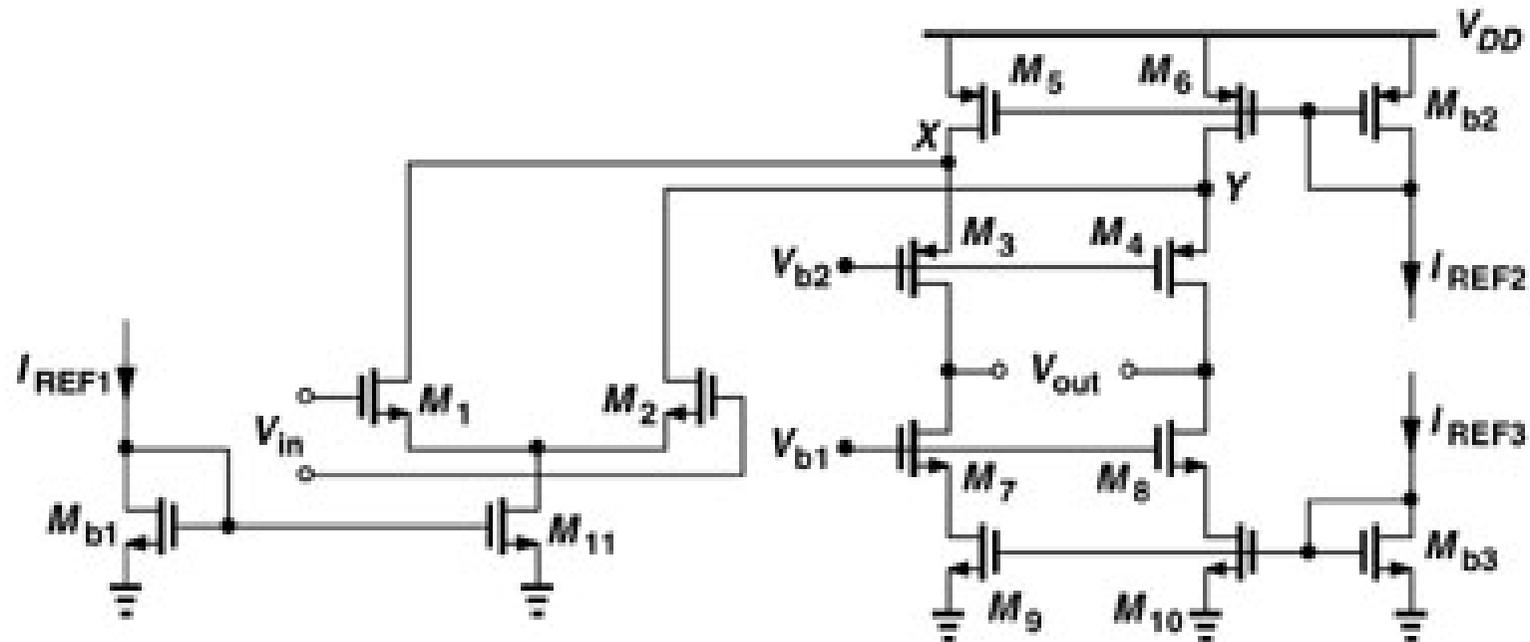

Study the example, compare with example 9.5!

Two-Stage Op Amps

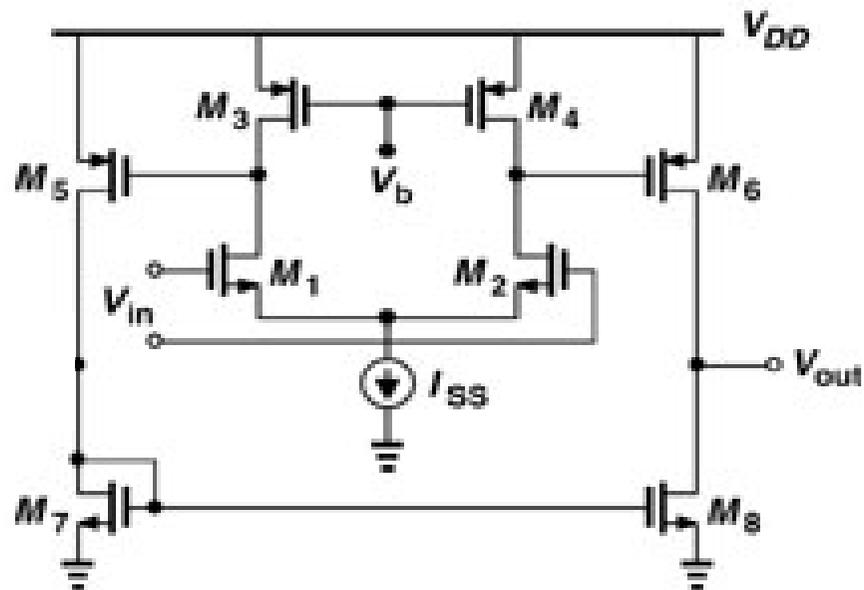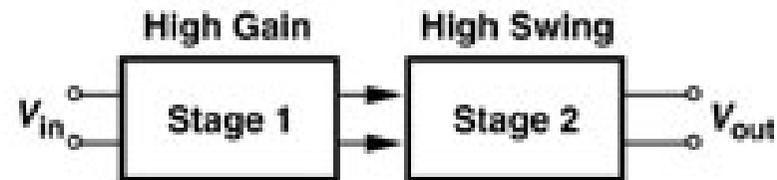


Gain= ?

Common Mode Feedback

In high gain amplifiers, we wish a p -type current source to balance a n -type current source.

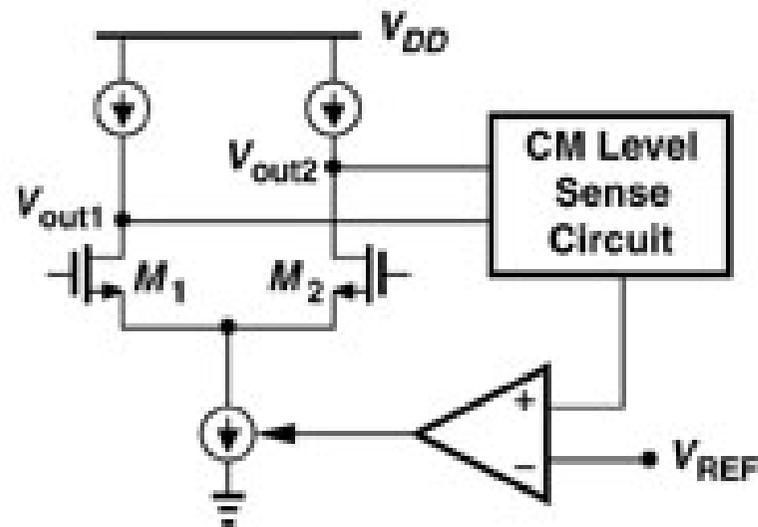Mismatches can drive p -type or n -type current source into triode region.



If the output CM level requires calculation on device properties, then it is poorly defined.