

Lecture 10

IL2218 Analog electronics, advanced course


- Ch 9 Operational amplifiers
 - One stage OP amps
 - Folded Cascode OP amps
 - Design example 9.6
 - Two stage OP amps
- Ch 10 Stability
 - Multipole systems
 - Phase margin

2012-02-20

IL2218 Analog electronics, advanced course KTH/ICT/EKT VT12 /BM

1


Telescopic Cascode Op Amps

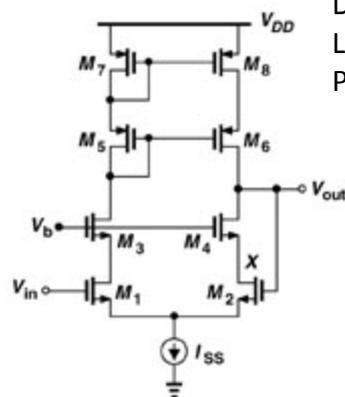

Drawbacks:

Limited output swing

Problem to short input and output

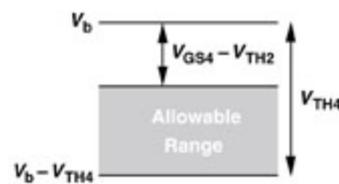

$$V_{\max} - V_{\min} = V_{TH4} - (V_{GS4} - V_{TH2})$$


Maximized by minimizing the overdrive of M_4 , but always less than V_{TH2}

2012-02-20

IL2218 Analog electronics, advanced course KTH/ICT/EKT VT12 /BM

2


Folded Cascode Amplifier

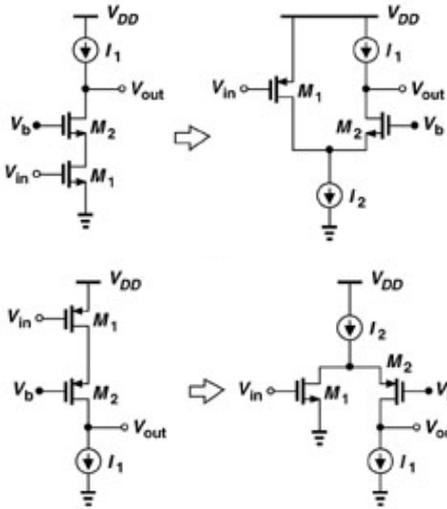


The small signal current generated by M_1 flows through M_2 and the load

$$A_v \approx g_{m1} R_{out}$$

Folded Cascode Op Amps

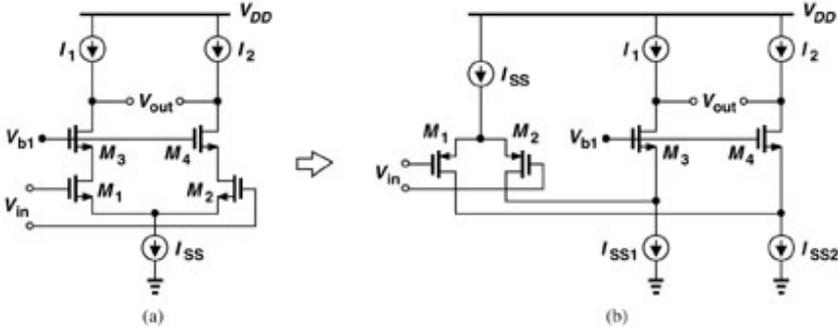

Folded Cascode Op Amps

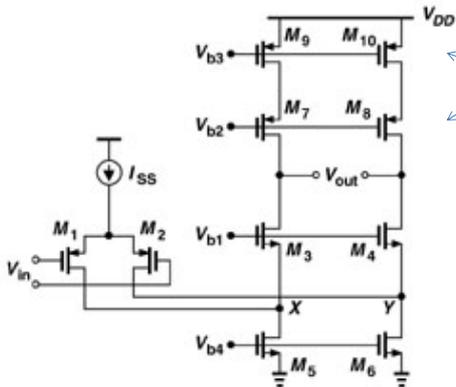

Why, so many transistors?

Swing


Lower end $V_{OD3} + V_{OD5}$

Upper end $V_{DD} - (|V_{OD7}| + |V_{OD9}|)$

$$|A_v| \approx g_{m1} \{ [(g_{m3} + g_{mb3})r_{o3}(r_{o1} \parallel r_{o5})] // [(g_{m7} + g_{mb7})r_{o7}r_{o9}] \}$$


Compared to telescopic: Lower gain, pole at lower frequency

Design example 9.6

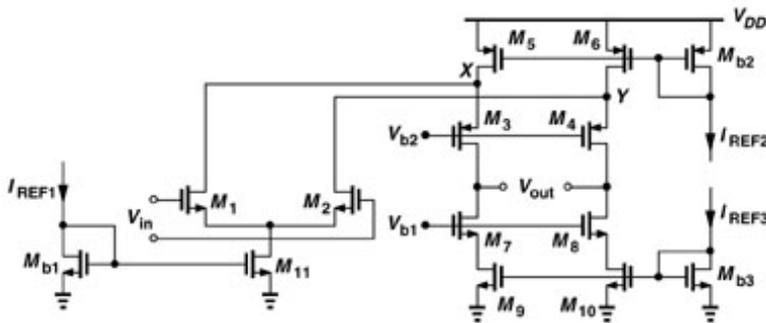

Study the example, compare with example 9.5!

Two-Stage Op Amps

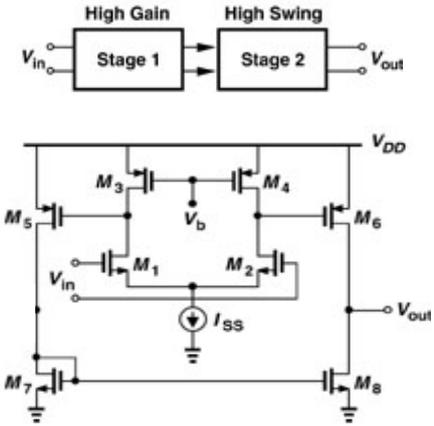


Gain= ?

Common Mode Feedback


In high gain amplifiers, we wish a *p*-type current source to balance a *n*-type current source.

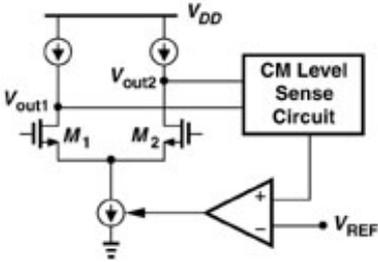Mismatches can drive *p*-type or *n*-type current source into triode region.



If the output CM level requires calculation on device properties, then it is poorly defined.


Stability (chapter 10)

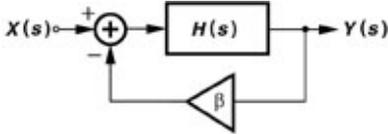

$$\frac{Y}{X}(s) = \frac{H(s)}{1 + \beta H(s)}$$

May oscillate at ω if $|\beta H(j\omega)| = 1$ and $\angle \beta H(j\omega) = -180$ (Barkhausen criteria)


Unstable and Stable Systems

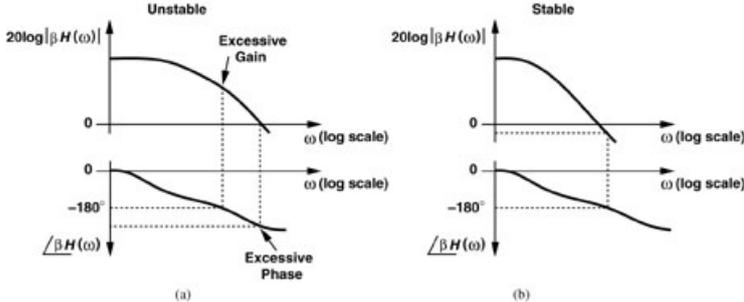


Bode plot for open loop system, poles and zeroes for loop gain

Phase margin


Loop gain
Closed loop gain

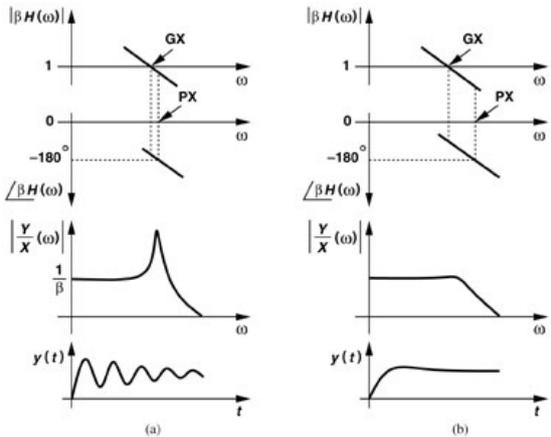

Phase margin and step response

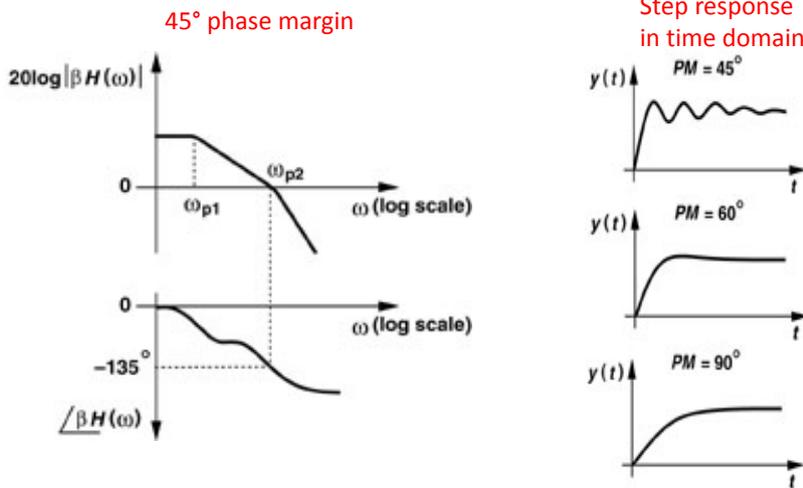


Location of system poles

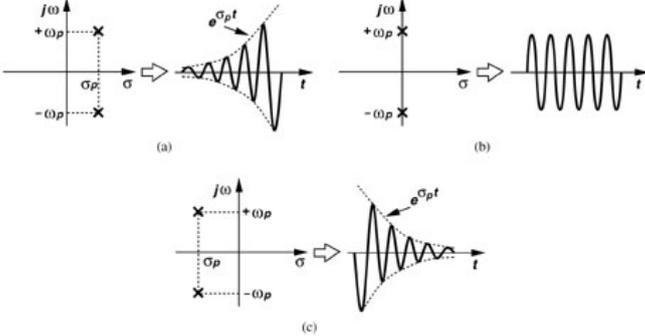


Stability can be studied by plotting the location of poles of the closed loop system.

One-pole system

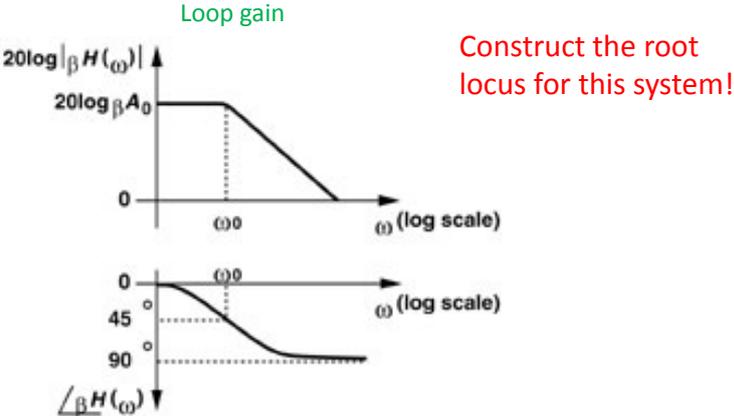

Two-pole system

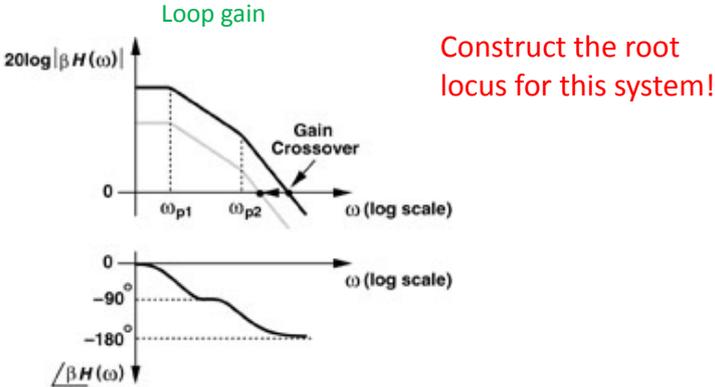

Three-pole system

