

Sinusoidal Steady State

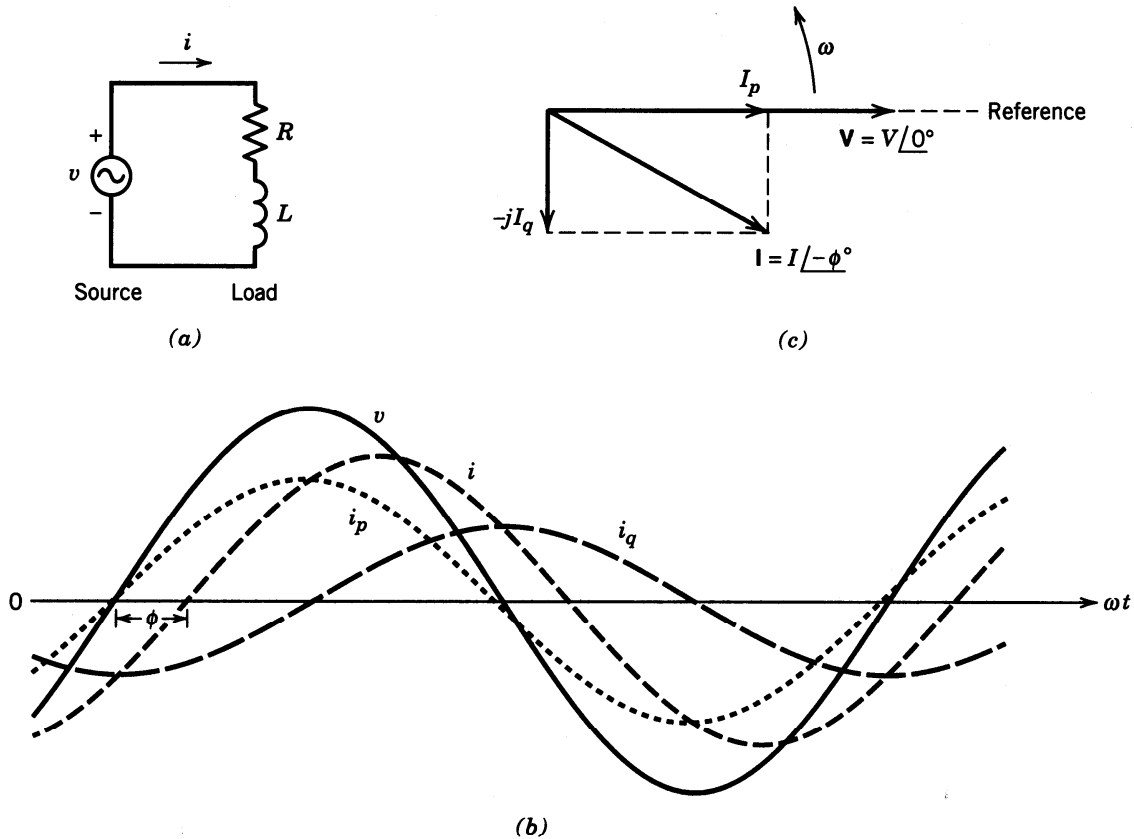


Figure 3-2 Sinusoidal steady state.

Three-Phase Circuit

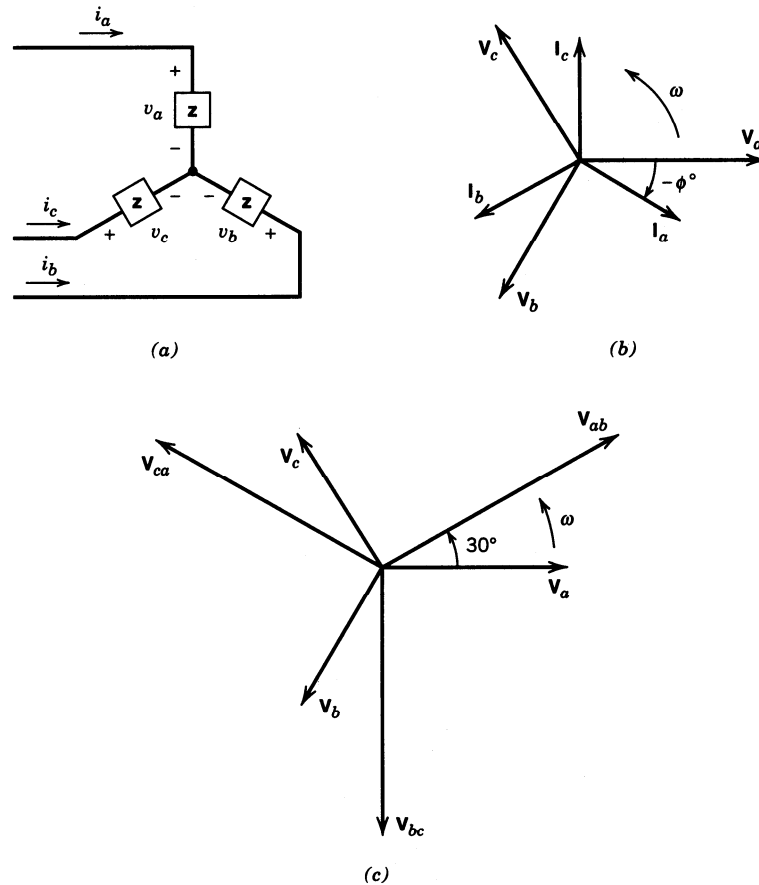


Figure 3-3 Three-phase circuit.

Diode Rectifier

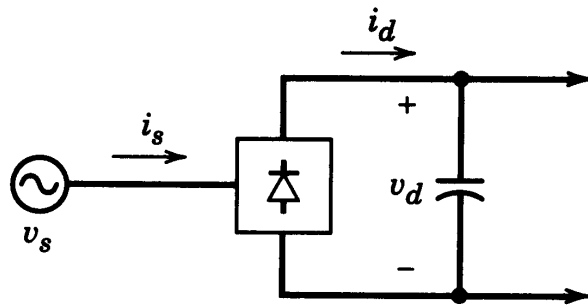


Figure 5-1 Block diagram of a rectifier.



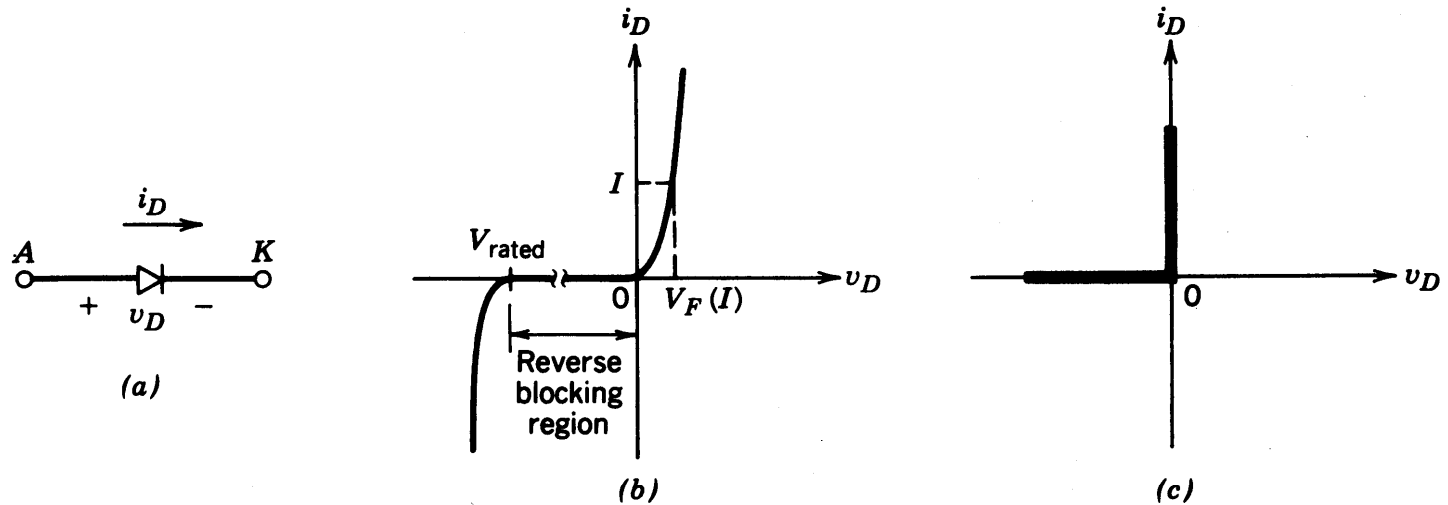


Figure 2-1 Diode: (a) symbol, (b) i - v characteristic, (c) idealized characteristic.

A Simple Circuit

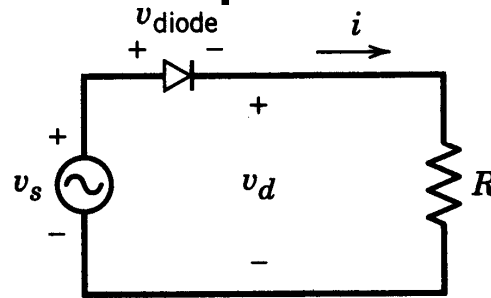

(a)

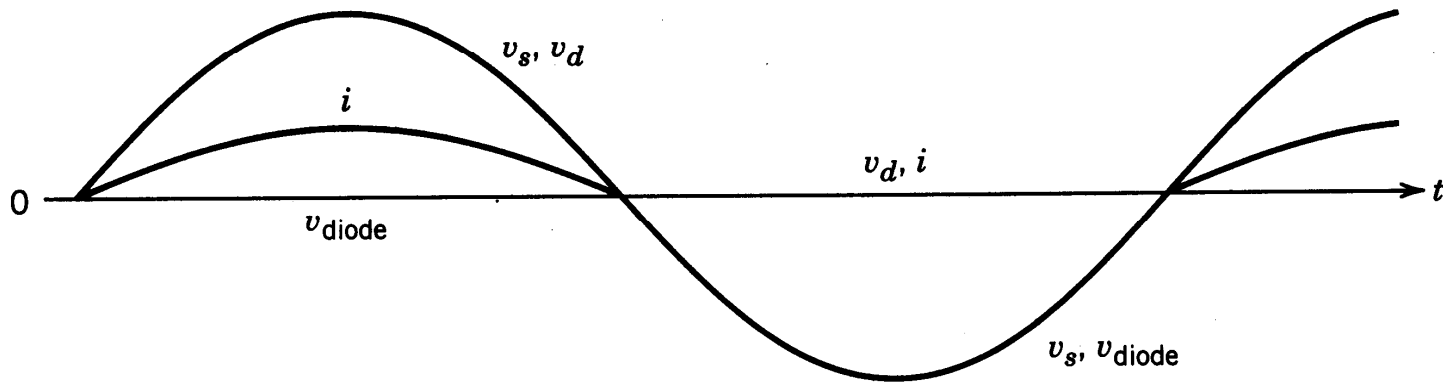

(b)

Figure 5-2 Basic rectifier with a load resistance.

- Resistive load

A Simple Circuit (R - L Load)

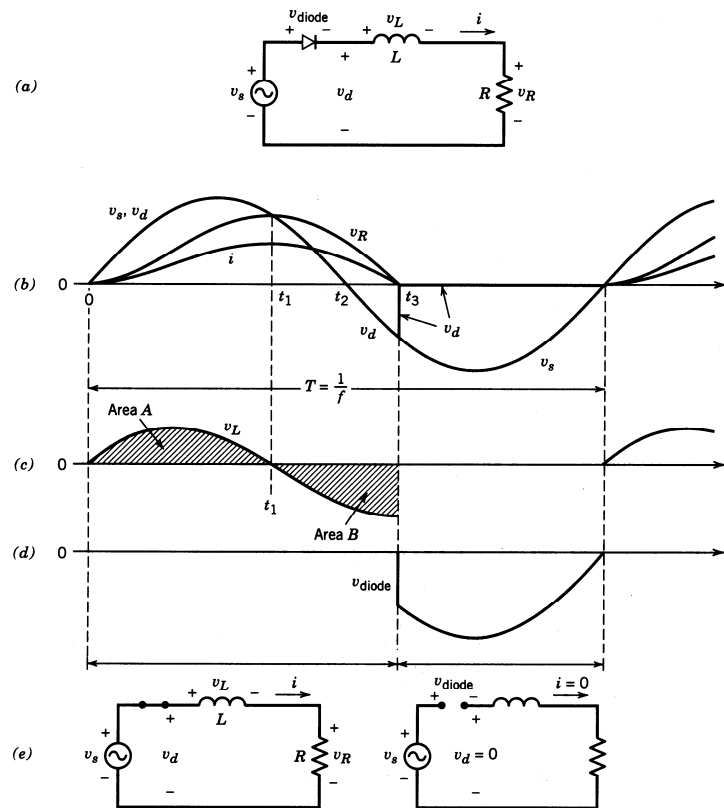


Figure 5-3 Basic rectifier with an inductive load.

- The current continues to flow for a while even after the input voltage has gone negative

A Simple Circuit (Load has a dc back-emf)

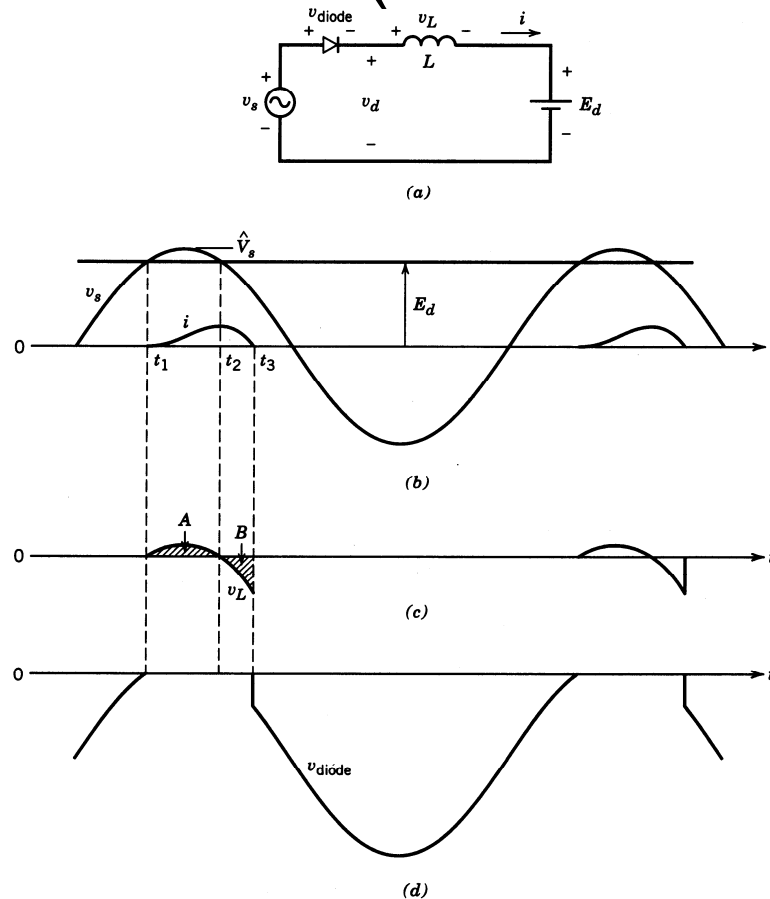


Figure 5-4 Basic rectifier with an internal dc voltage.

- Current begins to flow when the input voltage exceeds the dc back-emf
- Current continues to flow for a while even after the input voltage has gone below the dc back-emf

Single-Phase Diode Rectifier Bridge

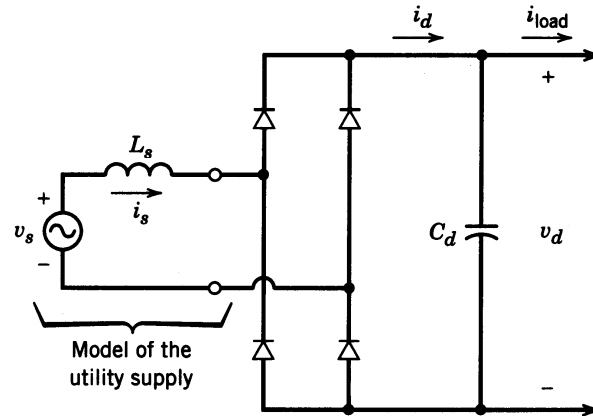


Figure 5-5 Single-phase diode bridge rectifier.

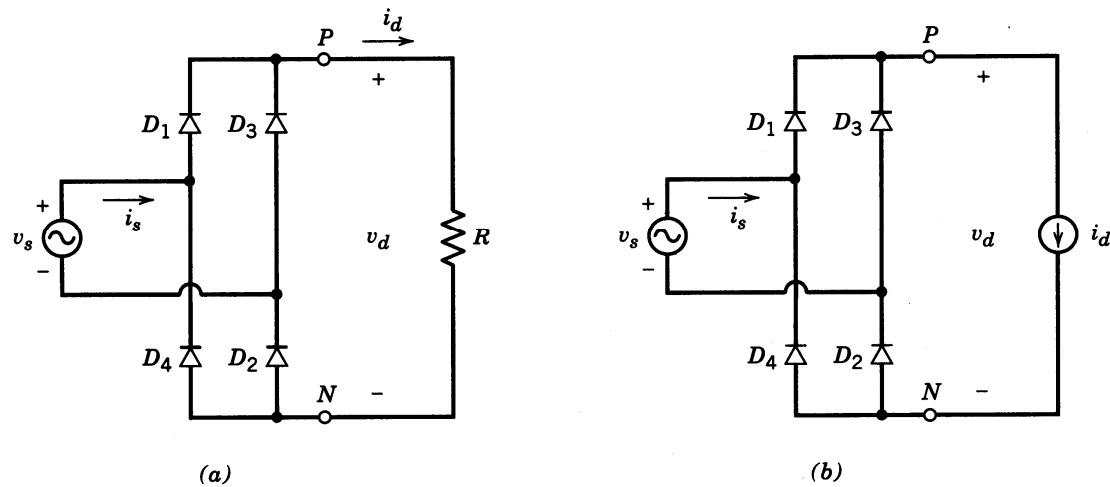


Figure 5-6 Idealized diode bridge rectifiers with $L_s = 0$.

Redrawing Diode-Rectifier Bridge

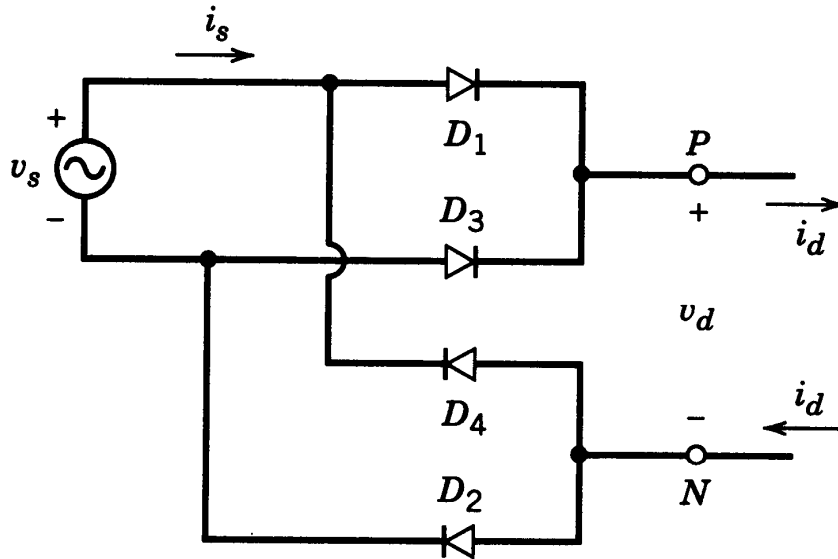


Figure 5-7 Redrawn rectifiers of Fig. 5-6.

- Two groups, each with two diodes

Waveforms with a purely resistive load and a pure direct current at the output

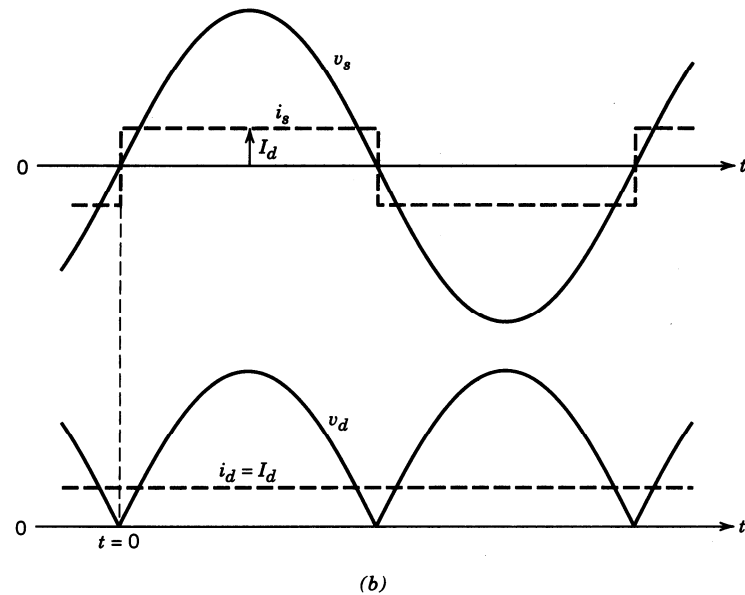
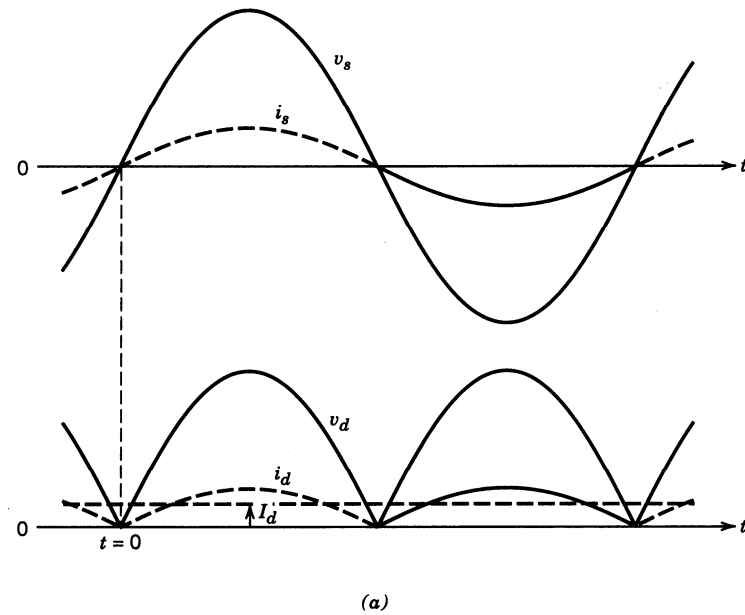


Figure 5-8 Waveforms in the rectifiers of (a) Fig. 5-6a and (b) Fig. 5-6b.

- In both cases, the dc-side voltage waveform is the same

Fourier Analysis

Table 3-1 Use of Symmetry in Fourier Analysis

<i>Symmetry</i>	<i>Condition Required</i>	<i>a_h and b_h</i>
Even	$f(-t) = f(t)$	$b_h = 0 \quad a_h = \frac{2}{\pi} \int_0^{\pi} f(t) \cos(h\omega t) d(\omega t)$
Odd	$f(-t) = -f(t)$	$a_h = 0 \quad b_h = \frac{2}{\pi} \int_0^{\pi} f(t) \sin(h\omega t) d(\omega t)$
Half-wave	$f(t) = -f(t + \frac{1}{2}T)$	$a_h = b_h = 0$ for even h $a_h = \frac{2}{\pi} \int_0^{\pi} f(t) \cos(h\omega t) d(\omega t)$ for odd h $b_h = \frac{2}{\pi} \int_0^{\pi} f(t) \sin(h\omega t) d(\omega t)$ for odd h
Even quarter-wave	Even and half-wave	$b_h = 0$ for all h $a_h = \begin{cases} \frac{4}{\pi} \int_0^{\pi/2} f(t) \cos(h\omega t) d(\omega t) & \text{for odd } h \\ 0 & \text{for even } h \end{cases}$
Odd quarter-wave	Odd and half-wave	$a_h = 0$ for all h $b_h = \begin{cases} \frac{4}{\pi} \int_0^{\pi/2} f(t) \sin(h\omega t) d(\omega t) & \text{for odd } h \\ 0 & \text{for even } h \end{cases}$

Diode-Rectifier Bridge Input Current

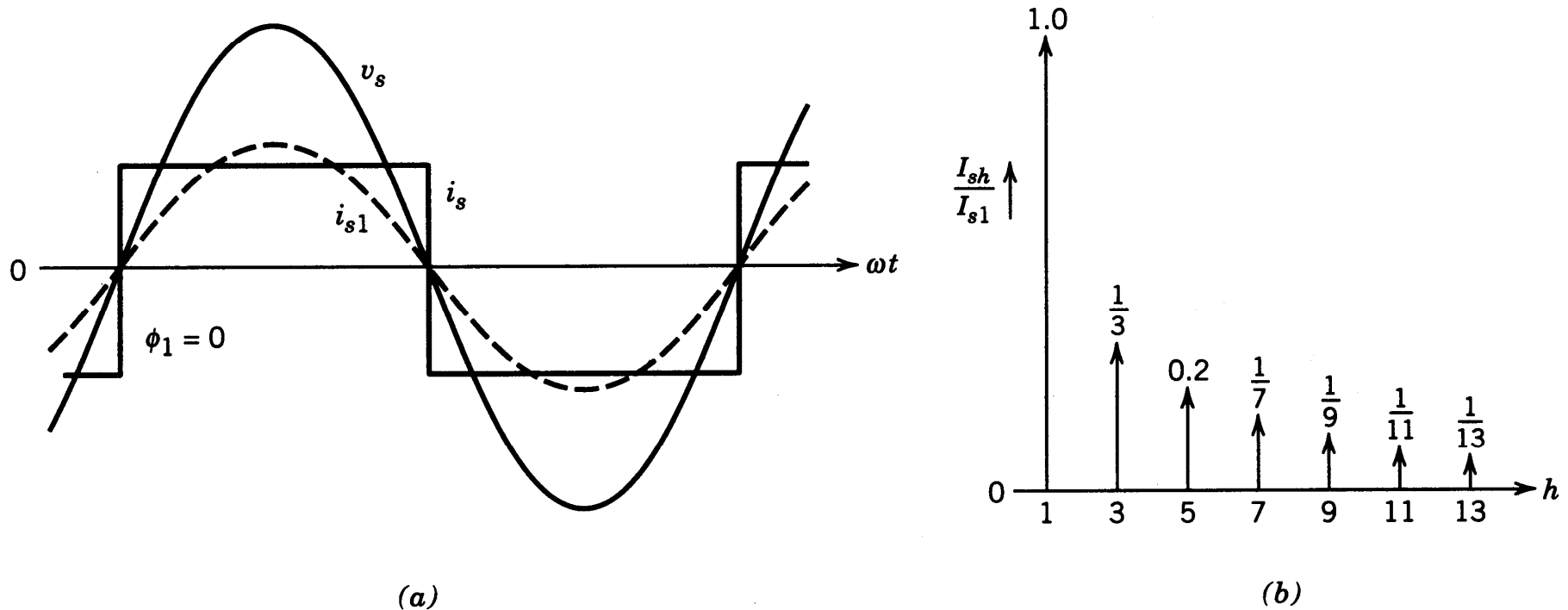


Figure 5-9 Line current i_s in the idealized case.

- Idealized case with a purely dc output current

Diode-Rectifier Bridge Analysis with AC-Side Inductance

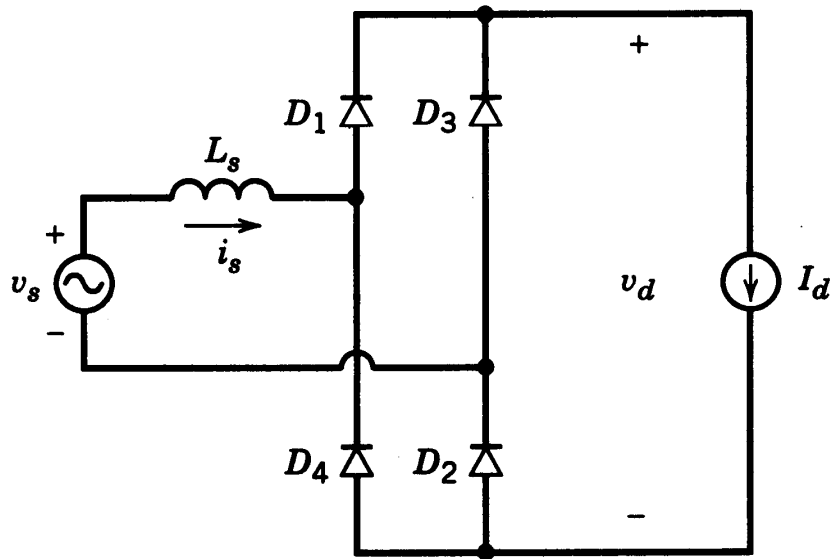


Figure 5-10 Single-phase rectifier with L_s .

- Output current is assumed to be purely dc

Understanding Current Commutation

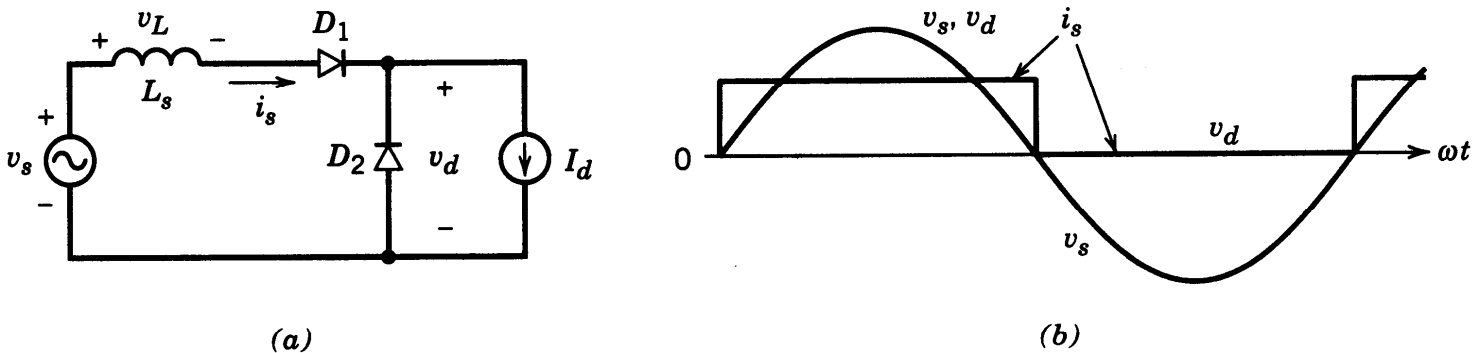


Figure 5-11 Basic circuit to illustrate current commutation. Waveforms assume $L_s = 0$.

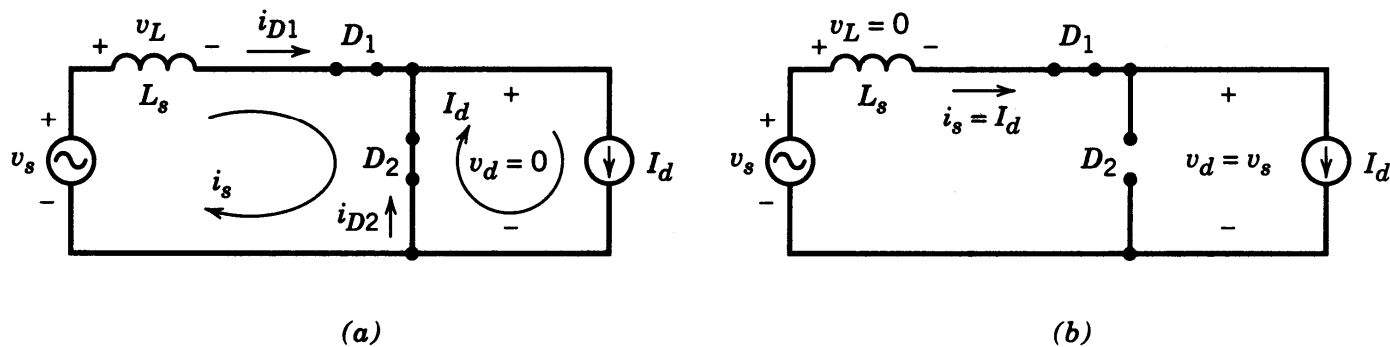


Figure 5-12 (a) Circuit during the commutation. (b) Circuit after the current commutation is completed.

Current Commutation Waveforms

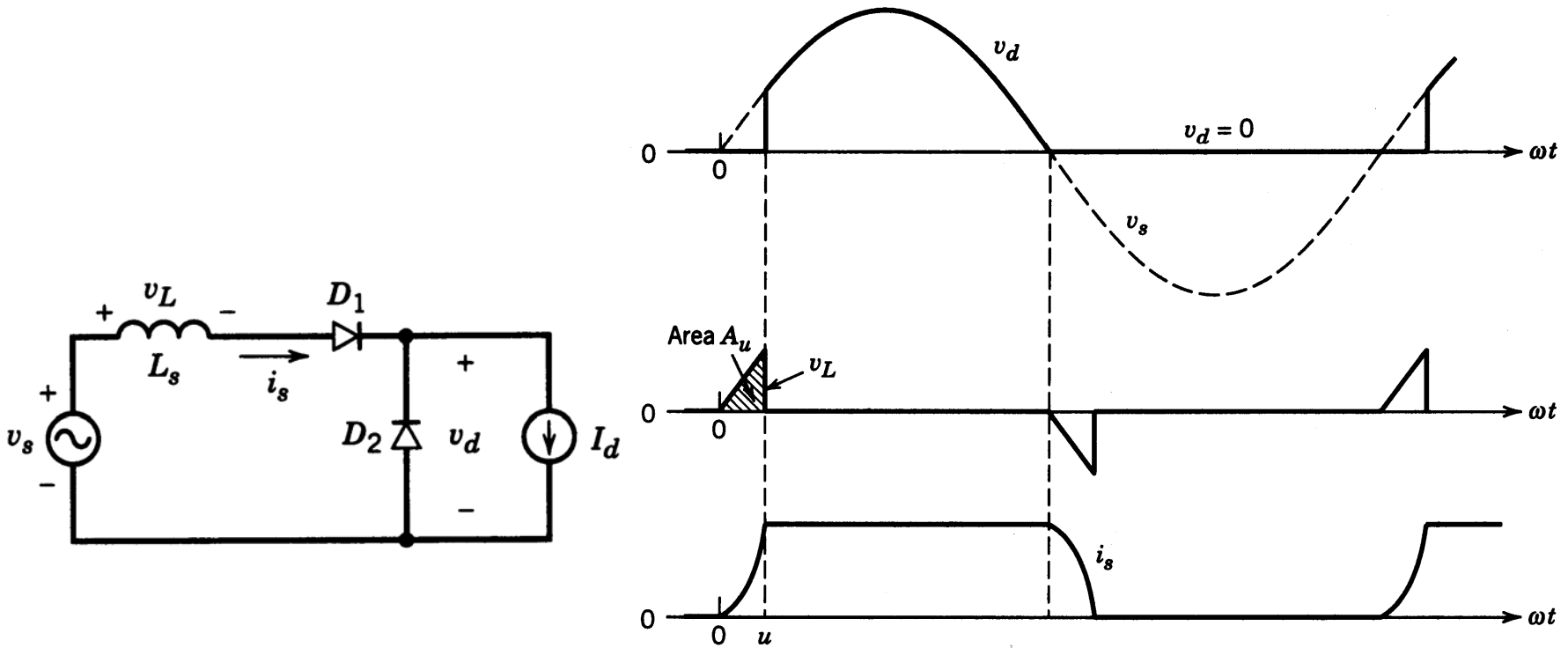


Figure 5-13 Waveforms in the basic circuit of Fig. 5-11. Note that a large value of L_s is used to clearly show the commutation interval.

- Shows the volt-seconds needed to commutate current

Current Commutation in Full-Bridge Rectifier

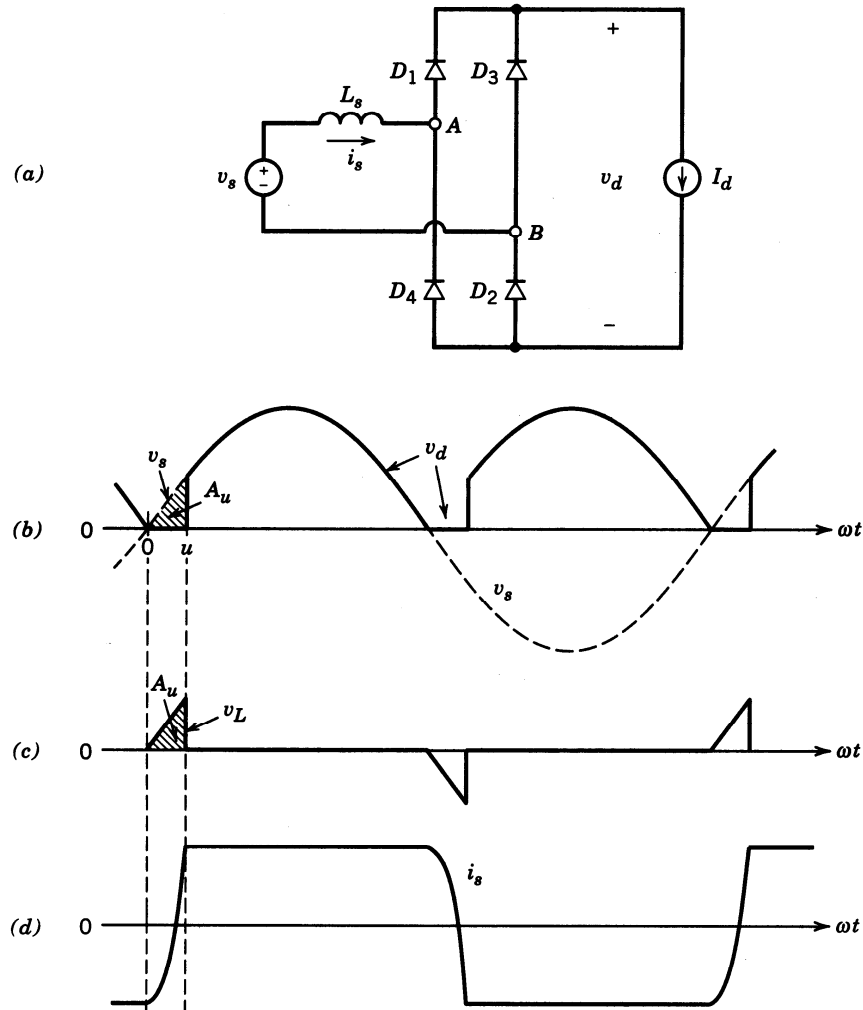


Figure 5-14 (a) Single-phase diode rectifier with L_s . (b) Waveforms.

- Shows the necessary volt-seconds