

Analysis assuming Fictitious Filters

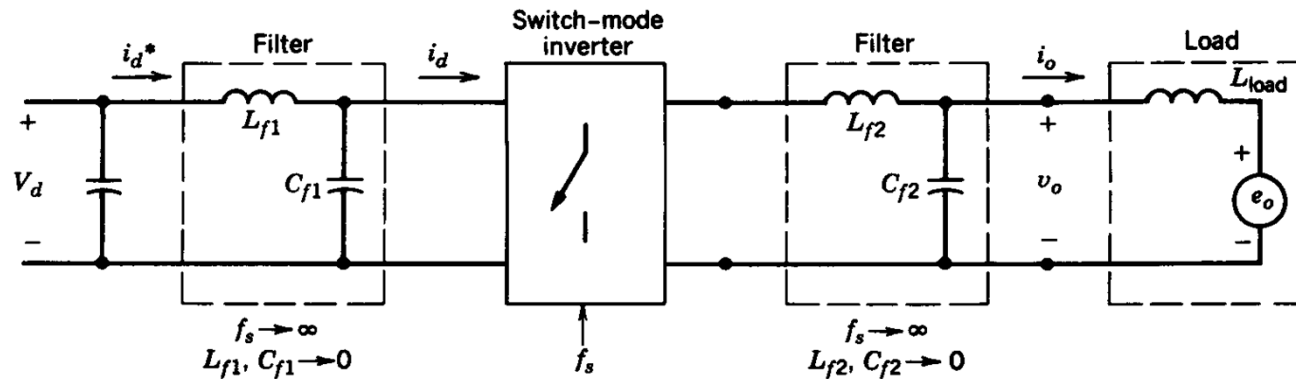


Figure 8-13 Inverter with “fictitious” filters.

- Small fictitious filters eliminate the switching-frequency related ripple

DC-Side Current

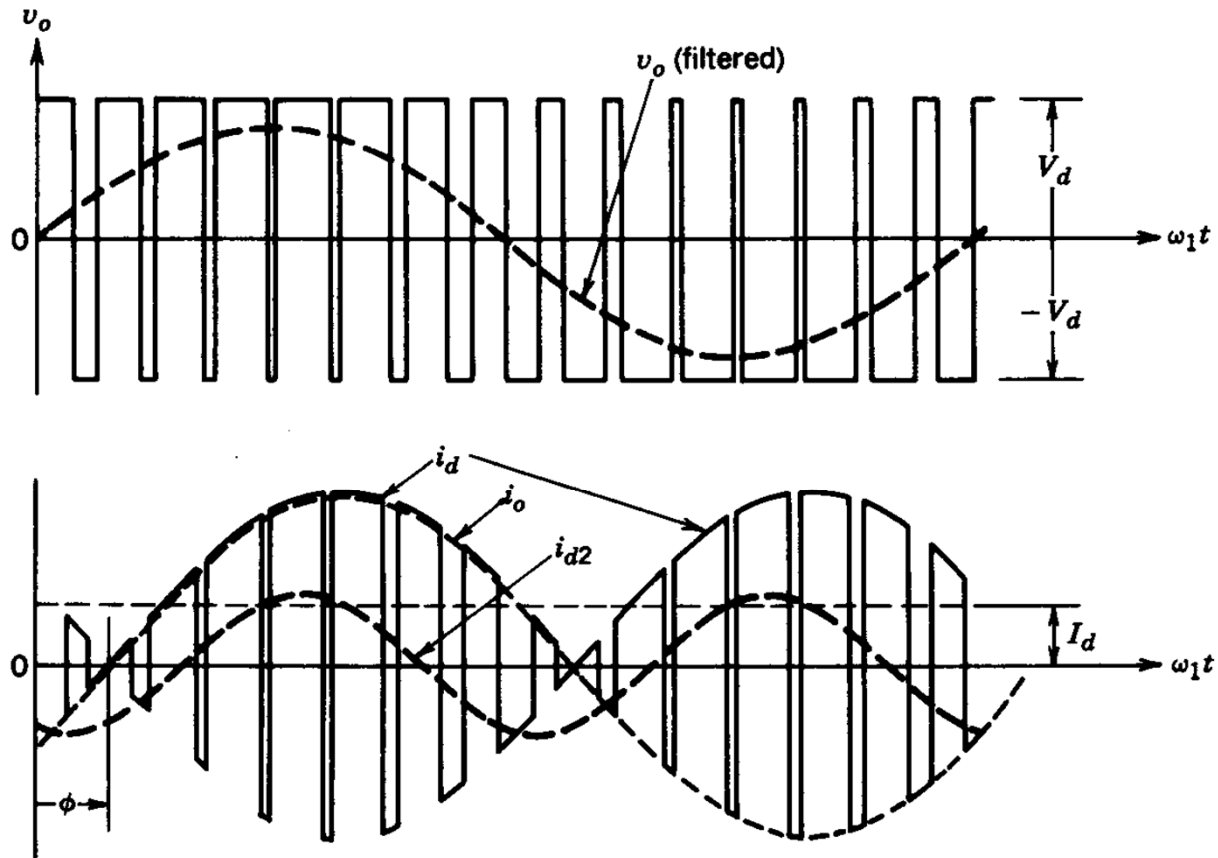


Figure 8-14 The dc-side current in a single-phase inverter with PWM bipolar voltage switching.

- Bi-Polar Voltage switching

Output Waveforms: Uni-polar Voltage Switching

- Harmonic components around the switching frequency are absent

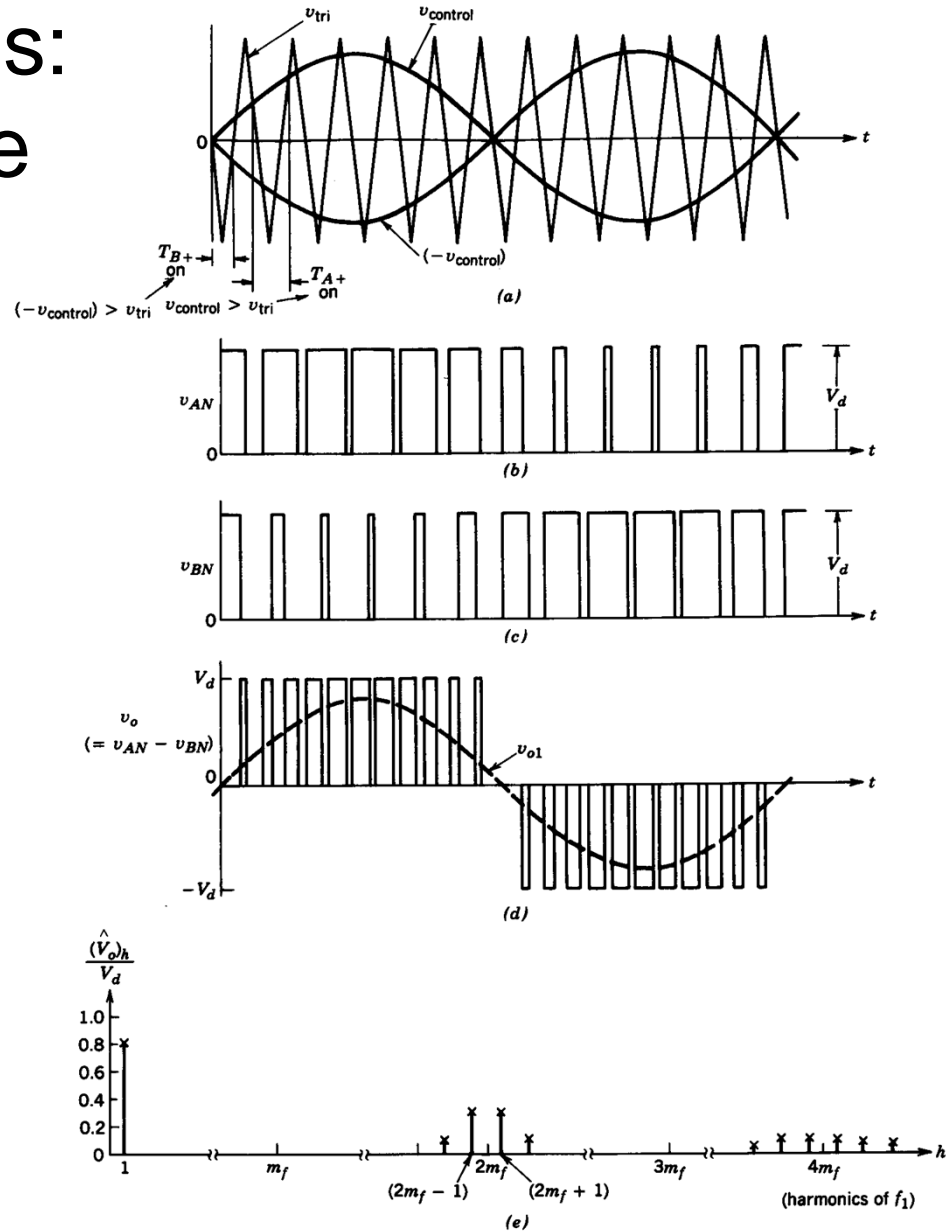


Figure 8-15 PWM with unipolar voltage switching (single phase).

Sinusoidal Synthesis by Voltage Shift

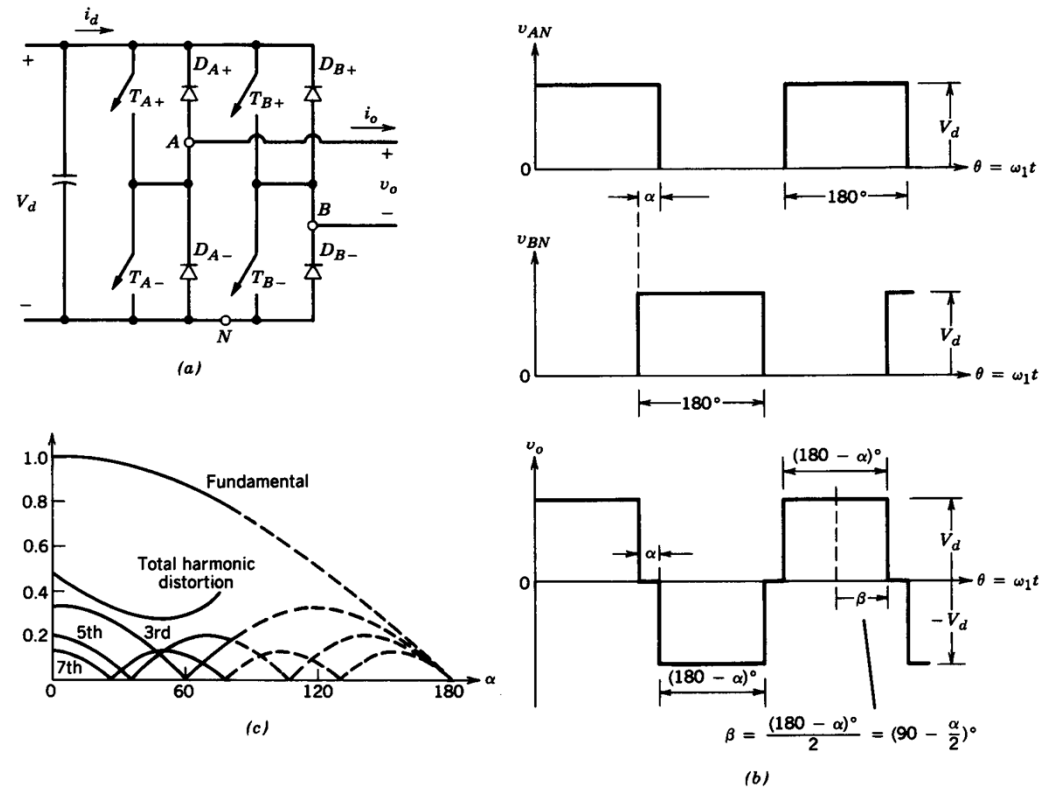


Figure 8-17 Full-bridge, single-phase inverter control by voltage cancellation: (a) power circuit; (b) waveforms; (c) normalized fundamental and harmonic voltage output and total harmonic distortion as a function of α .

- Phase shift allows voltage cancellation to synthesize a 1-Phase sinusoidal output

Single-Phase Inverter

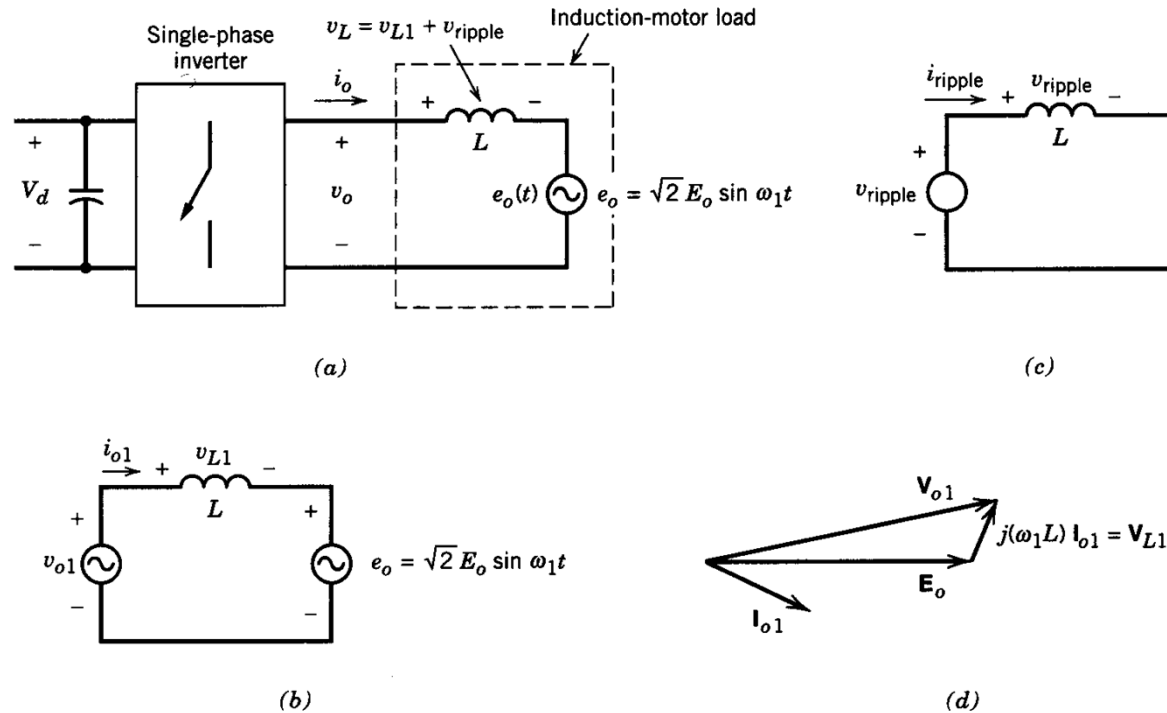


Figure 8-18 Single-phase inverter: (a) circuit; (b) fundamental-frequency components; (c) ripple frequency components; (d) fundamental-frequency phasor diagram.

- Analysis at the fundamental frequency

Square-Wave and PWM Operation

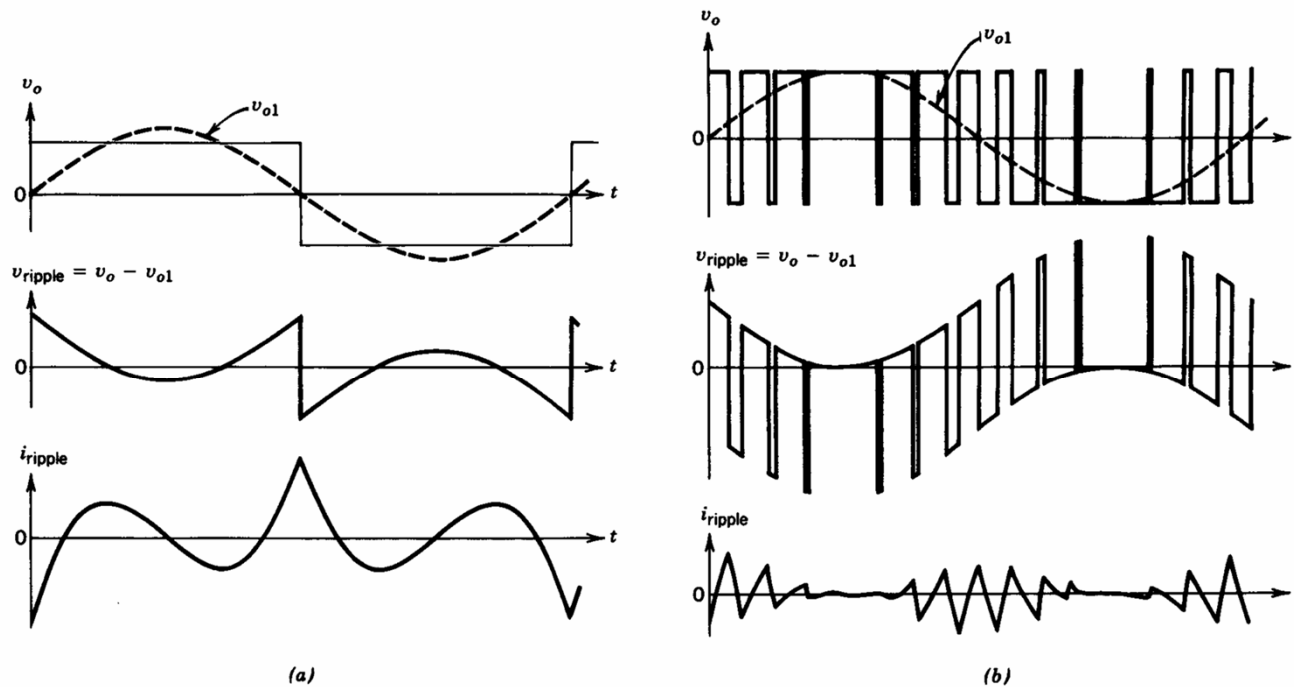


Figure 8-19 Ripple in the inverter output: (a) square-wave switching; (b) PWM bipolar voltage switching.

- PWM results in much smaller ripple current

Three-Phase Inverter

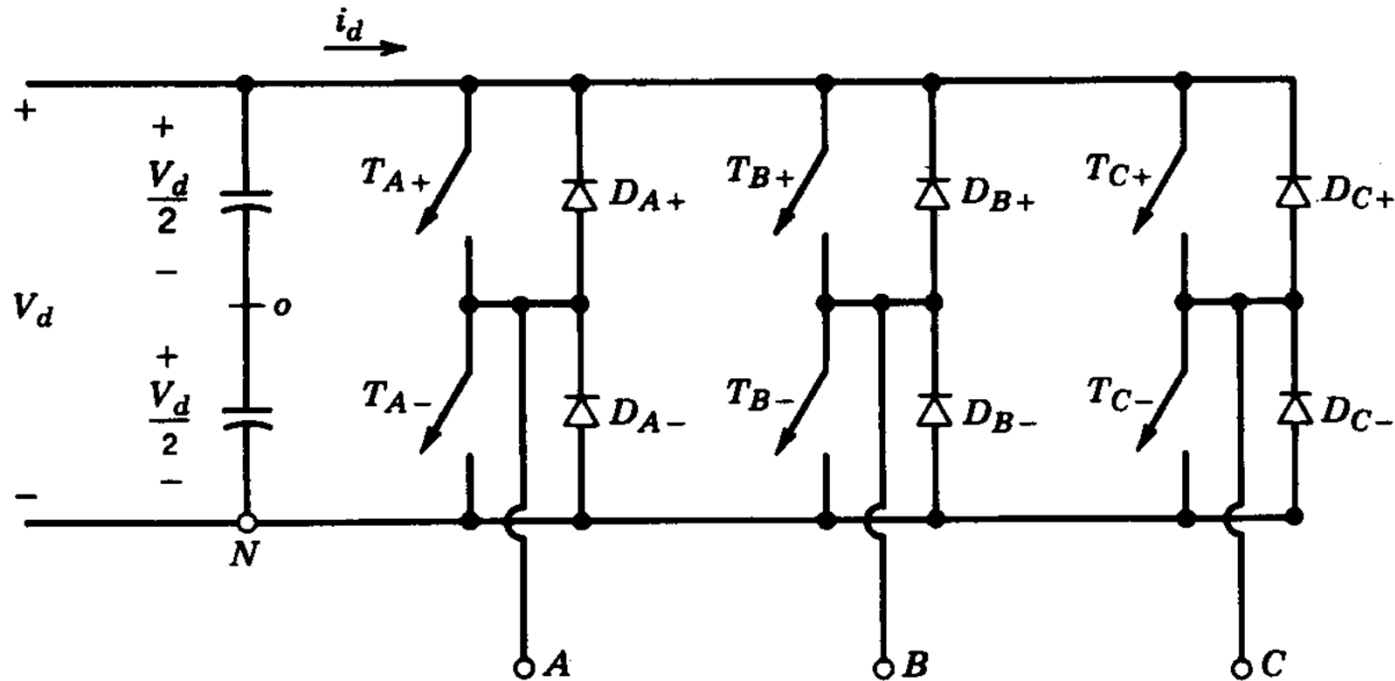


Figure 8-21 Three-phase inverter.

- Three inverter legs; capacitor mid-point is fictitious

Three-Phase PWM Waveforms

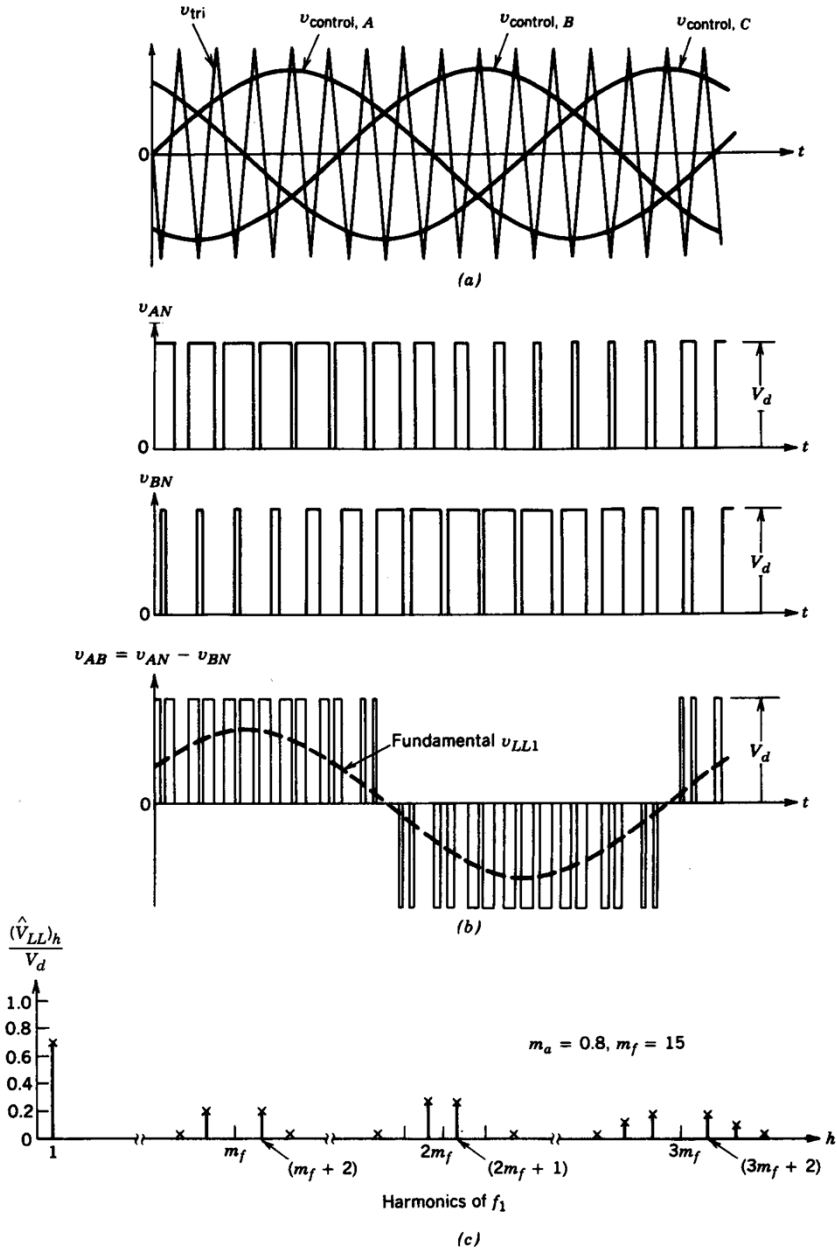


Figure 8-22 Three-phase PWM waveforms and harmonic spectrum.

Three-Phase Inverter: Square-Wave Mode

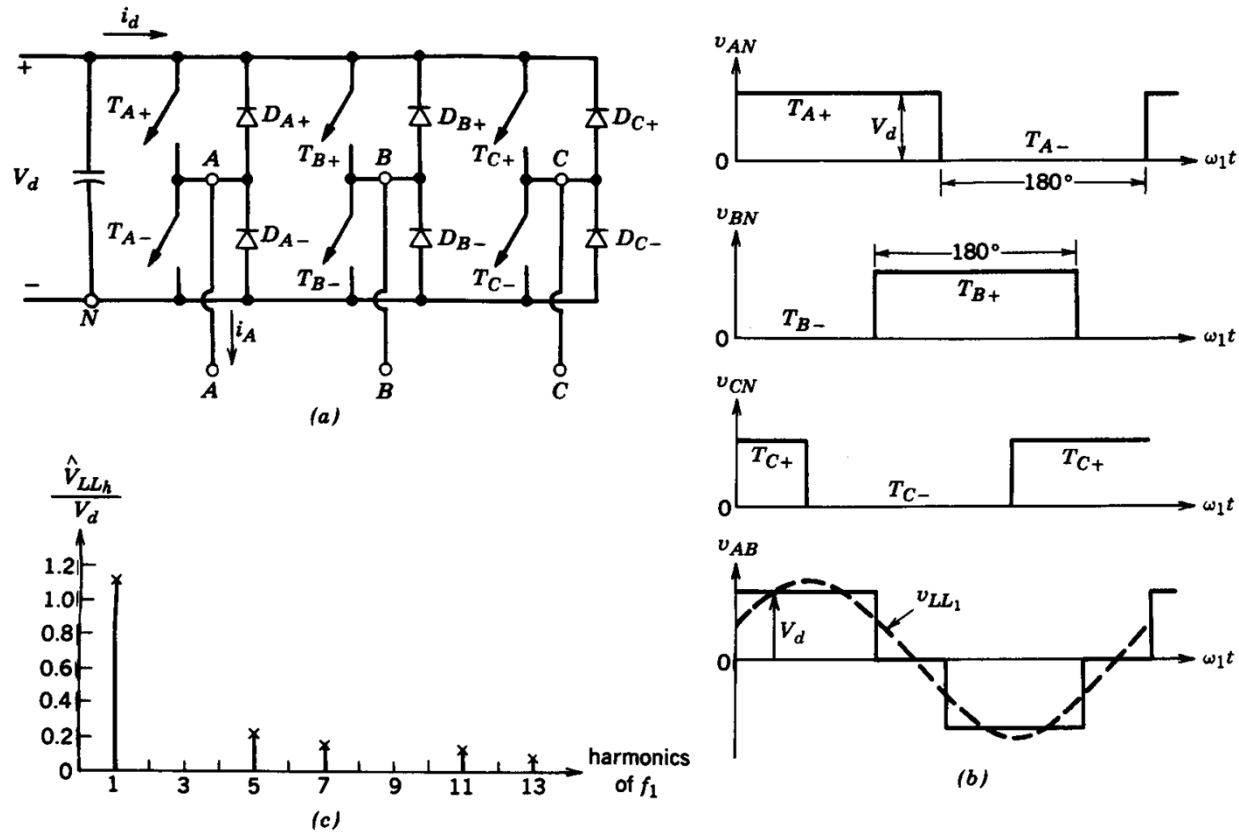


Figure 8-24 Square-wave inverter (three phase).

- Harmonics are of the fundamental frequency

Programmed Harmonic Elimination

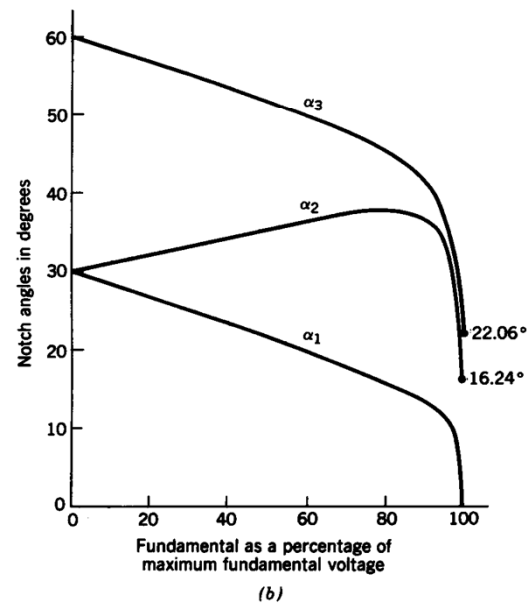
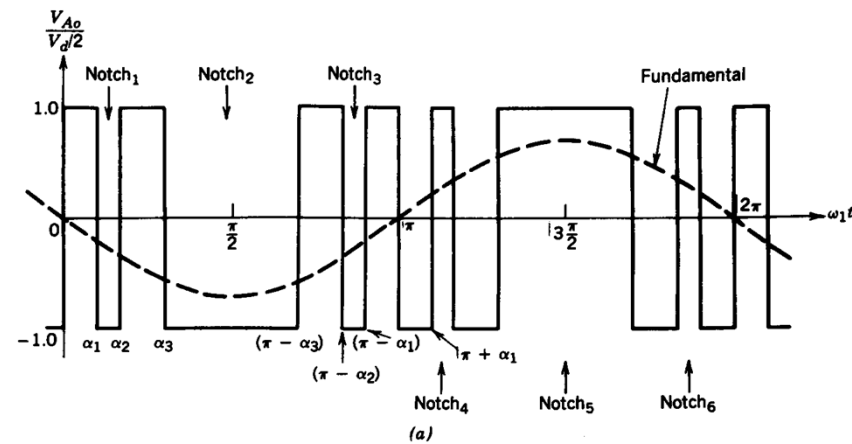


Figure 8-34 Programmed harmonic elimination of fifth and seventh harmonics.

- Angles based on the desired output

Three-Phase Inverter: Fundamental Frequency

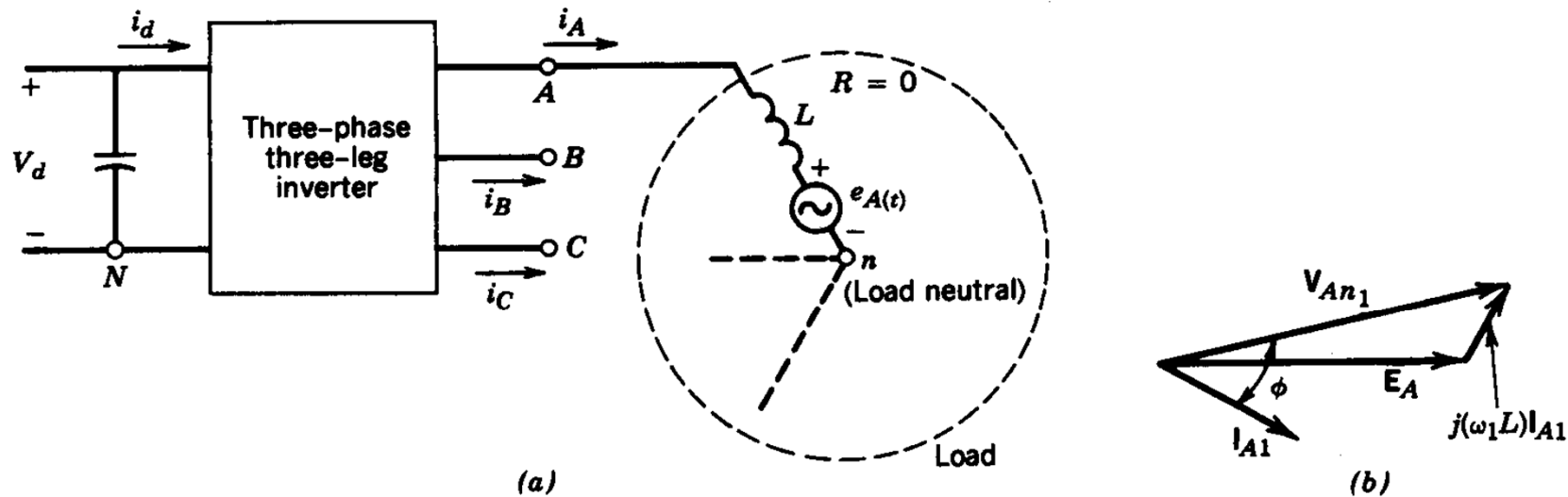


Figure 8-25 Three-phase inverter: (a) circuit diagram; (b) phasor diagram (fundamental frequency).

- Analysis at the fundamental frequency can be done using phasors

Square-Wave and PWM Operation

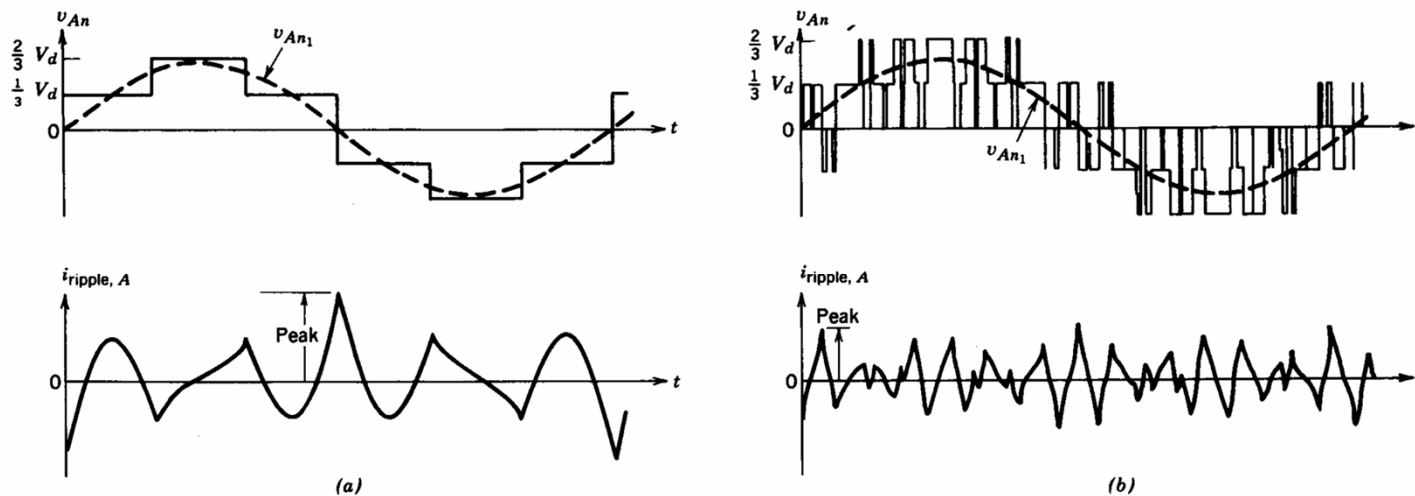


Figure 8-26 Phase-to-load-neutral variables of a three-phase inverter: (a) square wave; (b) PWM.

- PWM results in much smaller ripple current

Effect of Blanking Time

- Results in nonlinearity

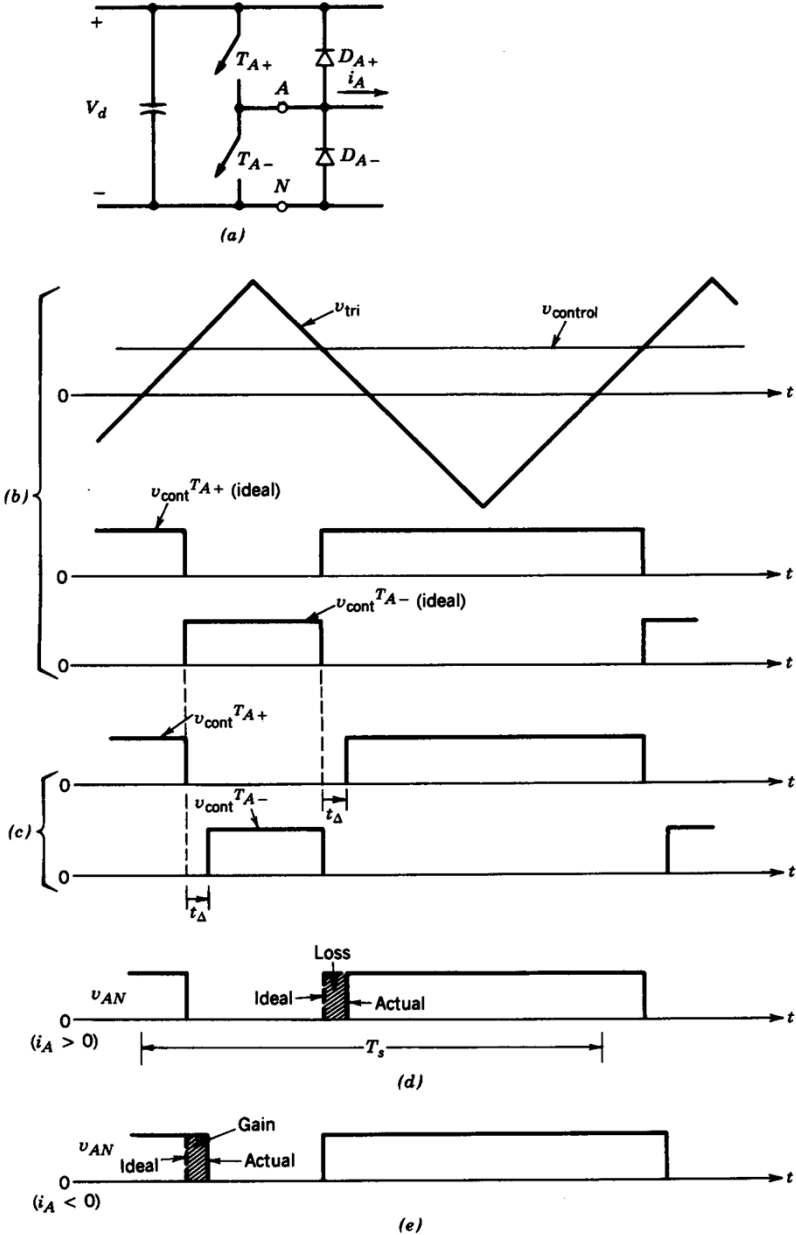


Figure 8-31 Effect of blanking time t_{Δ} .

Effect of Blanking Time

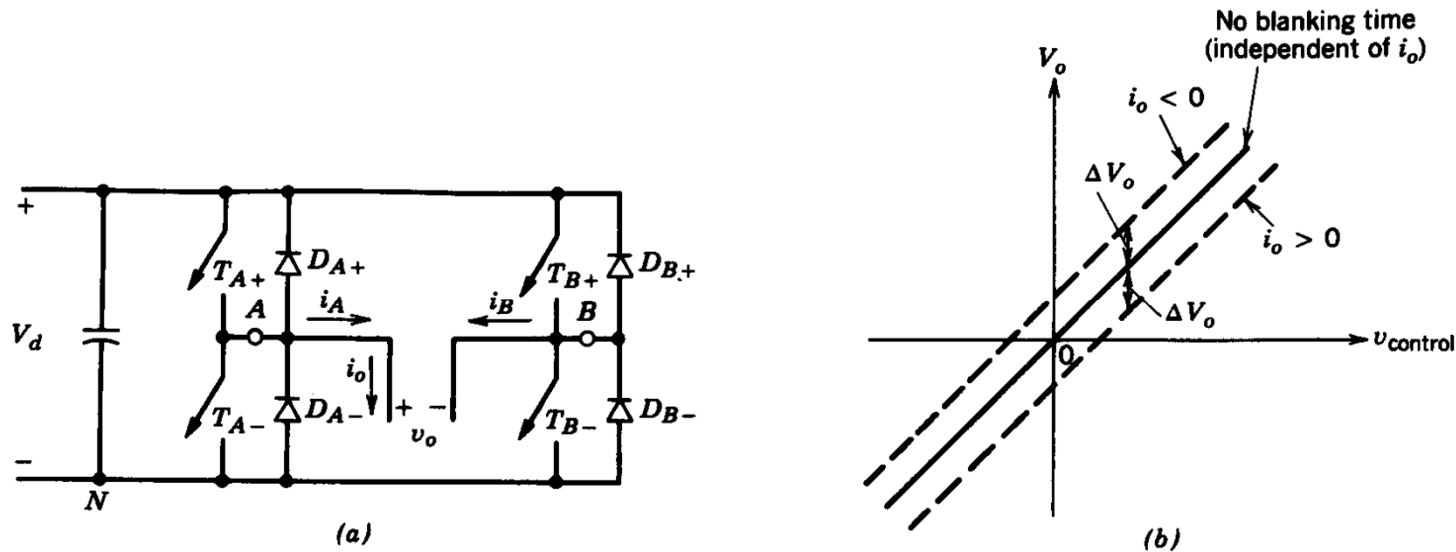


Figure 8-32 Effect of t_{Δ} on V_o , where ΔV_o is defined as a voltage drop if positive.

- Voltage jump when the current reverses direction

Effect of Blanking Time

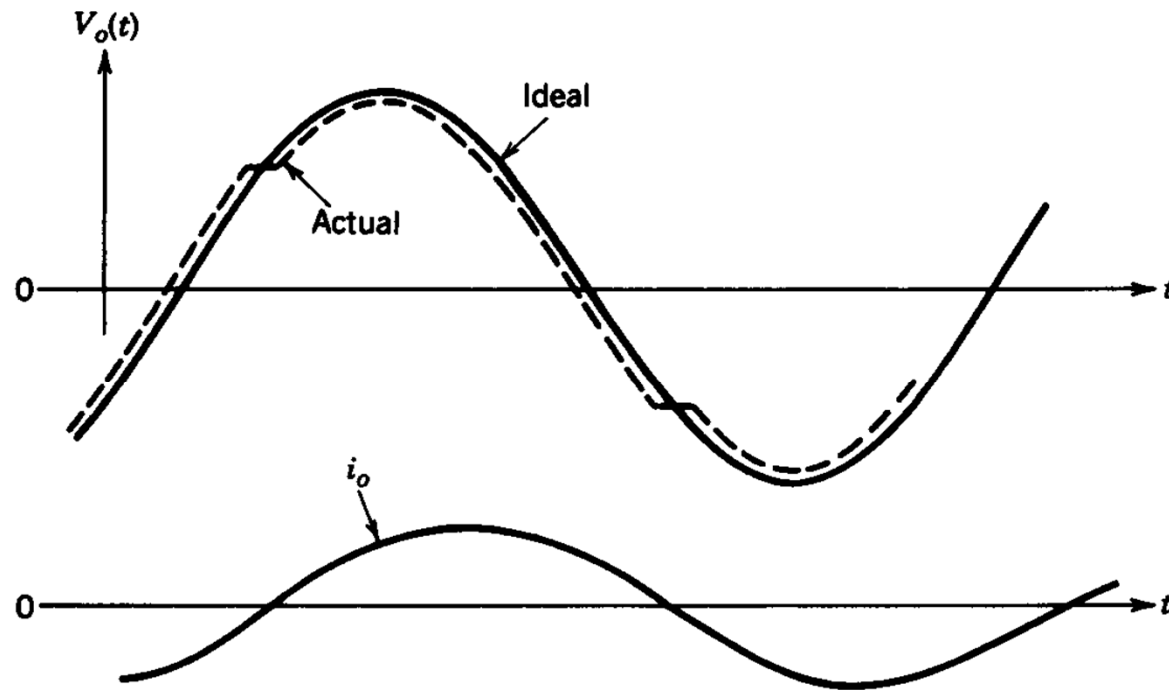


Figure 8-33 Effect of t_Δ on the sinusoidal output.

- Effect on the output voltage

Tolerance-Band Current Control

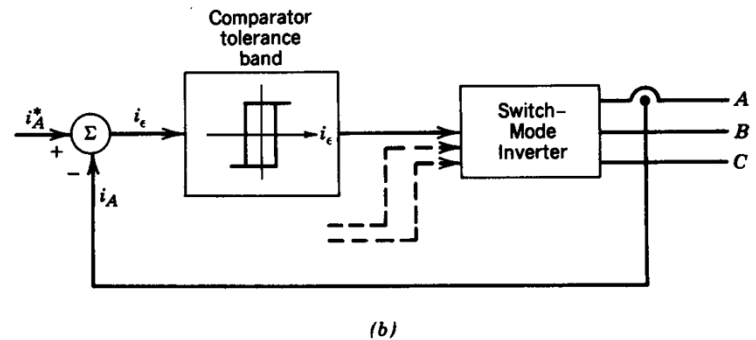
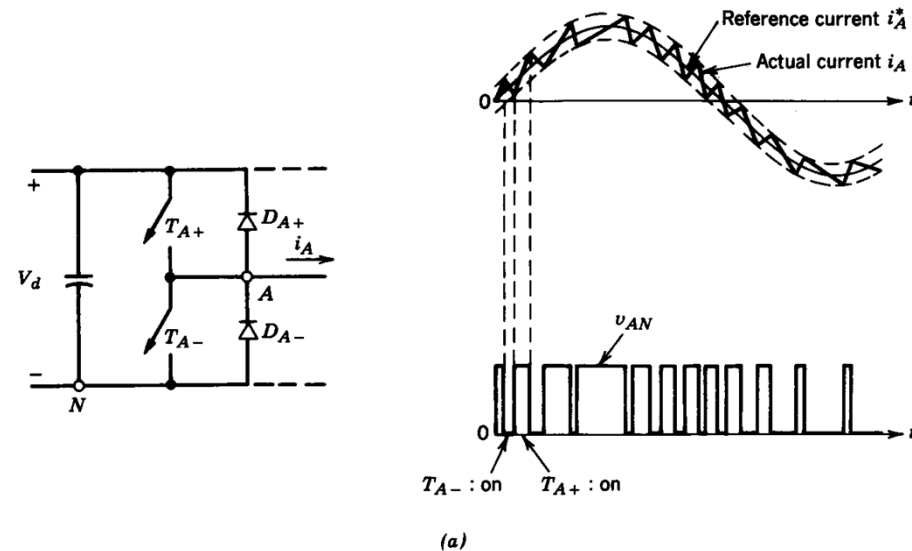


Figure 8-35 Tolerance band current control.

- Results in a variable frequency operation

Transition from Inverter to Rectifier Mode

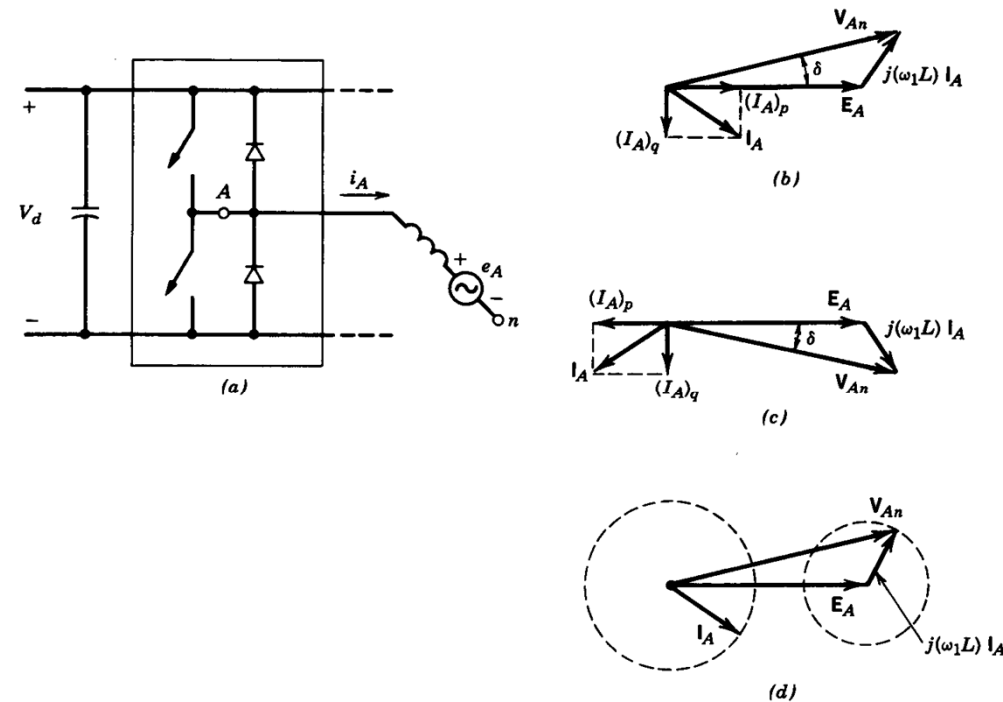


Figure 8-37 Operation modes: (a) circuit; (b) inverter mode; (c) rectifier mode; (d) constant I_A .

- Can analyze based on the fundamental-frequency components