

Linear Power Supplies

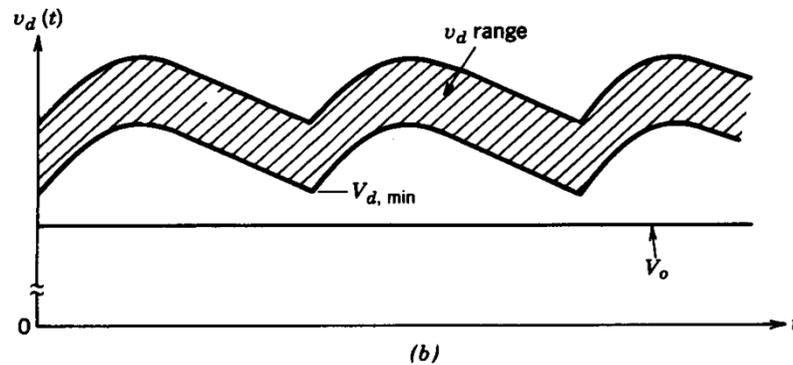
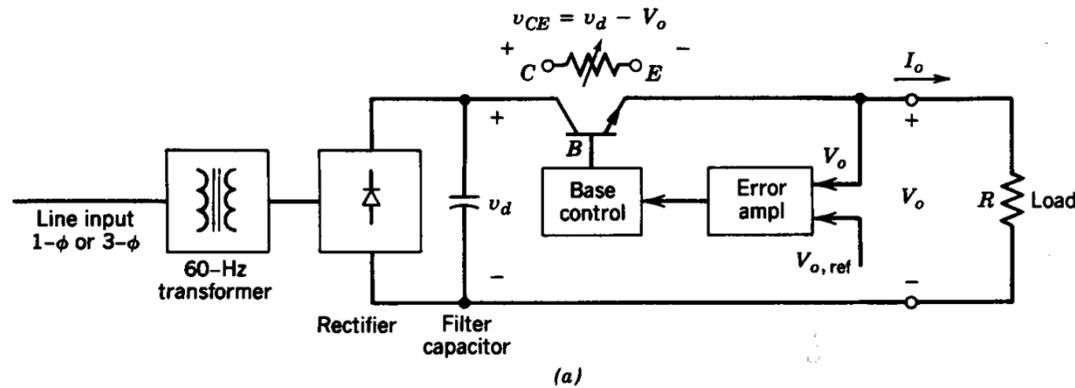


Figure 10-1 Linear power supply: (a) schematic; (b) selection of transformer turns ratio so that $V_{d,\min} > V_o$ by a small margin.

- Very poor efficiency and large weight and size

Switching DC Power Supply: Block Diagram

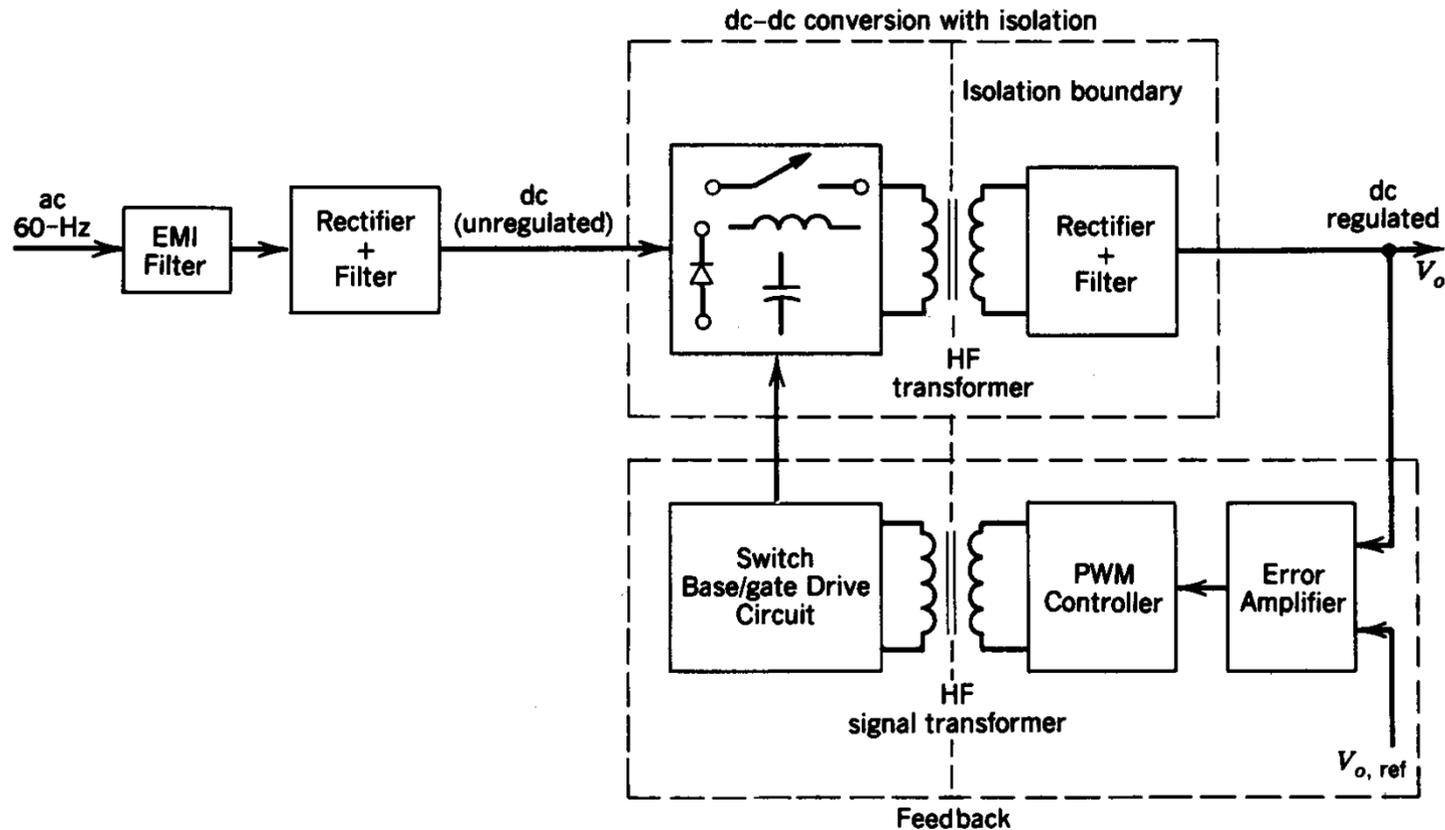


Figure 10-2 Schematic of a switch-mode dc power supply.

- High efficiency and small weight and size

Ferrite Core Material

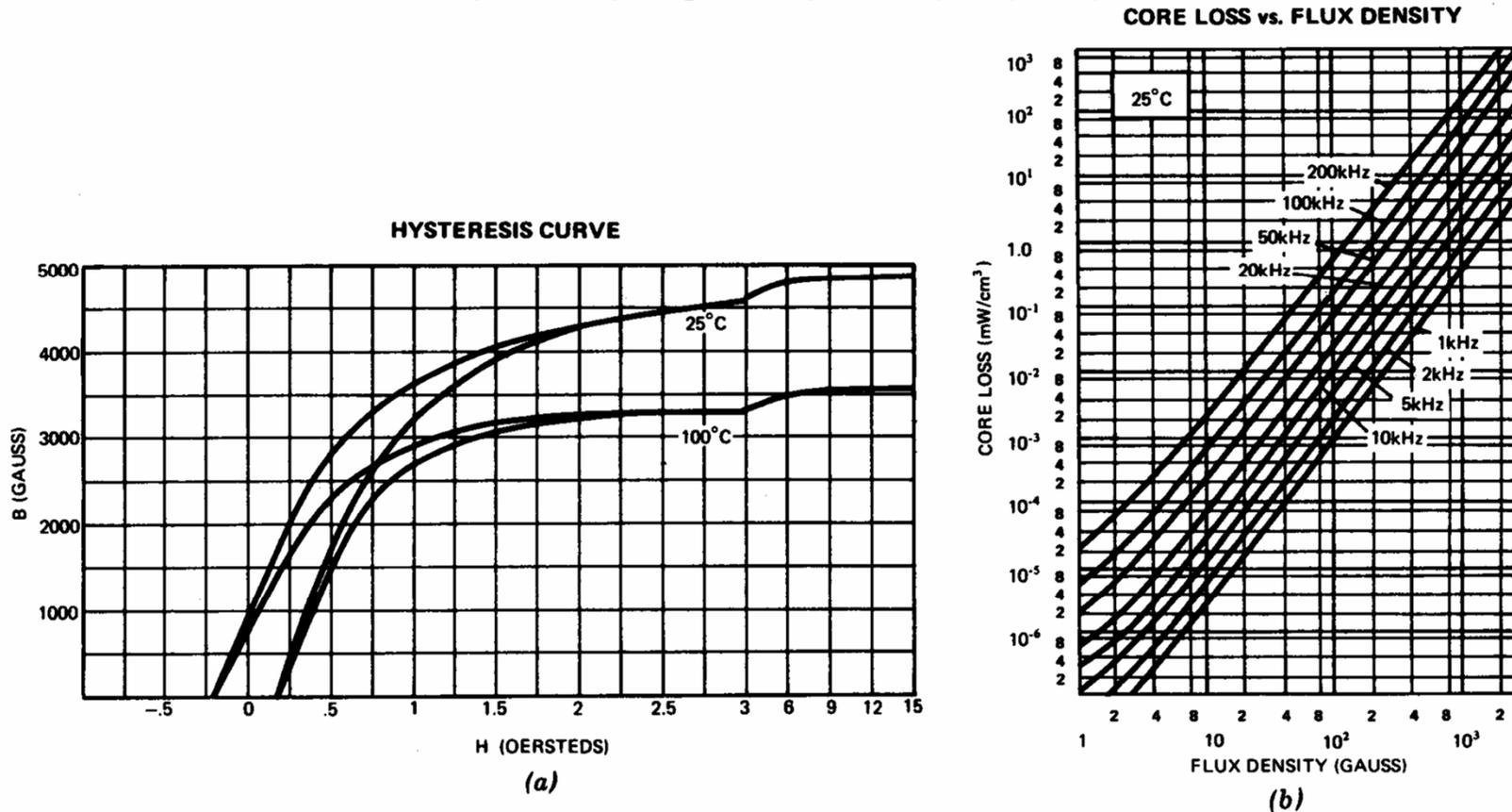


Figure 10-17 3C8 ferrite characteristic curves: (a) B-H loop; (b) core loss curves. (Courtesy of Ferroxcube Division of Amperex Electronic Corporation.)

- Several materials to choose from based on applications

Flyback Converter

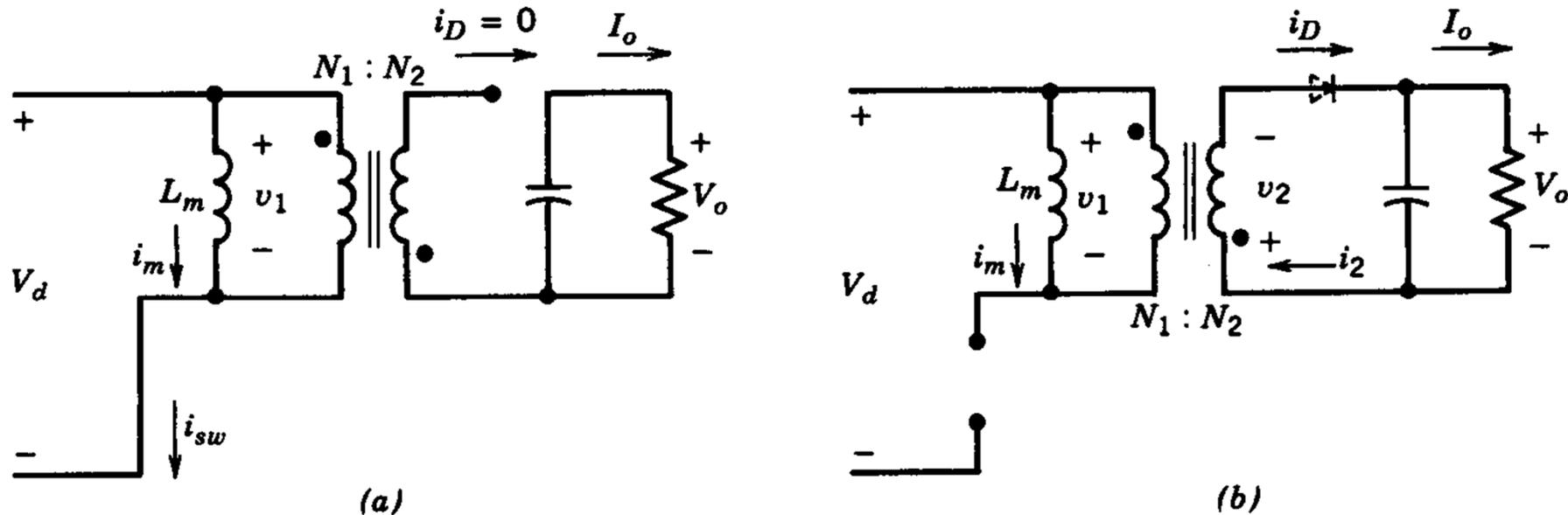


Figure 10-7 Flyback converter circuit states: (a) switch on; (b) switch off.

- Switch on and off states (assuming incomplete core demagnetization)

Flyback Converter


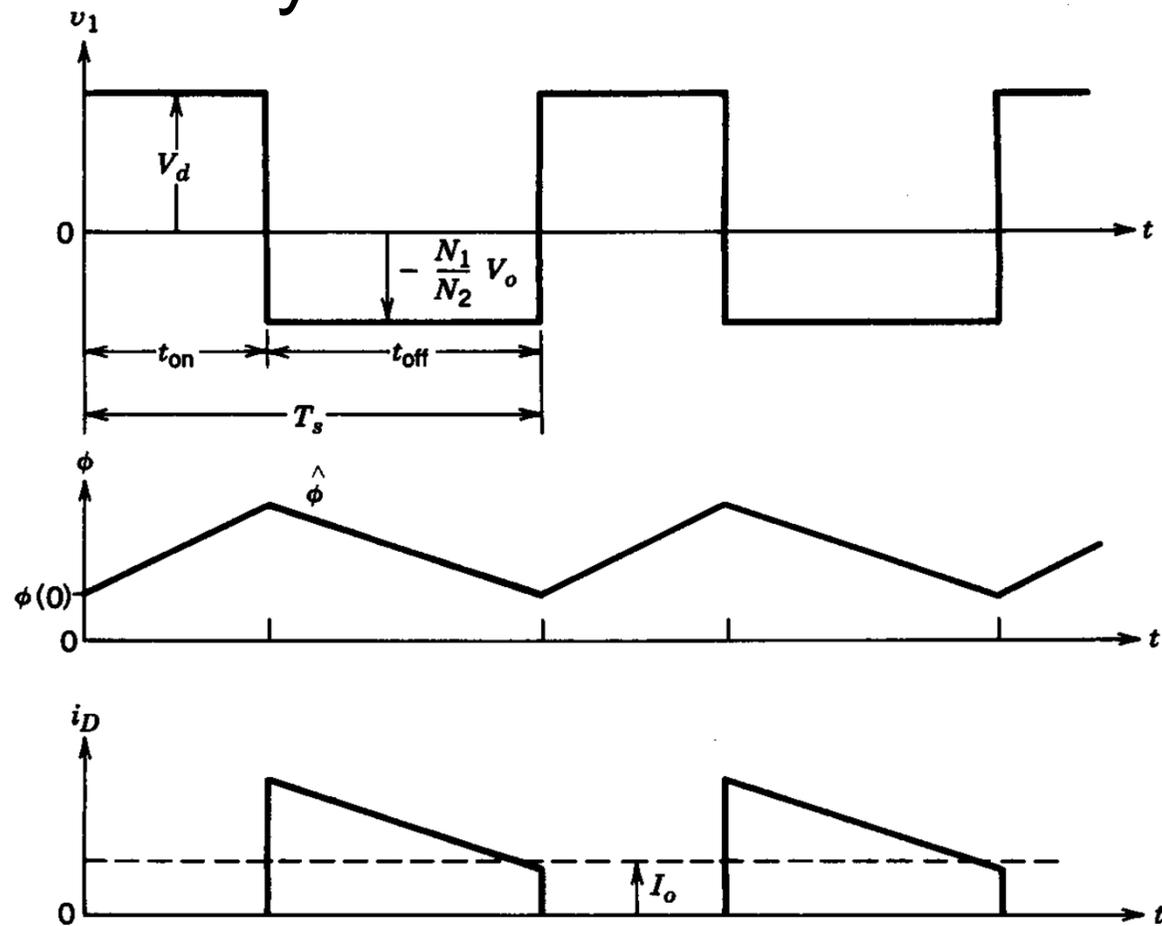


Figure 10-8 Flyback converter waveforms.

- Switching waveforms (assuming incomplete core demagnetization)

Forward Converter: in Practice

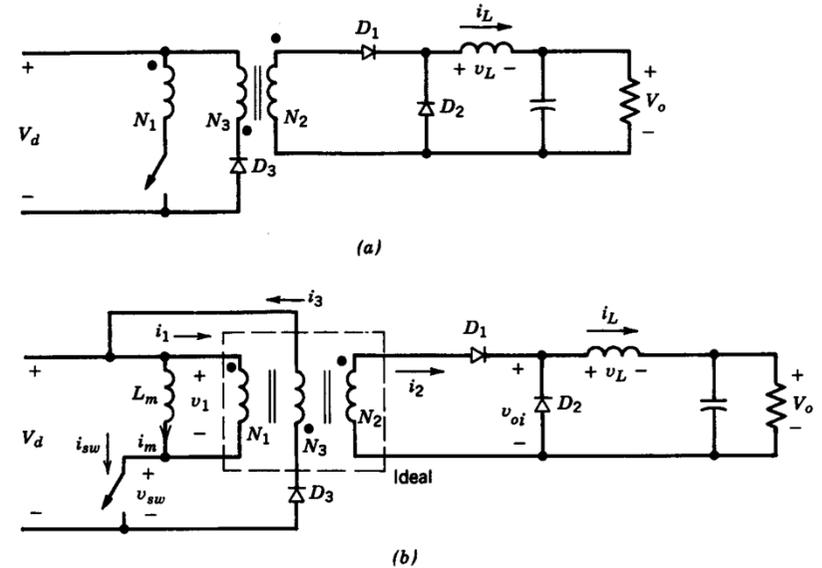

- Switching waveforms (assuming incomplete core demagnetization)

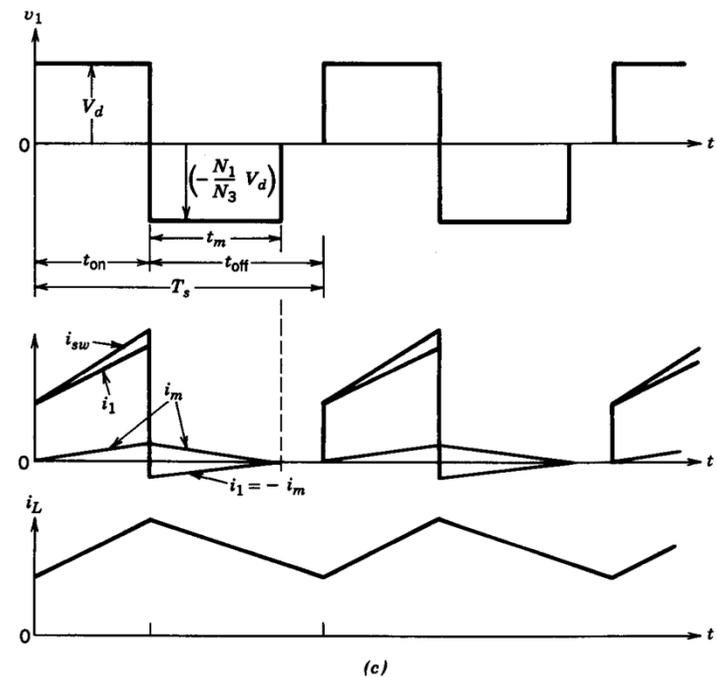


Figure 10-11 Practical forward converter.

Control to Regulate Voltage Output

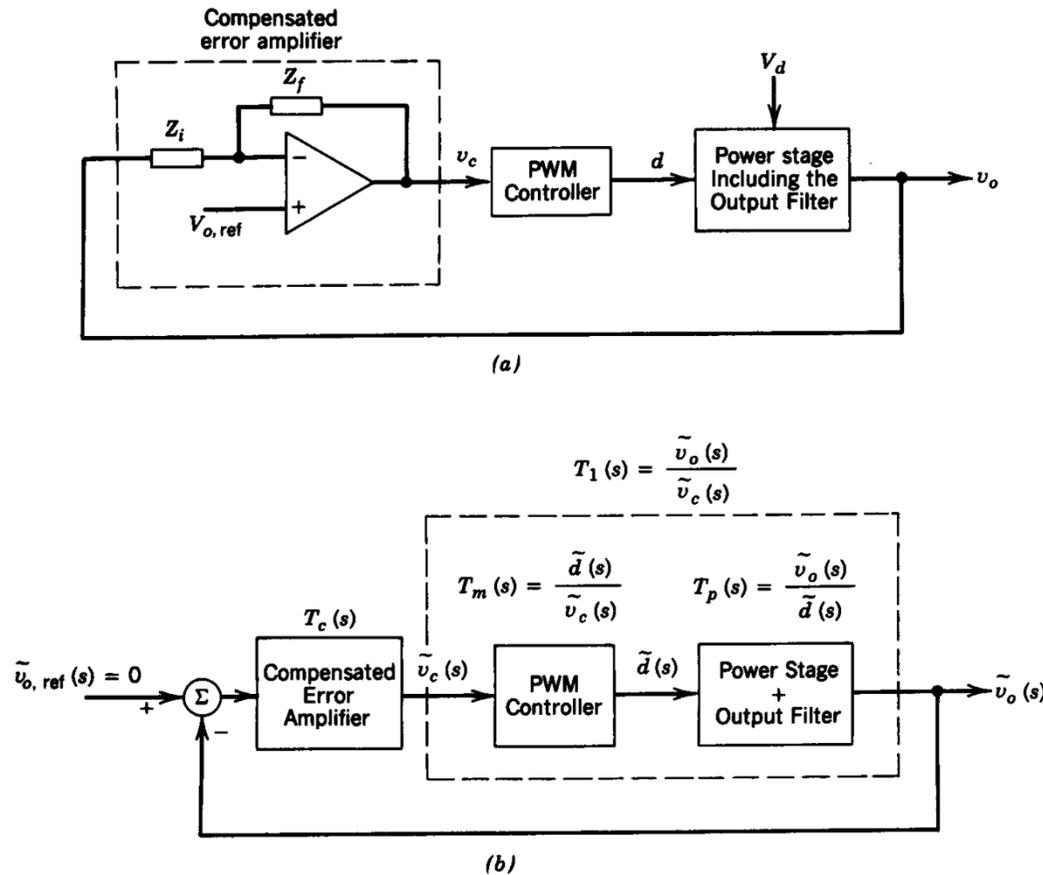


Figure 10-19 Voltage regulation: (a) feedback control system; (b) linearized feedback control system.

- Linearized representation of the feedback control system

State-space averaging description

State-space model

$$\begin{aligned} \dot{x} &= Ax + Bu \\ y &= Cx(+Du) \end{aligned} \quad x = \{\text{e.g.}\} = \begin{bmatrix} v_c \\ i_L \end{bmatrix}$$

Averaging

$$\begin{aligned} \dot{x} &= A_1x + B_1v_d \quad \text{during } t_{on} \\ \dot{x} &= A_2x + B_2v_d \quad \text{during } t_{off} \end{aligned}$$

Weighted sum

$$\dot{x} = [A_1d + A_2(1-d)]x + [B_1d + B_2(1-d)]v_d$$

Small perturbations

$$x = X + \tilde{x}, \quad d = D + \tilde{d}, \quad v_d = V_d$$

Simplify

$$\dot{\tilde{x}} = A\tilde{x} + [(A_1 - A_2)X + (B_1 - B_2)V_d]\tilde{d}$$

$$A = A_1D + A_2(1-D)$$

Transfer function

Laplace domain $\tilde{x} = [sI - A]^{-1} [(A_1 - A_2)X + (B_1 - B_2)V_d] \tilde{d}$

Transfer function $T_p(s) = \frac{\tilde{v}_o(s)}{\tilde{d}(s)}$