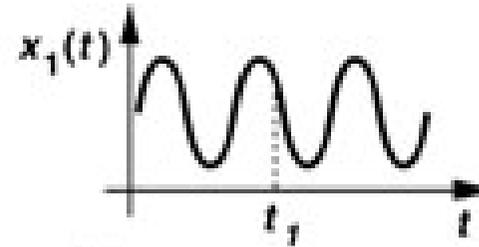


Lecture 7


IL2218 Analog electronics, advanced course

- Noise in MOS
 - Thermal noise
 - Flicker noise
- Noise calculations
- Input referred noise

Noise




(a)

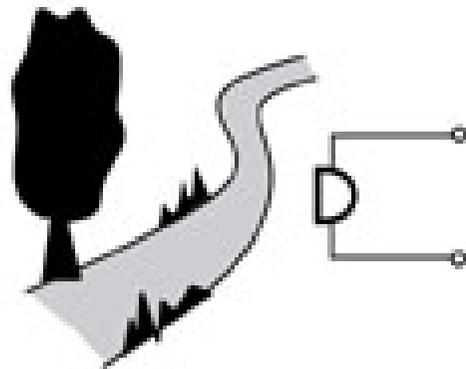

(b)

Noise power


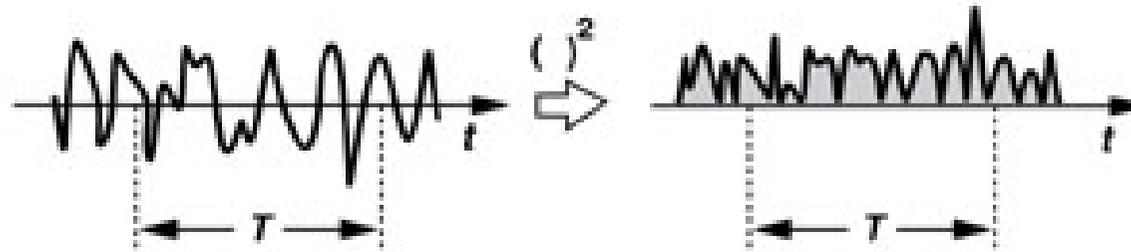


$$P_{av} = \lim_{T \rightarrow \infty} \frac{1}{T} \int_{-T/2}^{+T/2} x^2(t) dt$$


$$P_{av} = P_{av1} + P_{av2}$$

Superposition holds for the power of uncorrelated sources

Noise shaping

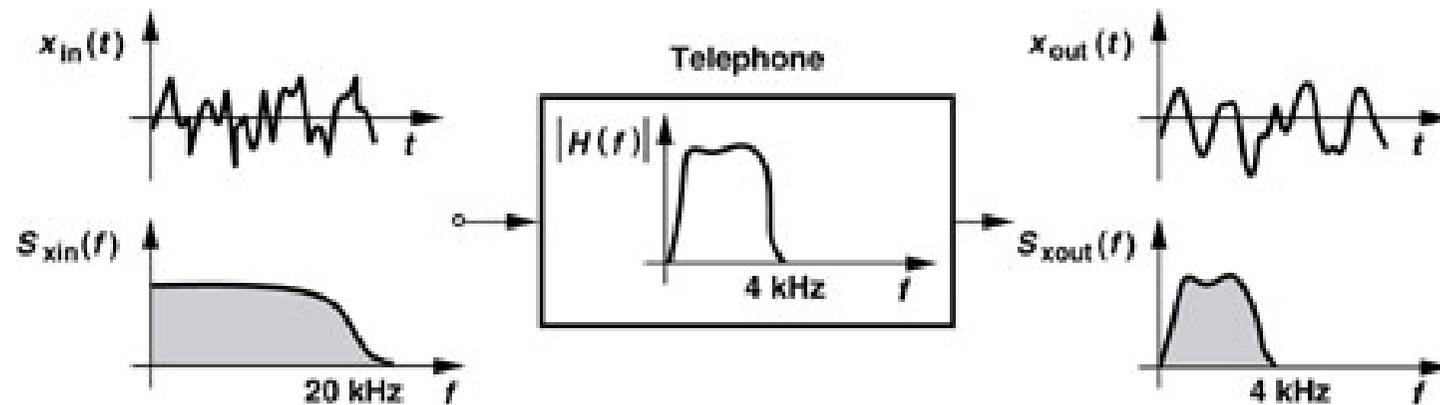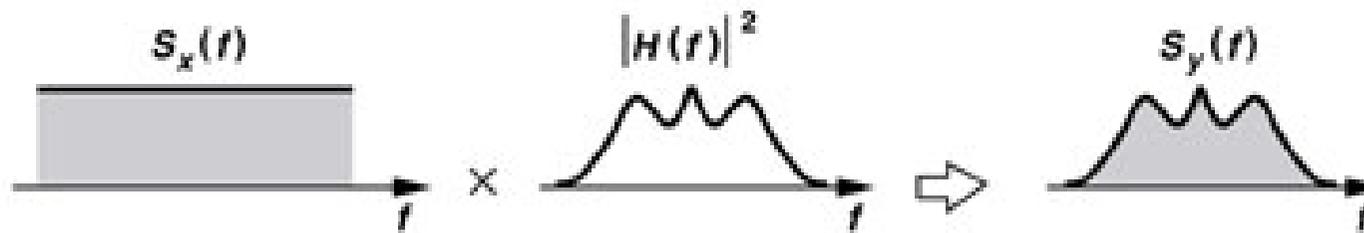

Thermal noise in resistor

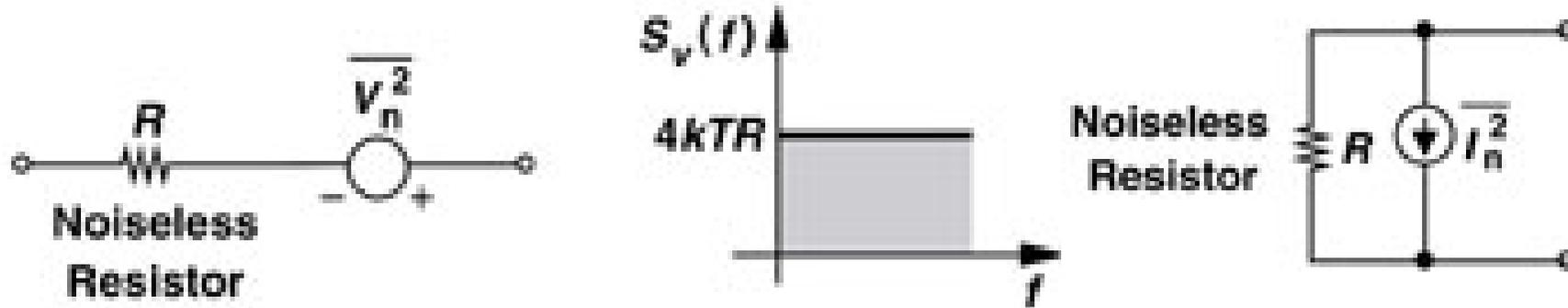


$$\overline{V_n^2} = 4kTR(\Delta f)$$

$$\overline{I_n^2} = \frac{4kT}{R}$$

$$R = 50, T = 300K \rightarrow V_n = 0.91 \text{ nV} / \sqrt{\text{Hz}}$$


Thermal noise in MOS transistor

Thermal noise in channel

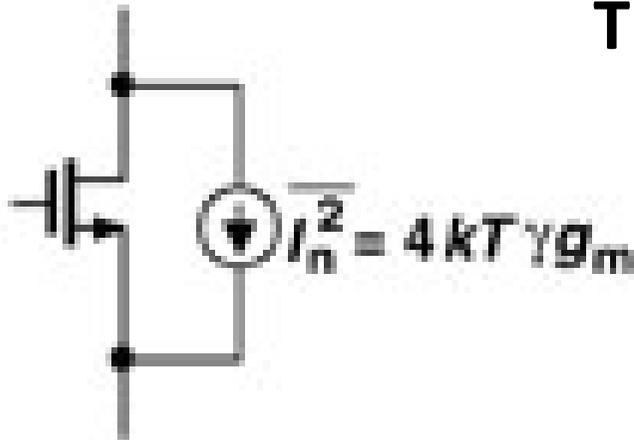

Parameter γ is typically 2/3 for long channel, as high as 2.5 for submicron devices.



MOS ohmic noise sources

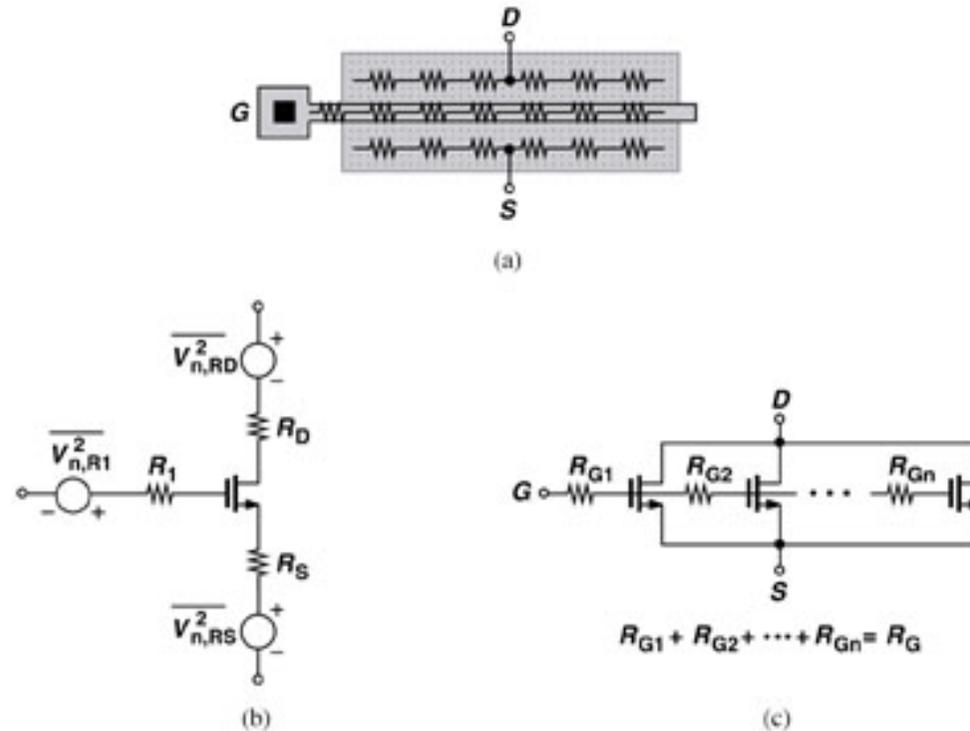

Can be reduced by proper layout. Noise in ohmic sections can usually be neglected.

Flicker noise

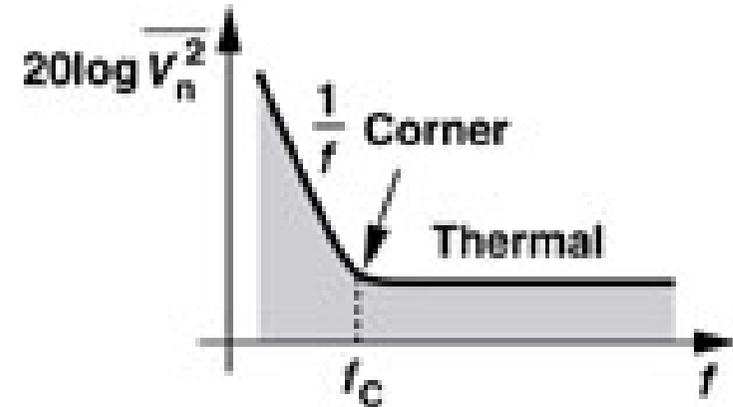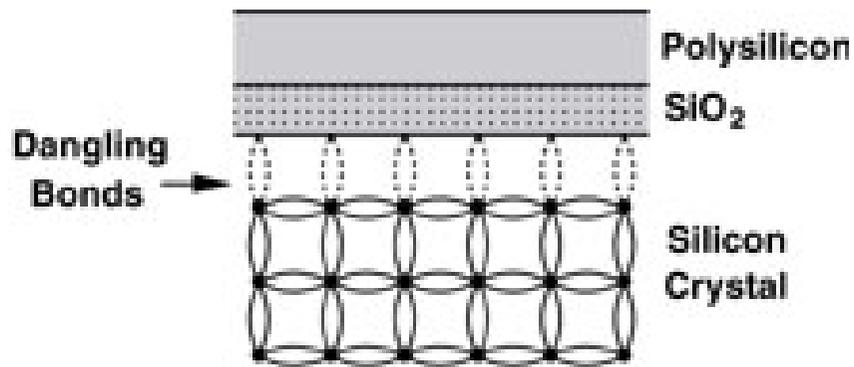Generated when charges at interface is trapped and released



Corner frequency f_c



$$\overline{V_n^2} = \frac{K}{C_{ox} WL} \frac{1}{f}$$

$$4kT \left(\frac{2}{3} g_m \right) \approx \frac{K}{C_{ox} WL} \frac{1}{f_c} g_m^2$$

$$f_c \approx \frac{K}{C_{ox} WL} g_m \frac{3}{8kT}, \text{ app. for long channel}$$

Noise in circuits


Example 7.7

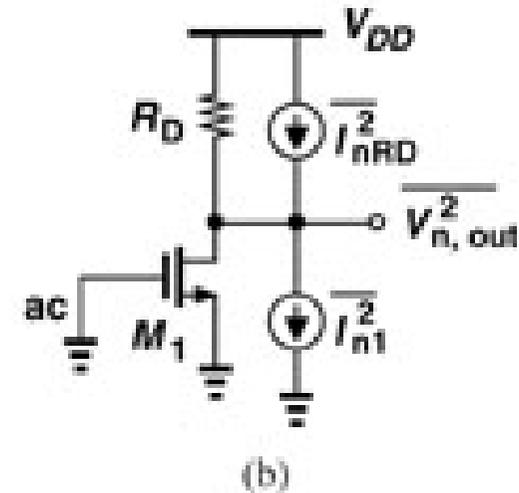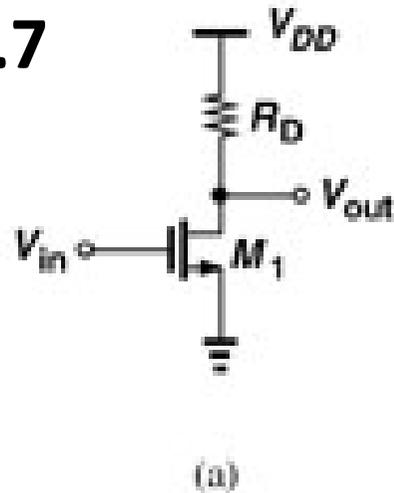

$$\overline{V_{n,out}^2} = \left(4kT \frac{2}{3} g_m + \frac{K}{C_{ox} WL} \frac{1}{f} g_m^2 + \frac{4kT}{R_D} \right) R_D^2$$


M1 thermal + M1 flicker + R_D thermal

Input referred noise

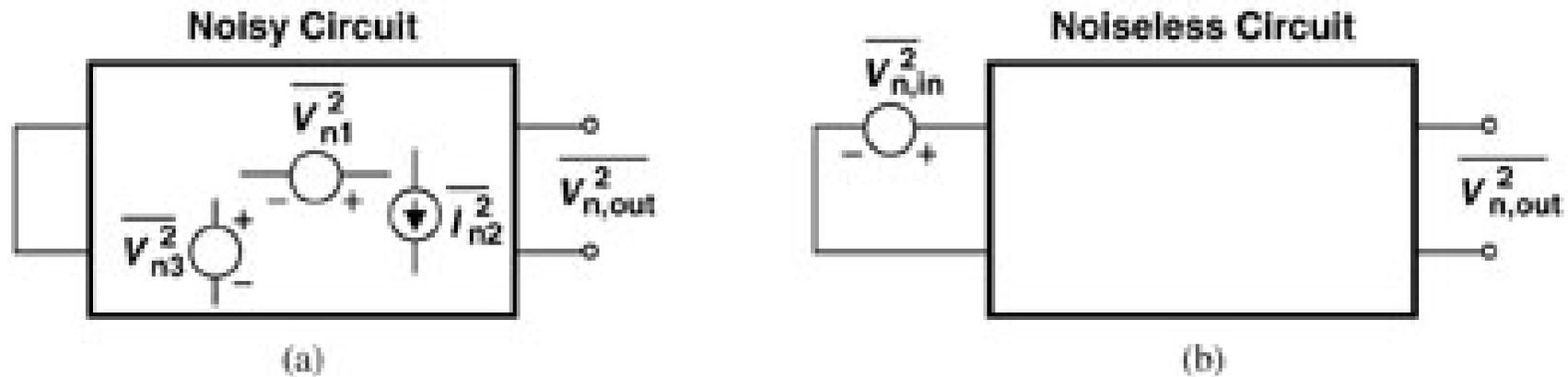

Input referred noise is a fictitious quantity that allows comparison between different circuits.

Input referred noise, example 7.7



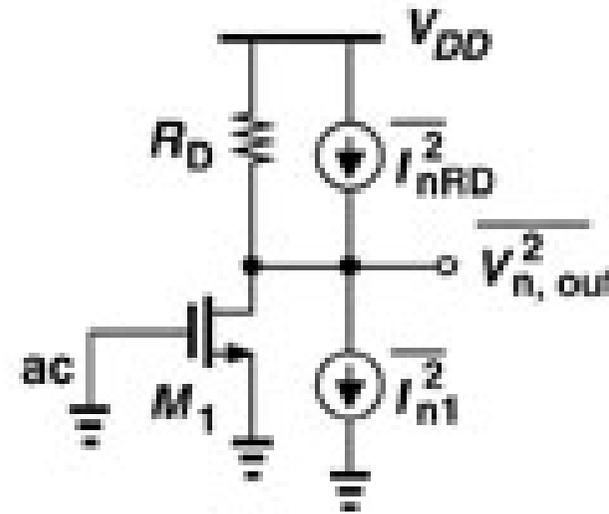


$$\overline{V_{n,in}^2} = \frac{\overline{V_{n,out}^2}}{A_v^2} = \frac{\overline{V_{n,out}^2}}{g_m^2 R_D^2}$$

$$\overline{V_{n,in}^2} = \left(4kT \frac{2}{3} g_m + \frac{K}{C_{ox} WL} \frac{1}{f} g_m^2 + \frac{4kT}{R_D} \right) R_D^2 \frac{1}{g_m^2 R_D^2}$$

$$= 4kT \frac{2}{3g_m} + \frac{K}{C_{ox} WL} \frac{1}{f} + \frac{4kT}{g_m^2 R_D}$$

Input referred noise voltage and current

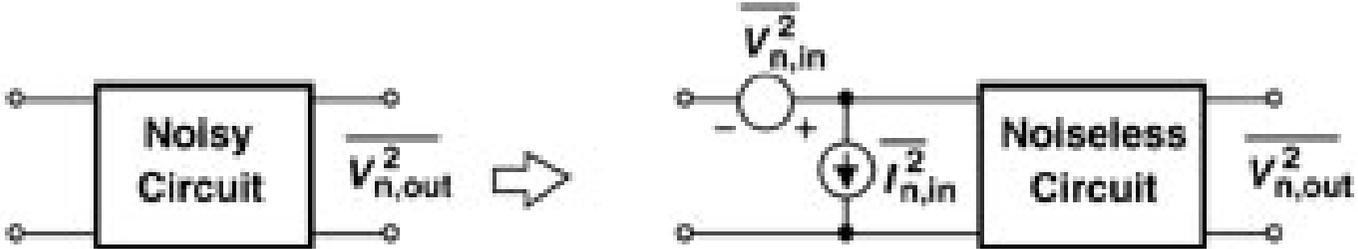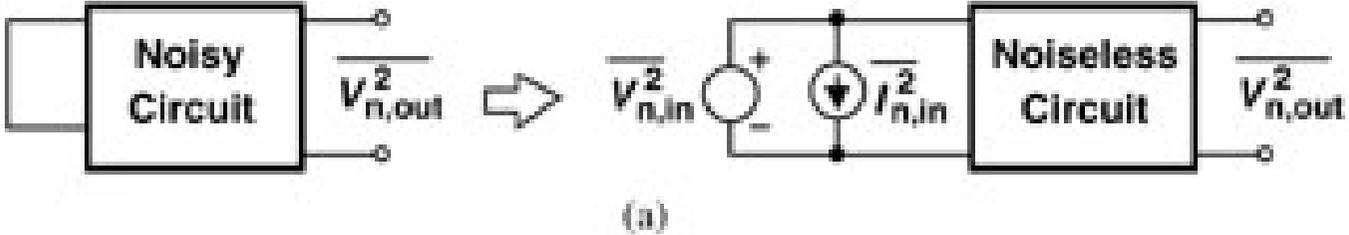
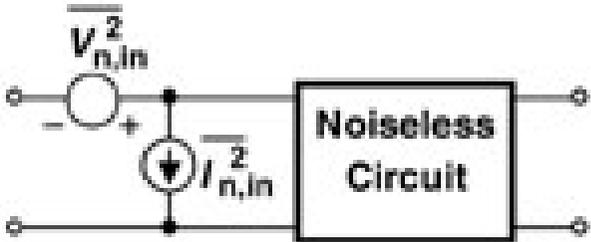


Output noise current transformed to input noise voltage

$$\overline{V_{n,gate}^2} = \frac{\overline{I_{n,drain-source}^2}}{g_m^2}$$

A noise source can be transformed from a drain-source current to a gate series voltage for arbitrary Z_s . (page 224)

Common source amplifier

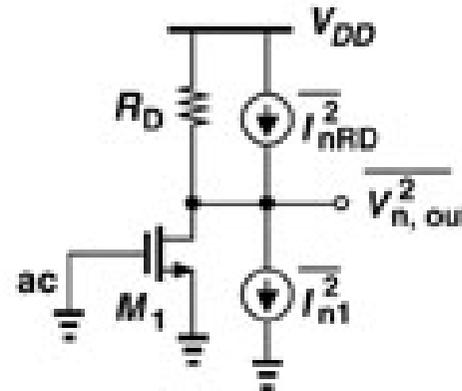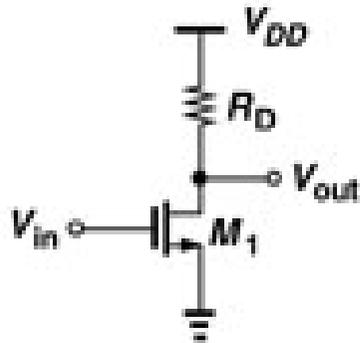

$$\overline{V_{n,in}^2} = 4kT \left(\frac{2}{3g_m} + \frac{1}{g_m^2 R_D} \right) + \frac{K}{C_{ox}} \frac{1}{WL f}$$

$$\overline{I_{n,in}^2} = \frac{1}{Z_{in}^2} \left[4kT \left(\frac{2}{3g_m} + \frac{1}{g_m^2 R_D} \right) + \frac{K}{C_{ox}} \frac{1}{WL f} \right]$$

$$\overline{I_{n,in}^2} \approx 0 \text{ for low frequencies}$$