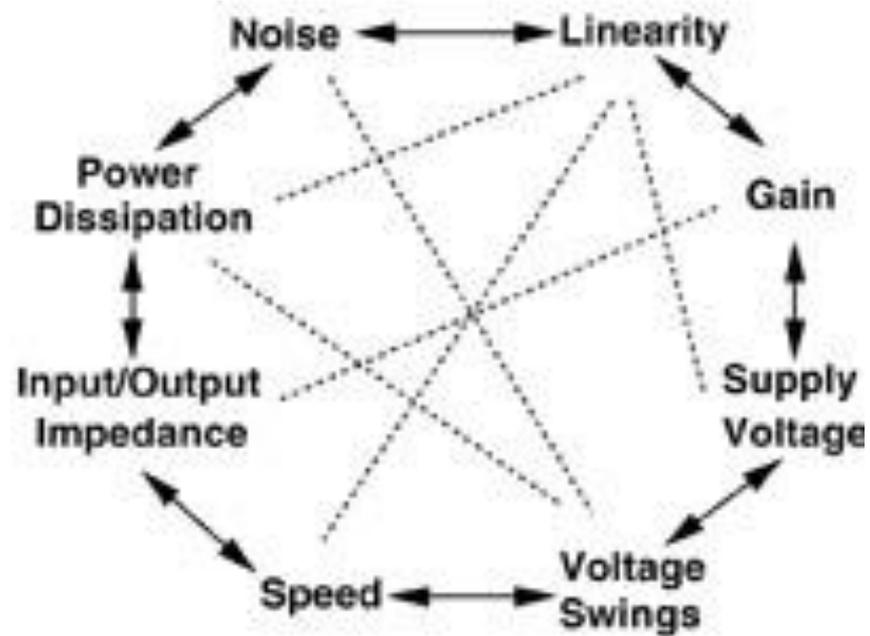


Lecture 5


IL2218 Analog electronics, advanced course

- Some reflections of what we have done this far in the course
- Capacitances in MOS transistor
- Miller theorem
- Poles associated to nodes, approximation
- Poles and zeroes in CS amplifier stage
- Exact transfer function of CS amplifier



Trade offs in analog design



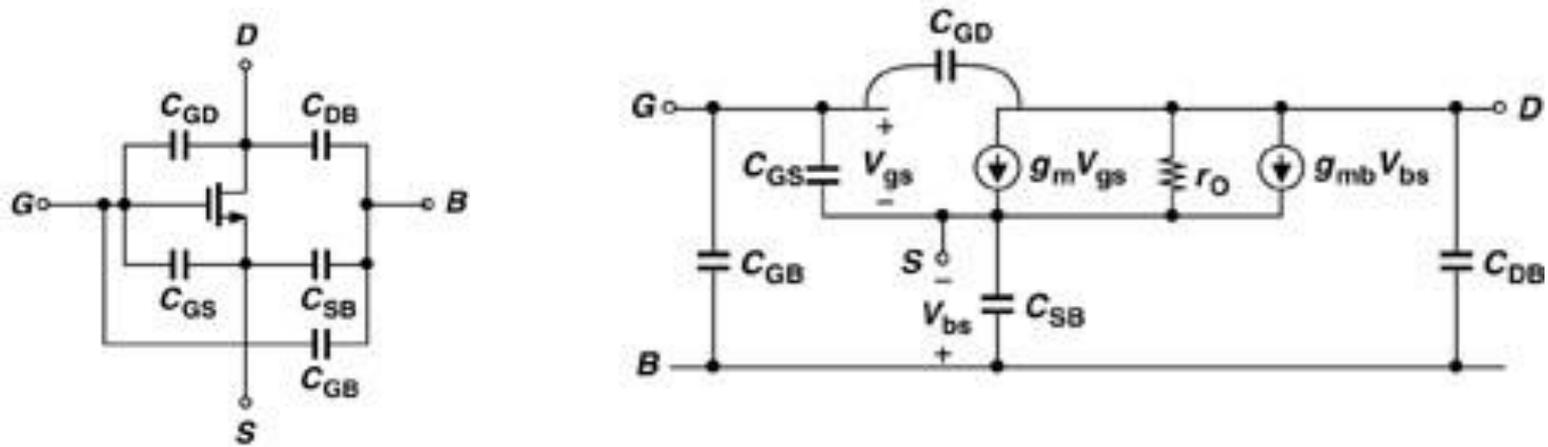
Complete small signal model with capacitances




Explain the capacitances!

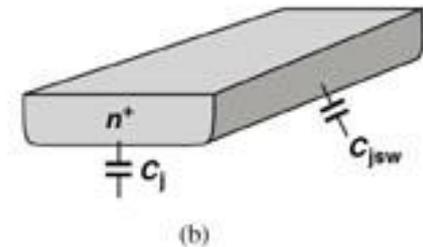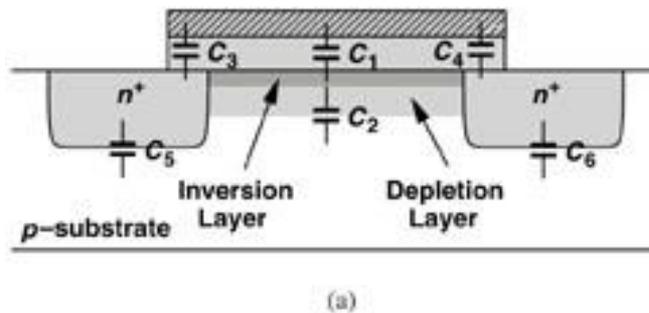

Gate-source and gate-drain capacitance

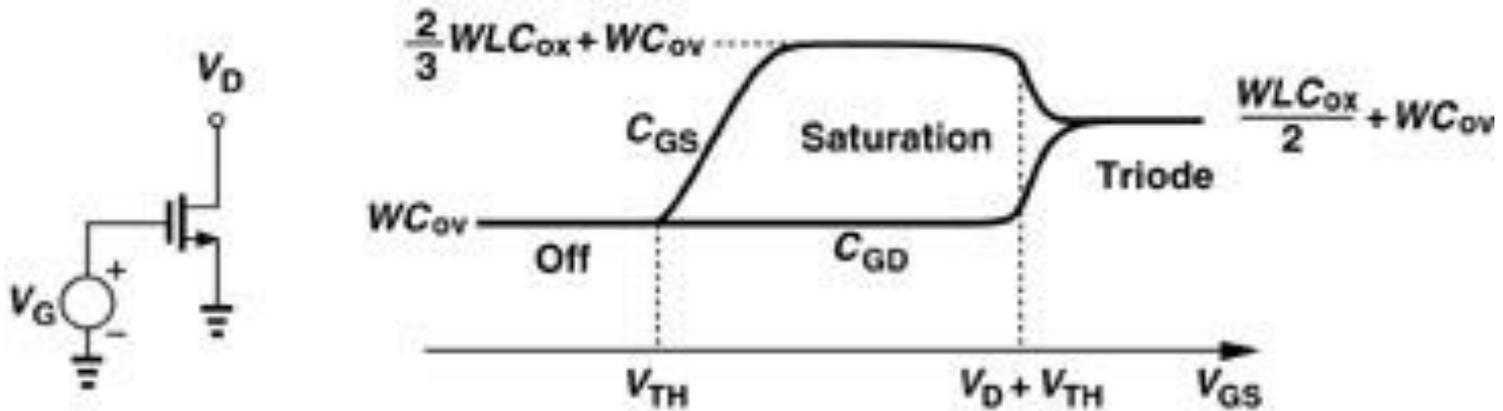

MOS layout

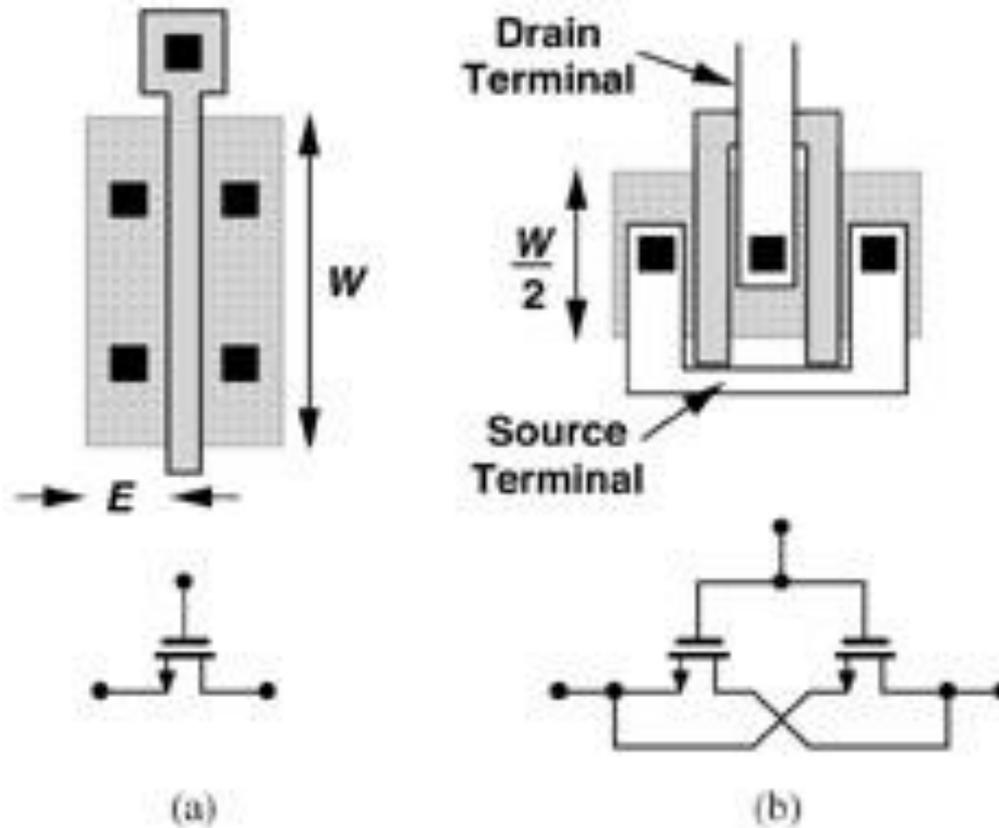

From "Introduction to Pspice", page 13

From Pspice output file

CBD	2.73E-14
CBS	4.24E-14
CGSOV	0.00E+00
CGDOV	1.50E-14
CGBOV	0.00E+00
CGS	4.35E-14
CGD	0.00E+00
CGB	0.00E+00


Something to think about:

Why are some of the capacitances zero?


Table 2.1

```
.model nMOS NMOS
+ LEVEL=1 VTO=0.7 GAMMA=0.45 PHI=0.9
+ NSUB=9E+14 LD=0.08E-6 UO=350 LAMBDA=0.1
+ TOX=9E-9 PB=0.9 CJ=0.56E-3 CJSW=0.35E-11
+ MJ=0.45 MJSW=0.2 CGDO=0.3E-9 JS=1.0E-8
```


Miller capacitance

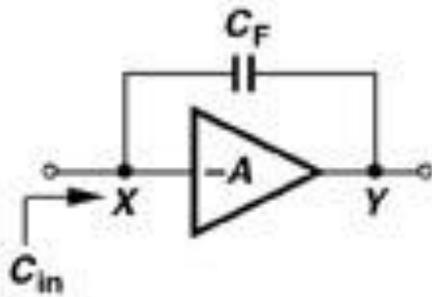

(a)

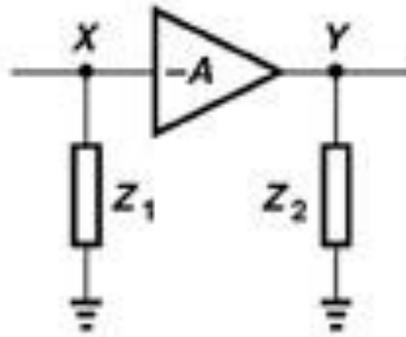

(b)

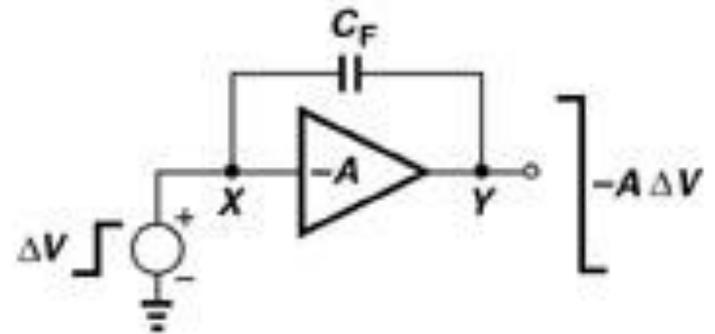


(c)

$$C_1 = (1 + A) C_F$$


$$C_2 = C_F \left(1 + \frac{1}{A}\right) \approx C_F$$

Poles associated to nodes

Non-Interacting Poles

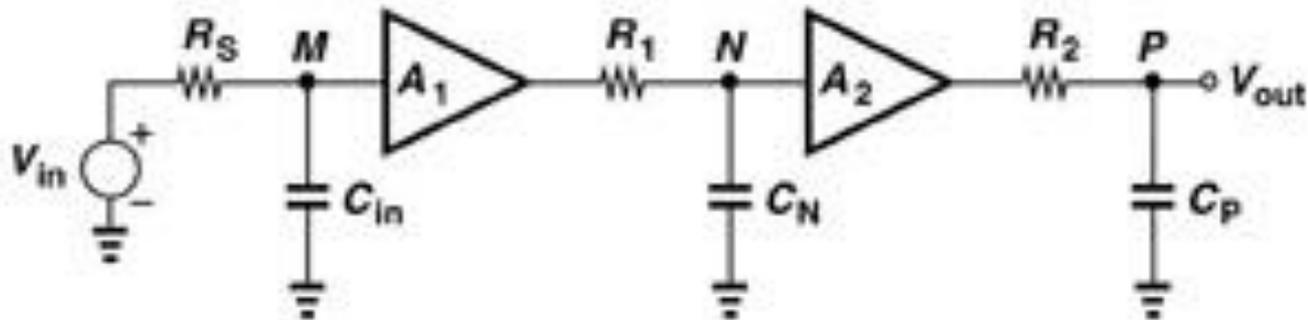


Interacting Poles

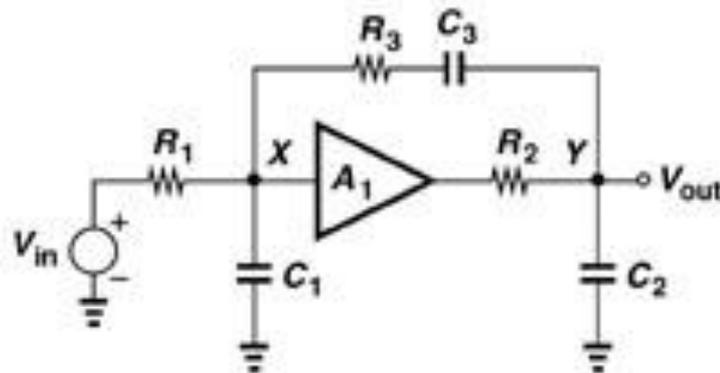

CS amplifier


Neglecting input/output interaction,

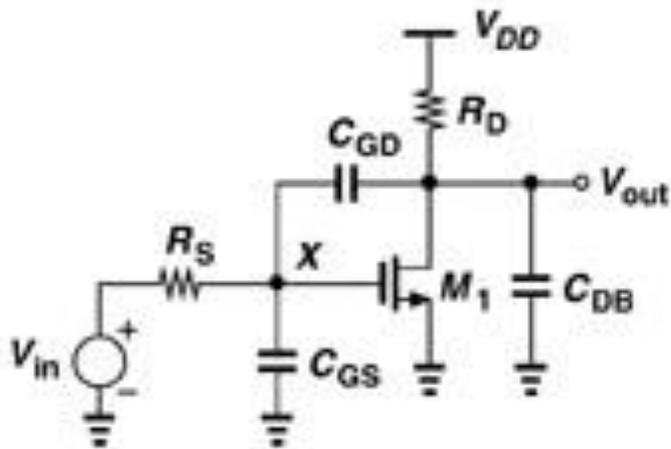

$$f_{p,in} = \frac{1}{2\pi R_S [C_{GS} + (1 + g_m R_D) C_{GD}]}$$

$$f_{p,out} = \frac{1}{2\pi [(C_{GD} + C_{DB}) R_D]}$$

CS amplifier, exact transfer function

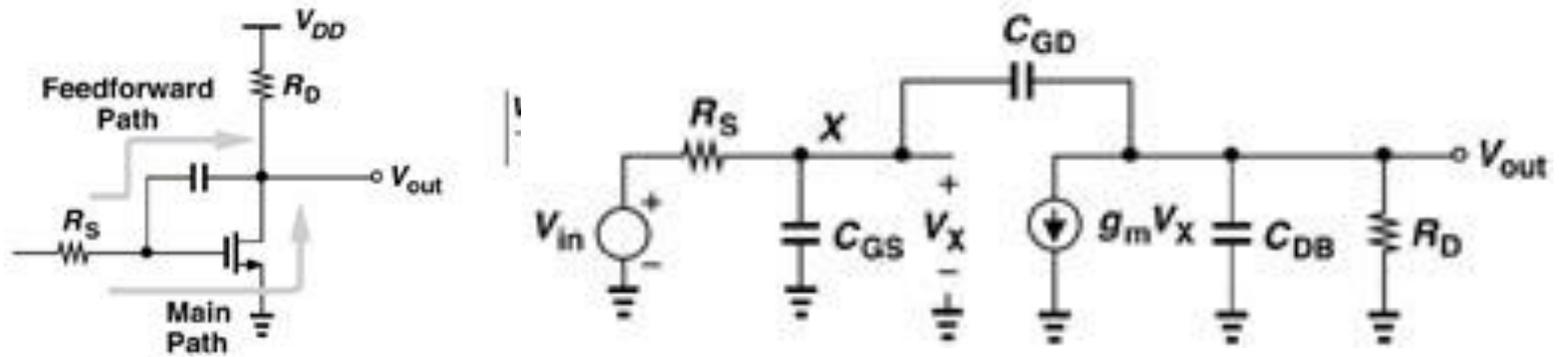

$$\frac{V_{out}}{V_{in}}(s) = \frac{(sC_{GD} - g_m)R_D}{s^2 R_S R_D (C_{GS} C_{GD} + C_{GS} C_{SB} + C_{GD} C_{DB}) + s [R_S (1 + g_m R_D) C_{GD} + R_S C_{GS} + R_D (C_{GD} + C_{DB})] + 1}$$

$$\text{Assume } |\omega_{p2}| \gg |\omega_{p1}| \quad D = \left(\frac{s}{\omega_{p1}} + 1 \right) \left(\frac{s}{\omega_{p2}} + 1 \right) \approx \frac{s^2}{\omega_{p1} \omega_{p2}} + \frac{s}{\omega_{p1}} + 1,$$

$$f_{p,in} = \frac{1}{2\pi \left(R_S [C_{GS} + (1 + g_m R_D) C_{GD}] + R_D (C_{GD} + C_{DB}) \right)}$$

$$f_{p,out} = \frac{R_S(1 + g_m R_D)C_{GD} + R_S C_{GS} + R_D (C_{GD} + C_{DB})}{2\pi R_S R_D (C_{GS} C_{GD} + C_{GS} C_{DB} + C_{GD} C_{DB})}$$

$$f_{p,out} \approx \frac{1}{2\pi R_D (C_{GD} + C_{DB})}, \text{ for large } C_{GS}$$

$$f_{p,out} \approx \frac{g_m R_S R_D C_{GD}}{2\pi R_S R_D (C_{GS} C_{GD} + C_{GS} C_{DB} + C_{GD} C_{DB})}$$

$$\approx \frac{gm}{2\pi (C_{GS} + C_{DB})}, \text{ for large } C_{GD}$$

Zero in transfer function

Right half plane zero



$$\frac{V_{out}}{V_{in}}(s) = \frac{(sC_{GD} - g_m)R_D}{s^2 R_S R_D (C_{GS} C_{GD} + C_{GS} C_{SB} + C_{GD} C_{DB}) + s \left[R_S (1 + g_m R_D) C_{GD} + R_S C_{GS} + R_D (C_{GD} + C_{DB}) \right] + 1}$$

$$\frac{sC_{GD} - g_m}{\dots} \rightarrow f_z = \frac{+g_m}{2\pi C_{GD}}$$

Feedforward path

